

MICROELECTRONIC CIRCUIT DESIGN

Second Edition

Richard C. Jaeger and Travis N. Blalock

Answers to Selected Problems – Updated 10/23/06

Chapter 1

- 1.3** 1.52 years, 5.06 years
1.5 2.00 years, 6.65 years
1.8 113 MW, 511 kA
1.10 2.44 mV, 5.71 V
1.12 19.53 mV/bit, 10001110₂
1.16 0.002 A, 0.002 cos (1000 t) A
1.19 [5 + 2 sin (2500 t) + 4 sin (1000 t)] V
1.21 14.7 V, 3.30 V, 76.7 μ A, 300 μ A
1.23 150 μ A, 100 μ A, 8.20 V
1.25 40 Ω , 0.025 v_s
1.27 56 k Ω , 1.07 \times 10⁻³ v_s
1.29 1.00 M Ω , $2.00 \times 10^8 i_s$
1.33 5/-45°, 100/-12°
1.35 -90.1 sin 750 πt mV, 11.0 sin 750 πt μ A
1.37 1 + R₂/R₁
1.39 -1.875 V, -2.500 V
1.41 Band-pass amplifier
1.43 25.0 sin (2000 πt) + 15.0 cos (8000 πt) V
1.45 0 V
1.47 [1980 Ω , 2020 Ω], [1900 Ω , 2100 Ω], [1800 Ω , 2200 Ω]
1.52 6200 Ω , 800 ppm/ $^{\circ}$ C
1.58 3.29, 0.995, -6.16; 3.295, 0.9952, -6.155

Chapter 2

- 2.4** For Ge: 35.9/cm³, $2.27 \times 10^{13}/\text{cm}^3$, $8.04 \times 10^{15}/\text{cm}^3$
2.7 $2.13 \times 10^6 \text{ cm/s}$, $7.80 \times 10^5 \text{ cm/s}$, $3.41 \times 10^4 \text{ A/cm}^2$, $1.25 \times 10^{-10} \text{ A/cm}^2$
2.8 305.2 K

- 2.10** -5×10^4 cm/s
- 2.13** 1.60×10^6 A/cm², 0.800 A
- 2.15** 316.6 K
- 2.19** Acceptor, donor
- 2.20** 100 V/cm
- 2.22** 5×10^4 atoms
- 2.24** $3.00 \times 10^{16}/\text{cm}^3$, $3.33 \times 10^5/\text{cm}^3$
- 2.28** $2 \times 10^{17}/\text{cm}^3$, $500/\text{cm}^3$, $2 \times 10^{17}/\text{cm}^3$, $0.0227/\text{cm}^3$
- 2.30** $3 \times 10^{17}/\text{cm}^3$, $333/\text{cm}^3$
- 2.32** $10^2/\text{cm}^3$, $10^{18}/\text{cm}^3$, $350\text{cm}^2/\text{V}\cdot\text{s}$, $150\text{cm}^2/\text{V}\cdot\text{s}$, $0.042 \Omega\cdot\text{cm}$, *p*-type
- 2.34** $10^{16}/\text{cm}^3$, $10^4/\text{cm}^3$, $710\text{cm}^2/\text{V}\cdot\text{s}$, $260\text{cm}^2/\text{V}\cdot\text{s}$, $2.40 \Omega\cdot\text{cm}$, *p*-type
- 2.38** $2.5 \times 10^{15}/\text{cm}^3$
- 2.40** Yes—add equal amounts of donor and acceptor impurities. Then $n = n_i = p$, but the mobilities are reduced. See Prob. 2.26.
- 2.42** $1.4 \times 10^{17}/\text{cm}^3$
- 2.44** 6.64 mV, 12.9 mV, 25.9 mV
- 2.46** $-12.0 \times 10^3 \exp(-5000x)$ A/cm²; -1.20 mA
- 2.48** (b) -553 A/cm², -603 A/cm², +20 A/cm², -7 A/cm², +46.7 A/cm², -638 A/cm²
- 2.50** 1.108 μm

Chapter 3

- 3.1** $10^{18}/\text{cm}^2$, $10^2/\text{cm}^3$, $10^{15}/\text{cm}^3$, $10^5/\text{cm}^3$, 0.748 V, 0.984 μm
- 3.3** 0.806 V, 1.02 μm , 1.02 μm , $1.02 \times 10^{-4} \mu\text{m}$, 15.8 kV/cm
- 3.6** 1.80 V, 3.06 μm
- 3.10** 1600 A/cm²
- 3.13** $5 \times 10^{20}/\text{cm}^4$
- 3.17** 290 K
- 3.20** 312K
- 3.21** 1.39, 3.17 pA
- 3.22** 0.748 V; 0.691 V; 0 A; -0.909×10^{-17} A; -1.00×10^{-17} A
- 3.25** 1.35 V; 1.38 V
- 3.28** 0.518 V; 0.633 V
- 3.31** 0.757 V; 0.721 V
- 3.34** -1.96 mV/K
- 3.37** 0.576 V, 2.74 μm , 11.7 μm , 36.2 μm
- 3.39** 374 V

- 3.41** 4 V, 0 Ω
- 3.43** 9.80 nF/cm²; 37.6 pF
- 3.45** 400 fF, 10 fC; 100 pF, 2.5 pC
- 3.49** 13.9 MHz; 21.9 MHz
- 3.51** 0.495 V, 0.725 V
- 3.53** 0.708 V, 0.718 V
- 3.56** Load line: (450 μ A, 0.500 V); SPICE: (443 μ A, 0.575 V)
- 3.59** (0.600 mA, -4 V)
- 3.65** Load line: (51 μ A, 0.49 V); Mathematical model: (49.93 μ A, 0.5007 V); Ideal diode model: (100 μ A, 0 V); CVD model: (40.0 μ A, 0.600 V)
- 3.69** (a) (0.500 mA, 0 V); (0.465 mA, 0.700 V)
- 3.71** (a) (-6.67 V, 0 A), (0 V, 1.67 mA); (-6.15 V, 0 A), (0.75 V, 1.62 mA)
- 3.73** (a) (1.00 mA, 0 V) (0 mA, -2 V) (1.00 mA, 0) (d) (0 A, -0.667 V) (0 mA, -1.33 V) (0.567 mA, 0 V)
- 3.76** (1.50 mA, 0 V) (0 A, -5 V) (1.00 mA, 0)
- 3.78** (I_Z , V_Z) = (343 μ A, 4.00 V)
- 3.81** 12.6 mW
- 3.83** 0.501 W, 3.50 W
- 3.88** 0.975 (V_P – V_{on})
- 3.91** -7.91 V; 1.05 F; 17.8 V; 3530 A; 841 A ($\Delta T = 0.628$ ms)
- 3.94** -7.91V, 0.158 F, 17.8 V, 3540 A, 839 A
- 3.97** 3.33 F; 12 V; 4.24 V; 1540 A; 7530 A
- 3.100** 7.91 V; 0.527 F; 16.8 V; 210 A; 1770 A
- 3.103** 417 μ F, 2000 V, 1414 V, 0.375 ms, 314 A
- 3.107** 417 μ F; 4000 V; 1410 V; 44.4 A; 314 A
- 3.114** $\delta = 2/3$; $C = 74.1 \mu$ F \rightarrow 82 μ F; $L = 1.48$ mH \rightarrow 1.5 mH
- 3.117** $V_O = \frac{V_S}{1 - \delta} - V_{on}$; 6.75 V; 37.5 mV; 44.4 mA
- 3.118** $\eta = \frac{100\%}{1 + (1 - \delta) \frac{V_{on}}{V_S}}$; 96.4%;
- $$\eta = \frac{100\%}{1 + (1 - \delta) \frac{V_{onD}}{V_S} + \delta \frac{V_{onS}}{V_S}}$$
- 3.121** $\delta = 0.300$; $C = 2.08 \mu$ F \rightarrow 2.2 μ F; $L = 7.00$ mH \rightarrow 6.8 mH
- 3.124** $V_O = V_S\delta - V_{on}(1 - \delta)$; 4.63 V; 116 mV; 46.3 mA; slightly reduced output voltage, <50 percent of ripple voltage and current
- 3.137** Slopes: 0, +0.5, 0.667; breakpoints: -2 V, 0 V
- 3.140** Slopes: +0.25, +0.5, +0.25, 0; breakpoints: 0 V, 2 V, 4 V

- 3.142** 5 mA, 4.4 mA, 3.6 mA, 8.6 ns
3.146 (0.969 A, 0.777 V); 0.753 W; 1 A, 0.864 V
3.148 1.11 μ m, 0.875 μ m; far infrared, near infrared

Chapter 4

- 4.3** 10.5×10^{-9} F/cm²
4.4 34.5 μ A/V², 86.3 μ A/V², 173 μ A/V², 345 μ A/V²
4.8 (a) 4.00 mA/V² (b) 4.00 mA/V², 8.00 mA/V²
4.11 208 μ A; -218 μ A
4.15 93.0 Ω ; 148 Ω
4.18 450 μ A/V²
4.20 13.6 A/V²
4.22 125 μ A/V²; 1.5 V; enhancement mode; 5/1
4.26 57.5 μ A, linear region; 195 μ A, saturation region; 0 A, cutoff
4.27 saturation; cutoff; saturation; linear; linear; saturation
4.34 1.72 mA; 1.56 mA
4.37 2.26 mA, 4.52 mA, 2.48 mA
4.38 6.00 mA; 6.00 mA (our linear region model does not contain λ)
4.41 97.9 μ A; 98.1 μ A
4.44 31.5 μ A; 28.8 μ A
4.46 4.85 V
4.48 13.8 μ A/V²; 34.5 μ A/V²; 69.0 μ A/V², 138 μ A/V²
4.51 5.00 μ A; 9.00 μ A; 0.550 μ A; 4.10 μ A
4.54 235 Ω ; 94.1 Ω ; 250/1
4.57 0.629 A/V²
4.60 0.360 μ A
4.62 $V_{TN} > 0$; depletion mode; no
4.71 1.73×10^{-7} F/cm²; 4.32 fF
4.74 8.63 nF
4.81 (390 μ A, 1.1 V); triode region
4.84 (70.2 μ A, 9.47 V)
4.86 (42.3 μ A, 9.00 V)
4.91 134 μ A; 116 μ A
4.94 510 k Ω , 470 k Ω , 12 k Ω , 12 k Ω 20/1
4.97 (124 μ A, 2.36 V)
4.100 (32.5 μ A, 1.26 V)
4.103 (23.0 μ A, 1.12 V)

- 4.107** (58.3 μ A, 9.20 V)
4.111 (227 μ A, 3.18 V)
4.112 4.52 mA; 10.8 mA
4.114 (9/10) = 1.11/1
4.116 (a) (124 μ A, 5.70 V) (b) (182 μ A, 1.34 V)
4.118 4.04 V, 2.71 mA, 10.8 mA
4.119 3.61 mA; 6.77 mA; 2.61 mA
4.121 (59.8 μ A, 6.03 V), 138 k Ω
4.126 (a) (98.4 μ A, 2.15 V)
4.130 341 k Ω
4.133 (200 μ A, 13 V)
4.137 (36.3 μ A, 12.9 mV); (31.7 μ A, 1.54 V); (28.2 μ A, 2.69 V)
4.140 44.3 k Ω , V \geq 5 V
4.143 1.52 V, 0.77 V
4.149 34.5 fF, 17.3 ff
4.154 (500 μ A, 5.00 V); (79.9 μ A, 0.250 V); (159 μ A, 3.70 V)
4.156 2.50 k Ω ; 10.0 k Ω
4.157 0.5 mA, 0, 1.17 V; 1.38 mA, 0.62 mA, -0.7 V
4.160 (69.5 μ A, 3.52 V); (131 μ A, 3.52 V)
4.162 (69.5 μ A, 5.05 V); (456 μ A, 6.20 V))

Chapter 5

- 5.4** 0.0167, 0.667, 3.00, 0.909, 49.0, 0.9950, 0.9990, 5000
5.5 2 fA; 1.01 fA, -0.115 V
5.9 2.02 fA
5.11 1.07 mA; -1.07 mA
5.14 0.599 V
5.17 0.606 V
5.20 723 μ A
5.20 723 μ A
5.28 979 μ A, 930 μ A, 48.9 μ A
5.35 saturation, forward-active region, reverse-active region, cutoff
5.39 83.3, 87.5, 100
5.46 21.5 mV, 25.8 mV, 30.2 mV
5.48 2.31 mA; 388 μ A; 0
5.52 12 fF; 1.2 pF; 120 pF
5.54 600 MHz, 3 MHz

- 5.56** 0.282 μm
- 5.59** $I_C = 16.3 \text{ pA}$, $I_E = 17.1 \text{ pA}$, $I_B = 0.857 \text{ pA}$, forward-active region; although I_C , I_E , I_B are all very small, the Transport model still yields $I_C \approx \beta_F I_B$
- 5.61** 50, 1.73 fA
- 5.63** 6.25 MHz
- 5.65** 0.500, 17.3 aA
- 5.67** $-23.7 \mu\text{A}$, $+31.6 \mu\text{A}$, $-55.3 \mu\text{A}$
- 5.69** v_{ECSAT} is identical to Eq. (5.46)
- 5.73** 0.812 V, 0.730 V
- 5.75** 71.7, 43.1 V
- 5.77** 100 μA , 4.52 μA , 95.5 μA , 0.589 V, 0.593 V, 0.592 V; 2.19 mA, 0.100 mA, 2.09 mA, 0.666 V, 0.666 V
- 5.82** (80.9 μA , 3.80 V); (404 μA , 3.80 V)
- 5.86** (42.2 μA , 4.39 V)
- 5.92** (7.8 mA, 4.1 V)
- 5.94** (5.0 mA, 1.3 V)
- 5.96** $56 \text{ k}\Omega$ (or $62 \text{ k}\Omega$), $1.5 \text{ M}\Omega$; 12.4 μA , 0.799 V
- 5.100** 101 μA , 98.4 μA
- 5.107** 5.24 V
- 5.109** 3.21 Ω
- 5.112** 60.7 μA , 86.0 μA , 4.00 V, 5.95 V
- 5.116** 4.4 percent; 70 percent
- 5.118** 4.74 mA, 9.71 mA, 1.28 V, 3.73 V

Chapter 6

- 6.1** 10 $\mu\text{W/gate}$, 2 μA
- 6.3** 5 V, 0 V, 0 W, 0.25 mW; 3.3 V, 0 V, 0 V, 0.11 mW
- 6.5** $V_{OL} = 0 \text{ V}$, $V_{OH} = 3.3 \text{ V}$, $V_{REF} = 1.1 \text{ V}$; $Z = A$
- 6.7** 3 V, 0 V, 2 V, 1 V, -3
- 6.9** 2 V, 2 V, 3 V, 2 V
- 6.11** 3.3 V, 0 V, 1.8 V, 1.5 V, 1.5 V, 1.5 V
- 6.13** -0.78 V, -1.36 V
- 6.15** 1 ns
- 6.17** 5 μW , 1.52 μA , 5 fJ
- 6.19** 2.20 RC ; 2.20 RC
- 6.21** -0.78 V, -1.36 V, 0.5 ns, 0.5 ns, 8 ns, 9 ns, 4 ns, 4 ns
- 6.24** $Z = 0\ 0\ 0\ 1\ 0\ 0\ 1\ 1$
- 6.26** $Z = 0\ 1\ 0\ 1\ 0\ 1\ 0\ 1$

- 6.29** 2; 1
- 6.31** $Z = AB; Z = A + B$
- 6.33** 16.2
- 6.35** $Y = \overline{ABC}$
- 6.37** $V_{\text{REF}} = 2.8 \text{ V}$
- 6.41** 0.583 pF
- 6.44** 20 $\mu\text{W}/\text{gate}$, 4 $\mu\text{A}/\text{gate}$
- 6.49** 0.984 V, 3.13 V
- 6.53** 40.3 k Ω ; 4.90/1; 1.47 V, 0.653 V
- 6.56** 1000 Ω ; 2500 Ω ; a resistive channel exists connecting the source and drain; 20/1
- 6.59** 1.83 V
- 6.62** 0.774 V, 0.610 V
- 6.66** 3.74/1, 1/1.41
- 6.69** 0.190 V
- 6.71** ratioed logic so $V_{OH} = 3.39 \text{ V}$, $V_{OL} = 0.25 \text{ V}$; $P = 0.18 \text{ mW}$
- 6.77** 6.80 V
- 6.81** 1.89
- 6.83** 4.90/1, 1/1.41, 0.777 V, 1.36 V
- 6.85** 2.33/1, 1/1.55
- 6.90** 3.53/1, 1/3.39
- 6.94** $Y = \overline{(A + B)(C + D)(E + F)}$, 6.18/1, 1/2.15
- 6.98** $Y = \overline{ACE + ACDF + BF + BDE}$, 1.40/1, 24.7/1, 16.5/1
- 6.101** 1/4.30, 3.09/1
- 6.104** $Y = \overline{(C + E)[A(B + D) + G] + F}$; 1/1.08, 4.12/1, 6.18/1, 12.4/1
- 6.107** 3.15/1, 6.06/1, 6.24/1, 6.42/1
- 6.110.** +5 V, 0.163 V
- 6.113** 1.85/1, 8.24/1, 12.4/1, 24.8/1
- 6.118** $I'_{DS} = 2I_{DS}$, $P'_D = 2P_D$
- 6.121** 1 ns
- 6.123** 60.2 ns, a potentially stable state exists with no oscillation
- 6.124** 105 ns, 6.23 ns, 17.9 ns
- 6.128** 192 ns, 4.44 ns, 11.8 ns
- 6.136** 2.63/1, 25.3/1, 13.6 ns, 2.07 ns
- 6.142** (a) 1/3.39 (d) 1/9.20 (f) 1/2.25
- 6.146** -4.00 V, -0.300 V
- 6.148** 1.28/1, 7.09/1
- 6.150** 1.61 V, 4.68 V

6.152 $Y = \overline{A + B}$

Chapter 7

7.1 $27.7 \mu\text{A}/\text{V}^2; 11.1 \mu\text{A}/\text{V}^2$

7.3 $250 \text{ pA}; 450 \text{ pA}; 450 \text{ pA}$

7.6 $3.3 \text{ V}, 0 \text{ V}$

7.8 cut off, triode, triode, triode, saturation, saturation

7.11 $2.5 \text{ V}; 2.16 \text{ V}$

7.13 $2.1628 \text{ V}, 2.16 \text{ V}$

7.15 $27.0/1, 1/1.17$

7.17 $2.57 \text{ V}, 1.70 \text{ V}; 1.69 \text{ V}, 1.17 \text{ V}$

7.21 $1.61 \text{ ns}, 3.22 \text{ ns}$

7.23 $2.18 \text{ ns}, 4.36 \text{ ns}$

7.25 $4.33/1, 10.8/1$

7.27 $7.11/1, 17.8/1$

7.29 $2.2 \text{ ns}, 2.3 \text{ ns}, 1.2 \text{ ns}, 1.1 \text{ ns}, \langle C \rangle = 177 \text{ fF}$

7.31 $2 \mu\text{W/gate}, 16.0 \text{ fF}, 36.7 \text{ fF}$

7.34 $4 \text{ W}; 1.74 \text{ W}$

7.36 $22.6 \mu\text{A}; 2.25 \mu\text{A}$

7.41 $\alpha\Delta T, \alpha^2 P, \alpha^3 PDP$

7.46 $5/1, 8/1; 15/1, 24/1$

7.50 $3.2/1, 2/1$

7.56 $8.13 \text{ ns}, 8.13 \text{ ns}, 8.13 \text{ ns}$

7.57 (a) 5 transistors

7.59 $Y = \overline{(A + B)(C + D)E} = \overline{ACE + ADE + BDE + BCE}, 15/1, 18/1, 30/1$

7.61 $4/1, 15/1$

7.63 $4/1, 6/1, 10/1$

7.65 $20/1, 24/1, 40/1$

7.72 $11.1 \text{ ns}, 2.6 \text{ ns}$

7.74 $19.5 \text{ ns}, 48.8 \text{ ns}$

7.79 $V_{DD} \rightarrow \frac{2}{3}V_{DD} \rightarrow \frac{1}{2}V_{DD}; R \geq \frac{2V_{IH}}{V_{DD} - V_{IH}} = \frac{2V_{IH}}{NM_H}, C_1 \geq 2.88C_2$

7.85 $N = 6, A = 462 \text{ A}_o$

7.87 $500 \Omega, 1250 \Omega$

7.89 $\approx 160/1$

$$7.94 \quad N_{ML} = \frac{V_{DD} + 3V_{TN} + V_{TP}}{4} \quad | \quad N_{MH} = \frac{V_{DD} - V_{TN} - 3V_{TP}}{4}$$

Chapter 8

- 8.1.** 268,435,456 ; 1,073,741,824
8.2. 3.73 pA
8.5 2.67 μ V
8.10. “1” level is discharged by junction leakage current
8.12. –19.8 mV; 2.48 V
8.16. 1.60 V, +5.00 V; –1.83 V
8.18 58.5 mW
8.21. 361 μ A, 1.85 W
8.23. 0.266 V
8.24. 0.95 V
8.31. 11,304; 11,304
8.35. $V_{DD} \rightarrow \frac{2}{3}V_{DD} \rightarrow \frac{1}{2}V_{DD}; R \geq \frac{2V_{IH}}{V_{DD} - V_{IH}} = \frac{2V_{IH}}{NM_H}$
8.37. $W_3 = 00101011_2$
8.42. 1.16/1

Chapter 9

- 9.1** 1.38 V, 1.12
9.3 –1.75 V, 0 V
9.5 –1.0 V, –1.4 V, –1.2 V, 132 mV, 10.4 mW
9.9 –0.700 V, –1.70 V, –1.20 V, 1.00 V
9.11 –0.700 V, –1.50 V, –1.10 V, 2.67 k Ω ; 0.314 V, –0.100 V, +0.300 V
9.12 53.3 μ A
9.15 4.20 k Ω , 1.17 k Ω , 200 Ω , 185 Ω
9.17 0.324 V
9.21 0.340 V
9.23 50.0 μ A, –2.30 V
9.25 9.25 k Ω , 10.0 k Ω , 58.5 k Ω , 210 k Ω
9.28 +0.600 V, –0.560 V, 314 Ω
9.31 5.15 mA
9.34 0.13 mA
9.38 500 Ω , 60.0 mA
9.40 (c) 0 V, –0.7 V, 3.93 mA (d) –3.7 V, 0.982 mA (e) 2920 Ω

- 9.43** $Y = A + \overline{B}$
- 9.47** -0.892 V; -1.14 V
- 9.51** -1.00 V; -0.974 V; -0.948 V; -0.922 V
- 9.55** 23.2 μ A
- 9.57** -0.850 V; 3.59 pJ
- 9.59** 0 V, -0.600 V, 5.67 mW; $Y = A + B + C$, $Y = \overline{A + B + C}$, 5 vs. 6
- 9.62** 5.00 k Ω , 5.40 k Ω , 31.6 k Ω , 113 k Ω
- 9.65** 2.23 k Ω , 4.84 k Ω , 120 k Ω
- 9.67** 2.98 pA, 74.5 fA
- 9.69** 160; 0.976; 5; 0.773 V
- 9.70** 0.691 V, 0.710 V
- 9.75** 40.2 mV, 0.617 mV
- 9.77** 3 V, 0.15 V, 0.66 V, 0.80 V, 33
- 9.79** 0.682 V, 2.47 mA
- 9.83** 44.8 k Ω , 22.4 k Ω
- 9.85** 5 V, 0.15 V, 0; -1.06 mA, 31; -1.06 mA vs. -1.01 mA, 0 mA vs. 0.2 mA
- 9.93** 8
- 9.95** 234 mA, 34.9 mA
- 9.99** (I_B , I_C): (a) (135 μ A, -169 μ A); (515 μ A, 0); (169 μ A, 506 μ A); (0, 0) (b) all 0 except $I_{B1} = I_{E1} = 203 \mu$ A
- 9.105** 1.85 V, 0.15 V; 62.5 μ A, -650 μ A; 13
- 9.107** $Y = \overline{ABC}$; 1.9 V; 0.15 V; 0, -408 μ A
- 9.109** 1.5 V, 0.25 V; 0, -1.00 mA; 16
- 9.111** 963 μ A, 963 μ A, 0
- 9.116** (I_B , I_C): (532 μ A, 0); (0, 0); (0, 0); (3.75 μ A, 150 μ A)
- 9.120** $Y = A + B + C$; 0 V, -1.0 V; -0.90 V
- 9.121** $Y = A + B + C$; 0 V, -0.80 V; -0.40 V

Chapter 10

10.3 Using MATLAB:

```
t = linspace(0,.004);
vs = sin(1000*pi*t)+0.333*sin(3000*pi*t)+0.200*sin(5000*pi*t);
vo= 2*sin(1000*pi*t+pi/6)+sin(3000*pi*t+pi/6)+sin(5000*pi*t+pi/6); plot(t,vs,t,vo)par
500 Hz: 1 0°, 1500 Hz: 0.333 0°, 2500 Hz: 0.200 0°; 2 30°, 1 30°, 1 30° 2 30°, 3 30°, 5 30° yes
10.5 35.0 dB, 111 dB, 73.2 dB
10.8 12.7,  $2.00 \times 10^5$ ,  $1.59 \times 10^4$ 
10.12 -10 (20 dB), 0.1 V
```

10.14 $8 -\sin(1000t)$; there are only two components; dc: 8 V, 159 Hz: -4 V

$$\left(g_{12} - \frac{g_{11}g_{22}}{g_{21}}\right)^{-1} \rightarrow -\frac{g_{21}}{g_{11}g_{22}}; \left(g_{22} - \frac{g_{21}g_{12}}{g_{11}}\right)^{-1} \rightarrow \frac{1}{g_{22}};$$

10.17 11.2%

10.21 $10 \text{ k}\Omega$, 1, -101, $4.17 \mu\text{S}$

10.23 $24.3 \text{ M}\Omega$, $240 \text{ k}\Omega$, $24.2 \text{ M}\Omega$, $240 \text{ k}\Omega$

10.26 $102 \text{ k}\Omega$, 0.0164, 98.3, $16.4 \mu\text{S}$

10.28 $3.50 \text{ k}\Omega$, $1.00 \text{ k}\Omega$, -6.00 $\text{M}\Omega$, $61.0 \text{ k}\Omega$

10.30 1 mS , -1, 2001, $20 \text{ k}\Omega$

10.32 0.101 S , $50.0 \mu\text{S}$, -0.100 S , $50.0 \mu\text{S}$

$$\text{10.35 } y_{11} - \frac{y_{12}y_{21}}{y_{22}} \rightarrow y_{11}; \frac{y_{12}}{y_{22}} \rightarrow 0; -\frac{y_{21}}{y_{22}}, \frac{1}{y_{22}}$$

$$\text{10.37 } \left(g_{11} - \frac{g_{12}g_{21}}{g_{22}}\right)^{-1} \rightarrow \frac{1}{g_{11}}; \left(g_{21} - \frac{g_{22}g_{11}}{g_{12}}\right)^{-1} \rightarrow 0;$$

10.41 45.3 mV; 1.00 W

10.45 -8180

10.47 0, ∞ , 125 mW, ∞

10.50 -3.52 dB, 23.9 kHz

10.54 -0.828 dB, 145 Hz

10.57 60 dB, 10 kHz, 10 Hz, 9.99 kHz, band-pass amplifier

10.59 80 dB, ∞ , 50 Hz, ∞ , high-pass amplifier

10.62 28.3 Hz, 100 kHz

10.69 $0.477 \sin(10\pi t + 63.4^\circ) \text{ V}$, $0.999 \sin(1000\pi t - 1.72^\circ) \text{ V}$, $0.477 \sin(10^5\pi t - 78.7^\circ) \text{ V}$

10.71 $0.06 \sin(2\pi t + 88.9^\circ) \text{ V}$, $2.12 \sin(100\pi t + 45.0^\circ) \text{ V}$, $3.00 \sin(10^4\pi t + 0.57^\circ) \text{ V}$

$$\text{10.75 } \frac{10^8 \pi}{s + 10^7 \pi}; -\frac{10^8 \pi}{s + 10^7 \pi}$$

10.78 12.8 kHz, -60 dB/decade

10.79 $10 \sin(1000\pi t + 10^\circ) + 3.33 \sin(3000\pi t + 30^\circ) + 3.00 \sin(5000\pi t + 50^\circ) \text{ V}$; Using MATLAB:

```
t = linspace(0,.004);
vs = sin(1000*pi*t)+0.333*sin(3000*pi*t)+0.200*sin(5000*pi*t);
vo = 10*sin(1000*pi*t+pi/18)+3.33*sin(3000*pi*t+3*pi/18)+2.00*sin(5000*pi*t+5*pi/18);
plot(t, 10*vs, t, vo)
```

Chapter 11

11.1 79.9 dB, 120 dB, 89.9 dB; 5.05 mV

11.3 $\geq 4.95 \text{ M}\Omega$

- 11.5** 0.100 mV, 140 dB
- 11.7** (a) -46.8, 4.7 kΩ, 0, 33.4 dB
- 11.10** 83.9, ∞, 0, 83.9 dB
- 11.13** $(0.510 \sin 3770t - 1.02 \sin 10000t)$ V, 0
- 11.15** -10, 110 kΩ, 10 kΩ
- 11.18** -12, $(-6 + 1.2\sin 4000\pi t)$ V
- 11.22** (a) 79.6 pF (b) 82 pF, 19.4 kHz
- 11.26** -5.00, 20.0 kΩ; +6.00, 47.0 kΩ, 0, 36.0 kΩ (not a useful circuit)
- 11.30** 0.484 A; 0.730 V; 0.730 V; ≥ 7.03 W (choose 10 W), 7.27 W
- 11.33** $\frac{v_1 - v_2}{R}$; ∞; $R(1 + A)$
- 11.35** 3.99 V, 3.99 V, 1.99 V, 1.99 V, 3.99 V, 199 μA; -5 MΩ
- 11.37** 3.6 kΩ, 49.6 kΩ
- 11.39** -1.20 V; -1.80 V; 0 to -3.00 V in 0.20-V steps
- 11.40** A and B taken together, B and C taken together
- 11.43** 48.0, ∞, 0
- 11.47** -100, 8.62 kΩ, 0
- 11.50** 785 MΩ, 3.75 mΩ
- 11.56** Noninverting to achieve R_{IN} with an acceptable value for resistor R_2 : R_{OUT} can be met; R_{IN} is not achievable
- 11.58** -16.2 v_S , 85.9 mΩ
- 11.60** 0.25 percent
- 11.62** 60 dB
- 11.67** $0.500 \sin 5000\pi t$, $10 \sin 120\pi t$; -10, -0.037; 48.6 dB; $-5.00 \sin 5000 \pi t - 0.370 \sin 120\pi t$
- 11.71** -26.0 mV, 0, -26.0 mV, yes, 90.9 kΩ
- 11.74** $A_V = 10,000 [u(v_{ID} + 0.0005) - u(v_{ID} - 0.0015)]$
- 11.76** 10.1 kΩ, 1.00 MΩ
- 11.77** -0.460 V; -0.546 V; -18.7 percent
- 11.79** 10.0 V, 0 V; 15.0 V, 0.125 V
- 11.81** One possibility: 1 kΩ, 20 kΩ
- 11.87** $\left(1 + \frac{R_2}{R_1}\right) \frac{sC(R_1||R_2) + 1}{sCR_2 + 1}$
- 11.89** 3 stages: 1 kΩ, 20 kΩ, 200 pF
- 11.94** $A_V(s) = -\frac{3.653 \times 10^{13}}{s^2 + 3.142 \times 10^7 s + 1.916 \times 10^{12}}$; bode (-3.65e13,[13,142e7 1.916e12])
- 11.97** 20 kΩ, 200 kΩ, 796 pF
- 11.98** -20, 143 kHz; 78.1 dB, 72.9 kHz
- 11.101** Two stages

11.105 6.91, 145 kHz, [6.35, 7.53], [133 kHz, 157 kHz]

11.107 1.89 V/ μ s

11.109 10 V/ μ s

11.110 250 k Ω , 1 k Ω , 2.55 μ F, 8×10^4 , 50 Ω ; add two 10^9 - Ω resistors

11.116 200,000, 10^{12} Ω , 1 k Ω , unspecified, 12.7 μ F

11.118 0.010 μ F, 0.005 μ F, 1.13 k Ω , 20.0 kHz; 0.005 μ F, 0.0025 μ F

Chapter 12

12.1 (a) 0.005 μ F, 0.01 μ F, 1.13k Ω , 1, 20 kHz

12.5 $\frac{K}{s^2 R_1 R_2 C_1 C_2 + s[R_1 C_1(1 - K) + C_2(R_1 + R_2)] + 1}; \frac{K}{3 - K}$

12.7 -1; -1

12.11 1 k Ω , 100 k Ω , 0.0159 μ F

12.13 1 rad/s, 0.0640 rad/s, 15.6; $\left(\frac{20}{s^2 + 0.1s + 1}\right)$

12.15 5.48 kHz, 1.34 kHz, 4.05, 63.1 dB

12.18 0

12.21 (0, T/2): 0 V, (T/2, 3T/2): 1 V, (3T/2, 5T/2): 4 V, (5T/2, 7T/2): 8 V, (7T/2, 9T/2): 12 V, (9T/2, 5T): 15 V

12.24 12.6 kHz, 1.58, 7.96 kHz

12.27 -1.125 V; -1.688 V; $n \times (-0.1875)$ V

12.30 000: 0, 001: 0.1220, 010: 0.2564, 100: 0.5000; 0.0716 LSB, 0.0434 LSB; 0.376 LSB, 0.188 LSB

12.33 1.43 percent, 2.5 percent, 5 percent, 10 percent

12.35 -0.3125 V, -0.6250 V, -1.250 V, -2.500 V

12.37 1.0742 k Ω , 0.188 LSB, 0.094 LSB; 1.2929 k Ω , 0.224 LSB, 0.417 LSB

12.40 (a) $(2^{n+1}-1)C$ (b) $(3n+1)C$

12.43 -2.500 V, -1.875 V, -1.250 V, -0.625 V, 0 V, +0.625 V, 1.250 V, +1.875 V

12.45 (3.415468 V, 3.415781 V)

12.49 0001011111, 95 μ s

12.51 167 ns

12.53 $RC \geq 0.0448$ s; $v_o(200 \text{ ms}) = 22.32$ V

12.55 For $\theta = 0$, $\frac{V_M T_T}{RC} \left(\frac{\sin \omega T_T}{\omega T_T} \right)$

12.57 $-V_1 V_2 / (10^4 I_s)$

12.59 0.759 V

12.60 2.40 Hz

12.65 2.38 V, 2.62 V, 0.240 V

12.67 0.487 V, -0.487 V, 0.974 V

12.70 0 Hz

12.73 841 μ s, 416 μ s

Chapter 13

13.1 $0.700 + 0.005 \sin 2000\pi t$ V; $1.03 \sin 2000\pi t$ V; $5.00 - 1.03 \sin 2000\pi t$ V; 2.82 mA

13.3 Bypass, coupling, coupling; 0 V

13.6 Coupling, coupling (ignore repeated question)

13.9 Coupling, coupling, coupling; 0V

13.12 Coupling, coupling

13.14 (1.78 mA, 6.08 V)

13.16 (98.4 μ A, 4.96 V)

13.20 (82.2 μ A, 6.04 V)

13.24 (307 μ A, 3.88 V)

13.28 (338 μ A, 5.40 V)

13.32 (1.00 mA, 7.50 V)

13.42 Thévenin equivalent source resistance, gate-bias voltage divider, gate-bias voltage divider, source-bias resistor—sets source current, drain-bias resistor—sets drain-source voltage, load resistor

13.45 11.3 μ A, 50 mV

13.48 (188 μ A, $V_{CE} \geq 0.7$ V), 7.52 mS, 532 k Ω

13.51 (1.88 μ A, $V_{CE} \geq 0.7$ V), 75.0 μ S, 53.3 M Ω

13.53 (b) +16.7%, -13.6%

13.54 90, 120; 95, 75

13.58 -120

13.60 Yes, using $I_C R_C = (V_{CC} + V_{CE})/2$

13.62 2.5 mA; 30.7 V

13.64 -314, -314

13.66 -95

13.67 (-95.0, -94.1)

13.71 3

13.74 1.25 A

13.77 10%, 20%

13.80 Virtually any desired Q-point

13.81 (156 μ A, 9 V)

13.87 $400 = 133,000i_P + v_{PK}$; (1.4 mA, 215 V); 1.6 mS, 55.6 k Ω , 89, -62.7

13.88 FET

13.91 111 μ A, 1400

- 13.94** Yes, it is possible although the required value of $V_{GS} - V_{TN}$ (6.70 V) is getting rather large
- 13.97** 0.5 V, (125 μ A, 7.5 V)
- 13.98** 2.5 V, 25 V
- 13.100** 3
- 13.102** -10.9
- 13.105** -7.27
- 13.110** 833 μ A
- 13.112** 33.3 k Ω , 94.4 k Ω
- 13.115** 647 Ω , 3.62 k Ω
- 13.116** (b) 1 M Ω , 0, -7.45 M Ω , 3.53 M Ω
- 13.118** 6.8 M Ω , 45.8 k Ω
- 13.120** 10 M Ω , 508 k Ω
- 13.122** 1 M Ω , 6.82 k Ω
- 13.125** -15.0 v_S , 45.8 k Ω
- 13.129** -60.7, 630 Ω , 960 Ω ; gain reduced by 25 percent due to lower input resistance
- 13.131** 62.9 k Ω , 96.0 k Ω , -64.4
- 13.133** 50 mA/V², 842 k Ω
- 13.139** 1.38 μ W, 0.581 mW, 0.960 mW, 0.887 mW, 2.43 mW
- 13.143** 0.497 mW, 0.554 mW, 2.07 mW, 24.6 μ W, 24.6 μ W, 5.58 mW
- 13.146** $V_{CC}/15$
- 13.147** 3.38 V, 13.6 V
- 13.150** 32.9 μ A, 2.30 V
- 13.152** 356 μ A, 2.02 V
- 13.153** 500 μ A, 1.76 V

Chapter 14

- 14.1** (a) C-C, (b) not useful, (h) C-B, (o) C-D
- 14.8** -5.00, ∞ , 20.0 k Ω , ∞ ; -10.0, ∞ , 10.0 k Ω , ∞
- 14.10** (a) -6.91 (e) -120
- 14.11** 6.58 k Ω , 66.7 k Ω
- 14.16** -120, -60.9, 2.83 k Ω , 8.20 k Ω , 6.76 mV
- 14.17** -14.7, -11.6, 368 k Ω , 75 k Ω , 183 mV
- 14.19** -3.07, 84.9, 1.00 M Ω , 39.0 k Ω , 1.49 V
- 14.24** 0.909, ∞ , 100 Ω , ∞
- 14.27** 0.982, 1.29, 31.6 k Ω , 9.19 Ω , 2.83 V
- 14.28** 0.956, 969, 1.00 M Ω , 555 Ω , 628 V
- 14.30** (0.005 + 0.2 V_{R4}) V

- 14.33** 48.8, 2.00 k Ω , ∞ , 1; 14.3, 2.00 k Ω , ∞ , 1
- 14.34** 48.8, 1.98 k Ω , 4.92 M Ω , 1; 23.7, 1.98 k Ω , 10.1 M Ω , 1
- 14.38** 5.51, 0.178, 2.73 k Ω , 24.0 k Ω , 0.398 V
- 14.39** 36.5, 0.274, 252 Ω , 39.0 k Ω , 14.9 mV
- 14.43** 44.5 Ω
- 14.45** 632 Ω
- 14.47** $(\beta_o + 1)r_o = 153 \text{ M}\Omega$
- 14.48** $A_v = 398$ with $R_{in} = 1 \text{ M}\Omega$: A C-E amplifier operating at low current should be able to achieve both high A_v and high R_{in} . It would be difficult to achieve $A_V = 52 \text{ dB}$ with an FET stage.
- 14.51** A follower has a gain of approximately 0 dB. The input resistance of a C-C amplifier is approximately $(\beta_o + 1)R_L \approx 101(10 \text{ k}\Omega) = 1 \text{ M}\Omega$. Therefore a C-D stage would be preferred to achieve the gain of approximately 1 with $R_{in} = 25 \text{ M}\Omega$.
- 14.52** A noninverting amplifier is needed. Either the C-B or C-G amplifier should be able to achieve $A_V = +10$ with $R_{in} = 2 \text{ k}\Omega$ with proper choice of the Q-point.
- 14.55** 1.66 Ω
- 14.59** $\mu_f v_s, R_5 + r_o(1 + g_m R_5) \cong r_o(1 + g_m R_5)$
- 14.61** $v_s, (R_{th} + r_\pi)/(1 + \beta_o)$
- 14.63** (a) $z_{21} = R_B \frac{(\beta_o + 1)R_E}{r_\pi + (\beta_o + 1)R_E} \cong R_B \quad z_{12} = \frac{R_B R_E}{R_B + r_\pi + (\beta_o + 1)R_E} \cong \frac{R_B}{(\beta_o + 1)} \quad \frac{z_{21}}{z_{12}} \cong \beta_o + 1$
- 14.65** (a) $g_{21} = +g_m R_D \quad g_{12} = \frac{R_D}{R_D + r_o} \cong \frac{R_D}{r_o} \quad \frac{g_{21}}{g_{12}} \cong g_m r_o = \mu_f$
- 14.68** $(1/g_m)(1 + R_L/r_o)$ for $\mu_f \gg 1$
- 14.69** -0.984, 0.993, 0.703 V
- 14.72** SPICE: (106 μA , 7.14 V), -14.2, 369 k Ω , 65.8 k Ω
- 14.74** SPICE: (9.81 μA , 5.74 V), 0.983, 11.0 M Ω , 2.58 k Ω
- 14.78** SPICE: (268 μA , 8.60 V), 4.26, 1.27 k Ω , 18.8 k Ω
- 14.79** SPICE: (5.59 mA, 5.93 V), -3.27, 10.0 M Ω , 1.53 k Ω
- 14.81** SPICE: (3.84 mA, 10.0 V), 0.953, 1.00 M Ω , 504 Ω
- 14.83** (a) 0.01 μF , 270 μF , 0.15 μF , (b) 2.7 μF
- 14.86** (a) 0.50 μF , 0.68 μF
- 14.89** (a) 8200 pF, 820 pF (b) 0.042 μF , 1800 pf, 0.015 μF
- 14.91** 33.3 mA
- 14.93** $R_1 = 120 \text{ k}\Omega, R_2 = 110 \text{ k}\Omega$
- 14.95** The second MOSFET
- 14.97** $A_v^{\max} = 54.8, A_v^{\min} = 44.8$ beyond the Monte Carlo results by approximately 2 percent of nominal gain.

14.101 Voltage is not sufficient—transistor will be saturated.

14.105 95.2, 1000 Ω , ∞ , 1; A_v is 2 \times larger, R_{in} is 2 \times smaller

Chapter 15

15.1 4.12, 1 M Ω , 64.3 Ω

15.2 4.44

15.5 2.19

15.7 711, 8.29 k Ω , 401 Ω

15.10 466, 73.8 k Ω , 20 k Ω

15.16 (a) (5.00 mA, 10.3 V), (1.88 mA, 3.21 V), (2.47 mA, 6.86 V) (b) (5.00 mA, 9.45 V), (2.38 mA, 0.108 V), (3.15 mA, 4.60 V) Q_2 is saturated! The circuit will no longer function properly as an amplifier.

15.17 (a) (325 μ A, 7.14 V), (184 μ A, 7.85 V), 86.1 dB

15.20 (a) (50.0 μ A, 1.58 V), (215 μ A, 13.2 V), -63.2, 1 M Ω , 1.91 k Ω

15.22 (a) (223 μ A, 2.87 V), (1.96 mA, 5.00 V), -218, 7.61 k Ω , 241 Ω (b) -1.49, 75.6 k Ω

15.25 (a) (4.44 μ A, 1.40 V), (23.3 μ A, 2.30 V) (b) (4.08 μ A, 1.42 V), (23.6 μ A, 2.28 V)

15.35 $I_{C2} = \beta_F I_{C1}$, $g'_m = g_m$, $r'_\pi = \beta_o r_\pi$, $r'_o = \frac{r_o}{2}$, $\beta'_o = \beta_o(\beta_o + 1)$, $\mu'_f = \frac{\mu_f}{2}$

15.38 $I_{C2} = \beta_F I_{C1}$, $g'_m = g_m$, $r'_\pi = \beta_o r_\pi$, $r'_o = r_o \beta'_o$, $\mu'_f = \mu_f$

15.42 (8.52 μ A, 1.42 V), (8.40 μ A, 0.940 V), -48.1, cascode amplifier

15.43 (a) (20.7 μ A, 5.87 V) (b) -273, 243 k Ω , 660 k Ω (c) -0.604, 47.1 dB, 27.3 M Ω

15.46 (a) (8.43 μ A, 1.36 V) (b) -33.7, -1.02 k Ω , ∞ for differential output, 24.4 dB for single-ended output, 594 k Ω , 200 k Ω , 4.90 M Ω , 50 k Ω

15.48 $R_{EE} = 1.1$ M Ω , $R_C = 1.0$ M Ω

15.50 (200 μ A, 4.90 V); differential output: -312, 0, ∞ ; single-ended output: -155, -0.0965, 64.2 dB; 25.0 k Ω , 40.4 M Ω , 78.0 k Ω , 39.0 k Ω

15.54 $V_O = 1.09$ V, $v_o = 0$; $V_O = 1.09$ V, $v_o = 219$ mV; 5.00 mV

15.56 (47.4 μ A, 6.23 V); Differential output: -379, 0, ∞ ; single-ended output: -190, -0.661, 49.2 dB; 158 k Ω , 22.7 M Ω

15.60 -16.1 V, -13.1 V, -3.00 V

15.61 -283, 4.94×10^{-3} , 95.2 dB

15.66 (24.2 μ A, 5.36 V); $A_{dd} = -45.9$, $A_{cc} = -0.738$, differential CMRR = ∞ , single-ended CMRR = 24.7 dB, ∞ , ∞

15.69 (91.3 μ A, 12.9 V); $A_{dd} = -16.7$, $A_{cc} = -0.486$, differential CMRR = ∞ , single-ended CMRR = 25.1 dB, ∞ , ∞

15.74 (150 μ A, 7.60 V); $A_{dd} = -26$, $A_{cc} = -0.233$, differential CMRR = ∞ , single-ended CMRR = 34.9 dB, ∞ , ∞

- 15.77** (142 μA , 7.27 V); $A_{dd} = -21.7$, $A_{cc} = -0.785$, differential CMRR = ∞ , single-ended CMRR = 22.9 dB, ∞ , ∞
- 15.79** (20.0 μA , 6.67 V); $A_{dd} = -26.8$, $A_{cc} = -0.119$, differential CMRR = ∞ , single-ended CMRR = 41.0 dB, ∞ , ∞
- 15.80** -3.08 V, -1.22 V, 62.1 mV
- 15.83** (99.0 μA , 10.8 V); $A_{dd} = -30.1$, $A_{cc} = -0.165$, 553 k Ω
- 15.88** (24.8 μA , 12.0 V), (500 μA , 12.0 V), 1040, 202 k Ω , 20.6 k Ω , 147 M Ω , v_1
- 15.92** (a) (98.8 μA , 14.3 V), (300 μA , 14.3 V) (b) 551, 40.5 k Ω , (c) 49.0 k Ω (d) 34.6 M Ω , (e) v_2
- 15.97** (98.8 μA , 14.3 V), (300 μA , 14.3 V), 27800, 40.5 k Ω
- 15.102** (a) (250 μA , 15.6 V), (500 μA , 15.0 V) (b) 4300, ∞ , 165 k Ω (c) v_2 (d) v_1
- 15.107** (250 μA , 4.92 V), (6.10 μA , 4.30 V), (494 μA , 5.00 V), 4230, ∞ , 97.5 k Ω
- 15.113** (250 μA , 10.9 V), (2.00 mA, 9.84 V), (5.00 mA, 12.0 V), 866, ∞ , 127 Ω
- 15.115** (300 μA , 5.10 V), (500 μA , 2.89 V), (2.00 mA, 5.00 V), 529, ∞ , 341 Ω
- 15.120** (99.0 μA , 5.00 V), (500 μA , 3.41 V), (2.00 mA, 5.00 V), 11400, 50.5 k Ω , 224 Ω
- 15.121** (4.95 μA , 2.36 V), (24.5 μA , 3.07 V), (245 μA , 3.00 V), 249, 1.01 M Ω , 1.63 k Ω , v_B , v_A , 900, r_{π^3} and r_{π^4} are low, R_{INS} is low.
- 15.123** (99.0 μA , 1.40 V), (990 μA , 12.0 V), 189, 50.6 k Ω , 1.06 k Ω
- 15.127** (24.8 μA , 17.3 V), (24.8 μA , 17.3 V), (9.62 μA , 15.9 V), (490 μA , 16.6 V), (49.0 μA , 17.3 V), (4.95 mA, 18.0 V), 88.5 dB, 202 k Ω , 18.1 Ω
- 15.129** 36.8 μA
- 15.131** 196 μA
- 15.135** 22.8 μA
- 15.137** 5 mA, 0 mA, 10 mA, 12.5 percent
- 15.138** 100 percent
- 15.141** 70 mA, 19.6 V
- 15.144** 6.98 mA, 0 mA
- 15.145** 25.0 m Ω
- 15.147** (a) 22.8 μA , 43.9 M Ω
- 15.151** Two of many: 75 k Ω , 62 k Ω , 150 Ω ; 68 k Ω , 12 k Ω , 1 k Ω
- 15.155** 96.7 μA , 16.3 M Ω
- 15.158** 20.2 μA , 101 M Ω
- 15.164** 16.9 μA , 168 M Ω , 5.11 μA , 555 M Ω , 16.9 μA , 168 M Ω
- 15.166** 44.1 μA , 22.1 M Ω , 10.0 μA , 210 M Ω
- 15.170** 100 μA , 657 G Ω
- 15.171** (9.34 μA , 9.03 V), (4.62 μA , 7.62 V), 96.5 dB
- 15.173** $\beta_{o1}\mu_{f1}/2$
- 15.174** 3.16 V

Chapter 16

- 16.1** $4.06 \text{ k}\Omega \leq R \leq 4.31 \text{ k}\Omega$
- 16.4** 19.8 percent, 13.3 percent
- 16.6** 7.69 percent, 0.813 μA , 0.855 μA
- 16.11** 274 μA , 383 $\text{k}\Omega$, 574 μA , 192 $\text{k}\Omega$
- 16.16** (a) 944 μA , 68.9 $\text{k}\Omega$, 1.52 mA, 41.5 $\text{k}\Omega$
- 16.24** 125 μA , 690 μA , 1.31 mA, 600 $\text{k}\Omega$, 100 $\text{k}\Omega$, 66.4 $\text{k}\Omega$
- 16.27** 10
- 16.34** 12.3 μA , 31.3 $\text{M}\Omega$, 29.3 μA , 15.2 $\text{M}\Omega$
- 16.38** 172 $\text{k}\Omega$, 9.78 $\text{k}\Omega$, 0.445
- 16.42** $-V_{EE} + 1.16 \text{ V}$ for $V_{CB3} \geq 0$
- 16.47** $-V_{EE} + 1.91 = -8.09 \text{ V}$
- 16.48** 3.80/1
- 16.50** 17.5 μA , 1.16 $\text{G}\Omega$; 20.3 kV; 2.11 V
- 16.55** 16.9 μA , 163 $\text{M}\Omega$, 2750 V; $2V_{BE} = 1.4 \text{ V}$
- 16.65** 318 μA , 295 μA , 66.5 μA
- 16.68** 187 μA
- 16.72** 46.5 μA , 140 μA
- 16.77** 26.4 μA
- 16.82** 30.7 μA , 15.3 μA
- 16.85** 462 μA , 308 μA
- 16.96** 79.1, 6.28×10^5 , 122 dB
- 16.100** 1200, 0, ∞
- 16.104** (100 μA , 8.70 V), (100 μA , 7.45 V), (100 μA , 2.50 V), (100 μA , 1.25 V), 323, 152
- 16.106** (125 μA , 1.54 V), (125 μA , 2.79 V), (125 μA , 2.50 V), (125 μA , 1.25 V); 19600
- 16.109** 171 μA
- 16.110** (b) 100 μA
- 16.111** (125 μA , 8.63 V), (125 μA , 1.31 V), (125 μA , 10.0 V), (125 μA , 8.71 V), (125 μA , 1.29 V),
(125 μA , 6.00 V), (125 μA , 2.75 V); 43.4; 14,900
- 16.113** 10,800
- 16.118** 6400; 80,000
- 16.119** 7500; 7500
- 16.122** 7.78, 574 Ω , 3.03×10^5 , 60.0 $\text{k}\Omega$
- 16.124** $\pm 1.4 \text{ V}$, $\pm 2.4 \text{ V}$
- 16.127** 271 $\text{k}\Omega$, 255 Ω
- 16.129** $V_{EE} \geq 2.8 \text{ V}$, $V_{CC} \geq 1.4 \text{ V}$; 3.8 V, 1.7 V
- 16.130** 0.406 mS, 2.83 $\text{M}\Omega$

- 16.134** (100 μA , 15.7 V), (50 μA , 12.9 V), (50 μA , 0.700 V), (50 μA , 1.40 V), (50 μA , 29.3 V), (100 μA , 0.700 V), (100 μA , 13.6 V), 1 mS, 752 k Ω

Chapter 17

17.1 $25, \frac{s^2}{(s + 1)(s + 20)}$, yes, $\frac{25s}{(s + 20)}$, 3.18 Hz, 3.19 Hz

17.4 200, $\frac{1}{\left(1 + \frac{s}{10^4}\right)\left(1 + \frac{s}{10^5}\right)}$ yes, 1.59 kHz, 1.58 kHz

17.7 200, $\frac{s^2}{(s + 1)(s + 2)}$, $\frac{1}{\left(1 + \frac{s}{500}\right)\left(1 + \frac{s}{1000}\right)}$, .356 Hz, 71.2 Hz; 0.380 Hz, 66.7 Hz

17.10 (b) -14.1 (23.0 dB), 11.8 Hz

17.12 19.3 dB, 151 Hz; 35.0 dB, 12.6 Hz

17.21 7.24 dB, 19.2 Hz

17.23 0.964, 0.627 Hz

17.24 0.152 μF

17.27 Cannot reach 1 Hz; $f_L = 13.1$ Hz for $C_1 = \infty$, limited by C_3

17.29 0.351 μF

17.31 308 ps

17.34 -100; -107

17.36 0.977; 0.978

17.37 -5100, -98.0, -5000, -100; -350, -42.9, -300, -50

17.40 -98.7, 1.42 MHz

17.46 -129, 1.10 MHz

17.50 $1/10^5 RC$; $1/10^6 RC$; $1/sRC$

17.52 $(2750 - j4.99)$ Ω , $(2730 - j226)$ Ω , $(836 - j1040)$ Ω

17.58 -9.44, 43.9 Hz, 9.02 MHz; 85.1 MHz

17.62 -1300; -92.3; -100, -1200

17.63 9.13, 40.9 MHz

17.66 2.30, 10.9 MHz

17.71 0.964, 114 MHz

17.73 $C_{GD} + C_{GS}/(1 + g_m R_L)$ for $\omega \ll \omega_T$

17.76 99.3 kHz

17.77 48.2 kHz

17.87 4 GHz, 39.8 ps

17.90 781 μA

- 17.91** 8.33 MHz
17.95 10.6 MHz, 33.3 V/ms
17.100 8 V/ μ s
17.104 22.5 MHz, 2.91, -41.1
17.105 20.1 pF, 12.6, $n = 2.81$, 21.9 pF
17.107 15.2 MHz; 27.5 MHz
17.108 13.4 MHz, 7.98, $112/-90^\circ$; 4.74 MHz, 5.21, $46.1/-90^\circ$
17.113 10.9 MHz, 16.4, -75.1; 10.1 MHz, 3.96, -35.4

Chapter 18

- 18.5** $1/(1+A\beta)$; 9.99×10^{-3} percent
18.8 100 dB
18.13 $800 \text{ M}\Omega$; $2.00 \text{ }\Omega$; $20.0 \text{ M}\Omega$; $50 \text{ m}\Omega$
18.15 $18.8 \text{ k}\Omega$, 1.02 mS , -75.0×10^3 , 3141, 0.0993, 10.0; 0.0993 @ 0; 75,000 @ 0.0993
18.17 0.999, 43.9 M Ω , 2.49 Ω , 98.9 ms
18.20 $A\beta/(1 + A\beta)$; 99.9 percent
18.22 -33.0 k Ω ; 8.11 k Ω ; 0.705 Ω
18.23 82.2 Ω ; 46.2 Ω ; -32.4 k Ω ; -32.4
18.24. 36.8 Ω ; 18.6 Ω ; -34.4 k Ω
18.26 0.973, 973 Ω
18.29 -446 k Ω , 50.4 k Ω , 2.45 k Ω
18.31 -11.0, 15.2 Ω , 2.72 M Ω
18.32 21.9 Ω ; 12.3 Ω ; -35.1
18.37 $\beta_o/(\beta_o + 1)$, $2/g_m$, $(\beta_o + 1)r_o$
18.40 58.2 dB
18.43 91.8
18.45 $(s/R_2C_2)/[s^2 + s(1/R_2C_2 + 1 / (R_1||R_2)C_1) + 1/R_1R_2C_1C_2]$
18.50 $T_V = 987$, $T_I = 110$, $T = 98.5$
18.59 114 dB, 0 Hz, 1000 Hz, 0 Hz, 101 kHz
18.62 46.1 kHz, 9.31 Hz, 81.0 kHz, 5.29 Hz
18.69 110 kHz; $A \leq 2000$; larger
18.71 yes, but almost no phase margin; 1.83°
18.73 90.0°
18.75 12° ; yes
18.81 phase margin is undefined; $|T(j\omega)| < 1$ for all ω
18.85 38.4°

18.86 $\omega = 1/RC$, $R_F = 2R$

18.88 63.7 kHz, 6.85 V

18.90 18.4 kHz, 10.7 V

18.95 9.00 MHz, 1.20

18.101 11.2 MHz, 18.1 MHz, 1.00

18.102 15.9155 mH, 15.9155 fF; 10.008 MHz, 10.003 MHz

18.103 9.190 MHz; 9.190 MHz