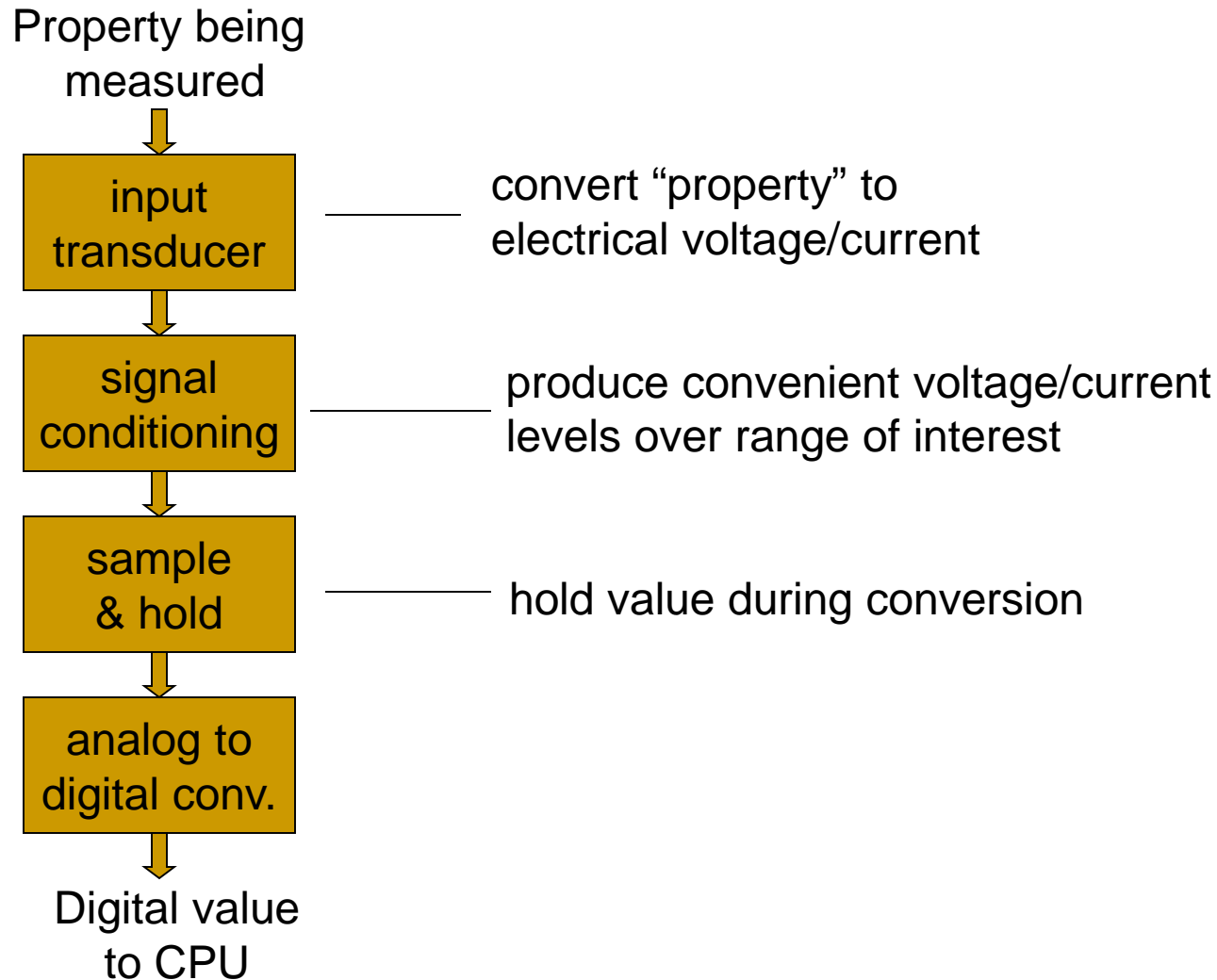

Analog Input/Output Subsystem Design

Reference:


STM32F4xx Reference Manual

(ADC, DAC chapters)


Analog input subsystem



Analog output subsystem

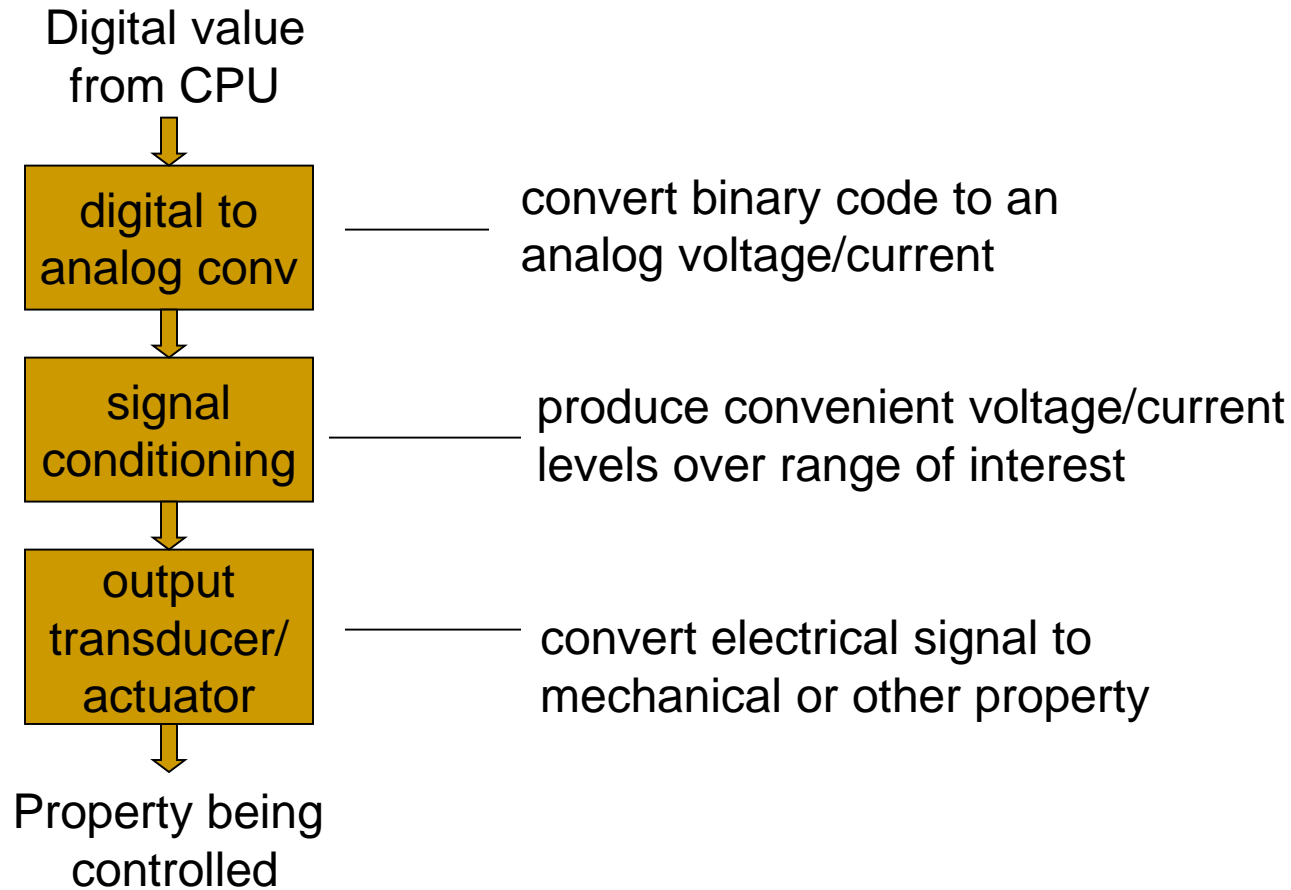

Typical analog input subsystem



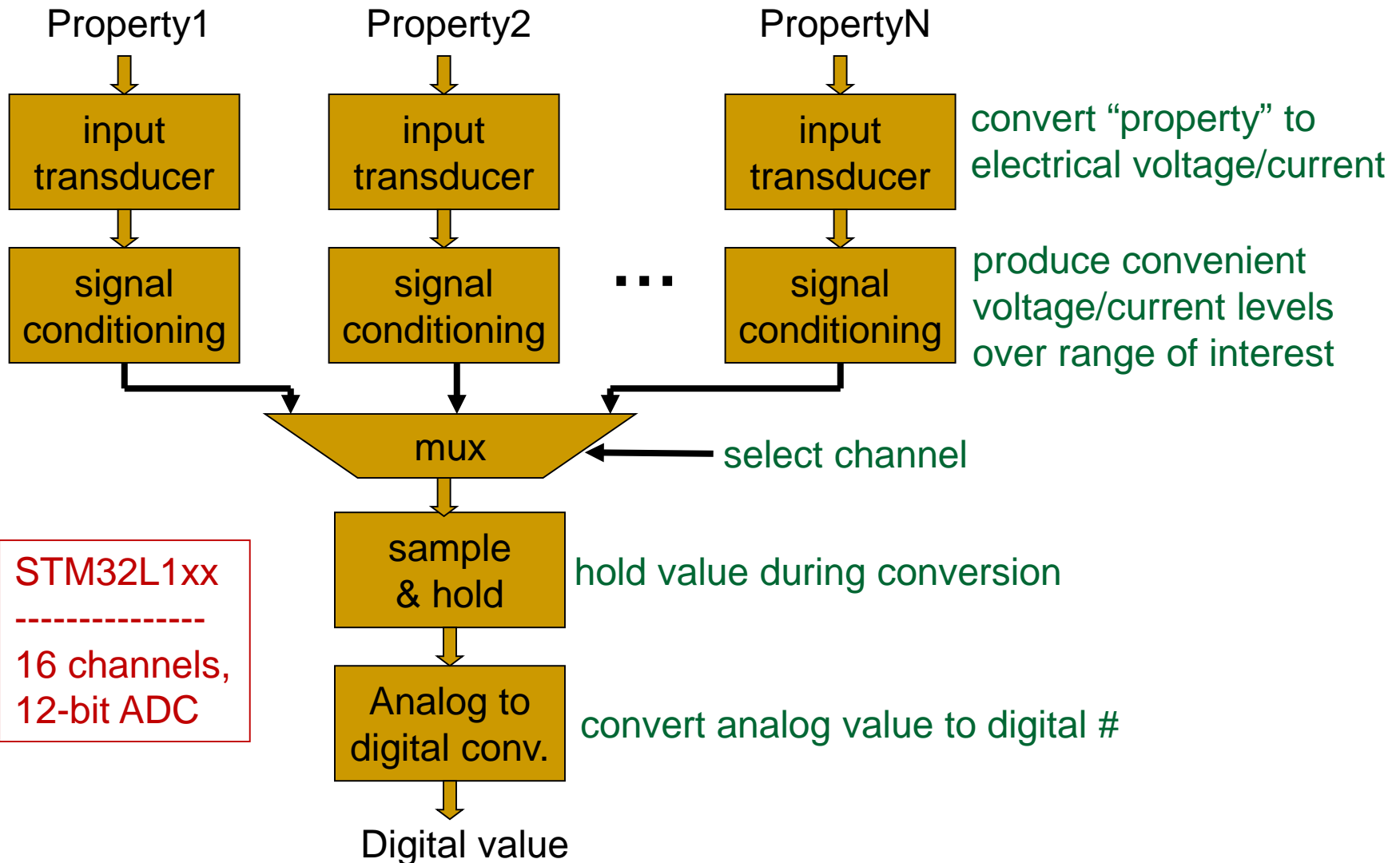


Analog subsystem properties

- Accuracy: degree to which measured value differs from true value
- Resolution/precision: degree to which two conditions can be distinguished
 - Related to #bits in digital value
- Range: minimum to maximum “useful” value
- Linearity: $y = Ax + B$ (correction req'd if not linear)
 - piecewise linear approximation over different ranges
- Repeatability: same measurement for a given value
 - affected by hysteresis or other phenomena
- Stability: value changes other than due to the property being measured (eg. T affecting P)


Analog to digital conversion errors

May need to correct in software

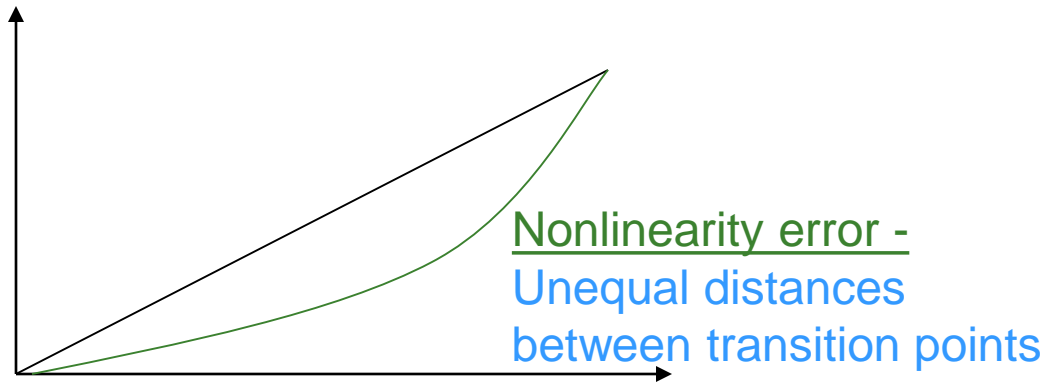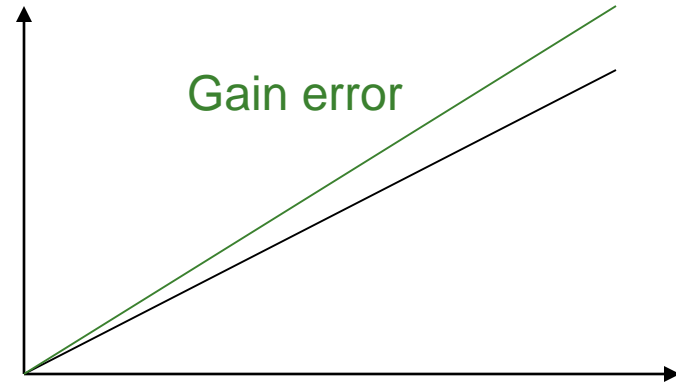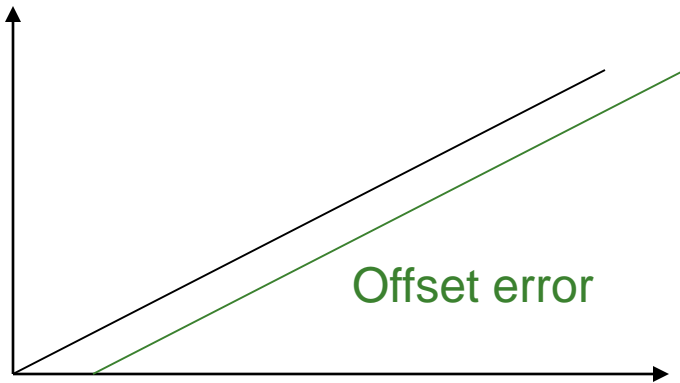

Quantization error:

 Difference between digital
& analog values
Usually want $\pm \frac{1}{2}$ LSB




Transducers

- Convert physical quantity to electrical signal
 - Self-generating – generates voltage/current signal
 - Non-self-generating – other property change (ex. R)
- Examples:
 - Force/stress (strain gage)
 - Temperature (thermocouple, thermistor, semicond.)
 - Pressure
 - Humidity (gypsum block)
 - Smoke
 - Light (phototransistor, photoconductive cell)
 - Acceleration (accelerometer)
 - Flow
 - Position (potentiometer, displacement)

Temperature sensors

 - Thermocouple – “Seeback EMF produced by heating junction of dissimilar metals (μV)



- Thermistor – mix of materials in ceramic

$$R_t = R_0 e^{\beta[1/T - 1/T_0]}$$

- Negative temperature coefficient: $R \wedge$ with $T \vee$
- Linear over small range


- Metal conductor:

$$R_t = R_0 [1 + \alpha(T - T_0)]$$

- Positive temp. coefficient: $R \wedge$ with $T \wedge$

Semiconductor temperature sensor

 
Base-emitter voltage approximately proportional to T



$$V_{BE} = \frac{kT}{q} \ln \left[\frac{I_C}{I_S} \right]$$

$$V_{BE} \propto T$$

 Analog Devices AD590 Temperature Transducer




- IC generates current proportional to temperature
- Generated current I_T is linear: $1 \mu\text{A}/^\circ\text{K}$

Example:


Design a temperature monitor with output in the range [0v..4v] over temperature range [-20°C .. +60°C]

(Use summing amplifier)

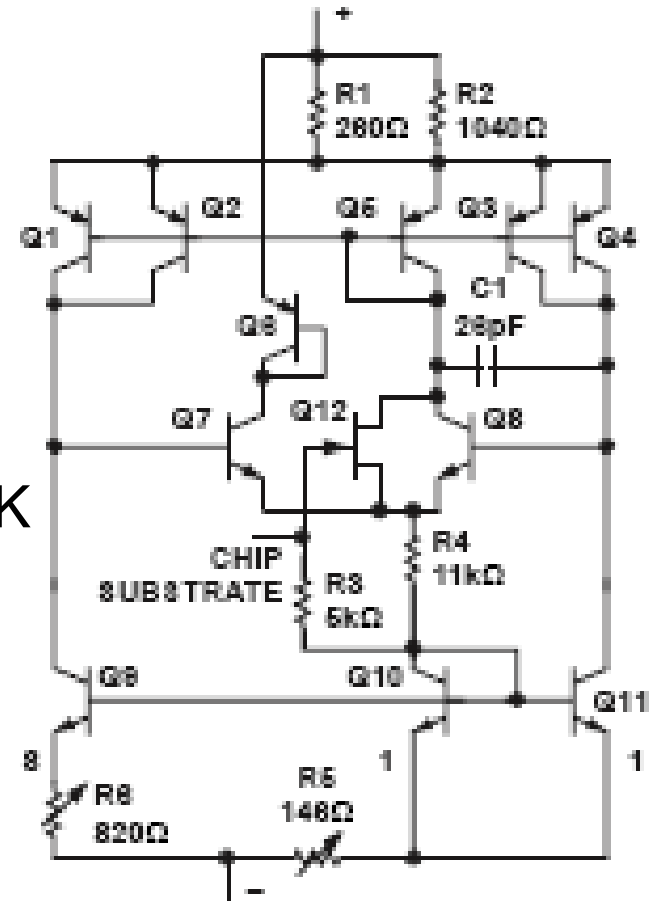

Strain Gage

 - Measure stress by measuring change or resistance of a conductor due to change of its length/area




$$R = \rho \left(\frac{L_0}{A_0} \right)$$

- Compression: L decreases, A increases
- Elongation: L increases, A decreases
- “Gage factor” (sensitivity): $S = \frac{\Delta R / R}{\Delta L / L}$

Wheatstone bridge

- Measure small resistance changes

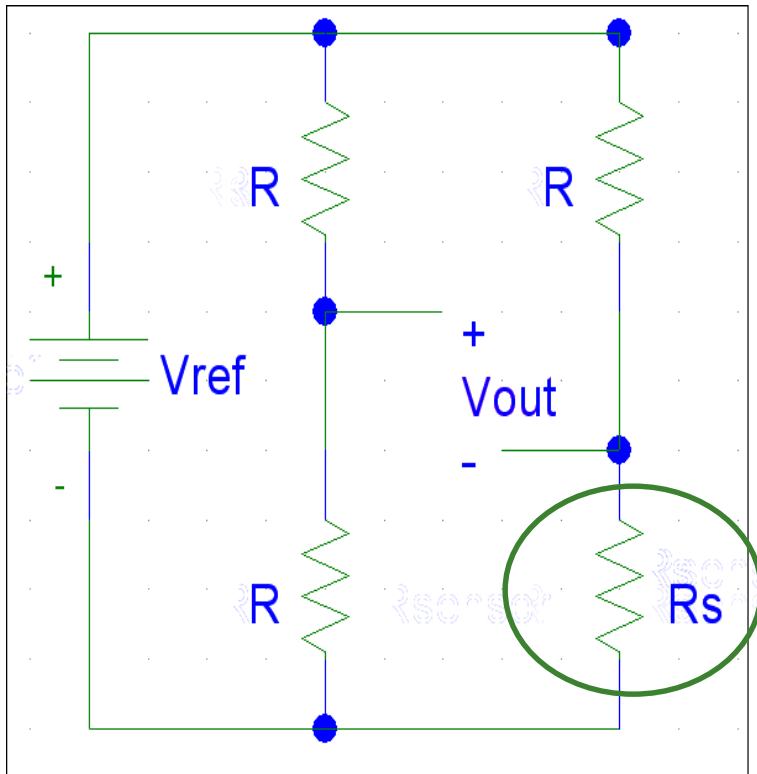

$$V_o = V_{ref} \left(\frac{R}{R + R} \right) - V_{ref} \left(\frac{R_s}{R + R_s} \right)$$
$$= V_{ref} \left[\frac{1}{2} - \frac{R_s}{R + R_s} \right]$$

“Balanced”: $V_o = 0$ when $R = R_s$

Some pressure sensors use bridge with all 4 R's variable

Signal conditioning


- Produce noise-free signal over “working” input range
 - Amplify voltage/current levels
 - Bias (move levels to desired range)
 - Filter to remove noise
 - Isolation/protection (optical/transformer)
 - Common mode rejection for differential signals
 - Convert current source to voltage
 - Conditioning often done with op amp circuits
-

Operational amplifiers

- Amplifier types:
 - Inverting amplifier
 - Non-inverting amplifier
 - Summing amplifier
 - Differential amplifier
 - Instrumentation amplifier
 - Tradeoffs
 - Inverting/noninverting
 - High input impedance
 - Defined gain
 - Common mode rejection
-

Basic op amp configurations


Inverting amplifier

 

$$\frac{V_i}{R1} = -\frac{V_o}{R2}$$

$$\frac{V_o}{V_i} = -\frac{R2}{R1}$$

Noninverting amplifier

 


$$V_i = V_o \left(\frac{R2}{R1 + R2} \right)$$

$$V_o / V_i = \frac{R1 + R2}{R2}$$

Noninverting version has high input impedance

Summing amplifier

 

$$\frac{V1}{R1} + \frac{V2}{R2} = -\frac{Vo}{R3}$$

$$Vo = -R3\left(\frac{V1}{R1} + \frac{V2}{R2}\right)$$

Potential application:

V1 = input voltage

V2/R2 provide an “offset” to V1/R1
(ex. to produce Vo=0 at some V1 value)


Differential amplifier

Eliminates “common mode”
voltage (noise, etc.)

$$\frac{V1 - V_x}{R1} = \frac{V_x - V_o}{R2} \quad \frac{V2 - V_x}{R1} = \frac{V_x}{R2}$$


$$V_x = \frac{R1V_o + R2V1}{R1 + R2} \quad V_x = \frac{V2R2}{R1 + R2}$$

$$V_o = \frac{R2}{R1} (V2 - V1)$$

 

Choose R1 to set input impedance; R2 to set gain


Instrumentation amplifier

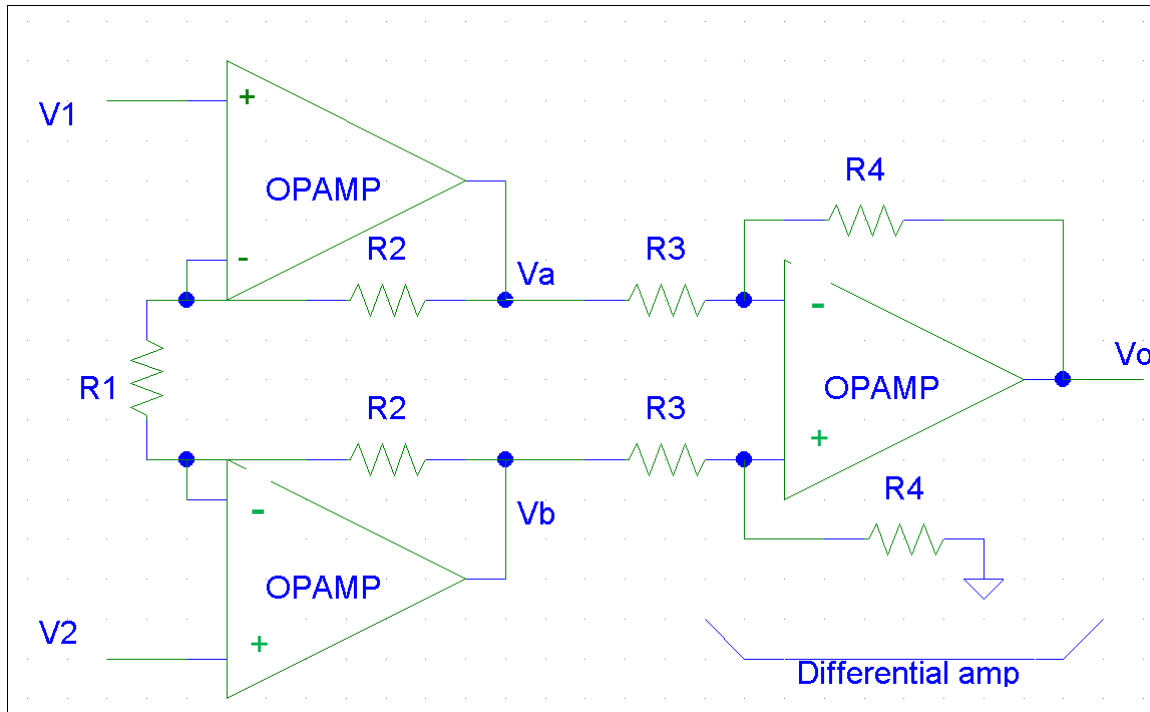

$$V_o = (V_2 - V_1) \left[1 + \frac{2R_2}{R_1} \right] \left(\frac{R_4}{R_3} \right)$$

- High input impedance, common mode rejection
- Can match R2, R3, R4 on chip and use external R1 to set gain

Sample-and-hold

 

- Required if A/D conversion slow relative to frequency of signal:
 - Close switch to “sample” V_{in} (charge C to V_{in})
 - Aperture (sampling) time = duration of switch closure
 - Open switch to “hold” V_{in}

 


Figure 17-4 Aperture time error.

Analog to digital conversion

- Given: continuous-time electrical signal


$$v(t), t \geq 0$$

- Desired: sequence of discrete numeric values that represent the signal at selected sampling times :

$$v(0), v(T), v(2T), \dots, v(nT)$$

- T = “sampling time”: $v(t)$ “sampled” every T seconds
 - n = sample number
 - $v(nT)$ = value of $v(t)$ measured at the n^{th} sample time and quantized to one of 2^k discrete levels
-

A/D conversion process

 


Sampled data sequence:

$n=1$ 2 3 4 5 6 7
 $d=10, 10, 10, 10, 11, 11, 11$

Binary values of d , where

$$v(nT) = (d/4)V_{\text{ref}}$$

 

A/D conversion parameters

- Sampling rate, F (sampling interval $T = 1/F$)
 - *Nyquist rate* $\geq 2 \times$ (highest frequency in the signal)
 - to reproduce sampled signals
 - CD-quality music sampled at 44.1KHz (ear can hear up to about 20-22KHz)
 - Voice in digital telephone sampled at 8KHz
 - Precision (# bits in sample value)
 - $k = \#$ of bits used to represent sample values
 - “precision”: each step represents $(1/2^k) \times V_{\text{range}}$
 - Ex. Temperatures $[-20^{\circ}\text{C} \dots +60^{\circ}\text{C}]$: if $k=8$, precision = $80^{\circ}\text{C}/256 = 0.3125^{\circ}\text{C}$
 - “accuracy”: degree to which converter discerns proper level (error when rounding to nearest level)
-

Analog to digital conversion

- More difficult than D/A conversion
 - Tradeoffs:
 - Precision (# bits)
 - Accuracy
 - Speed (of conversion)
 - Linearity
 - Unipolar vs. bipolar input
 - Encoding method for output
 - Cost
 - Often built around digital to analog converters
-

Digital to analog conversion


$$\text{Number} = b_n b_{n-1} \dots b_1 b_0 = b_n * 2^n + b_{n-1} * 2^{n-1} + \dots + b_1 * 2^1 + b_0 * 2^0$$

R-2R Ladder Network

$$V_o = V_R \sum_{k=0}^n b_k \left(\frac{1}{2^k} \right)$$


Equivalent resistance = R

Equivalent resistance = R

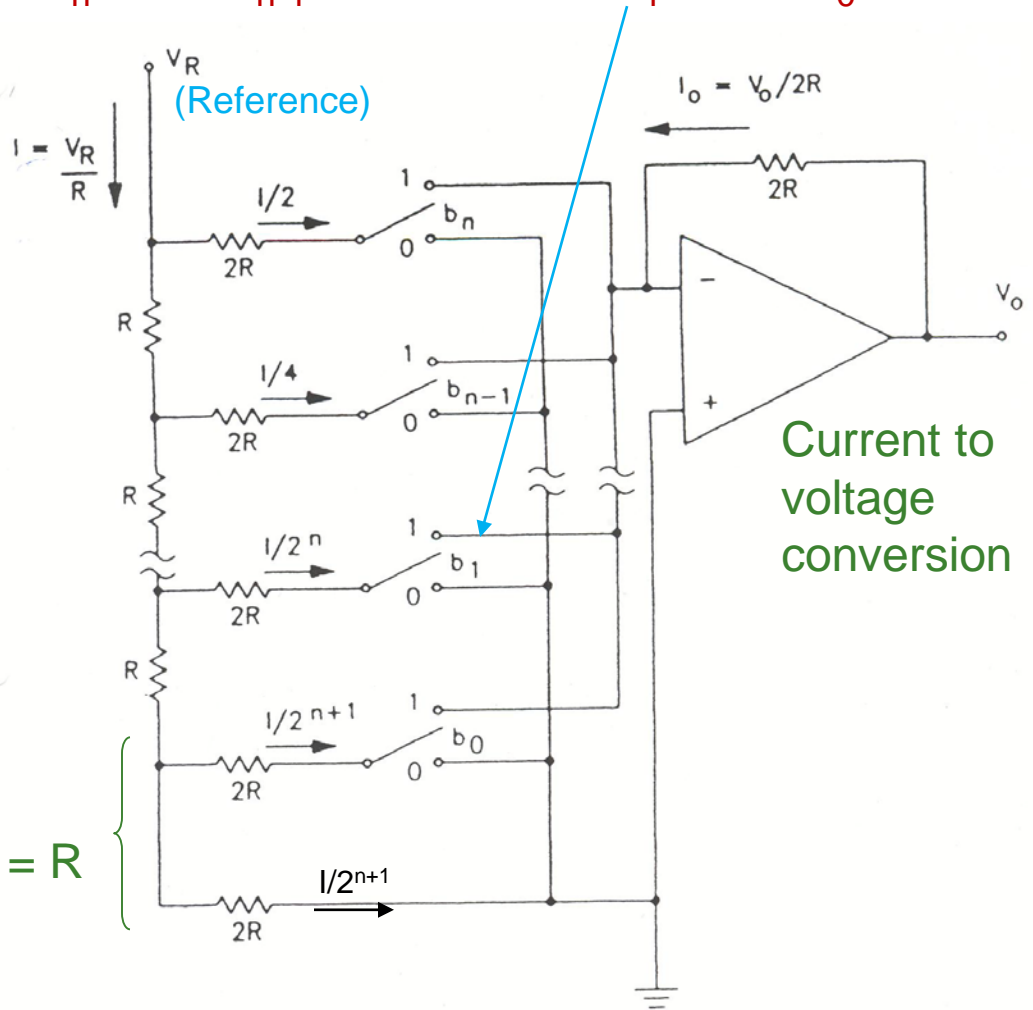


Flash A/D conversion

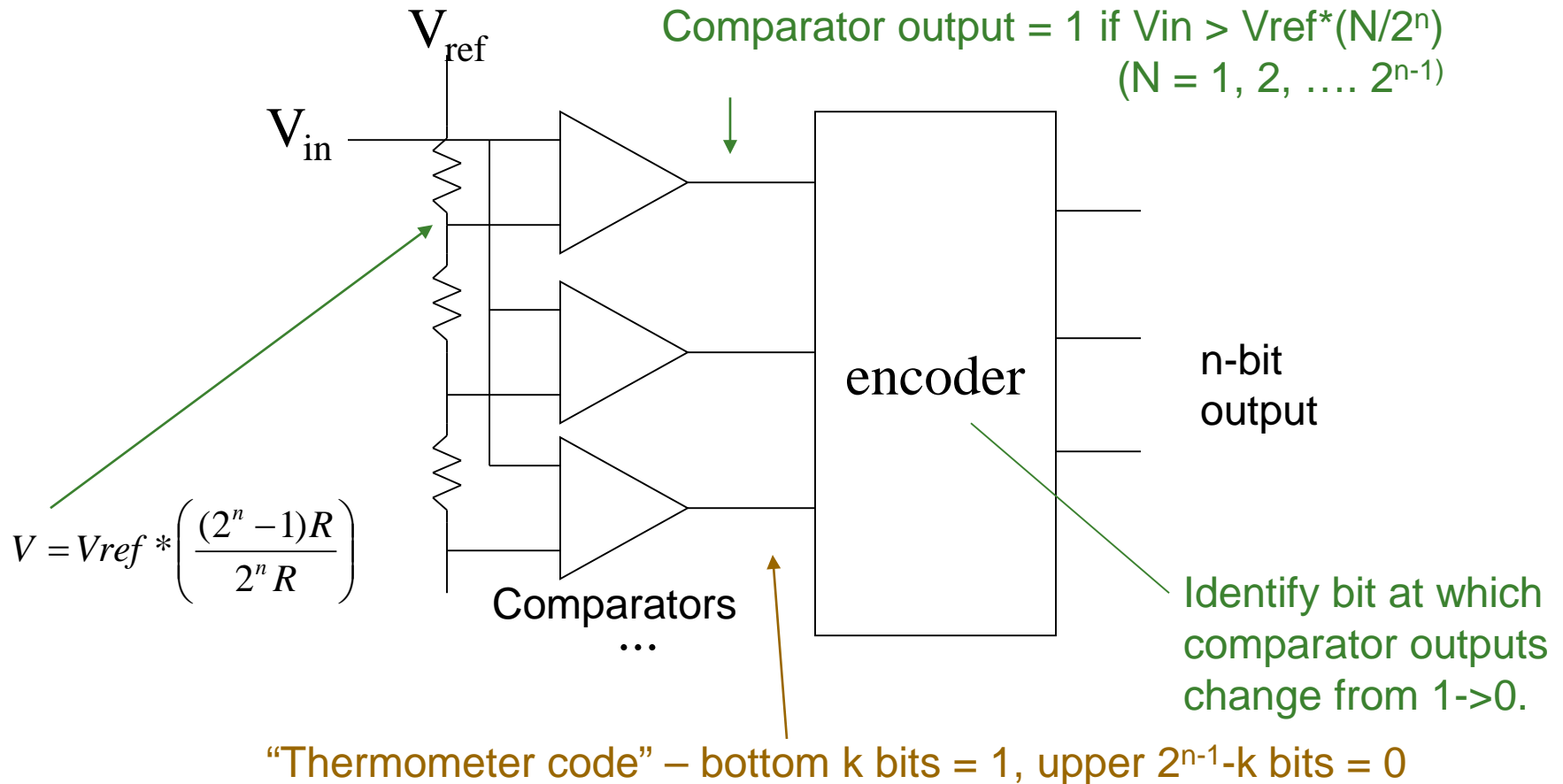- N-bit result requires 2^n comparators and resistors:



Dual-slope conversion

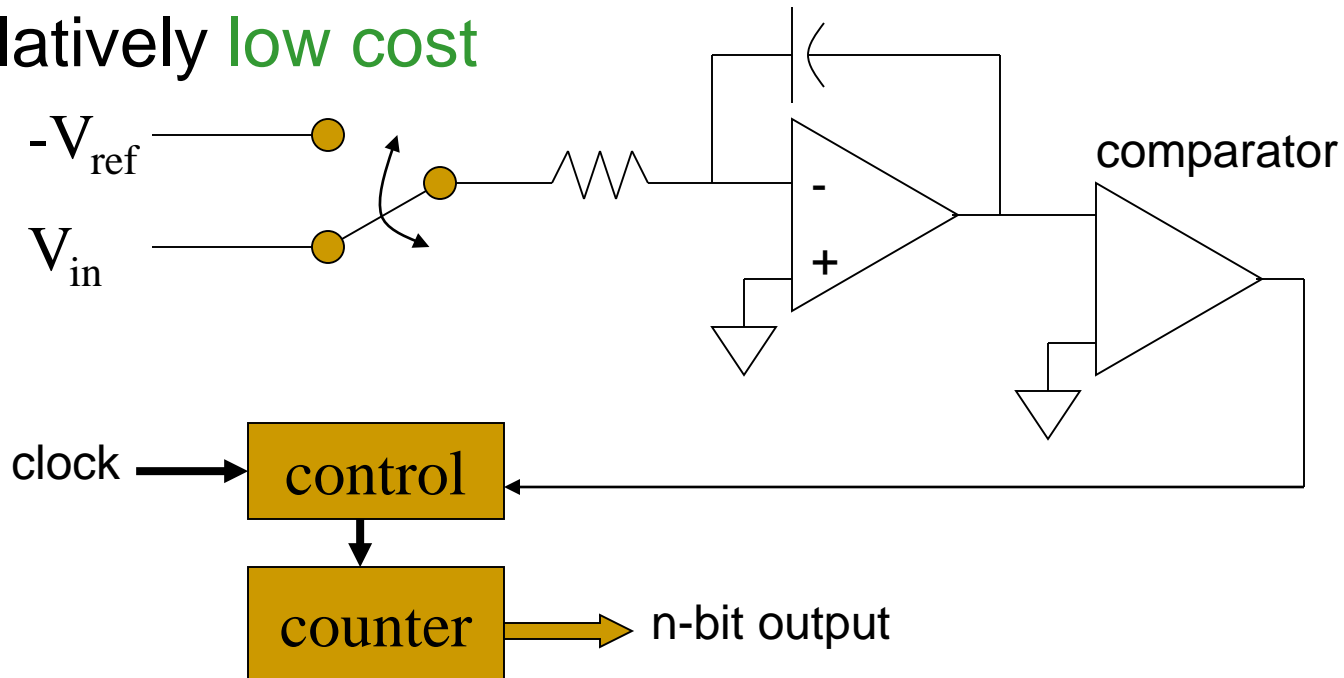
- Use counter to measure time required to charge/discharge capacitor (**relatively low speed**).
- Charging, then discharging eliminates non-linearities (**high accuracy**).
- Relatively **low cost**



Dual-slope conversion steps

 1. SW1 connects V_{in} for fixed time T
 - C charges with current = $V_{in}(t)/R$

$$V_o(t) = -\frac{1}{C} \int_0^T i_c(t) dt = -\frac{1}{RC} \int_0^T V_{in}(t) dt = -\frac{T}{RC} V_{in}$$



Dual-slope conversion steps

2. SW1 connects $-V_{ref}$ until V_o discharges to 0.

- C discharges with constant current = $-V_{ref}/R$

$$V_o(T + t_1) = -\frac{1}{RC} \int_0^T V_{in}(t) dt + \frac{1}{RC} \int_T^{T+t_1} V_{ref} dt$$

- When $V_o(T+t_1) = 0$:


$$\frac{1}{RC} \int_0^T V_{in}(t) dt = \frac{1}{RC} \int_T^{T+t_1} V_{ref} dt$$

$$V_{in} = \left(\frac{t_1}{T} \right) V_{ref}$$

Slope $\propto V_{in}$

Constant slope


Use a counter
to measure t_1 .

 

Successive approximation analog to digital converter (ADC)

- Determine one bit at a time, from MSB to LSB
Used in most microcontrollers (low cost)

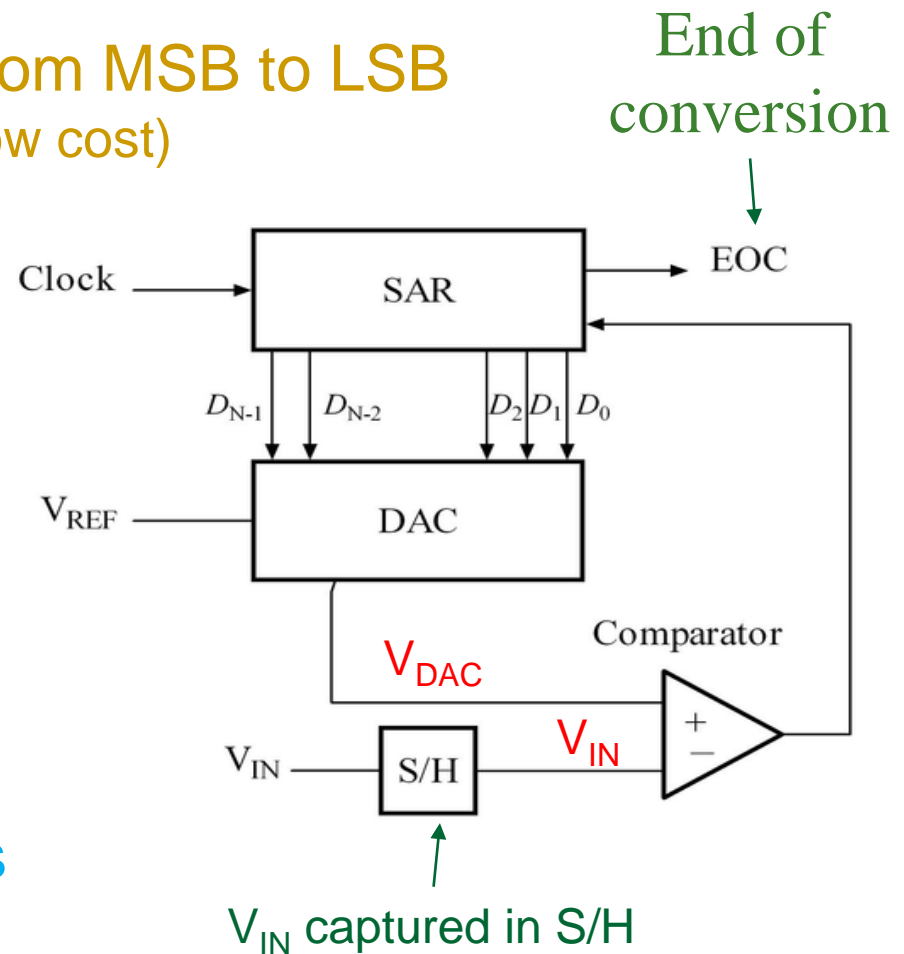
- Successive Approximation Register (SAR) sets $D_{N-1} = 1$
 - SAR outputs $D_{N-1} \dots D_0$, converted by DAC to analog V_{DAC}
 - V_{DAC} is compared to V_{IN}
 - Comparator output resets D_{N-1} to 0 in SAR if $V_{DAC} < V_{IN}$
 - Repeat 1-4 for $D_{N-2} \dots D_0$ (one clock period per bit)
- Final SAR value $D_{N-1} \dots D_0$ is digital representation of V_{IN}




Sigma Delta ADC

- High resolution (16 or more bits)
 - High integration
 - Reasonable cost
 - Often used to sample CD-quality audio
 - 16-bit resolution @ 44.1Ksamples/sec
 - Oversampling used to spread noise over wider frequency range
 - Digital filtering eliminates the noise
 - Gives good dynamic range with simple ADC
-


Sigma-Delta A/D Converter

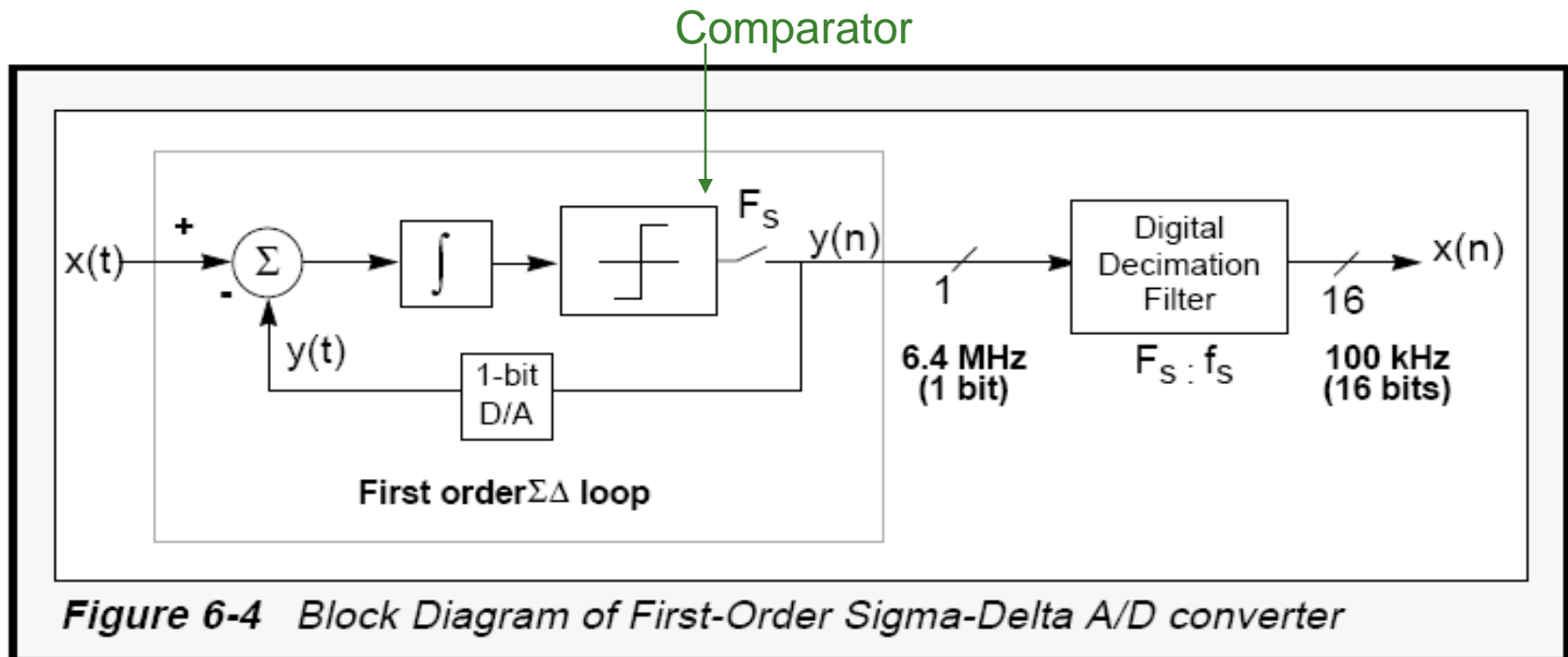

Sigma-Delta ADC

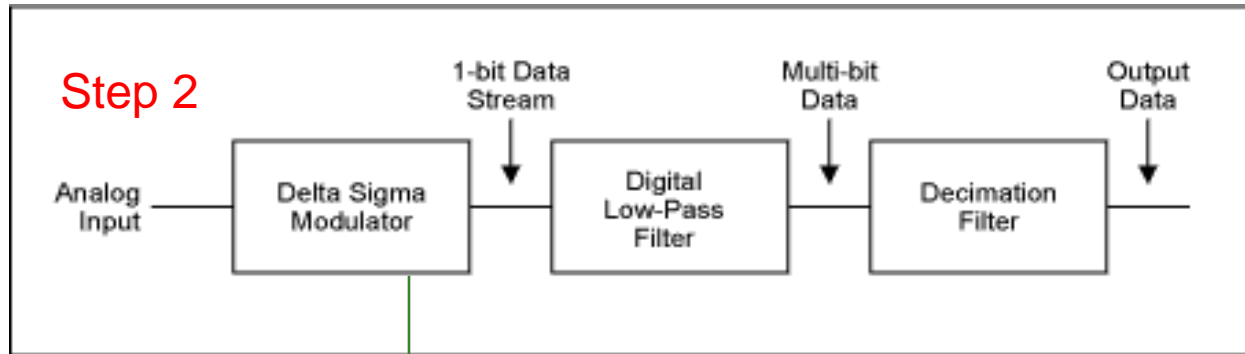

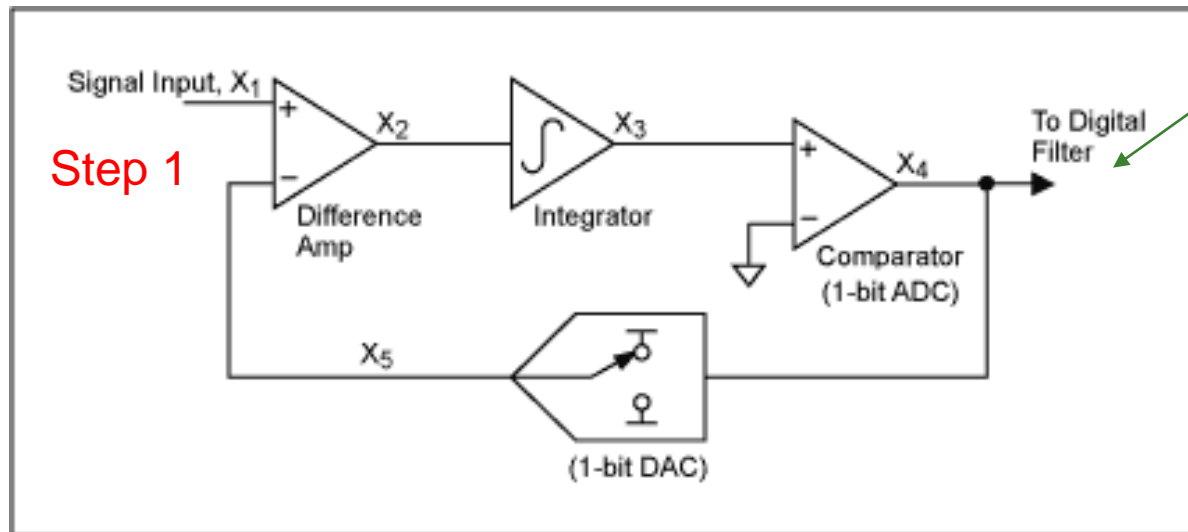Filtering extracts Info from serial data stream. (lower rate)



High rate bitstream


Density of 1's at modulator output proportional to the input signal.

Modulator operation


- Slope of integrator output depends on magnitude of V_{in}
 - “sigma” => summing/integration
 - Compare integrator output to 0v, producing “1” if positive and “0” if negative (1-bit ADC)
 - “delta” = difference
 - Density of 1’s in the bitstream proportional to magnitude of input voltage V_{in}
-

 Example


$\Delta\Sigma$ converter operation with 0 volt analog input



 
$\Delta\Sigma$ converter operation with small negative analog input



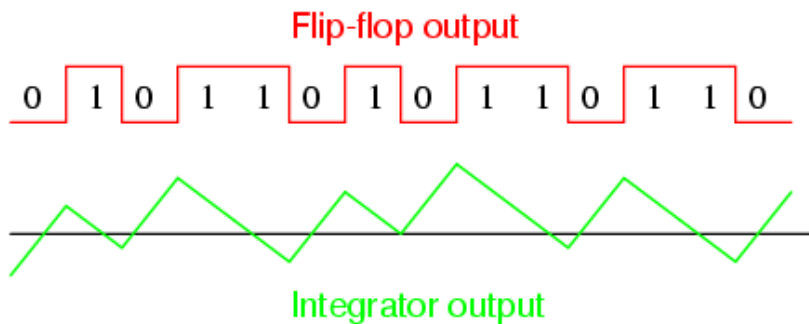$\Delta\Sigma$ converter operation with medium negative analog input




 $\Delta\Sigma$ converter operation with large negative analog input




Filtering determines average voltage (density of 1s) in bitstream

Maxim MAX1402 Sigma-Delta ADC

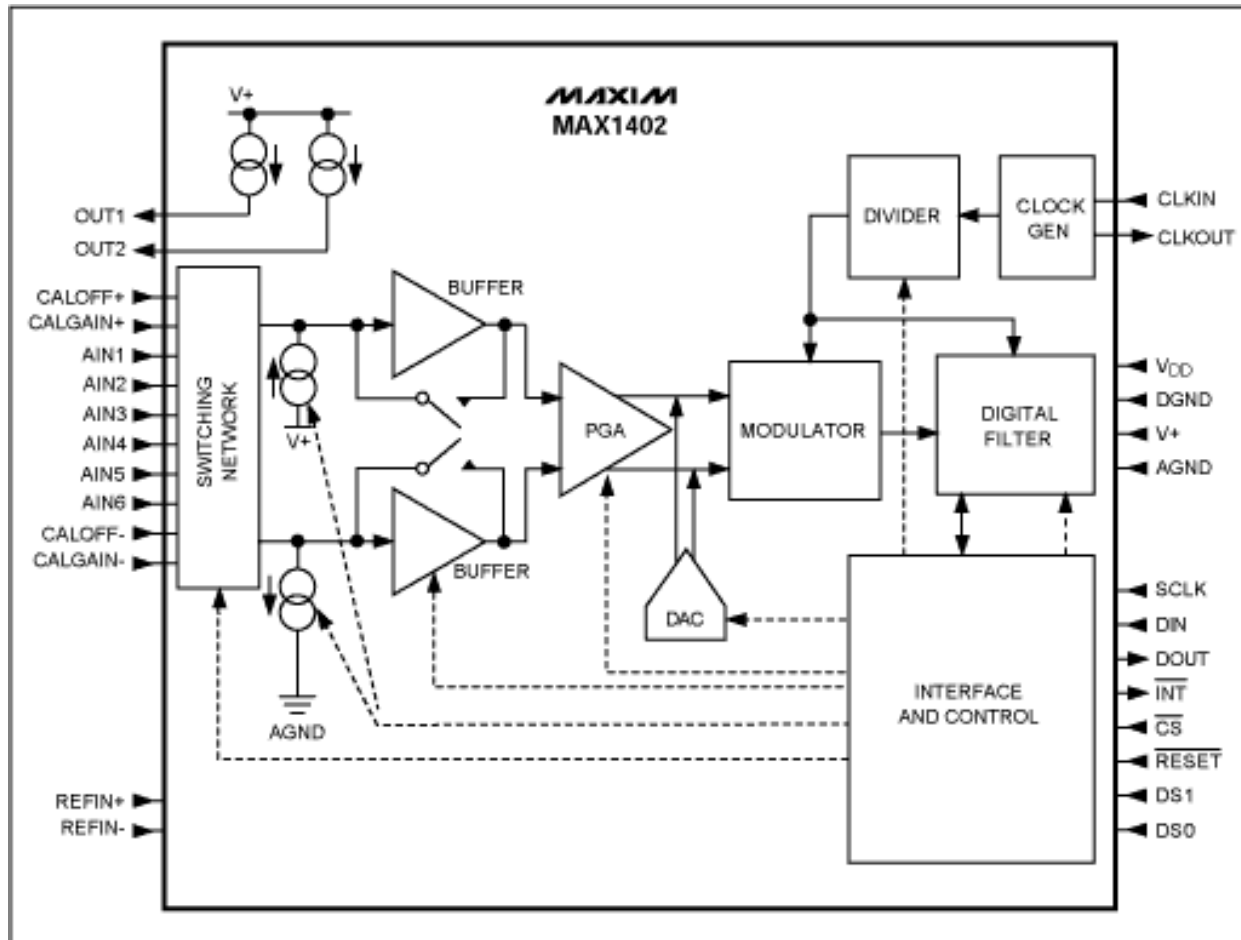


STM32F4xx D/A converter

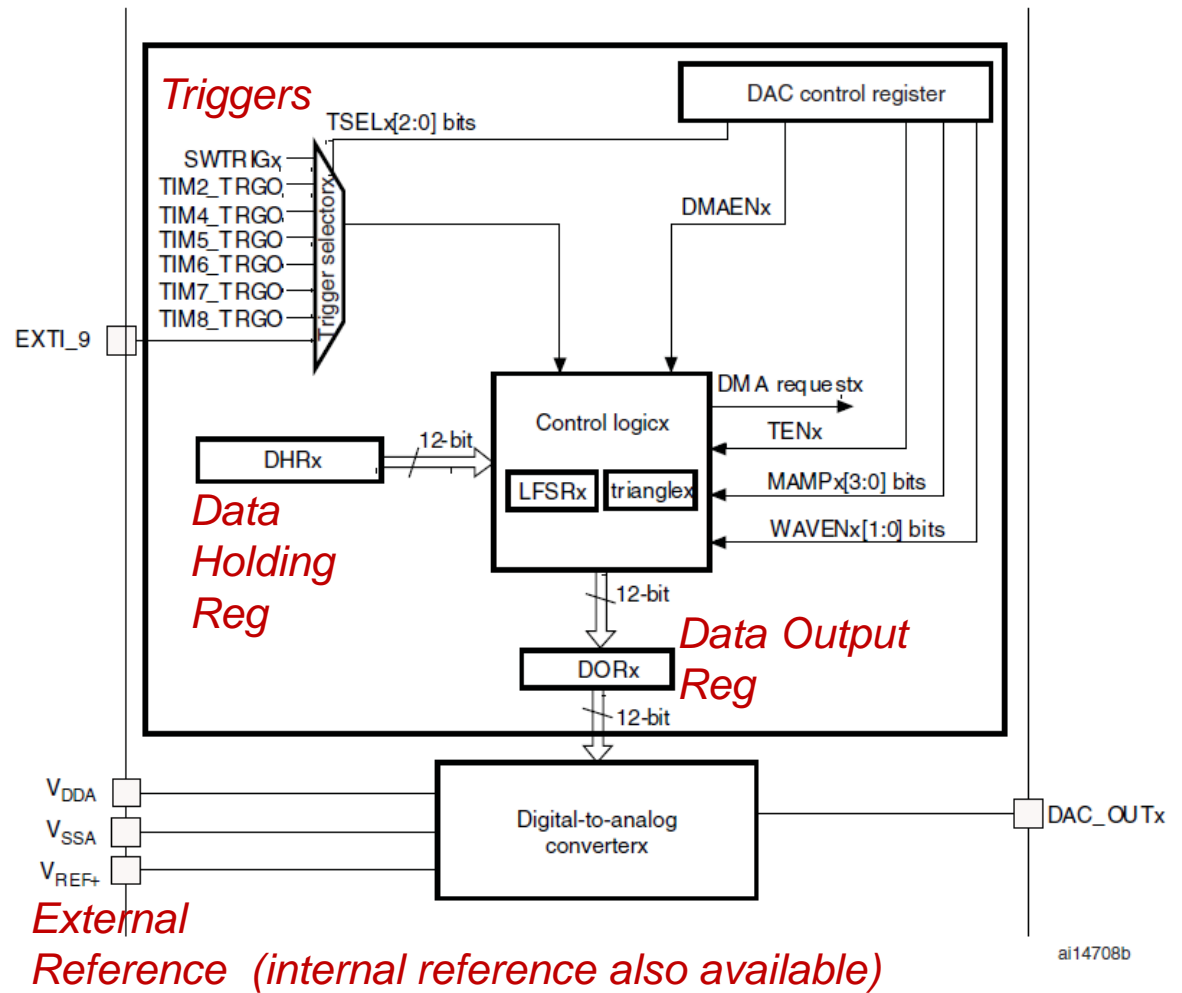- 8 or 12-bit modes
- 2 DACs/channels
 - Left/Right channel
 - Concurrent conversions
- Sample triggers:
 - SW trigger
 - Timer triggers
 - EXTI trigger
- DMA support
 - Memory -> DHRx



DAC data formats

Single DAC Channel

 

8-bit right aligned

12-bit left aligned

12-bit right aligned


DHR name (x = 1/2 channel):

DAC_DHR8Rx

DAC_DHR12Lx

DAC_DHR12Rx

Dual DAC Channels

 

8-bit right aligned

12-bit left aligned

12-bit right aligned

DHR name:


DAC_DHR8RD

DAC_DHR12LD

DAC_DHR12RD

DAC data conversion

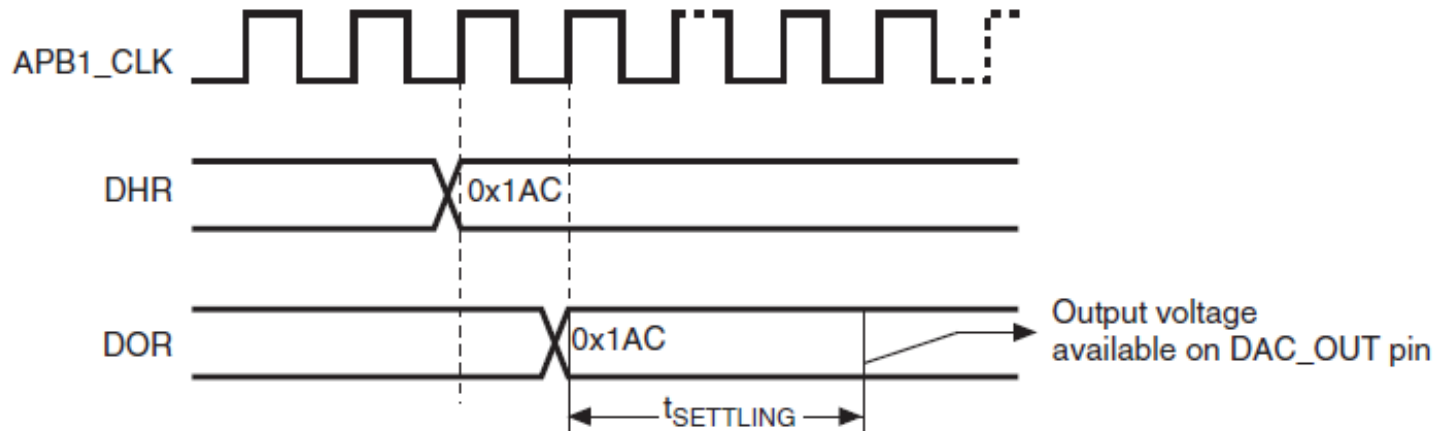Write data to DAC_DHRx register (trigger disabled: TEN=0):



$$\text{DACoutput} = V_{\text{REF}} \times \frac{\text{DOR}}{4095}$$

DAC control/status registers

DAC_CR (Upper half = channel 2; Lower half = channel 1)

31	30	29	28	27	26	25	24	23	22	21	20	19	18	17	16
Reserved		DMAU DRIE2	DMA EN2	MAMP2[3:0]				WAVE2[1:0]		TSEL2[2:0]			TEN2	BOFF2	EN2
		rw	rw	rw	rw	rw	rw	rw	rw	rw	rw	rw	rw	rw	rw
15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0
Reserved		DMAU DRIE1	DMA EN1	MAMP1[3:0]				WAVE1[1:0]		TSEL1[2:0]			TEN1	BOFF1	EN1
		rw	rw	rw	rw	rw	rw	rw	rw	rw	rw	rw	rw	rw	rw

Trigger Select
Trigger Enable*
Channel Enable

* If TEN=0, start when DHR written

DAC_SWTRIGR = Software trigger – start when bit set by SW (reset by HW)


31	30	29	28	27	26	25	24	23	22	21	20	19	18	17	16
Reserved															
15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0
Reserved														SWTRIG2	SWTRIG1
														w	w

DAC_SR = Status Register – Indicates DMS underrun (no data before trigger)

STM32F4xx Successive-Approximation ADC

- 12-bit successive approximation A/D converter
 - Programmable precision: 6-8-10-12 bits
 - Conversion time = #bits + 3 clock cycles
 - 1.2 Msamp/sec @ $V_{DDA}=1.8-2.4v$
 - 1.4 Msamp/sec @ $V_{DDA}=2.4-3.6v$
 - “Regular” and “Injected” channel groups
 - Injected channels processed after, or between, regular channels
 - 19 multiplexed input channels
 - 16 external sources
 - 3 internal sources: V_{BAT} , V_{REFINT} , temperature sensor
 - External trigger option (16 sources)
 - Multiple conversion modes
 - Single, continuous, scan, discontinuous
 - DMA and/or interrupts are supported
 - DMA often used in “scan” mode, to unload the single data register
-

STM32 ADC block diagram

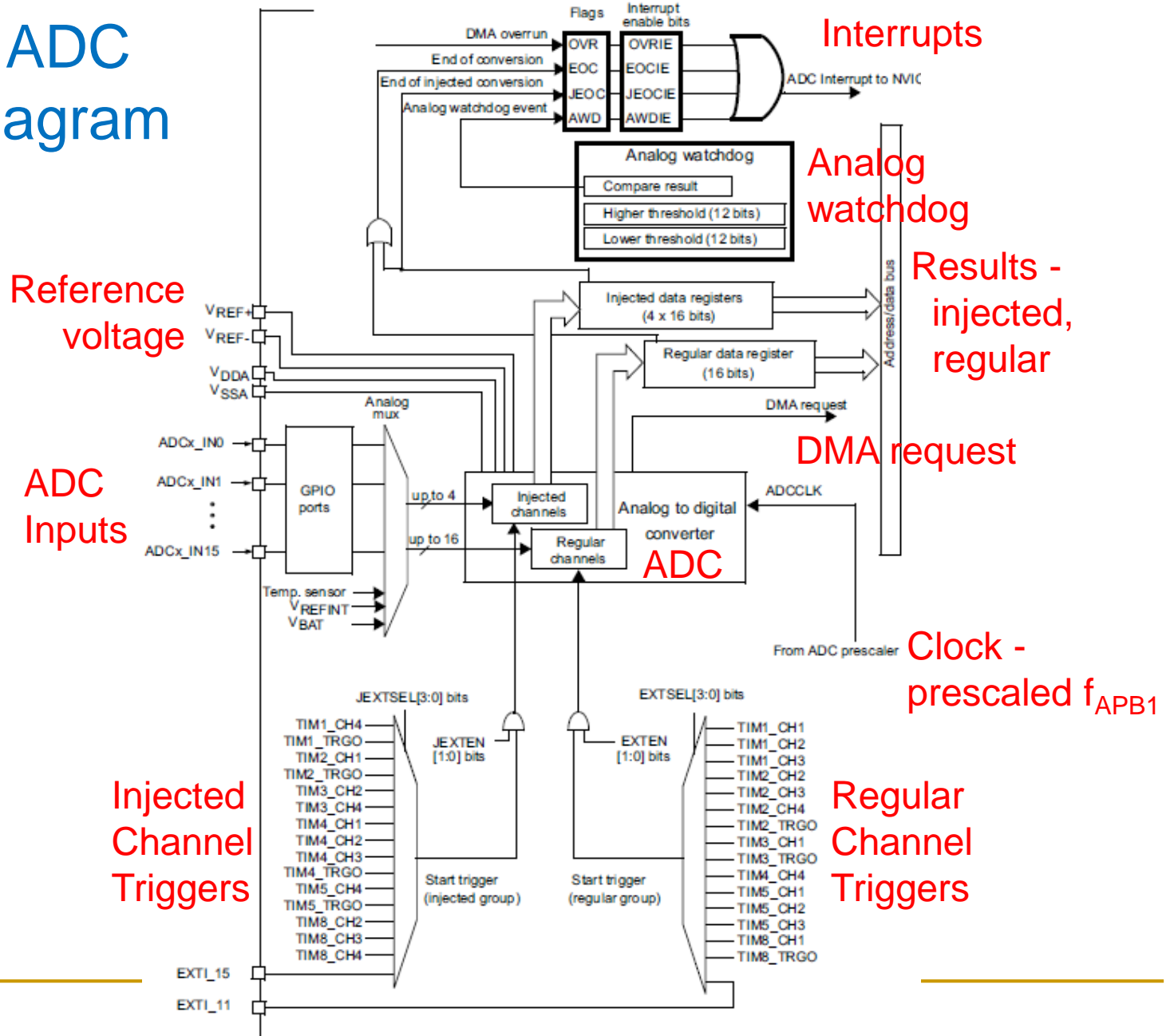

ADC clocking

- Analog circuitry clock: ADCCLK
 - Derive from APB2 clock ÷ prescale
 - $f_{ADC} = f_{PCLK2}/2, /4, /6, /8$ (bits **ADCPRE** in **ADC_CCR**)
 - f_{ADC} required range = 0.6MHz – 18MHz ($V_{DDA} = 1.8$ to $2.4v$)
= 0.6MHz – 36MHz ($V_{DDA} = 2.4$ to $3.6v$)
 - Sample time (t_s) = 3 to 480 clock cycles (8 choices)
 - $t_s = 0.10\mu s$ to $16\mu s$ @ $f_{ADC}=30MHz$
 - Set for *each channel* in **ADC_SMPR1**, **ADC_SMPR2**
 - Conversion time = **$t_s + n$** (#data bits) = 9 to 492 clocks
 - $0.50\mu s$ to $16.40\mu s$ for 12-bit data @ $f_{ADC}=30MHz$
 - $f_s \leq 2$ Msamples/sec @ $f_{ADC}=30MHz$, $t_s = 3$ ADC cycles
- Enable HSI clock in **RCC->CR**, which runs ADC conversions
 - **RCC->CR |= RCC_CR_HSION;** //HSION = bit 0 of RCC->CR
- Digital interface clock (register read/write)
 - Enable APB2 clock in **RCC_APB2ENR** (clock enable register)

Conversion modes

- **Single conversion** (default: `SCAN=0` in `CR1`, `CONT=0` in `CR2`)
 - Select an input channel (SQ1 field in in **ADC1->SQR5**)
 - Start the conversion (**software start or hardware trigger**)
 - EOC sets when conversion is complete
 - Read the result in the DR
 - **Scan mode** (enable with `SCAN=1` in `CR1`)
 - Perform a **sequence** of conversions of designated input channels
 - Define sequence length in **ADC1->SQR1**
 - Select channels in **ADC1->SQR1...ADC1->SQR5** (channels can be in any order)
 - Start the conversion sequence (**software start or hardware trigger**)
 - EOC sets after each conversion (`EOCS = 0`) or after the entire sequence is complete (`EOCS = 1`). `EOCS` is in **ADC1->CR2**
 - **Continuous mode** (enable with `CONT=1` in `CR2`)
 - Start 1st conversion/sequence (**software start or hardware trigger**)
 - Next conversion/sequence starts automatically after a conversion/sequence completes
-

Scan mode

- Convert multiple channels in a “sequence”
 - Enable via SCAN bit in **ADC_CR1**
 - Repeat if CONT bit set in **ADC_CR2**
 - EOC bit set in **ADC_SR** at end of sequence or after each conversion (select via EOCS bit)
 - Regular channel data to **ADC_DR**
 - Injected channel data to **ADC_JDR1 – ADC_JDR4**
 - Configure sequence via sequence registers
 - **ADC_SQR1** – seq. length and channel #s for conversions 13-16
 - **ADC_SQR2** – channel #s for conversions 7-12
 - **ADC_SQR3** – channel #s for conversions 1-6
 - **ADC_JSQR** – seq. length and channel #s for up to 4 injected channels
 - If JAUTO=1 (in **ADC_CR1**),
 - Injected group is converted after regular group after regular trigger
 - Injected group interrupts regular group after injection trigger
-

Discontinuous mode

- Convert a subset of a sequence on each external trigger
 - Regular group, on external trigger:
 - convert n (≤ 8) channels from a sequence
 - convert the next n channels on the next trigger
 - repeat until all channels in the sequence are done
 - restart the sequence on the next trigger
 - Injected group:
 - Similar, but only 1 channel per external trigger
-

STM32 ADC control register 1 (ADC_CR1)

31			30		29		28		27		26		25		24		23		22		21		20		19		18		17		16	
Reserved										OVR1E	RES			AWDEN	JAWDEN	Reserved																
										rw	rw	rw	rw	rw																		
15			14		13		12		11		10		9		8		7		6		5		4		3		2		1		0	
DISCNUM[2:0]			JDISCEN		DISCEN		JAUTO		AWDSGL		SCAN		JEOCIE		AWDIE		EOCIE		AWDCH[4:0]													
rw	rw	rw	rw	rw	rw	rw	rw	rw	rw	rw	rw	rw	rw	rw	rw	rw	rw	rw	rw	rw	rw	rw	rw	rw	rw	rw	rw	rw	rw	rw		

RES: resolution (00=12 bit, 01=10-bit, 10=8-bit, 11=6-bit)

SCAN: enable scan mode (channel #s in ADC_SQRx, ADC_JSQRx)

JAUTO: enable automatic injected group conversion after regular group

Interrupt enables:

EOCIE/JEOCIE: on end of conversion (regular/injected channel)

OVR1E: on overrun

Discontinuous mode:

DISCEN/JDISCEN: enable on regular/injected channels

DISCNUM: # channels to convert after trigger (1-8)

Analog Watchdog:

AWDEN/JAWDEN: enable on regular/injected channels

AWDCH: analog watchdog channel selection

AWDSGL: enable watchdog on single channel in scan mode

AWDIE: enable interrupt on analog watchdog

STM32 ADC control register 2(ADC_CR2)

31	30	29	28	27	26	25	24	23	22	21	20	19	18	17	16		
reserved	SWSTART	EXTEN			EXTSEL[3:0]				reserved	JSWSTART	JEXTEN			JEXTSEL[3:0]			
	rw	rw	rw	rw	rw	rw	rw	rw		rw	rw	rw	rw	rw	rw	rw	rw
15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0		
reserved				ALIGN	EOCS	DDS	DMA	Reserved						CONT	ADON		
				rw	rw	rw	rw							rw	rw		

ADON: 1=enable ADC, 0=disable ADC and power down

CONT: 1 = continuous conversions, 0 = single conversion

ALIGN: data alignment in 16-bit data register (0=right, 1=left)

EOCS: end of conversion selection

0=set EOC at end of sequence, 1=set EOC at end of each conversion

DMA: DMA enable

DDS: DMA disable selection

0=no new DMS request after last channel,

1=continue DMA requests as long as DMA=1

SWSTART/JSWSTART: start conversion of regular/injected channels

EXTEN/JEXTEN: external trigger event

00=disable, 01=rising edge, 10=falling edge, 11=both edges

EXTSEL/JEXTSEL[3:0]: select external event for trigger (regular/injected)

different sets of 16 sources for regular and injected mode

ADC status register ADC_SR

15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0
Reserved										OVR	STRT	JSTRT	JEOC	EOC	AWD
										rc_w0	rc_w0	rc_w0	rc_w0	rc_w0	rc_w0

OVR: overrun flag (set if data has been lost)

STRT/JSTRT: regular/injected channel conversion started flag

EOC/JEOC: end of conversion flag (regular/injected channel)

End of sequence (if EOCS=1) or one conversion (EOCS=0)

AWD: analog watchdog flag


“event: if voltage crosses values in ADC_LTR and ADC_HTR

All flags set by HW and cleared by SW

ADC converter characteristics

Type	Need SHA ?	Cycles/ conversion	Advantages	Disadvantages	Example
Flash	No	1	Fastest	Expensive, power	6-bit @ 400MHz
Successive Approximation	Yes	≥ 2	Fast, cheap	Slower than flash	8-bit @ 20 MHz
Integrating	Yes	Varies	Precise	Slow	22-bit @ 20Hz
Sigma-Delta	No	Many	Mostly digital, linear, high resolution	Complex digital circuit	16-bit @ 100 KHz

ADC converter comparison

 

ADC selection (Analog Devices, Inc.)

- <http://www.analog.com/en/analog-to-digital-converters/products/index.html>

