 


VHDL 4 - Modeling for Synthesis Register Transfer Level (RTL) Design

References: Roth/John Chapter 2.12-2.14, 4.2, 4.8

Register Transfer Language (RTL) Design

- ▶ A **system** is viewed as a structure comprising registers, functions and their control signals
- ▶ Show dataflow through the system
- ▶ Data = integers, addresses, instruct's
- ▶ Functions store and manipulate data
- ▶ Not gate/bit level



RTL register model

-- Model register to hold one datum of some type
-- Individual bits are not manipulated

```
library ieee; use ieee.std_logic_1164.all;  
entity Reg8 is  
    port (D: in std_logic_vector(7 downto 0);  
          Q: out std_logic_vector(7 downto 0);  
          LD: in std_logic);
```


```
end Reg8;  
architecture behave of Reg8 is  
begin  
    process(LD)  
    begin
```

```
        if (LD'event and LD='I') then  
            Q <= D; -- load data into the register
```

```
        end if;
```

```
    end process;
```


```
end;
```

 

Asynchronous control inputs

```
library ieee; use ieee.std_logic_1164.all;
entity Reg8 is
    port (D: in std_logic_vector(7 downto 0);
          CLK,PRE,CLR: in bit;
          Q: out std_logic_vector(7 downto 0));
end Reg8;
architecture behave of Reg8 is
begin
    process(clk,PRE,CLR)
    begin
        if (CLR='0') then
            Q <= "00000000";
        elsif (PRE='0') then
            Q <= (others => '1');
        elsif rising_edge(clk) then
            Q <= D;
        end if;
    end process;
end;
```

--Async PRE/CLR

 

-- async CLR has precedence
-- force register to all 0s
-- async PRE has precedence if CLR='0'
-- force register to all 1s
-- sync operation only if CLR=PRE='1'
-- load D on clock transition

Synchronous reset/set

--Reset function triggered by clock edge

```
process (clk)
begin
    if (clk'event and clk = '1') then
        if reset = '1' then -- reset has precedence over load
            Q <= "00000000" ;
        else
            Q <= D ;
        end if;
    end if;
end process;
```




Register with clock enable

```
-- "enable" effectively enables/disables clock
process (clk)
begin
    if rising_edge(clk) then -- detect clock transition
        if enable = '1' then -- enable load on clock transition
            Q <= D ;
        end if;
    end if;
end process;
```



Register with synchronous clear and load

 

Text Figure 2-42

```
process(CLK)
begin
    if CLK'event and CLK = '1' then
        if CLR = '1' then Q <= "0000"; --sync clear
        elsif Ld = '1' then Q <= D;      --sync load
        end if;
    end if;
end process;
```

Left shift register with synchronous clear & load

Text Figure 2-43

```
process(CLK)
begin
  if CLK'event and CLK = '1' then
    if CLR = '1' then Q <= "0000";
    elsif Ld = '1' then Q <= D;
    elsif LS = '1' then Q <= Q(2 downto 0) & Rin;
    end if;
  end if;
end process;
```

shift Q left

Register with parameterized width

```
-- One model of a given function with variable data size
library ieee; use ieee.std_logic_1164.all;
entity REGN is
    generic (N: integer := 8);          -- N specified when REG used
    port ( CLK, RST, PRE, CEN: in std_logic;
           DATAIN: in std_logic_vector (N-1 downto 0); -- N-bit data in
           DOUT:   out std_logic_vector (N-1 downto 0)  -- N-bit data out
         );
end entity REGN;
architecture RTL of REGN is
begin
process (CLK) begin
    if (CLK'event and CLK = '1') then
        if      (RST = '1') then DOUT <= (others => '0'); --reset to all 0s
        elsif (PRE = '1') then DOUT <= (others => '1'); --preset to all 1s
        elsif (CEN = '1') then DOUT <= DATAIN;           --load data
        end if;
    end if;
end process;
end architecture RTL;
```

Vectors: "100" = ('1','0','0') = ('1', others => '0')

Arbitrarily long: "00...0" = (others => '0')



Instantiating the parameterized register

```
library ieee; use ieee.std_logic_1164.all;
entity TOP is
port (    CLK,X,Y,A,B,C: in std_logic;
           DIN: in std_logic_vector(5 downto 0);
           Q1: out std_logic_vector(5 downto 0);
           Q2: out std_logic_vector(4 downto 0);
           Q3: out std_logic_vector(3 downto 0)
      );
end entity TOP;
architecture HIER of TOP is
component REGN is
generic (N: integer := 8);
port (    CLK, RST, PRE, CEN: in std_logic;
           DATAIN: in std_logic_vector (N-1 downto 0);
           DOUT:  out std_logic_vector (N-1 downto 0)
      );
end component REGN;
begin
R1: REGN generic map (6) port map --6-bit register
      (CLK, A, B, C, DIN, Q1);
R2: REGN generic map (5) port map --5-bit register (low 5 bits of DIN)
      (CLK, Y, X, C, DIN(4 downto 0),Q2);
R3: REGN generic map (4) port map --4-bit register (low 4 bits of DIN)
      (CLK=>CLK, RST=>A, PRE=>B, CEN=>C, DATAIN=>DIN(3 downto 0), DOUT=>Q3);
end architecture HIER;
```

Easier to identify signal to port connections.



2-to-1 mux with parameterized data size

```
entity muxN is
```

```
    generic (N: integer := 32); -- data size parameter
    port ( A,B: in std_logic_vector(N-1 downto 0);
           Y: out std_logic_vector(N-1 downto 0);
           Sel: in std_logic);
```

```
end muxN;
```

```
architecture rtl of muxN is
```

```
begin
```

```
    Y <= A when Sel = '0' else B; -- A,B,Y same type
```

```
end;
```

```
-- specify parameter N at instantiation time
```

```
M: muxN generic map (16)           16-bit vectors
                           port map(A=>In1, B=>In2, Y=>Out1);
```



Other types of generic parameters

entity and02 is

```
generic (Tp : time := 5 ns); -- gate delay parameter
port (A,B: in std_logic;
      Y: out std_logic);
```

end and02;

architecture eqn of and02 is

begin

```
Y <= A and B after Tp; -- gate with delay Tp
```

end;

.....

A_tech1: and02 generic map (2 ns) port map (M,N,P);

A_tech2: and02 generic map (1 ns) port map (H,K,L);

Gates with
different delays.



IEEE Std. 1076.3 Synthesis Libraries

- ▶ Supports arithmetic models
 - ▶ `ieee.numeric_std` (ieee library package)
 - ▶ defines UNSIGNED and SIGNED types as arrays of std_logic

```
type SIGNED is array(NATURAL range <>) of STD_LOGIC;
type UNSIGNED is array(NATURAL range <>) of STD_LOGIC;
```
 - ▶ defines arithmetic/relational operators on these types
 - ▶ Supports RTL models of functions
- ▶ Lesser-used packages:
 - ▶ `ieee.numeric_bit`
 - ▶ same as above except SIGNED/UNSIGNED are arrays of type `bit`
 - ▶ `ieee.std_logic_arith` (*from Synopsis*)
 - ▶ Non-standard predecessor of numeric_std/numeric_bit



NUMERIC_STD package contents

- ▶ Arithmetic functions: + - * / rem mod
 - ▶ Combinations of operand types for which operators are defined:
 - ▶ SIGNED + SIGNED return SIGNED
 - ▶ SIGNED + INTEGER return SIGNED
 - ▶ INTEGER + SIGNED return SIGNED
 - ▶ SIGNED + STD_LOGIC return SIGNED
 - ▶ **PLUS:** above combinations with UNSIGNED and NATURAL
- ▶ Other operators for SIGNED/UNSIGNED types:
 - ▶ Relational: = /= < > <= >=
 - ▶ Shift/rotate: sll, srl, sla, sra, rol, ror
 - ▶ Maximum(a,b), Minimum(a,b)
- ▶ Convert between types:
 - ▶ TO_INTEGER(SIGNED), TO_INTEGER(UNSIGNED)
 - ▶ TO_SIGNED(INTEGER,#bits), TO_UNSIGNED(NATURAL,#bits)
 - ▶ RESIZE(SIGNED or UNSIGNED,#bits) – changes # bits in the vector



Arithmetic with NUMERIC_STD package

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;
use IEEE.NUMERIC_STD.all;
entity Adder4 is
    port ( in1, in2 : in  UNSIGNED(3 downto 0) ;
           mySum : out UNSIGNED(3 downto 0) );
end Adder4;

architecture Behave_B of Adder4 is
begin
    mySum <= in1 + in2; -- overloaded '+' operator
end Behave_B;
```

UNSIGNED = UNSIGNED + UNSIGNED



Conversion of “closely-related” types

- ▶ **STD_LOGIC_VECTOR, SIGNED, UNSIGNED:**
 - ▶ All arrays of STD_LOGIC elements
 - ▶ Example: How would one interpret “1001” ?
 - ▶ STD_LOGIC_VECTOR: simple pattern of four bits
 - ▶ SIGNED: 4-bit representation of number -7 (2’s complement #)
 - ▶ UNSIGNED: 4-bit representation of number 9 (unsigned #)
- ▶ Vectors of same element types can be “converted” (re-typed/re-cast) from one type to another

```
signal A: std_logic_vector(3 downto 0) := "1001";
signal B: signed(3 downto 0);
signal C: unsigned(3 downto 0);
B <= signed(A);           -- interpret A value "1001" as number -7
C <= unsigned(A);        -- interpret A value "1001" as number 9
A <= std_logic_vector(B); -- interpret B as bit pattern "1001"
```

Conversion of “closely-related” types

For arrays of same dimension, *having elements of same type*


```
library IEEE;
use IEEE.STD_LOGIC_1164.all;
use IEEE.NUMERIC_STD.all;
entity Adder4 is
    port ( in1, in2 : in STD_LOGIC_VECTOR(3 downto 0) ;
           mySum : out STD_LOGIC_VECTOR(3 downto 0) );
end Adder4;
```

architecture Behave_B of Adder4 is

begin

mySum <=

SIGNED result

 
$$\text{STD_LOGIC_VECTOR}(\underbrace{\text{SIGNED}(\text{in1}) + \text{SIGNED}(\text{in2})}_{\text{Interpret STD_LOGIC_VECTOR as SIGNED}});$$

end Behave_B;

Interpret STD_LOGIC_VECTOR as SIGNED
Function: SIGNED = SIGNED + SIGNED

Interpret SIGNED result as STD_LOGIC_VECTOR.



Example – binary counter

```
library IEEE;  
use IEEE.STD_LOGIC_1164.all;  
use IEEE.NUMERIC_STD.all;  
ENTITY counter IS  
    port( Q: out std_logic_vector(3 downto 0);  
        ....
```

```
END counter;
```

ARCHITECTURE behavior OF counter IS

```
    signal Qinternal: unsigned(3 downto 0);  
begin
```

From NUMERIC_STD package
↓

```
    Qinternal <= Qinternal + 1;          -- UNSIGNED = UNSIGNED + NATURAL  
    Q <= std_logic_vector(Qinternal);   -- re-type unsigned as std_logic_vector
```



Using a “variable” to describe sequential behavior within a process

```
-- Assume Din and Dout are std_logic_vector
-- and numeric_std package is included
cnt: process(clk)
    variable count: integer; -- internal counter state
begin
    -- valid only within a process
    if clk='1' and clk'event then
        if Id='1' then
            count := to_integer(unsigned(Din)); --update immediately
        elsif cnt='1' then
            count := count + 1; --update immediately
        end if;
    end if;
    Dout <= std_logic_vector(to_unsigned(count,32)); --schedule ΔDout
end process;
```



Counting to some max_value (not 2^n)

-- full-sized comparator circuit generated to check count = max

```
process begin
    wait until clk'event and clk='1';
    if (count = max_value) then
        count <= 0;           --roll over from max_value to 0
    else
        count <= count + 1;  --otherwise increment
    end if;
end process;
```




Decrementer and comparator

-- comparison to 0 easier than a non-zero value (NOR gate)

```
process begin
    wait until clk'event and clk='1';
    if (count = 0) then
        count <= max_value; -- roll over from 0 to max_value
    else
        count <= count - 1; -- otherwise decrement
    end if;
end process;
```



FIGURE 2-44: VHDL Code for a Simple Synchronous Counter

 


library ieee;
use ieee.numeric_std.all;

```
signal Q: unsigned (3 downto 0);
-----
process (CLK)
begin
  if CLK'event and CLK = '1' then
    if ClrN = '0' then Q <= "0000";
    elsif En = '1' then Q <= Q + 1;
    end if;
  end if;
end process;
```

unsigned + natural

**FIGURE 2-45: 74163
Counter Operation**

 

Control Signals			Next State				
ClrN	LdN	PT	Q_3^+	Q_2^+	Q_1^+	Q_0^+	
0	X	X	0	0	0	0	(clear)
1	0	X	D_3	D_2	D_1	D_0	(parallel load)
1	1	0	Q_3	Q_2	Q_1	Q_0	(increment count)
1	1	1	present state + 1				(no change)

FIGURE 2-46: 74163 Counter Model

```
-- 74163 FULLY SYNCHRONOUS COUNTER

library IEEE;
use IEEE.numeric_bit.all;

entity c74163 is
    port(LdN, ClrN, P, T, Clk: in bit;
         D: in unsigned(3 downto 0);
         Cout: out bit; Qout: out unsigned(3 downto 0));
end c74163;

architecture b74163 of c74163 is
signal Q: unsigned(3 downto 0);      -- Q is the counter register
begin
    Qout <= Q;
    Cout <= Q(3) and Q(2) and Q(1) and Q(0) and T;
process(Clk)
begin
    if Clk'event and Clk = '1' then      -- change state on rising edge
        if ClrN = '0' then Q <= "0000";          -- synchronous clear
        elsif LdN = '0' then Q <= D;            -- synchronous load
        elsif (P and T) = '1' then Q <= Q + 1;   -- synchronous count
        end if;
    end if;
end process;
end b74163;
```

FIGURE 2-47: Two 74163 Counters Cascaded to Form an 8-Bit Counter

 


FIGURE 2-48: VHDL for 8-Bit Counter

```
--Test module for 74163 counter

library IEEE;
use IEEE.numeric_bit.ALL;

entity eight_bit_counter is
    port(ClrN, LdN, P, T1, Clk: in bit;
          Din1, Din2: in unsigned(3 downto 0);
          Count: out integer range 0 to 255;
          Carry2: out bit);
end eight_bit_counter;

architecture cascaded_counter of eight_bit_counter is
component c74163
    port(LdN, ClrN, P, T, Clk: in bit;
          D: in unsigned(3 downto 0);
          Cout: out bit; Qout: out unsigned(3 downto 0));
end component;

signal Carry1: bit;
signal Qout1, Qout2: unsigned(3 downto 0);
begin
    ct1: c74163 port map (LdN, ClrN, P, T1, Clk, Din1, Carry1, Qout1);
    ct2: c74163 port map (LdN, ClrN, P, Carry1, Clk, Din2, Carry2, Qout2);
    Count <= to_integer(Qout2 & Qout1);
end cascaded_counter;
```



Handling Overflow (Carry)

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;
use IEEE.NUMERIC_STD.all;

entity Adder_1 is
    port ( A, B : in  UNSIGNED(3 downto 0) ;
           C : out UNSIGNED(4 downto 0) ) ; -- C(4) = carry bit
end Adder_1;
```

```
architecture Synthesis_1 of Adder_1 is
begin
    C <= ('0' & A) + ('0' & B); -- leading '0' balances # bits
end Behave_B;
```

result bits for “+” is maximum of (#bits in A, #bits in B)
can also use: C <= resize(A,5) + resize(B,5)



FIGURE 2-38: VHDL Code for 4-Bit Adder Using Unsigned Vectors

```
library IEEE;
use IEEE.numeric_bit.all;

entity Adder4 is
    port(A, B: in unsigned(3 downto 0); Ci: in bit; -- Inputs
         S: out unsigned(3 downto 0); Co: out bit); -- Outputs
end Adder4;

architecture overload of Adder4 is
signal Sum5: unsigned(4 downto 0);
begin
    Sum5 <= '0' & A + B + unsigned'(0=>Ci);
    S <= Sum5(3 downto 0);
    Co <= Sum5(4);
end overload;
```


 


FIGURE 2-40: VHDL Code for 4-Bit Adder Using the std_logic_unsigned Package

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_unsigned.all;
entity Adder4 is
    port(A, B: in std_logic_vector(3 downto 0); Ci: in std_logic; --Inputs
          S: out std_logic_vector(3 downto 0); Co: out std_logic); --Outputs
end Adder4;

 
architecture overload of Adder4 is
signal Sum5: std_logic_vector(4 downto 0);
begin
    Sum5 <= '0' & A + B + Ci; --adder
    S <= Sum5(3 downto 0);
    Co <= Sum5(4);
end overload;
```



Multiple adder structures

$$z \leq a + b + c + d;$$

-- 3 adders stacked 3 deep

 

$$z \leq (a + b) + (c + d);$$

-- 3 adders stacked 2 deep


 


FIGURE 2-41: Cyclic Shift Register

 

```
process(CLK)
begin
    if CLK'event and CLK = '1' then
        Q1 <= Q3 after 5 ns;
        Q2 <= Q1 after 5 ns;
        Q3 <= Q2 after 5 ns;
    end if;
end process;
```

FFs generated from variables: 3-bit shift register example

-- External input/output din/dout

process (clk)

variable a,b: bit;

begin

if (clk'event and clk = '1') then

 dout <= b;


 b := a;

 a := din;

end if;

end process;

 -- Note: a,b used before being assigned new values



3-bit shift register example

Unexpected resulting structure

```
process (clk)
    variable a,b: bit;
begin
    if (clk'event and clk = '1') then
        a := din;      -- update a value to din
        b := a;        -- update b with new a value (din)
        dout <= b;    -- update dout with new b value (din)
    end if;
end process;
```

a,b updated before used so they effectively become
“wires”. End result is din -> dout on the clock transition.

