

Faults, Testing & Test Generation

Smith Text: Chapter 14.1, 14.3, 14.4


Mentor Graphics/Tessent:

“Scan and ATPG Process Guide”

“ATPG and Failure Diagnosis Tools Reference Manual”

(access via “mgcdocs”)

ASIC Design Flow

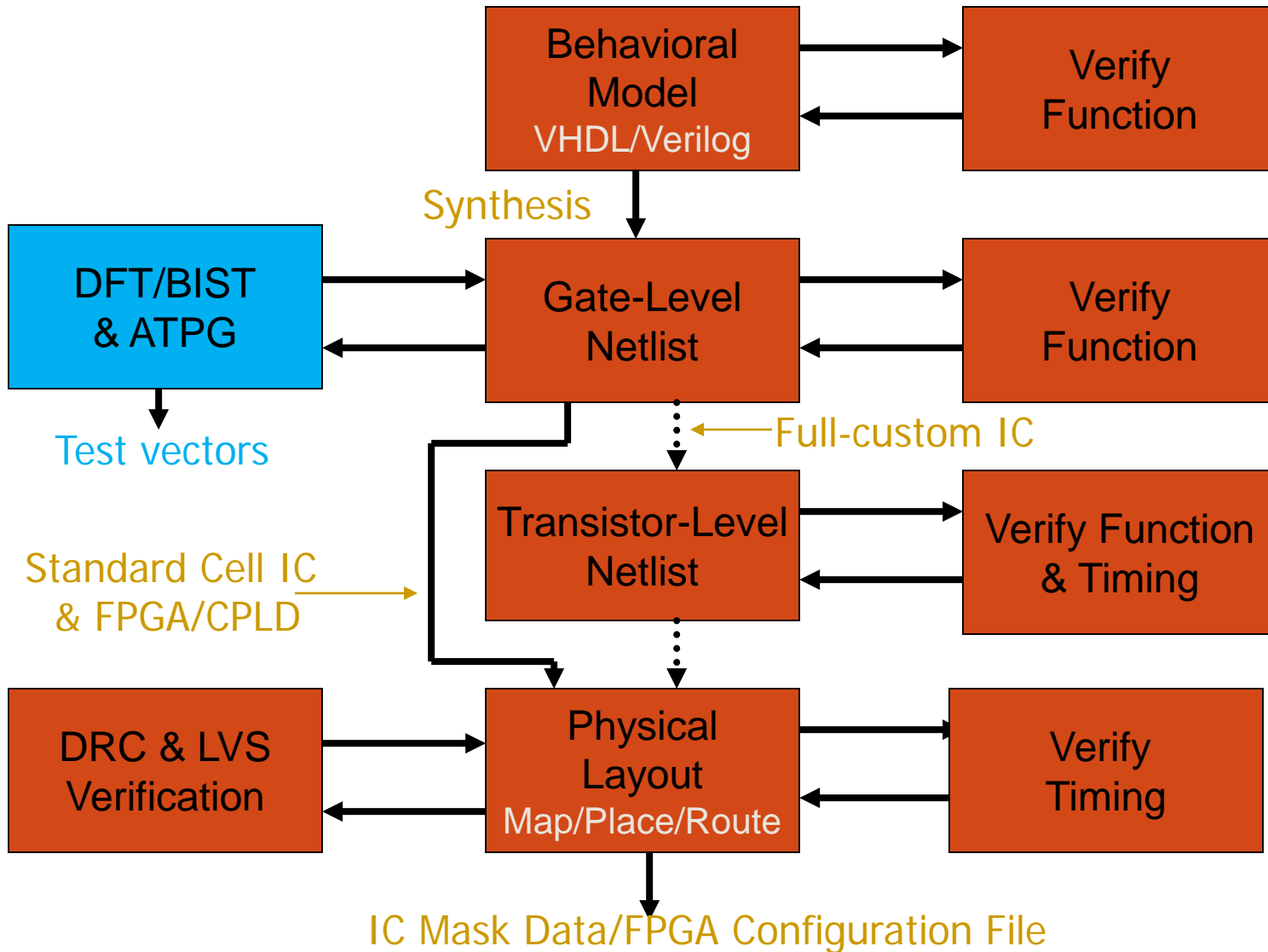

Importance of test (Ch. 14.1)

ASIC defect level	Defective ASICs	Total PCB repair cost	Total system repair cost
5%	5000	\$1 million	\$5 million
1%	1000	\$200,000	\$1 million
0.1%	100	\$20,000	\$100,000
0.01%	10	\$2,000	\$10,000


Parts shipped: 100,000 @ part cost = \$10

PCB cost: \$200, System cost: \$5,000, 100,000 systems shipped

System repair/replace cost: \$10,000


Q: What would it cost to reduce defect density from 5% to 1% ?

Top-down test design flow

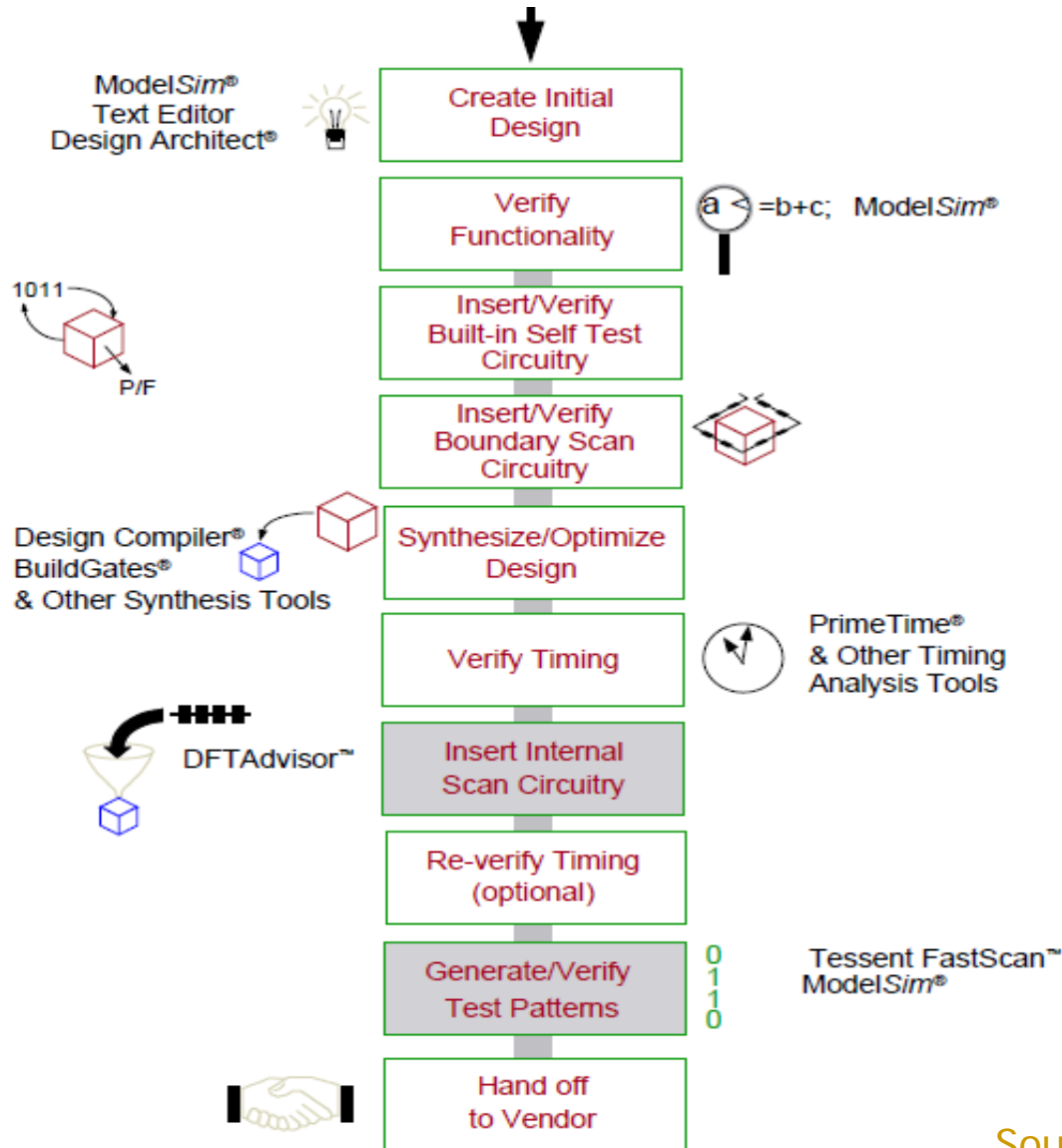


Fault models *(supported by FastScan)*

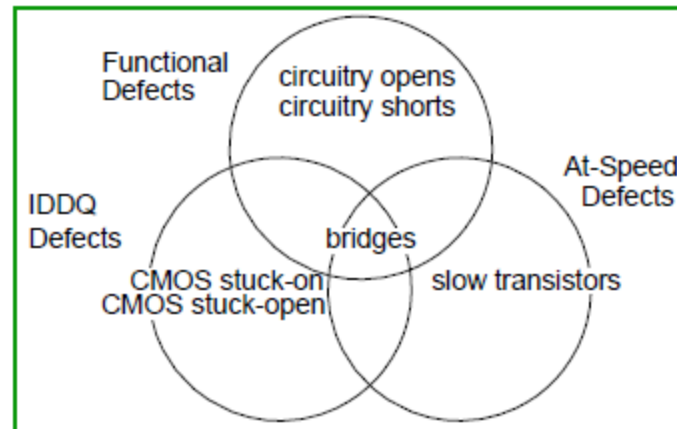- Map physical fault to a “logical” fault, i.e. faults that change the logic function of the circuit
 - Stuck-at: net effectively stuck at a logic 0/1
 - Bridging: value on one net affects another net
- “Parametric” faults alter physical properties other than logic function
 - Delay
 - Transition
 - IDDQ
 - Voltage level
 - Signal strength




Defects and physical faults

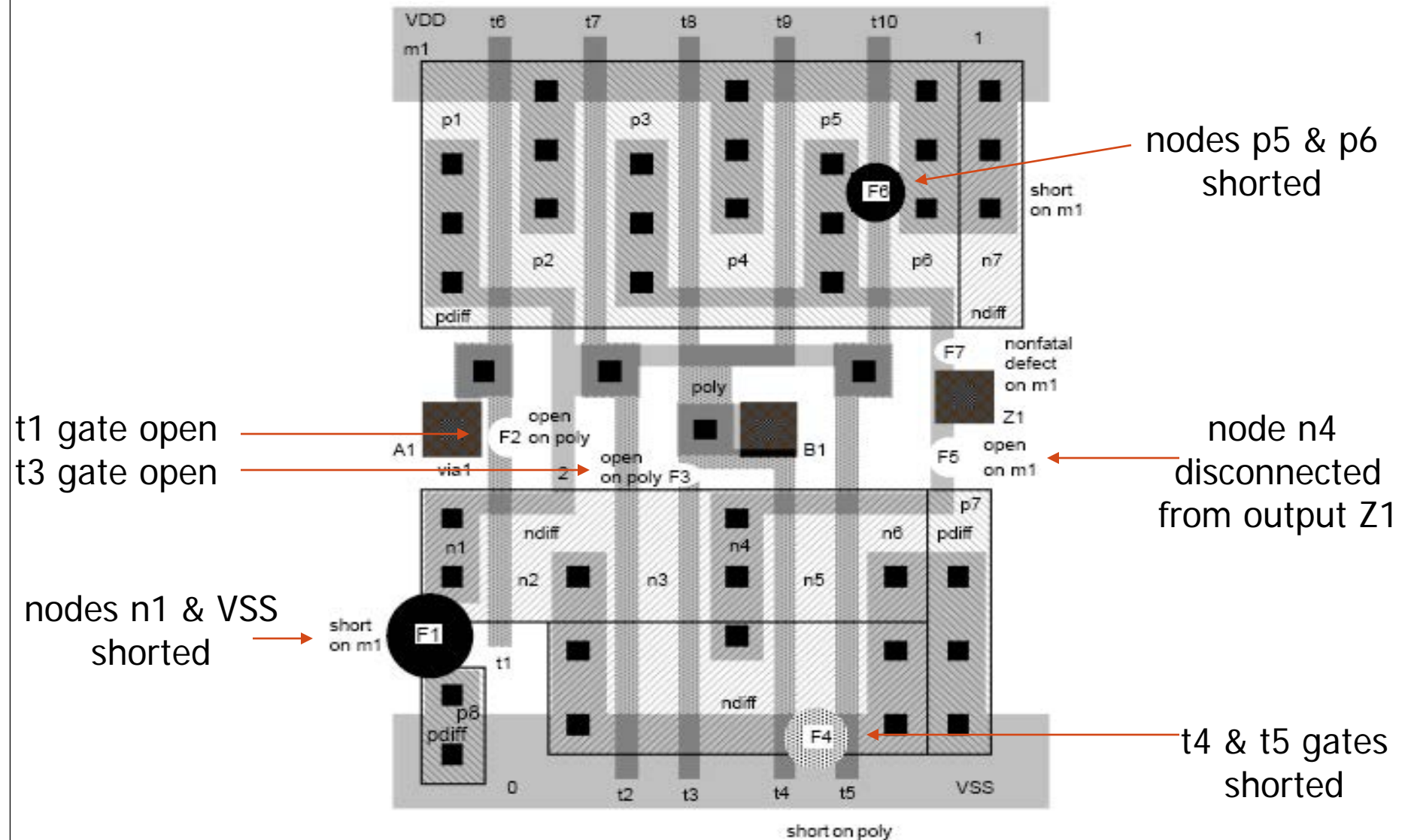


Smith Text: Figure 14.11

Defects translated to logical faults

(defects from previous slide)

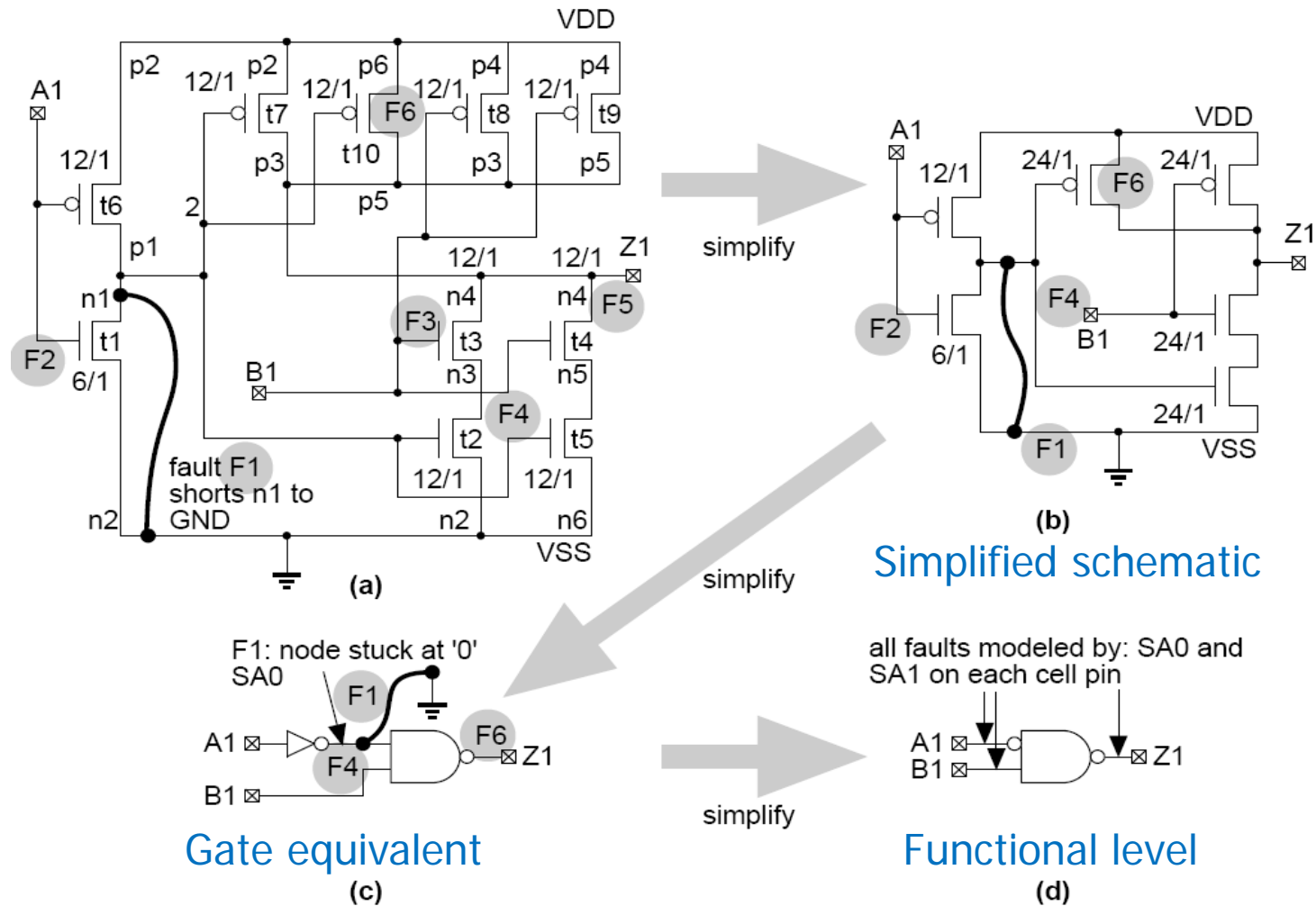

Stuck-at faults

 


Fault	Test (A,B)	Y(good)	Y(faulty)	Resulting function
A/0	11	1	0	Y=0
A/1	01	0	1	Y=B
B/0	11	1	0	Y=0
B/1	10	0	1	Y=A
Y/0	11	1	0	Y=0
Y/1	01,10,00	0	1	Y=1

Fault collapsing

- Fault A equivalent to fault B if every test for A is also a test for B and vice versa
 - Faults are indistinguishable
 - Group equivalent faults into a fault-equivalence class (FEC)
 - *Only one fault from a FEC needs to be tested*
- Fault A dominates fault B if any test for B also detects A, but only some of A tests detect B
 - *Need only test dominated fault B / omit dominating fault A*
 - Testing B guarantees A also tested

Fault collapsing example

 

$A/0 = B/0 = Y/0$ (remove B/0, Y/0)

A/1 dominated by Y/1 (remove Y/1)


B/1 dominated by Y/1 (remove Y/1)

Collapsed fault set = {A/0, A/1, B/1}

Min test set = {11, 01, 10}

Fault	Test (A,B)	Y(good)	Y(faulty)	Collapsing
A/0	11	1	0	A/0 equiv to B/0, Y/0
A/1	01	0	1	A/1 dom by Y/1
B/0	11	1	0	B/0 equiv to A/0, Y/0
B/1	10	0	1	B/1 dom by Y/1
Y/0	11	1	0	Y/0 equiv to A/0, B/0
Y/1	01,10,00	0	1	Y/1 dom A/1, B/1

Fault collapsing example

 

Equivalence classes:

- {A/0, B1/0, G/1} – keep G/1
- {B2/0, C/0, F/1} – keep F/1
- {G/0, K/0, Y/0} – keep G/0
- {D2/0, E/0, J/1, H/1, K/1, F/0, D1/0} – keep F/0

Fault dominance: (remove dominating)


- | | |
|-------------|-------------|
| A/1 <- G/0 | B1/1 <- G/0 |
| B2/1 <- F/0 | C/1 <- H/0 |
| D2/1 <- J/0 | E/1 <- J/0 |
| F/1 <- H/0 | D1/1 <- H/0 |
| H/0 <- K/0 | J/0 <- K/0 |
| G/1 <- Y/1 | K/1 <- Y/1 |

Collapsed fault set = {A/1, B1/1, B2/1, C/1, D1/1, D2/1, E/1, G/1, F/1, K/1}

Test generation: D Algorithm

- Select a fault on net N (ex. sa0)
- Produce an error at N (ex. N=1)
 - “D” denotes expected 1, actual 0 values
 - “D*” denotes expected 0, actual 1 values
- Propagate D condition to primary output
 - Set gate inputs to propagate D
- “Justify” D condition from primary inputs
 - Set gate inputs to create D condition

D Algorithm – tabular method

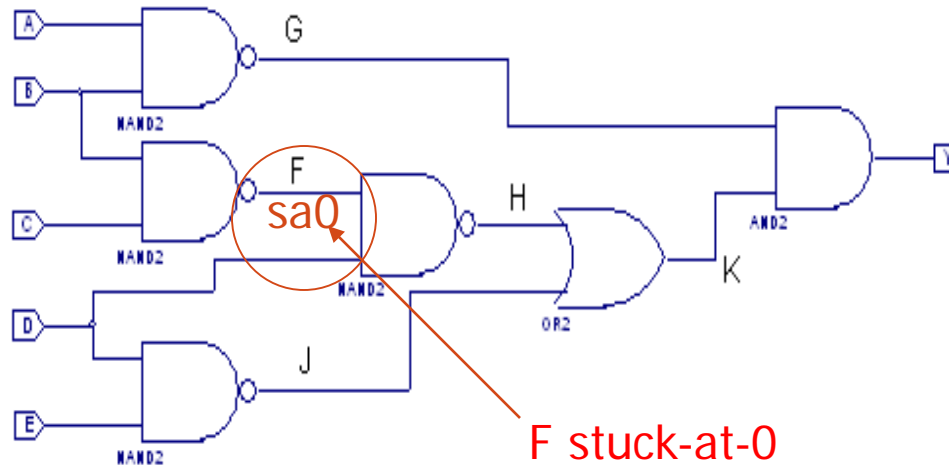

Step	A	B	C	D	E	F	G	H	J	K	Y
control						D					
observe				1		D		D*			
observe				1		D		D*	0	D*	
observe				1		D	1	D*	0	D*	D*
Consistency - J				1	1	D	1	D*	0	D*	D*
Consistency - G	x	0		1	1	D	1	D*	0	D*	D*
Consistency - F	x	0	x	1	1	D	1	D*	0	D*	D*


Test vectors: $ABCDE = \{-0-11, 0-011\} = \{00011, 10011, 00111, 10111, 01011\}$

Generate and verify a test set

- Collapse the fault set
 - minimize fault set required for 100% fault coverage
 - *“coverage” = (# faults detected) / (# possible faults)*
- Automatic test pattern generation (ATPG)
 - apply D algorithm or other method to derive test patterns for all faults in the collapsed fault set
 - “random patterns” detect many faults
 - *FastScan ATPG method:*
 - apply random patterns until new pattern detects < 0.5% of undetected faults
 - apply deterministic tests to detect remaining faults
- Fault simulation
 - verify fault coverage of test patterns
 - simulate fault, apply test pattern, and observe output
 - fault detected if output different from expected value
 - repeat for each fault & test pattern combination

Mentor Graphics “Tessent” *FastScan*

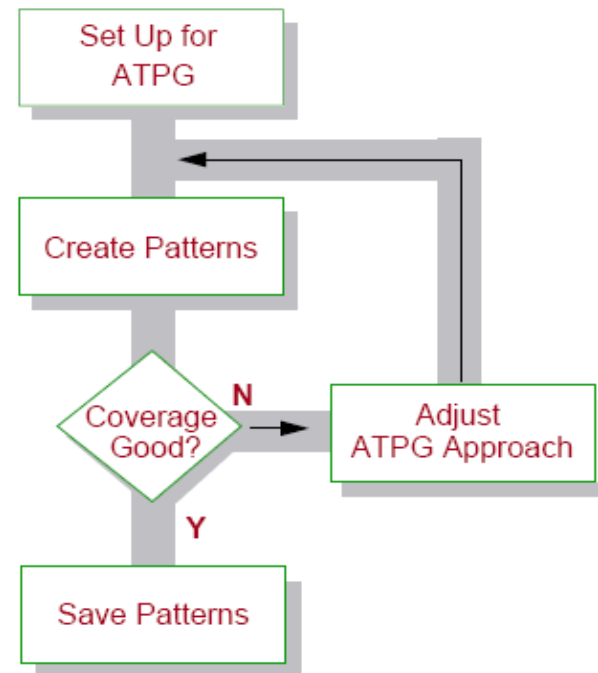- Perform design for testability (DFT), ATPG, and fault simulation
- **FastScan:** full-scan designs
 - *Legacy: FlexTest: non-scan through full-scan designs*
- Typical flow:
 1. Implement DFT
 2. Generate test patterns (ATPG)
 3. Verify fault coverage of patterns through fault simulation



Invoking *FastScan*


Command> `fastscan testckt.v -lib bicmos8hp.atpg -dofile dofile_name`

Verilog
netlist

file.v
(from synthesis)

cell_lib.atpg

dofile_name

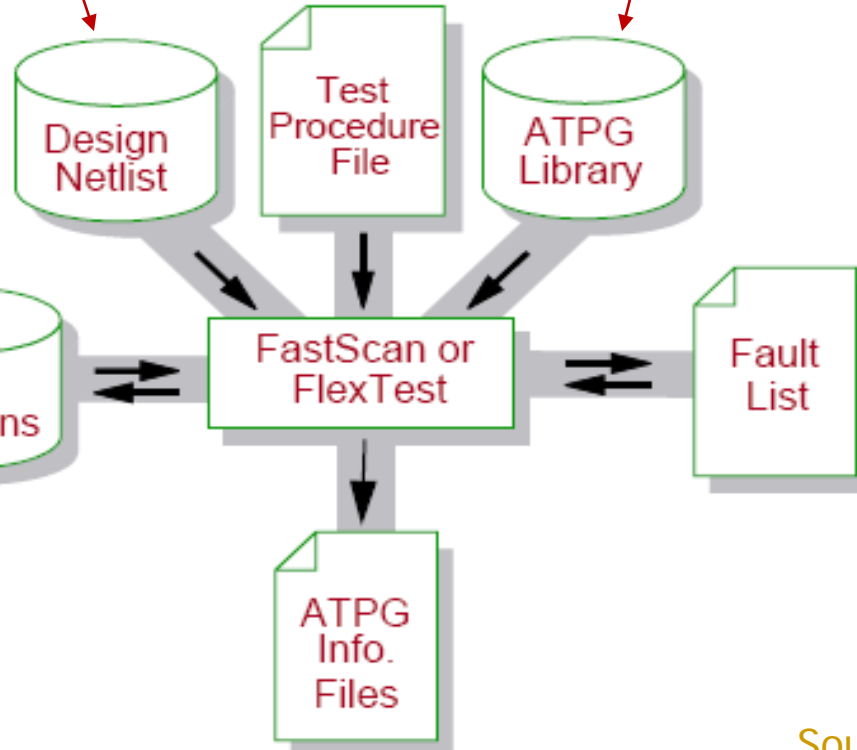


Source: ATPG Manual

FastScan Flow

Setup mode

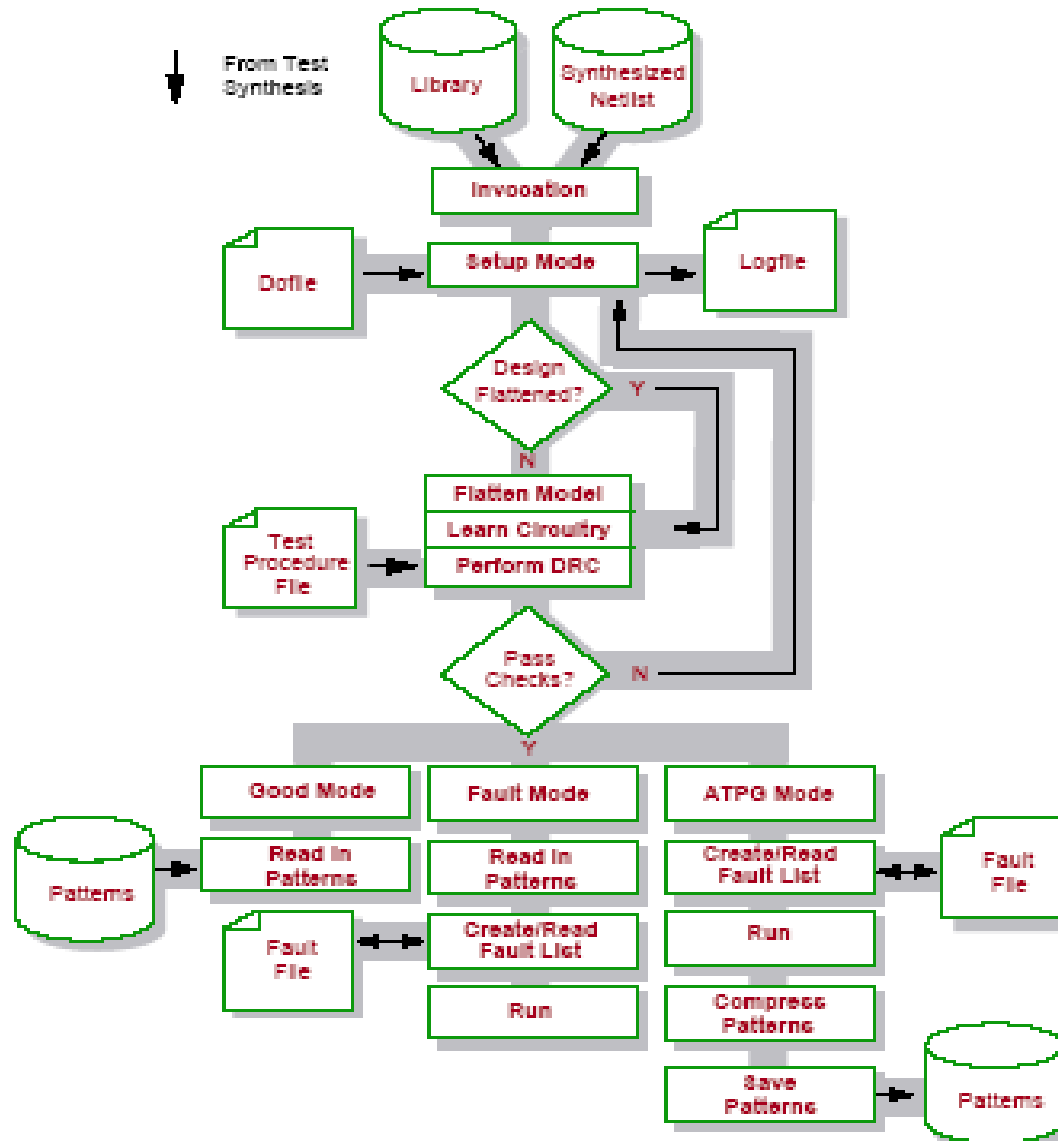- Flatten model
- Study circuit
- Perform DRC



set system mode
Good/Fault/ATPG

Save patterns &
fault lists

System mode = setup

`cmd> set system mode setup`

Add to lists:

clocks*

primary inputs/outputs*

scan chains

RAMs

**Normally found automatically*

Examples:

`add primary input /nx131`

`add clock X`

`report primary inputs`


Other system modes:

`atpg` – generate patterns

`fault` – fault simulation

`good` – fault-free simulation

“Legacy” FastScan/FlexTest control panel

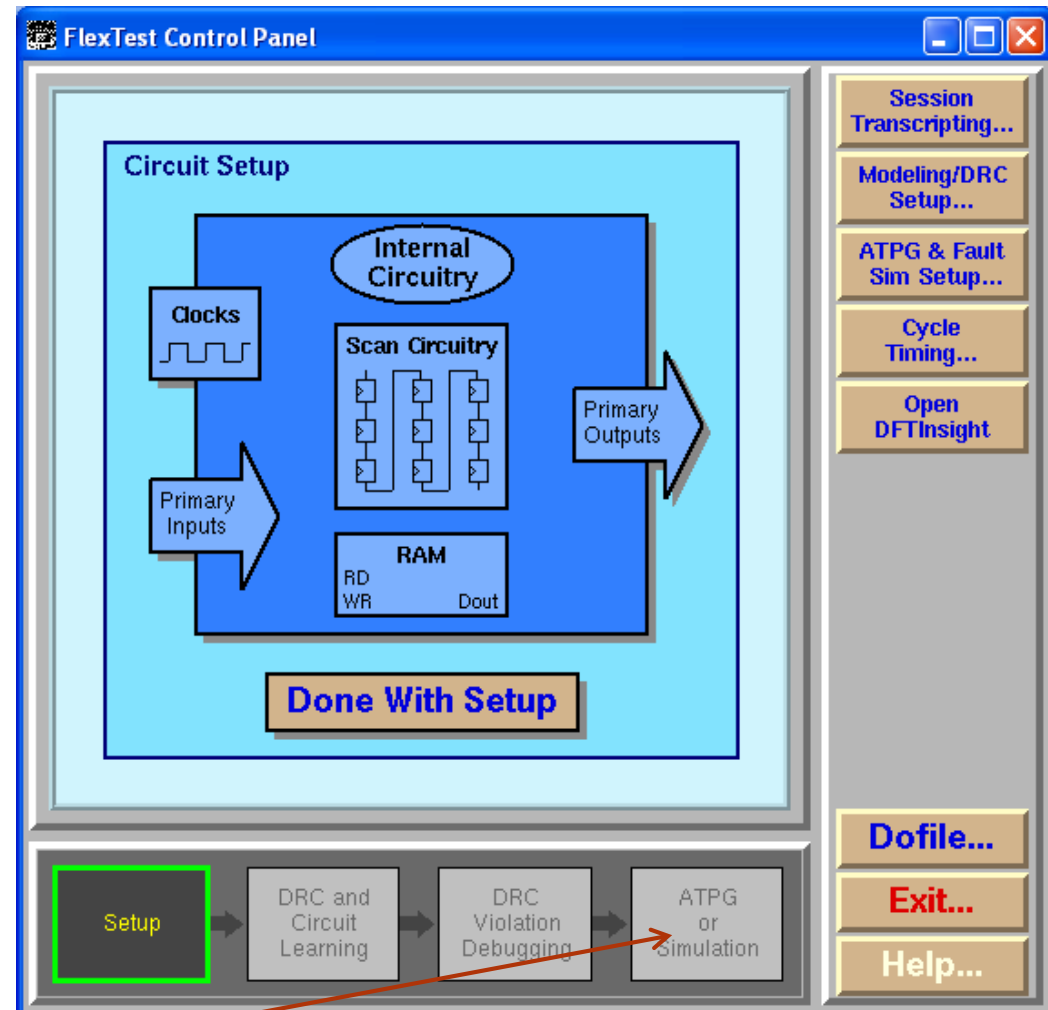

Testability design rule checks

When leaving setup: Check design issues that affect testability


Example: synchronous circuit DRC:

- System has a minimum number of clocks—optimally only one.
- Register all design inputs and account for metastability.
 - Treat metastability time as another delay in the path.
 - If the propagation delay plus the metastability time is less than the clock period, the system is synchronous.
 - If it is greater than or equal to the clock period, add an extra flip-flop to ensure the proper data enters the circuit.
- No combinational logic drives flip flop set/reset/clock inputs.
- No asynchronous signals set or reset the flip-flops.
- Buffers or other delay elements do not delay clock signals.
- Do not use logic to delay signals.
- Do not assume logic delays are longer than routing delays.

System mode = ATPG

Command> *set system mode atpg*

"Legacy" FlexTest ATPG control panel

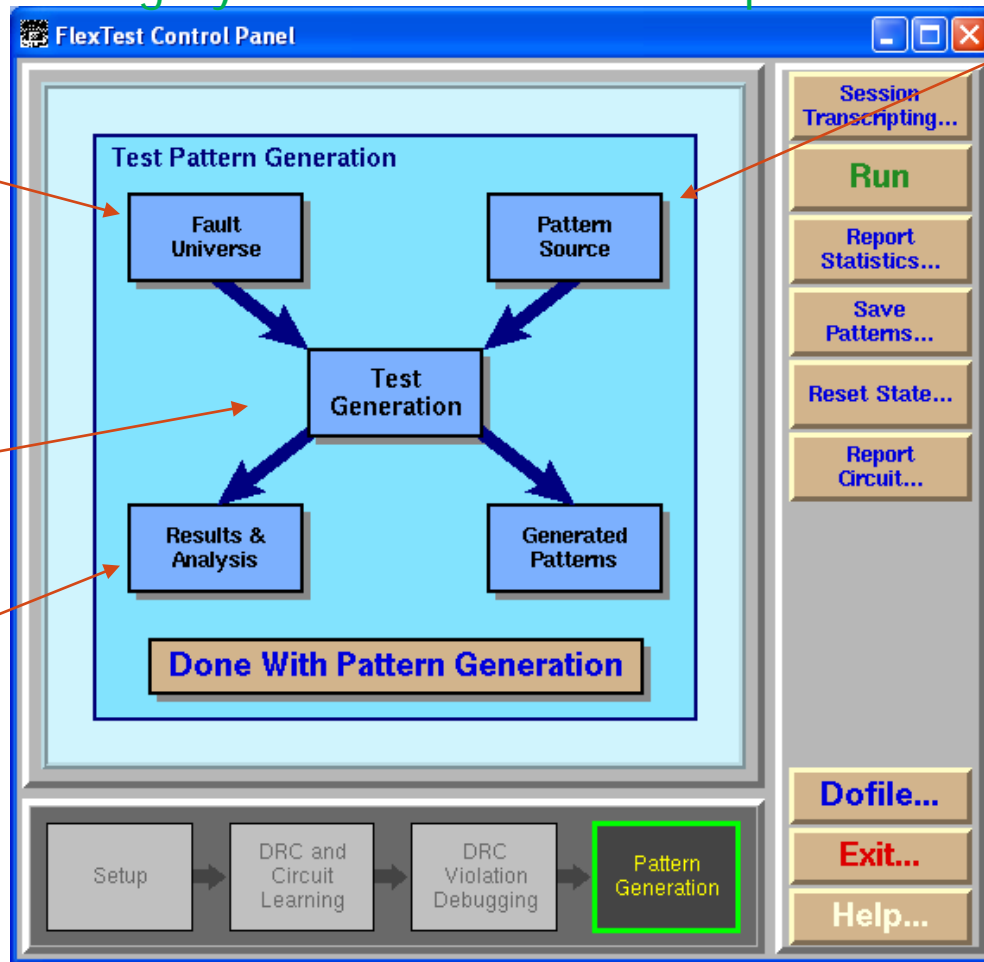

1. Select faults to be tested

2. Select auto test patterns or external test pattern file

3. Run the ATPG and fault simulation

4. Report results

Select fault types/models

- *set fault type Stuck* (default)
 - Fault model to be used for ATPG
 - Also: *Iddq*, *Toggle*, *Transition*, *Path_delay*, *Bridge*
 - Optionally specify “multiple detection” # to require multiple detections of each fault
- *add faults –all*
 - add faults to current fault list, discarding all patterns and setting all faults to undetected
 - options for each fault model; Ex. *stuck_at 01* (or *1* or *0*)
- *set fault mode uncollapsed* - include EQ faults
 - *set fault mode collapsed* (don't report EQ faults)
- *load faults filename* - load fault list from file
- *write faults filename* – write fault list to file
- *report faults* – print list of modeled faults

Select the test pattern source

- *set pattern source Internal*
 - Generate and use ATPG patterns
- *set pattern source External filename*
 - Load and use patterns from file
 - User guide defines pattern file formats
- *set pattern source Random*
 - Generate and use random patterns
- *set pattern source Bist*
 - BIST circuit generates patterns
- *create patterns -auto*
 - Perform ATPG to create patterns (-auto for stuck-at faults)

FastScan simulation modes

- Good – verify the simulation model
 - Use ATPG algorithm to generate test patterns
 - Apply patterns and capture outputs without simulating faults
 - Produces expected output for each test pattern
- Fault – determine fault coverage of a set of patterns
 - User provides a set of test patterns and fault list
 - Perform fault simulation using these patterns and faults to determine coverage
- ATPG -
 - Use ATPG algorithms to generate test patterns for given faults
 - Perform fault simulation using generated patterns to determine coverage of the ATPG-produced test set


Fault Simulation (Chap. 14.4)

- Deliberately induce faults to determine what happens to circuit operation
- Access limited to primary inputs (PIs) & primary outputs (POs)
- Apply pattern to PIs at start of test cycle
- At end of test cycle, compare POs to expected values
- Fault detected if POs differ from correct values
- Fault coverage = detected faults / modeled faults

Fault simulation with external file selected as “Pattern Source” *(This format was discontinued*)*

// FastScan test pattern file – define primary inputs and outputs

PI A
PI B
PI C
PI D
PI E
PO Y

 

// test patterns – bits in above order

000100
010000
011111
100111
100010

Notes:

1. These are “random” patterns.
2. * See next slide for correct ASCII pattern file format.

Test pattern file format (ASCII)

SETUP =

```
declare input bus "PI" = "/A", "/B", "/C", "/D" "/E";  
declare output bus "PO" = "/Y";
```

I/O pin names
(in order of vector bits)

end;

SCAN_TEST =

```
pattern = 0; ← Pattern #  
force "PI" "00010" 0; ← Input vector  
measure "PO" "0" 1; ← Expected output for this pattern
```


```
pattern = 1;  
force "PI" "01000" 0;  
measure "PO" "0" 1;
```

(3 lines per pattern)

end;

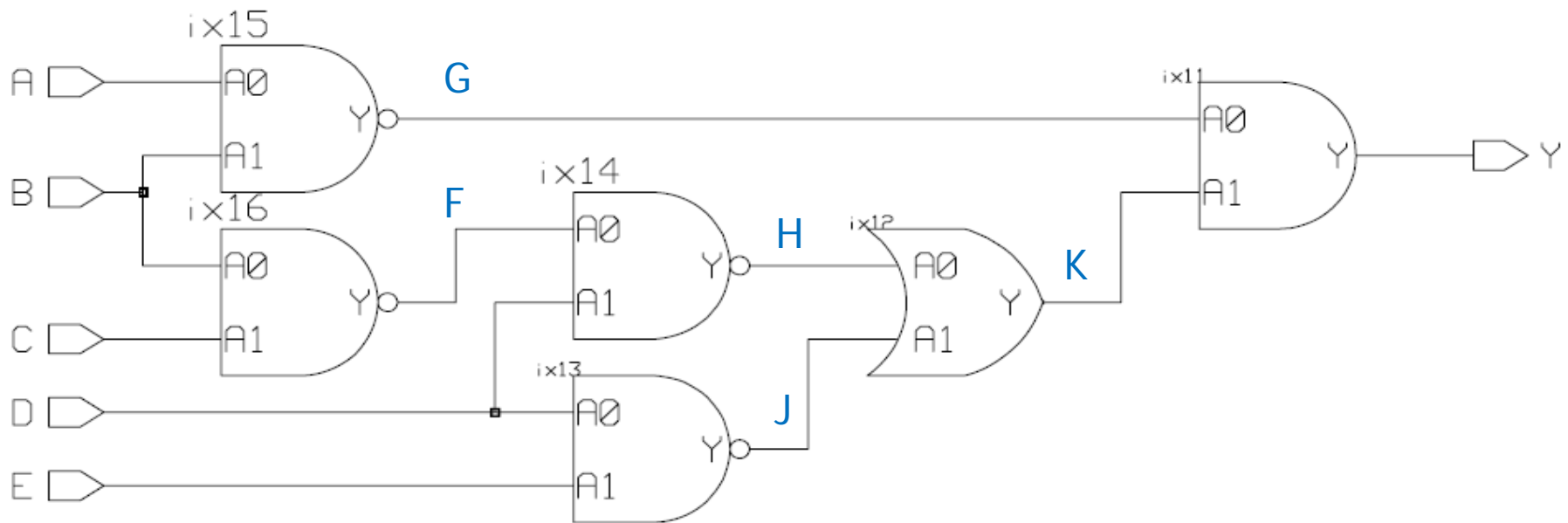Example circuit

Instance/pin names appear in FastScan report



Verilog netlist – testckt.v

// Verilog description of example circuit

```
module testckt ( A, B, C, D, E, Y ) ;  
    input A ;  
    input B ;  
    input C ;  
    input D ;  
    input E ;  
    output Y ;  
    wire F, G, H, J, K;  
  
    NAND2_B   ix15 (.Y (G), .A0 (A), .A1 (B)) ;  
    NAND2_B   ix16 (.Y (F), .A0 (B), .A1 (C)) ;  
    NAND2_B   ix14 (.Y (H), .A0 (F), .A1 (D)) ;  
    NAND2_B   ix13 (.Y (J), .A0 (D), .A1 (E)) ;  
    OR2_B     ix12 (.Y (K), .A0 (H), .A1 (J)) ;  
    AND2_B    ix11 (.Y (Y), .A0 (G), .A1 (K)) ;  
  
endmodule
```

Sample script to test my patterns

Command> `fastscan testckt.v -lib bicmos8hp.atpg -dofile mypats.do`

`mypats.do`

```
set system mode fault
set pattern source external mypats.txt
add faults -all
run
write fault mypats.flt-replace
exit
```

```
--do fault simulation
--use my patterns
--put all faults in the list
--run the simulation
--write results
```

FastScan fault simulation results

1	RE	/ix14/A1	0	DS	/ix16/Y	0	DS	/ix12/A1
1	RE	/ix13/A0	0	DS	/ix14/A1	0	DS	/ix13/Y
1	DS	/ix15/A1	1	DS	/Y	0	DS	/Y
1	DS	/B	1	DS	/ix11/Y	0	DS	/ix11/Y
1	DS	/D	0	DS	/B	0	DS	/ix11/A0
0	DS	/D	1	DS	/ix14/A0	0	DS	/ix15/Y
1	DS	/ix11/A1	1	DS	/ix16/Y	0	DS	/ix11/A1
1	DS	/ix12/Y	0	DS	/ix16/A1	0	DS	/ix12/Y
1	DS	/ix12/A1	0	DS	/C	1	UO	/ix16/A1
1	DS	/ix13/Y	0	DS	/ix16/A0	1	UO	/C
0	DS	/ix13/A1	0	DS	/ix12/A0	1	UO	/ix16/A0
0	DS	/E	0	DS	/ix14/Y	1	UC	/ix11/A0
0	DS	/ix13/A0	1	DS	/ix15/A0	1	UC	/ix15/Y
1	DS	/ix12/A0	1	DS	/A	0	UC	/ix15/A0
1	DS	/ix14/Y	1	DS	/ix13/A1	0	UC	/A
0	DS	/ix14/A0	1	DS	/E	0	UC	/ix15/A1


Test coverage = 38 detected/48 faults = 79%

DS – fault detected in simulation
RE – redundant fault

UO – unobserved fault
UC – uncontrolled fault

UT – untestable fault

Design individual tests for UC/UO faults

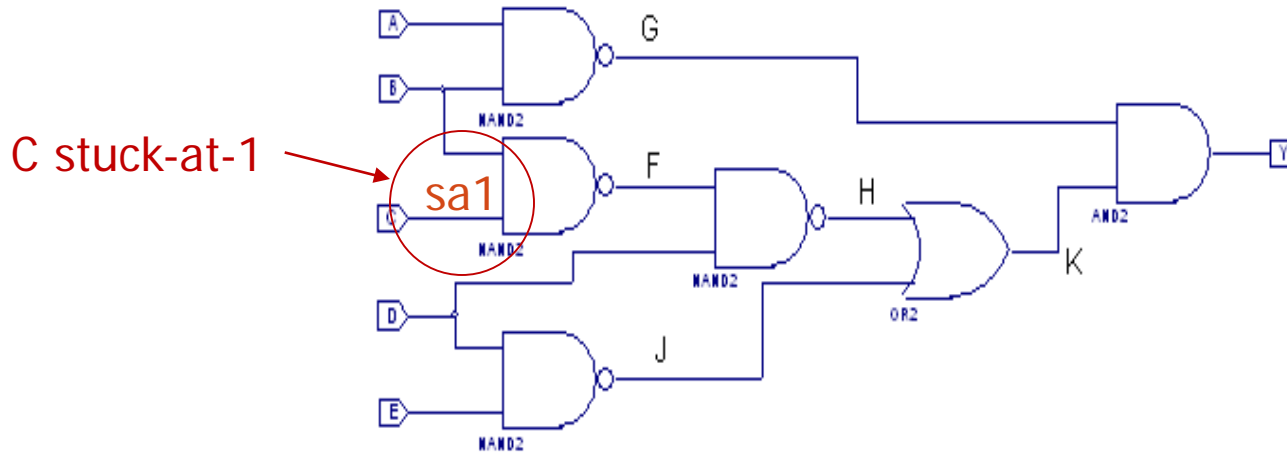

Step	A	B	C	D	E	F	G	H	J	K	Y
control			D*								
observe		1	D*			D					
observe				1		D		D*			
observe								D*	0	D*	
observe							1			D*	D*
Consistency - J				1	1				0		
Consistency - G	0	x					1				
Final values	0	1	D*	1	1	D	1	D*	0	D*	D*

Test vector: ABCDE = {01011} – Raised fault coverage to 80%

Sample script using ATPG

Command> fastscan testckt.v -lib bicmos8hp.atpg -dofile atpg.do

atpg.do

```
set system mode atpg
set fault type stuck
add faults -all
set pattern source internal
create patterns -auto
run
write fault atpg.flt -replace
save patterns atpg.pat -replace
report faults > atpg.faults
report statistics > atpg.stats
exit
```

```
--ATPG to produce patterns
--test stuck-at faults
--add all s-a faults to the list
--fault sim with atpg patterns
--create the patterns
--run fault simulation
--write fault list
--save the patterns
--report detected faults
--fault coverage statistics
```


ATPG statistics (stuck-at faults)

Fault Classes	#faults (total)
---------------	-----------------

-----	-----
FU (full)	48
-----	-----

DS (det_simulation)	46 (95.83%)
---------------------	-------------

RE (redundant)	2 (4.17%)
-----	-----

Coverage	
----------	--

-----	-----
test_coverage	100.00%

fault_coverage	95.83%
----------------	--------

atpg_effectiveness	100.00%
-----	-----

#test_patterns	8
----------------	---

#simulated_patterns	64
---------------------	----

Generated 8 test patterns

PI "01100"	PO "1"
------------	--------

PI "01011"	PO "0"
------------	--------

PI "00001"	PO "1"
------------	--------

PI "00111"	PO "0"
------------	--------

PI "00010"	PO "1"
------------	--------

PI "01111"	PO "1"
------------	--------

PI "11110"	PO "0"
------------	--------

PI "10100"	PO "1"
------------	--------

Red: the only one of my
"random" patterns used.

Tessent Documentation

- Open the Tessent InfoHub:

mgcdocs \$TESSENT_DOCS

- Click “Tessent” in left pane
- Under “ATPG and Tessent TestKompress”
 - “Scan and ATPG Process Guide”
 - describes basic test procedures and terminology
 - “ATPG and Failure Diagnosis Tools Reference Manual”
 - lists all commands that can be used in FastScan and related tools
 - “Tessent DFTAdvisor Reference Manual”
 - is the reference that we will use for DFT activities