

# Verilog Modeling for Synthesis

Multiplier Design (Nelson model)


# “Add and shift” binary multiplication

---


Multiplicand	→	1 1 0 1	(13)
Mutliplier	→	1 0 1 1	(11)
		<hr/>	
		1 1 0 1	
		1 1 0 1	
		<hr/>	
Partial products	}	1 0 0 1 1 1	
		0 0 0 0	
		<hr/>	
		1 0 0 1 1 1	
		1 1 0 1	
		<hr/>	
		1 0 0 0 1 1 1 1	(143)



# System Example: 8x8 multiplier

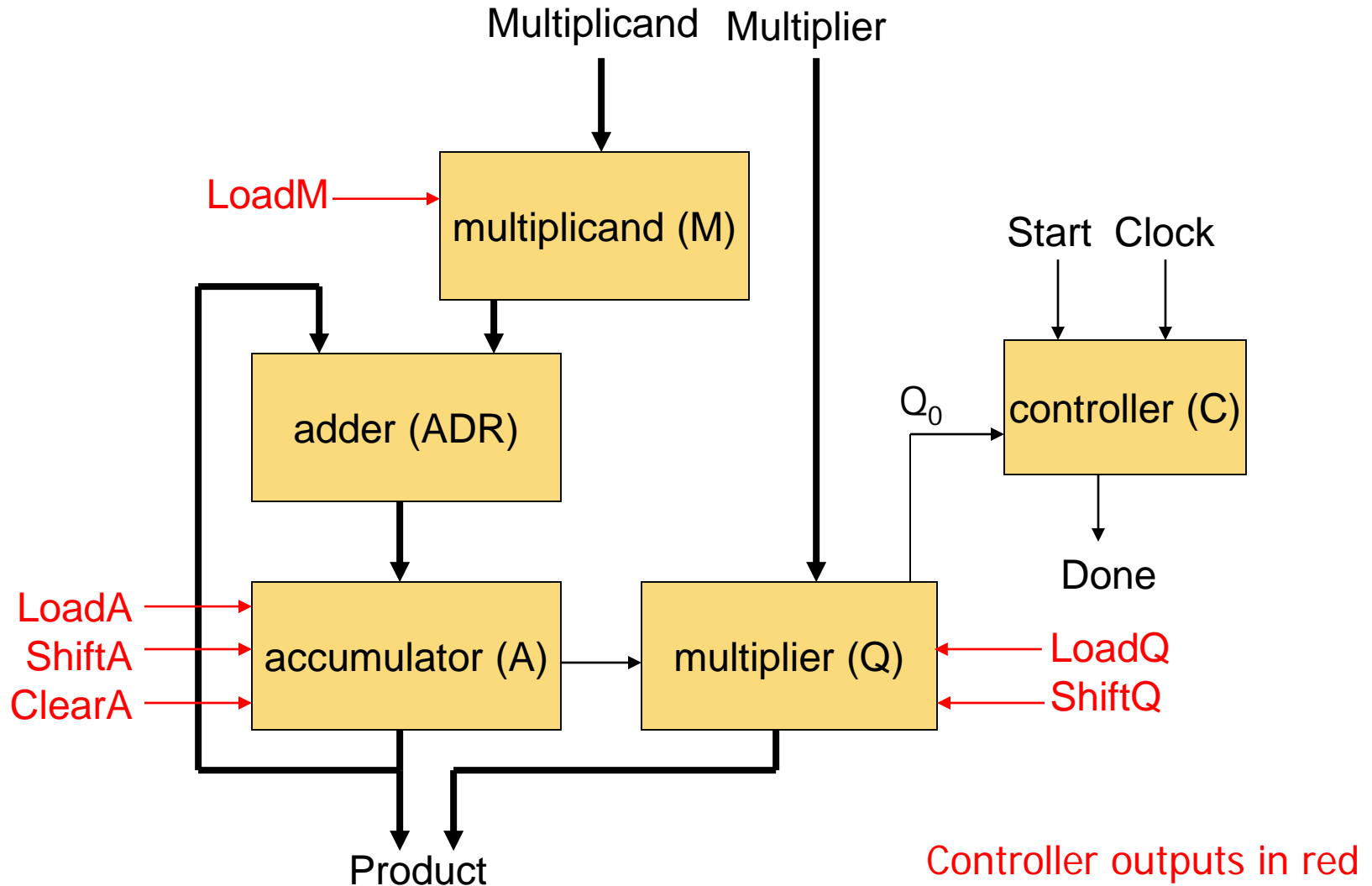


# Multiply Algorithm

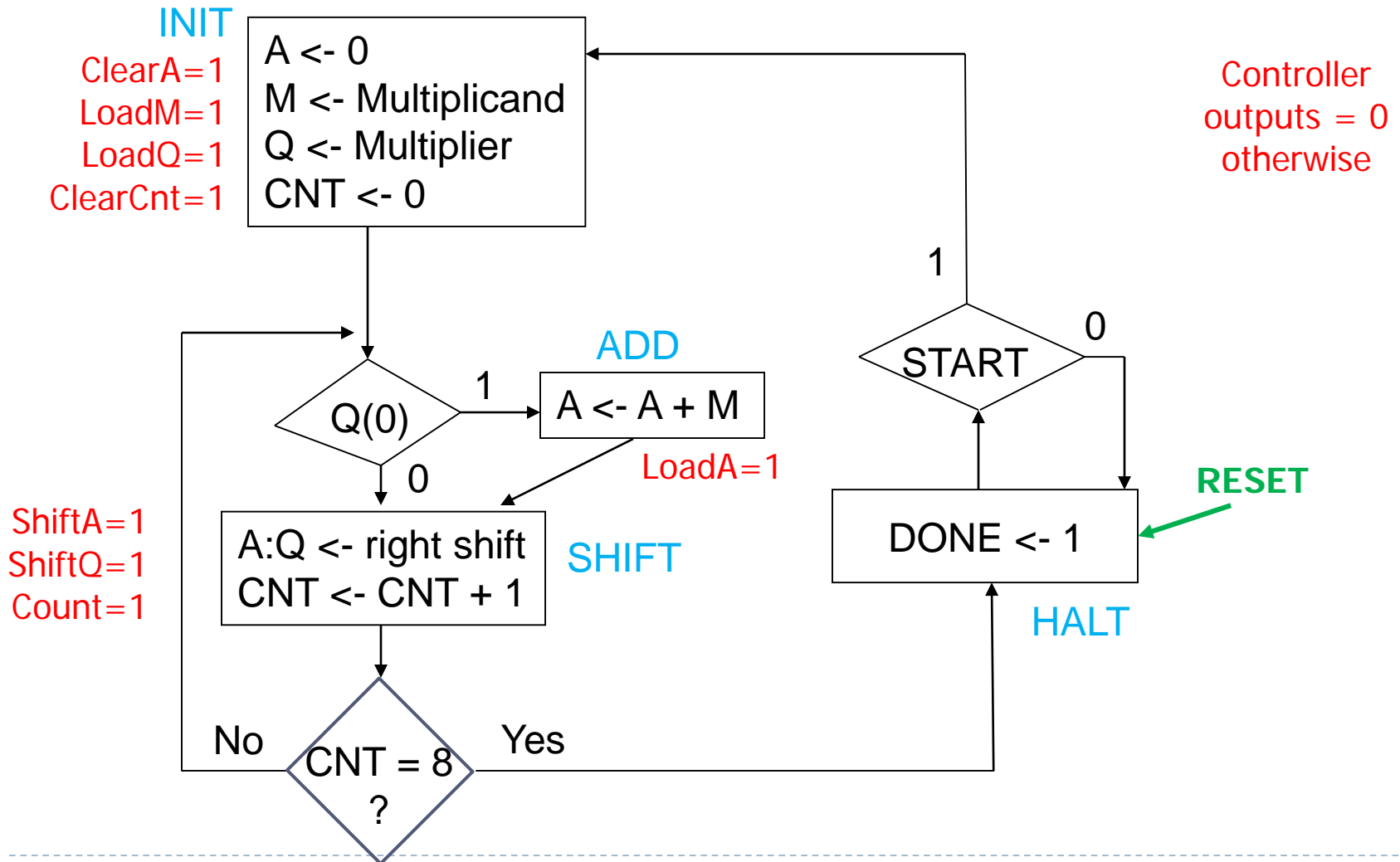

# Example: $6 \times 5 = 110 \times 101$

---



M	A	Q	CNT	State	
110	0000	101	0	INIT	Multiplicand->M, 0->A, Multiplier->Q, CNT=0
	+ 110			ADD	(Since Q0=1) A = A+M
	0110	101	0		
	0011	010	1	SHIFT	Shift A:Q, CNT+1=1 (CNT not 3 yet) (skip ADD, since Q0 = 0)
	0001	101	2	SHIFT	Shift A:Q, CNT+1=2 (CNT not 3 yet)
	+ 110			ADD	(Since Q0 = 1) A = A+M
	0111	101	2		
	0011	110	3	SHIFT	Shift A:Q, CNT+1=2 (CNT= 3)
	0011	110	3	HALT	Done = 1

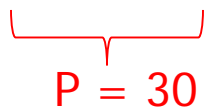
  
P = 30


  
# Timing considerations

Be aware of register/flip-flop setup and hold constraints



# Multiplier – Top Level

---

```
module MultiplierTop #(parameter N = 4) //N is data width
(
  input Clock, Reset, //control inputs
  input [N-1:0] Multiplicand, //N-bit data inputs
  input [N-1:0] Multiplier,
  output [2*N-1:0] Product, //2N-bit product output
  output Halt //indicates product ready
);
wire [N-1:0] RegQ, RegM, Sum; // Q and M register and adder outputs
wire [N:0] RegA; // A register output
wire Cout, Start, Add, Shift; // Adder carry and controller outputs

assign Product = {RegA[N-1:0],RegQ}; //product = A:Q
```

Continued on next slide

---



# Multiplier – Top Level (continued)

---

```
ShiftReg #(N) M_Reg          // Multiplicand register: load at start
(.Din(Multiplicand), .Dout(RegM), .ShiftIn(0), .Clock(Clock), .Clear(0), .Shift(0),
 .Load(Start));
```

```
ShiftReg #(N) Q_Reg          // Multiplier register: load at start, shift
(.Din(Multiplier), .Dout(RegQ), .ShiftIn(RegA[0]), .Clock(Clock), .Clear(0), .Shift(Shift),
 .Load(Start));
```

```
ShiftReg #(N+1) A_Reg        // Accumulator register: clear, load, shift
(.Din({Cout,Sum}), .Dout(RegA), .ShiftIn(0), .Clock(Clock), .Clear(Start), .Shift(Shift),
 .Load(Add));
```

```
AdderN #(N) Adder           // Accumulator register: clear, load, shift
(.A(RegA[N-1:0]), .B(RegM), .Cin(0), .Cout(Cout), .Sum(Sum));
```

```
MultControl #(N) Ctrl        // Controller
(.Clock(Clock), .Reset(Reset), .Q0(RegQ[0]), .Start(Start), .Add(Add), .Shift(Shift),
 .Halt(Halt));
```

**endmodule**

---





# Multi-function N-bit register: clear, load, shift

---

```
module ShiftReg #(parameter N = 4) // N is data width
(
  input [N-1:0] Din,           //parallel inputs
  output reg [N-1:0] Dout,     //register outputs
  input ShiftIn,              //shift input
  input Clock,                //clock
  input Clear,                //clear function select
  input Shift,                //shift function select
  input Load                   //load function select
);
always @(posedge Clock) //rising-edge triggered
begin
  if (Clear == 1)
    Dout <= 0; // clear the register
  else if (Load == 1)
    Dout <= Din; // load parallel inputs
  else if (Shift == 1)
    Dout <= {ShiftIn, Dout[N-1:1]}; // shift right
  else
    Dout <= Dout; // default is "hold"
end
endmodule
```

---



# N-bit adder (behavioral)

---

```
module AdderN #(parameter N = 4)
(
  input [N-1:0] A, B,           //N-bit adder inputs
  input Cin,                   //carry input
  output [N-1:0] Sum,          //N-bit adder output
  output Cout,                 //carry output
);
wire temp;                    //temp bit 0

// Cout = bit N+1, Sum = bits N:1, Cin+1 = carry into bit 1 if Cin=1
assign {Cout,Sum,temp} = {1'b0,A, Cin} + {1'b0, B, 1'b1};
endmodule
```



# Multiplier Controller

---

```
module MultControl #(parameter N = 4) //parameter for bit count
(
    input Clock, Reset, Q0,           //control and testable inputs
    output Start, Add, Shift, Halt    //controller outputs (Moore machine)
);

reg [4:0] state;                     //five states (one hot)
//One-hot state assignments for five states
parameter StartS=5'b00001, TestS=5'b00010, AddS=5'b00100, ShiftS=5'b01000,
        HaltS=5'b10000;

reg [N-1:0] Count; //iteration count
wire C0;          // C0 = 1 if count < N

// 2-bit counter for #iterations
always @(posedge Clock)
    if (Start == 1) Count <= 0; // clear in Start state
    else if (Shift == 1) Count <= Count + 1; // increment in Shift state

assign C0 = (Count == N-1) ? 1 : 0; //detect Nth iteration
```

---



# Controller – State transition process

---

//State transitions

```
always @(posedge Clock, posedge Reset) //detect positive edge of Clock or Reset
    if (Reset==1) state <= StartS;    //enter StartS state on Reset
    else
        case (state) // next states
            StartS: state <= TestS;    // go to TestS
            TestS: if (Q0) state <= AddS; // go to AddS if Q0=1
                   else state <= ShiftS; // go to ShiftS if Q0=0
            AddS:  state <= ShiftS;    // go to ShiftS
            ShiftS: if (C0) state <= HaltS; // go to HaltS if Count = N
                   else state <= TestS; // go to TestS if Count < N
            HaltS: state <= HaltS;    // stay in HaltS
        endcase

// Moore model outputs
assign Start = state[0]; // Start=1 in state StartS, else 0
assign Add = state[2];  // Add=1 in state AddS, else 0
assign Shift = state[3]; // Shift=1 in state ShiftS, else 0
assign Halt = state[4]; // Halt=1 in state HaltS, else 0
endmodule
```

---



# Multiplier simulation “do file”

---

```
add wave Clock Reset Multiplicand Multiplier Product
add wave RegM RegQ RegA Sum Cout Start Add Shift Halt
add wave /Multiplier/Ctrl/state /Multiplier/Ctrl/Count
force Clock 0 0, 1 5 -repeat 10
force Reset 0 0, 1 10, 0 20
force Multiplicand 16#F 0
force Multiplier 16#F 0
run 160
```

Computes 15 x 15 (4-bit inputs, 8-bit product)

---



# Simulation results

