

Figure 6.7: Final combinational circuit controllabilities.

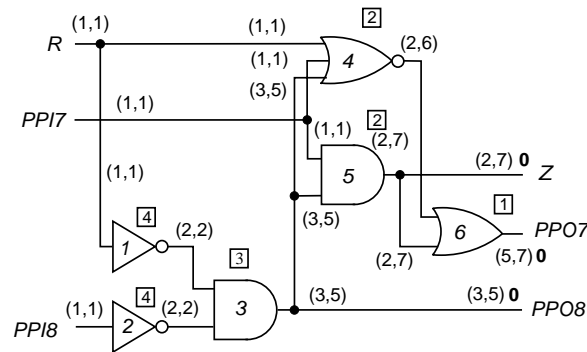


Figure 6.8: Combinational circuit with observabilities through level 1.

We now compute observabilities, which are shown in **boldface** in the figures after the  $(CC0, CC1)$  ordered pairs. We process logic gates in level order from POs backwards to PIs. In Figure 6.8, we assign 0 to PO  $Z$  and PPOs  $PPO7$  and  $PPO8$ . This causes observability 0 to be assigned to gate 6, as well. We cannot yet assign observabilities to gates 5 and 3, because they are fanout stems, and not all fanout branch observabilities are known. So, we process OR gate 6 at level 1 in Figure 6.9. For each input, according to Figure 6.3, we have:

$$\begin{aligned} CO(4) &= CC0(5) + CO(6) + 1 = 2 + 0 + 1 = 3 \\ CO(5) &= CC0(4) + CO(6) + 1 = 2 + 0 + 1 = 3 \end{aligned}$$

This is shown in Figure 6.9. Next, we process NOR gate 4 at level 2 in Figure 6.9. According to Figure 6.3, for a three-input NOR gate:

$$CO(\text{1st input}) = CC0(\text{2nd input}) + CC0(\text{3rd input}) + CO(\text{output}) + 1$$

Therefore,

$$\begin{aligned} CO(R) &= CC0(PPI7) + CC0(3) + CO(4) + 1 = 1 + 3 + 3 + 1 = 8 \\ CO(PPI7) &= CC0(R) + CC0(3) + CO(4) + 1 = 1 + 3 + 3 + 1 = 8 \\ CO(3) &= CC0(R) + CC0(PPI7) + CO(4) + 1 = 1 + 1 + 3 + 1 = 6 \end{aligned}$$