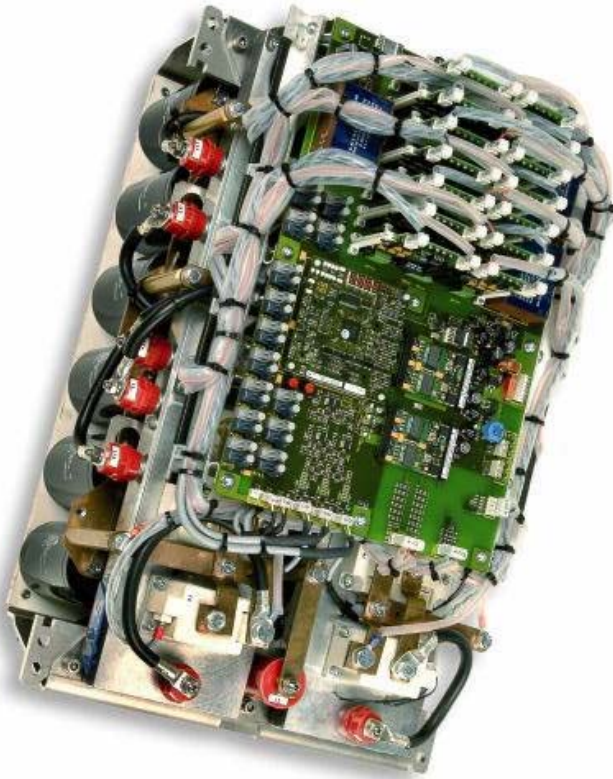




FUNDAMENTALS OF ENGINEERING (FE) EXAMINATION REVIEW



ELECTRICAL ENGINEERING

*Charles A. Gross, Professor Emeritus
Electrical and Comp Engineering
Auburn University Broun 212
334.844.1812
gross@eng.auburn.edu*

www.railway-technology.com

FE EXAM FORMAT

- 8 hours long
 - 4-hour morning session; 120 multiple-choice questions.
 - 4-hour afternoon session; 60 multiple-choice questions.
- Closed book
 - Reference material is supplied
- Morning session
 - material common to all engineering disciplines
- Afternoon session, examinees opt to take
 - a general exam, or
 - a discipline-specific exam

For more information:

<http://www.ncees.org/exams/fundamentals/>


EE Content (9 areas)

1.	Circuits	16%
2.	Power	13%
3.	Electromagnetics	7%
4.	Control Systems	10%
5.	Communications	9%
6.	Signal Processing	8%
7.	Electronics	15%
8.	Digital Systems	12%
9.	Computer Systems	10%

EE Review Problems

1. **dc Circuits**
2. **ac Circuits**
3. **1st Order Transients**
4. **3-phase Circuits; pf correction**
5. **Control**
6. **Signal Processing**
7. **Electronics**
8. **Digital Systems**

1. dc Circuits:

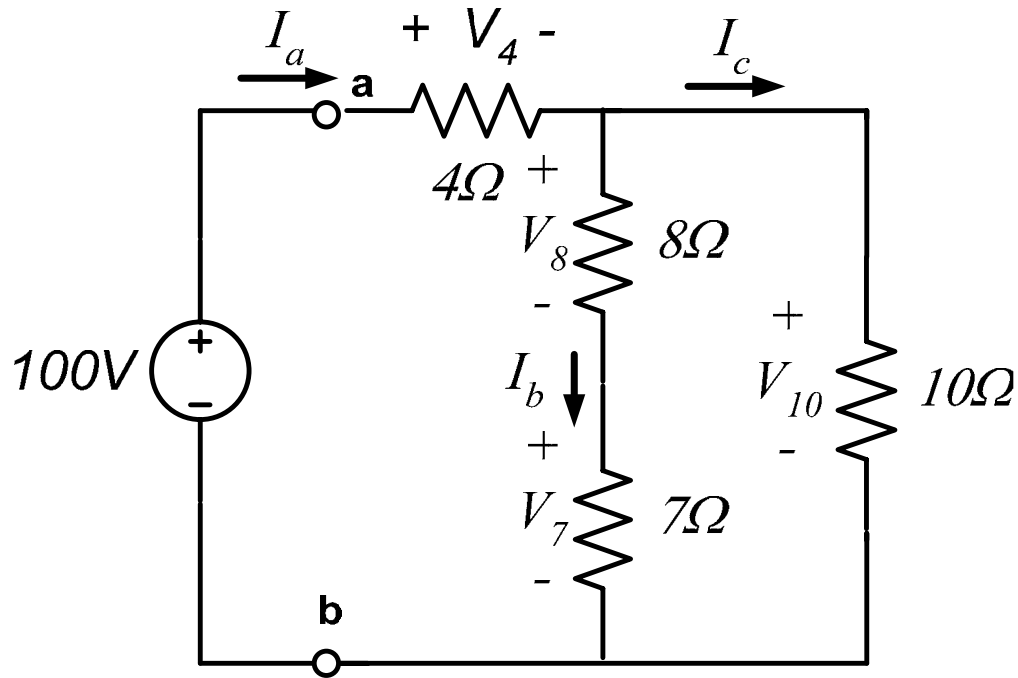

Find all voltages, currents, and powers.


Solution

The 8Ω and 7Ω resistors are in series:

$$R1 = 8 + 7 = 15\Omega$$

$R1$ and 10Ω are in parallel:
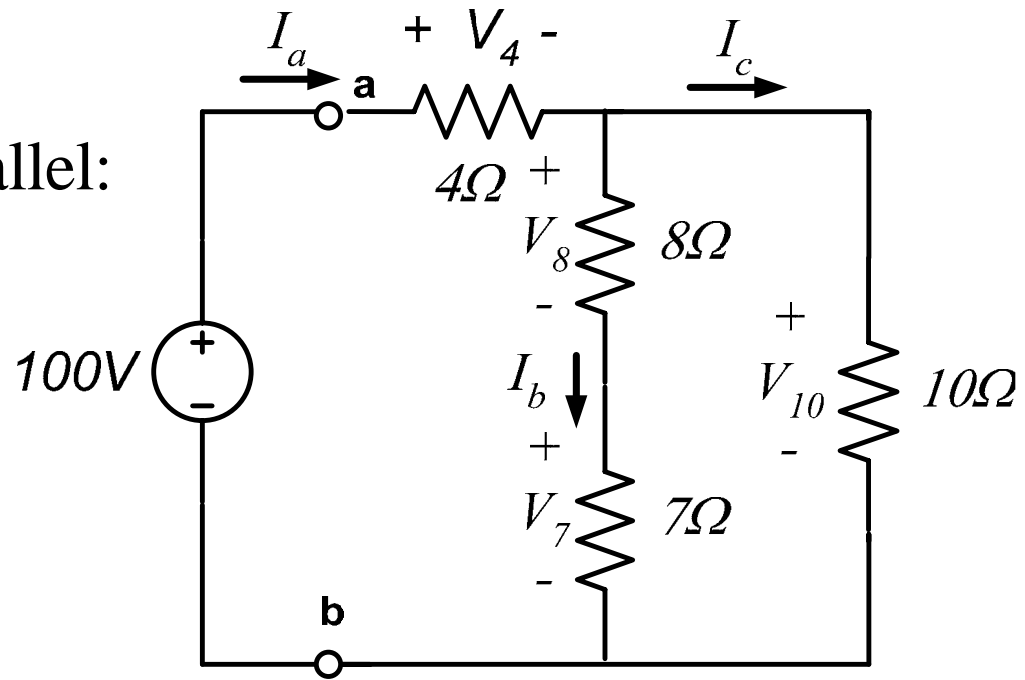
$$R2 = \frac{1}{\frac{1}{10} + \frac{1}{R1}}$$
$$= \frac{10(R1)}{10 + R1} = 6\Omega$$



Solution

4Ω and R_2 are in series:


$$R_{ab} = 4 + R_2 = 10\Omega$$

ΩL :

$$I_a = \frac{V_{ab}}{R_{ab}} = \frac{100}{10} = 10A$$

$$V_4 = 4 \cdot I_a = 40V \quad (\Omega L)$$

$$V_{10} = 100 - 40 = 60V \quad (KVL)$$

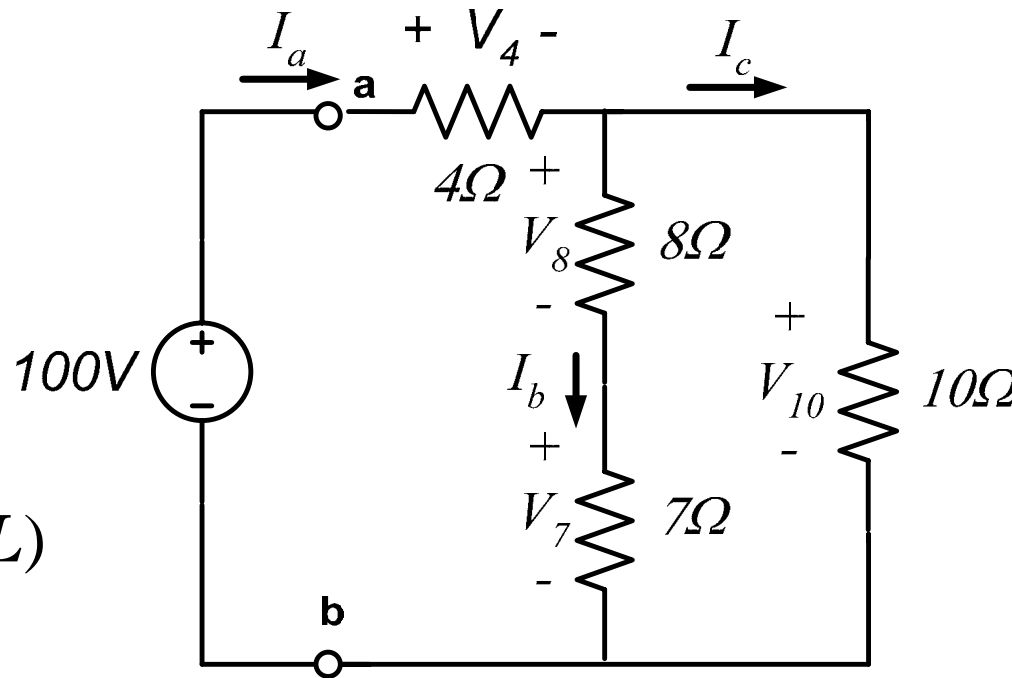

Solution


$$I_c = \frac{V_{10}}{10} = \frac{60}{10} = 6A \quad (\Omega L)$$

KCL:

$$I_b = I_a - I_c = 10 - 6 = 4A$$

$$V_8 = 8 \cdot I_b = 32V \quad (\Omega L)$$
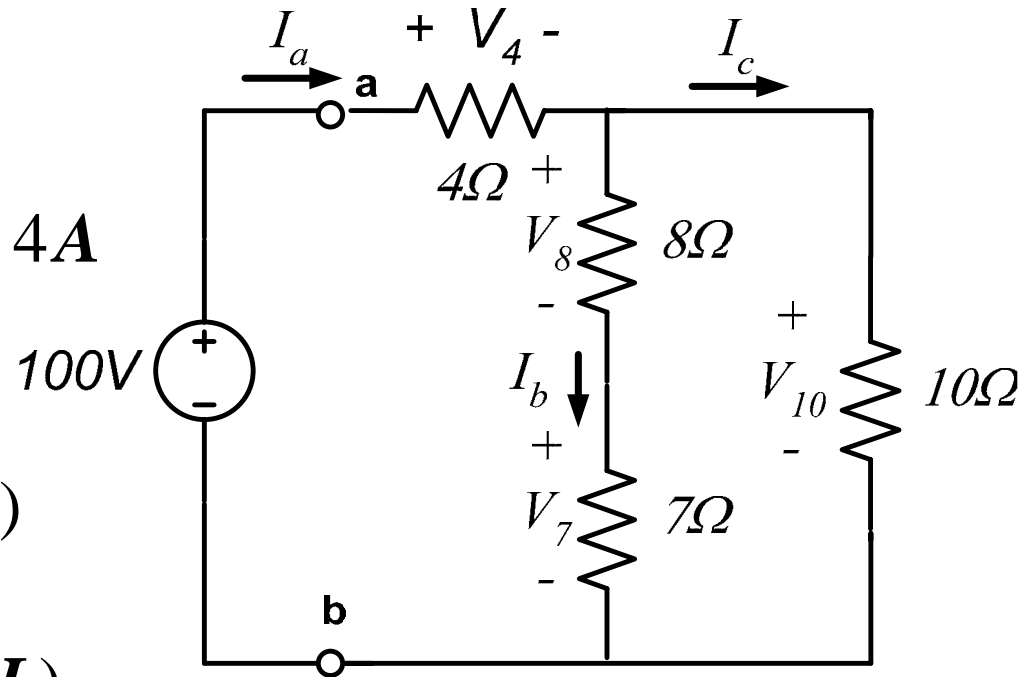
$$V_7 = 7 \cdot I_b = 28V \quad (\Omega L)$$



Absorbed Powers...

$$R_4 \cdot I_a^2 = 4(10)^2 = 400W$$

$$R_{10} \cdot I_c^2 = 10(6)^2 = 360W$$

$$R_7 \cdot I_b^2 = 7(4)^2 = 112W$$

$$R_8 \cdot I_b^2 = 8(4)^2 = 128W$$

Total Absorbed Power = 1000W

Power Delivered by Source = $V_s \cdot I_a = 100(10) = 1000W$


In General:

$$***P_{ABS} = P_{DEV}***$$

(Tellegen's

Theorem)

2. ac Circuits

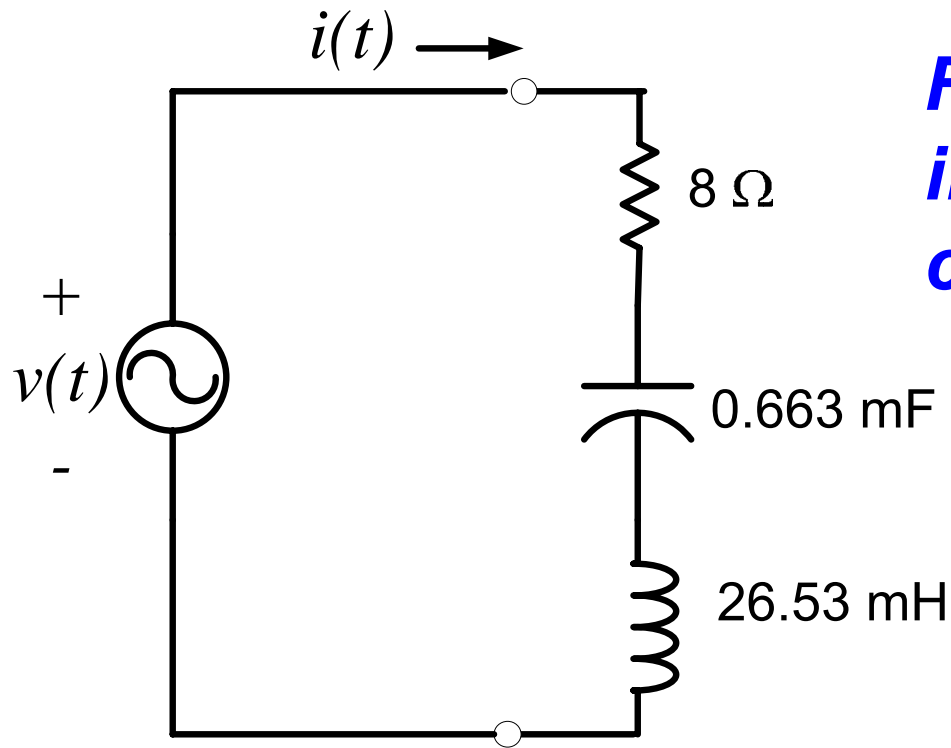

Find "everything" in the given circuit.

$$v(t) = 141.4 \cos(377t) \quad V$$

Solution

$$v(t) = 141.4 \cos(377t) \quad V$$

$$\text{(radian) frequency} = \omega = 377 \text{ rad} / s$$

$$\text{(cyclic) frequency} = f = \frac{\omega}{2\pi} = 60 \text{ Hz}$$

$$\text{Period} = \frac{1}{f} = \frac{1}{60} = 16.67 \text{ ms}$$

Solution

To solve the problem, we convert the circuit into an "ac circuit":

R, L, C elements $\rightarrow \bar{Z}$ (impedance)

v, i sources $\rightarrow \bar{V}, \bar{I}$ (phasors)

$$R: \bar{Z}_R = R + j0 = 8 + j0$$

$$L: \bar{Z}_L = 0 + j\omega L = 0 + j(0.377)(26.53) = 0 + j10$$

$$C: \bar{Z}_C = 0 + \frac{1}{j\omega C} = 0 - j \frac{1}{0.377(0.663)} = 0 - j4$$

Solution


$$v(t) = V_{MAX} \cos(\omega t + \alpha)$$

To convert to a phasor... $\bar{V} = \frac{V_{MAX}}{\sqrt{2}} \angle \alpha$

For example.. $v(t) = 141.4 \cos(377t)$

$$\bar{V} = \frac{V_{MAX}}{\sqrt{2}} \angle \alpha = 100 \angle 0^\circ$$

The "ac circuit"

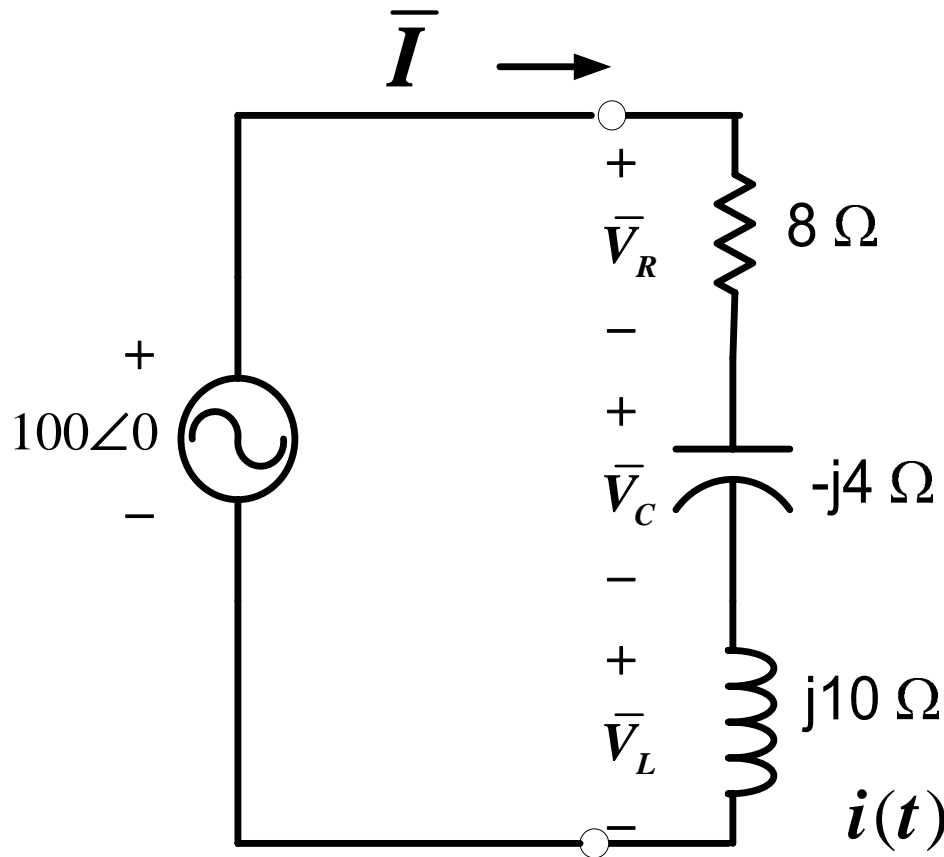

$\Omega L(ac)$:

$$\bar{I} = \frac{\bar{V}}{\bar{Z}}$$

$$= \frac{100}{8 + j10 - j4}$$

$$= 10\angle -36.9^\circ$$

$$i(t) = 14.14 \cdot \cos(377t - 36.9^\circ)$$

Solving for voltages

$$\bar{V}_R = \bar{Z}_R \cdot \bar{I} = (8)(10\angle -36.9^\circ) = 80\angle -36.9^\circ \text{ V}$$

$$v_R(t) = 113.1 \cdot \cos(377t - 36.9^\circ)$$

$$\bar{V}_C = \bar{Z}_C \cdot \bar{I} = (-j4)(10\angle -36.9^\circ) = 40\angle -126.9^\circ \text{ V}$$

$$v_C(t) = 56.57 \cdot \cos(377t - 126.9^\circ)$$

$$\bar{V}_L = \bar{Z}_L \cdot \bar{I} = (j10)(10\angle -36.9^\circ) = 100\angle 53.1^\circ \text{ V}$$

$$v_L(t) = 141.4 \cdot \cos(377t + 53.1^\circ)$$

Absorbed powers $\bar{S} = \bar{V} \cdot \bar{I}^* = P + jQ$

$$\bar{S}_R = \bar{V}_R \cdot \bar{I}^* = 80 \angle -36.9^\circ (10 \angle -36.9^\circ)^* = 800 + j0$$

$$\bar{S}_C = \bar{V}_C \cdot \bar{I}^* = 40 \angle -126.9^\circ (10 \angle -36.9^\circ)^* = 0 - j400$$

$$\bar{S}_L = \bar{V}_L \cdot \bar{I}^* = 100 \angle 53.1^\circ (10 \angle -36.9^\circ)^* = 0 + j1000$$

$$\bar{S}_{TOT} = \bar{S}_R + \bar{S}_C + \bar{S}_L = 800 + j600$$

$$P_{TOT} = 800 \text{ watts}; \quad Q_{TOT} = 600 \text{ vars};$$

$$S_{TOT} = |\bar{S}_{TOT}| = 1000 \text{ VA}$$

Delivered power

$$\bar{S}_S = \bar{V}_S \cdot \bar{I}^* = 100 \angle 0^\circ (10 \angle -36.9^\circ)^* = 800 + j600$$

$$\bar{S}_S = \bar{S}_{TOT} = 800 + j600$$


$$P_S = P_{TOT} = 800 \text{ watts}$$

$$Q_S = Q_{TOT} = 600 \text{ var s}$$

In General: $P_{ABS} = P_{DEV}$ $Q_{ABS} = Q_{DEV}$

(Tellegen's Theorem)

3. 1st Order Transients

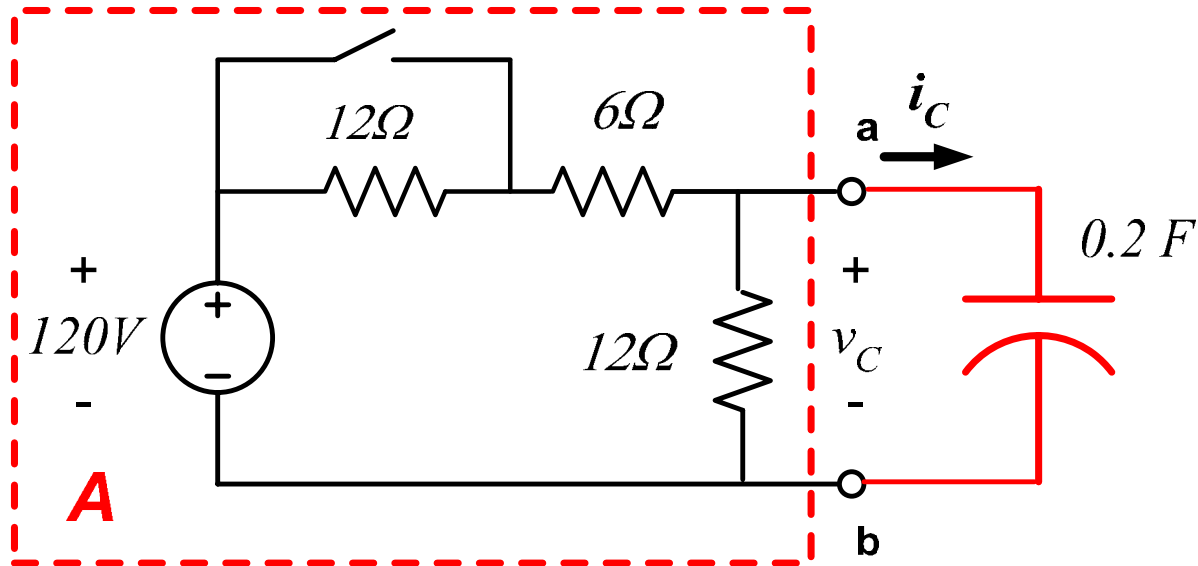

a. The switch is closed at $t = 0$. Find and plot $v_C(t)$.

Solution....

In general:

$$t \leq 0: \quad v_C(t) = K_1 + K_2$$
$$t > 0: \quad v_C(t) = K_1 + K_2 \cdot e^{-t/\tau}$$
$$\tau = R_{ab} \cdot C$$

Our job is to determine K_1 , K_2 , and $\tau (R_{ab})$

Solution....

For a capacitor:

$$i_C = C \cdot \frac{dv_C}{dt}$$


C's are OPENS to dc
 $v_C(t)$ cannot change in zero time

$$v_C(t) = K_1 + K_2 \cdot e^{-t/\tau}$$

$$v_C(0^-) = v_C(0) = v_C(0^+) = K_1 + K_2$$

$$v_C(\infty) = K_1$$


Solution: $T < 0$; switch and "C" OPEN

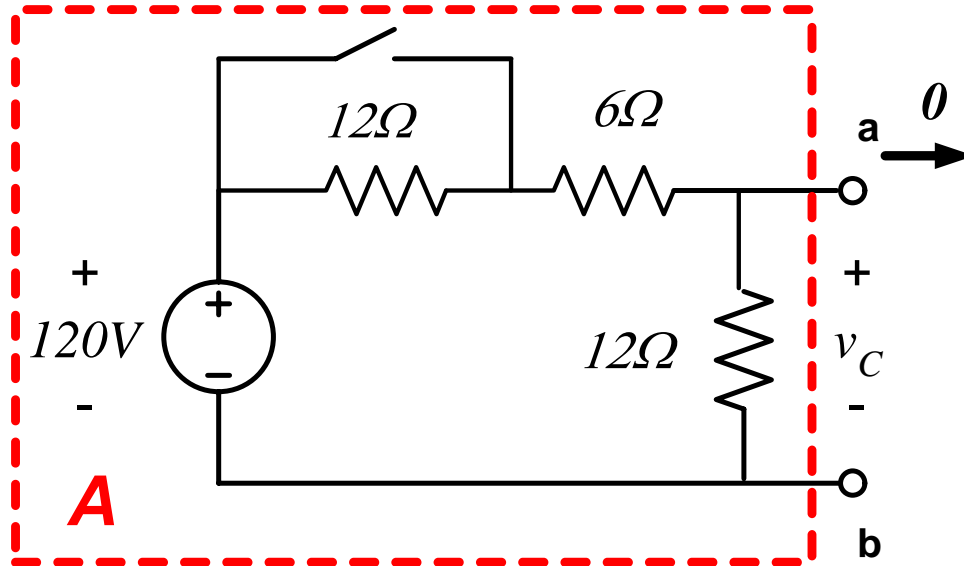

$$K_1 + K_2 = 48$$

$$v_C = \frac{120}{12 + 6 + 12}(12) = 48 \text{ V}$$

Solution: $T > 0$; switch CLOSED

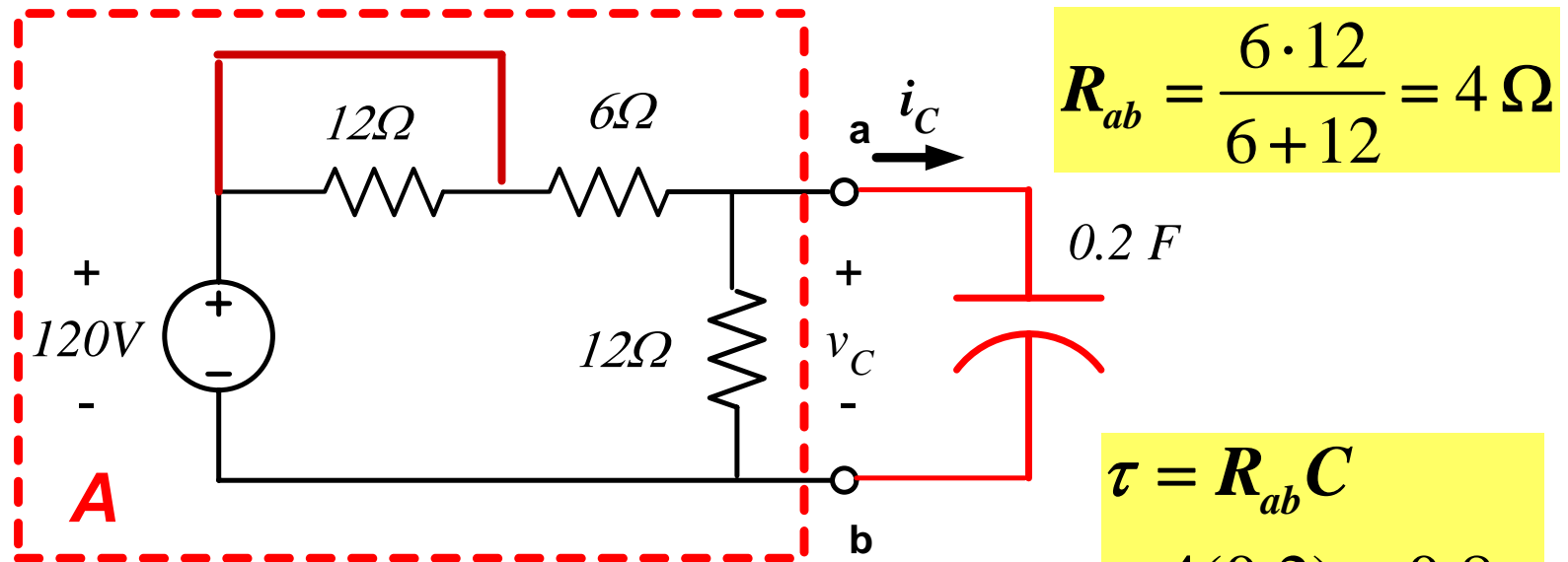

$$v_C(\infty) = \frac{120}{0 + 6 + 12}(12) = 80 \text{ V}$$

$$K_1 = 80$$


Solution....

$$t \leq 0: \quad v_C(t) = K_1 + K_2 = 48$$

$$t > 0: \quad v_C(t) = K_1 + K_2 \cdot e^{-t/\tau}$$

$$v_C(t) = 80 - 32 \cdot e^{-1.25t}$$

3. 1st Order Transients

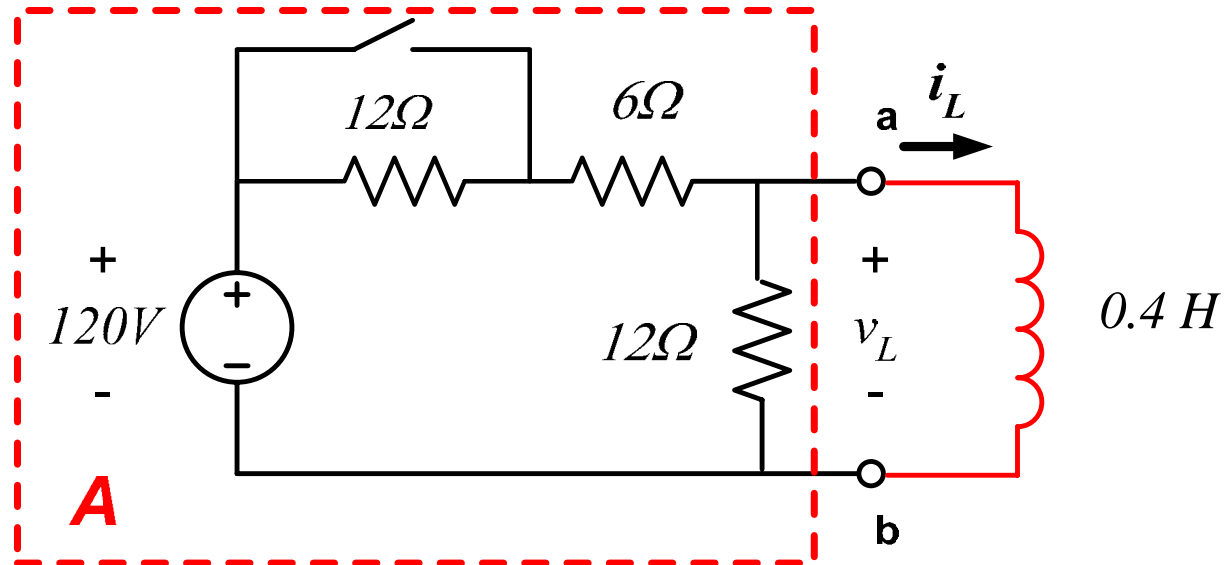

b. The switch is closed at $t = 0$. Find and plot $i_L(t)$.

Solution....

In general:

$$t \leq 0: \quad i_L(t) = K_1 + K_2$$

$$t > 0: \quad i_L(t) = K_1 + K_2 \cdot e^{-t/\tau}$$

$$\tau = \frac{L}{R_{ab}}$$

Our job is to determine K_1 , K_2 , and τ (R_{ab})

Solution....

For an inductor: $v_L = L \cdot \frac{di_L}{dt}$

L's are SHORTS to dc


$i_L(t)$ cannot change in zero time

$$i_L(t) = K_1 + K_2 \cdot e^{-t/\tau}$$

$$i_L(0^-) = i_L(0) = i_L(0^+) = K_1 + K_2$$

$$i_L(\infty) = K_1$$


Solution: $T < 0$; switch OPEN; L SHORT

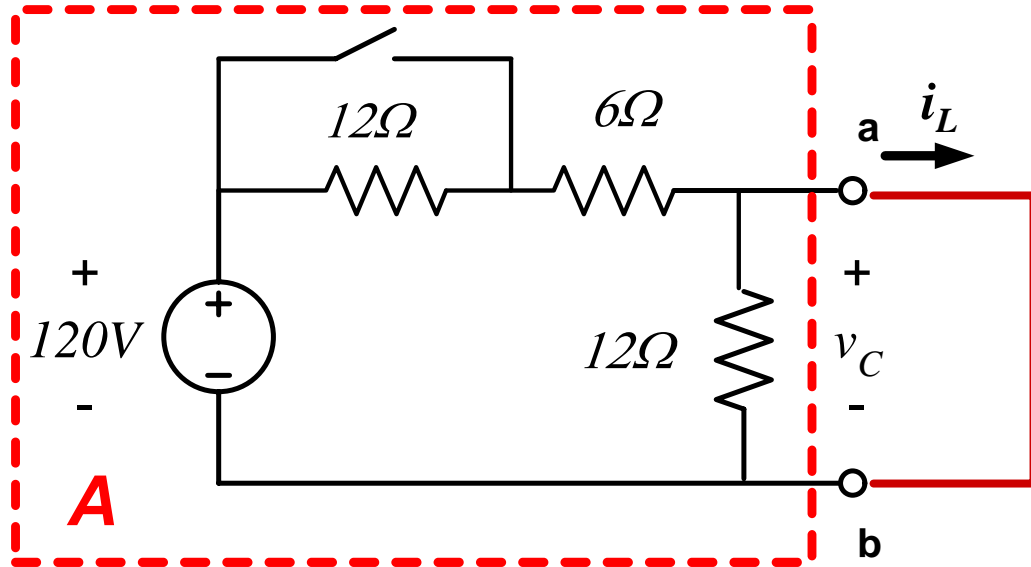

$$i_L = \frac{120}{12 + 6} = 6.667 \text{ A}$$

$$K_1 + K_2 = 6.667$$

Solution: $T > 0$; switch CLOSED

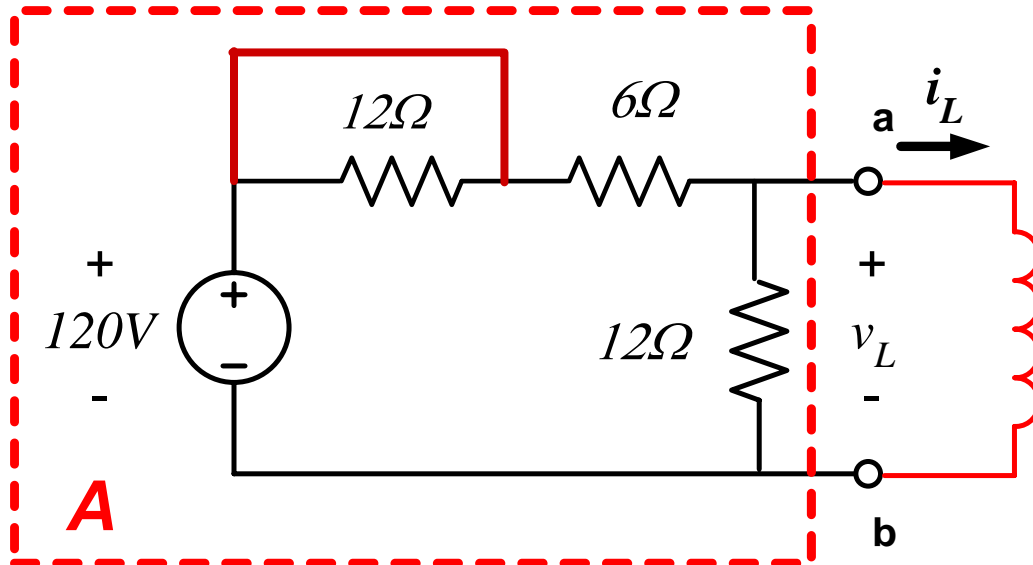

$$R_{ab} = \frac{6 \cdot 12}{6 + 12} = 4 \Omega$$

$0.4 H$

$$\tau = \frac{L}{R_{ab}} = \frac{0.4}{4} = 0.1 s$$

$$i_L(\infty) = \frac{120}{0 + 6 + 0} = 20 A$$

$$K_1 = 20$$


Solution....

$$t \leq 0: \quad i_L(t) = K_1 + K_2 = 6.667$$

$$t > 0: \quad i_L(t) = K_1 + K_2 \cdot e^{-t/\tau}$$


$$i_L(t) = 20 - 13.33 \cdot e^{-10t}$$

4. Three-Phase Circuits: pf correction

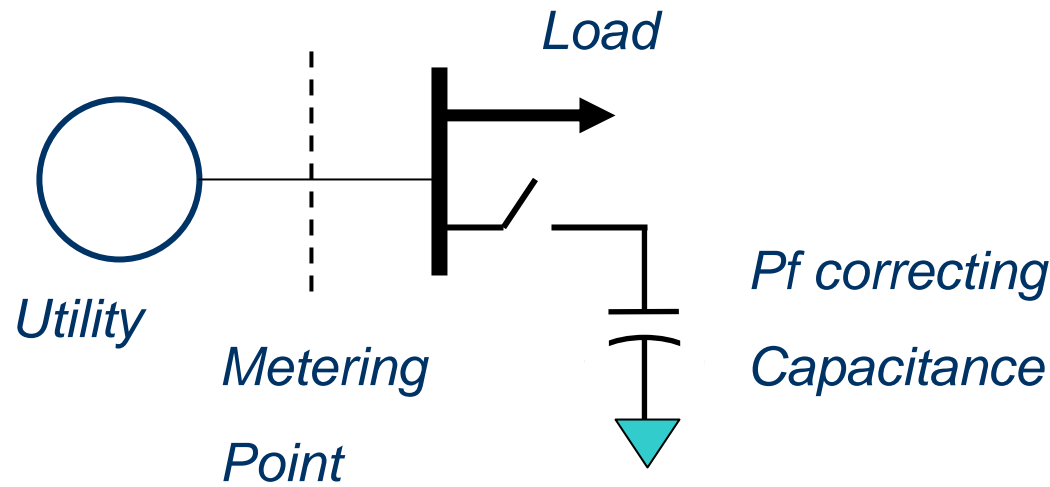

A 3ph-load of 3500 kVA @ pf = 0.7754 lag is supplied from a 12.47 kV system. The Utility will provide a discount, if $\text{pf} \leq 0.93$. Design an appropriate pf-correcting bank.

a. Find all voltages

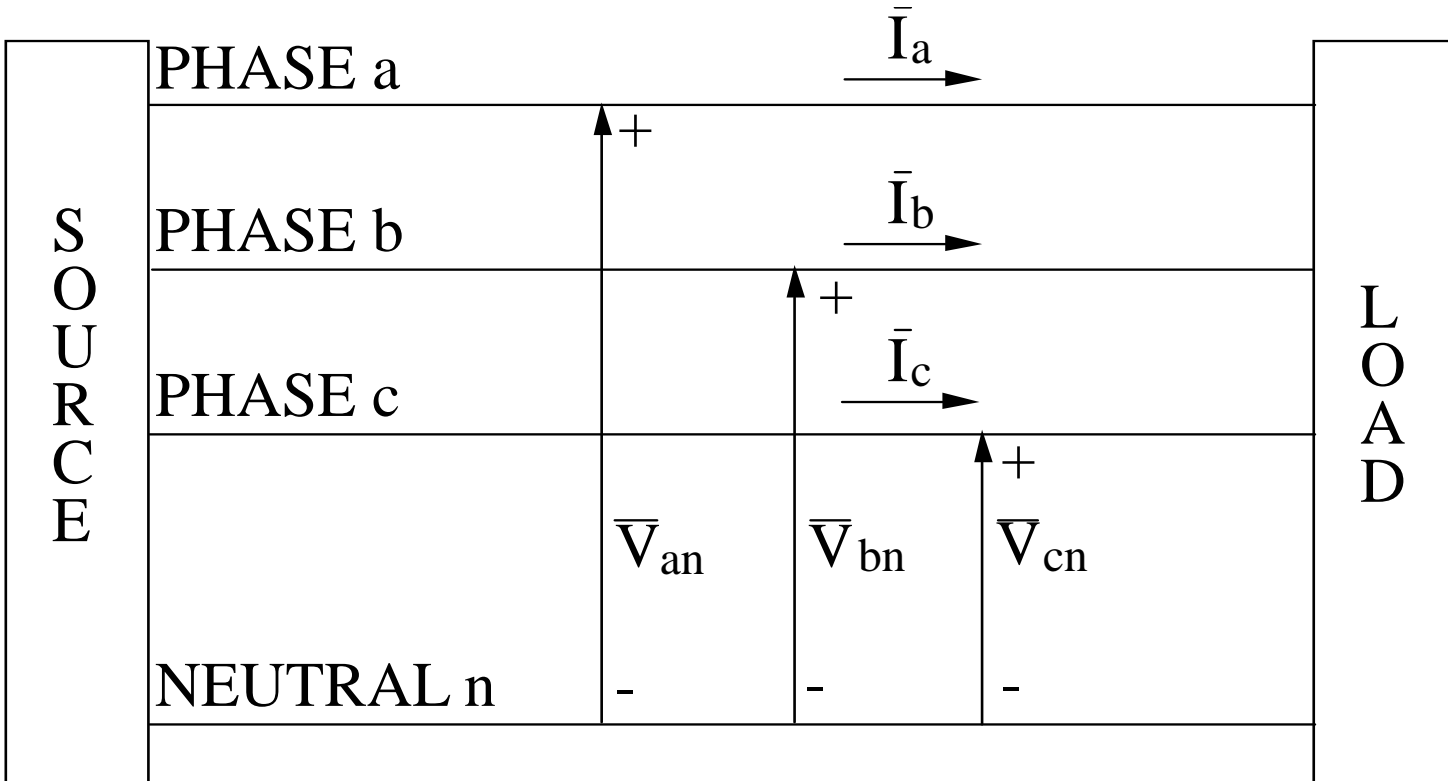

"PHASE" CONDUCTORS ARE ALSO CALLED "LINES"

"Balanced" voltage means equal in magnitude, 120° separated in phase

$$v_{an}(t) = V_{\max} \cos(\omega t) = \sqrt{2} \cdot V \cdot \cos(\omega t)$$


$$v_{bn}(t) = V_{\max} \cos(\omega t - 120^\circ) = \sqrt{2} \cdot V \cdot \cos(\omega t - 120^\circ)$$

$$v_{cn}(t) = V_{\max} \cos(\omega t + 120^\circ) = \sqrt{2} \cdot V \cdot \cos(\omega t + 120^\circ)$$


e.g.

$$V = 1000 \text{ V};$$

$$V_{\max} = 1414 \text{ V}$$

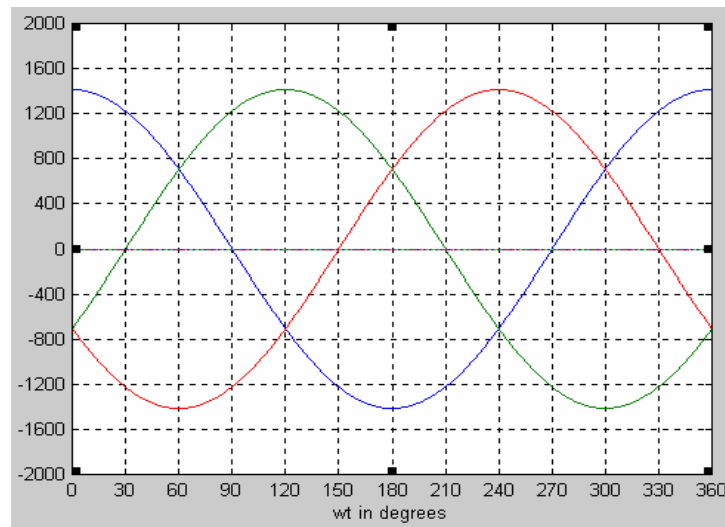

Phasor Diagram

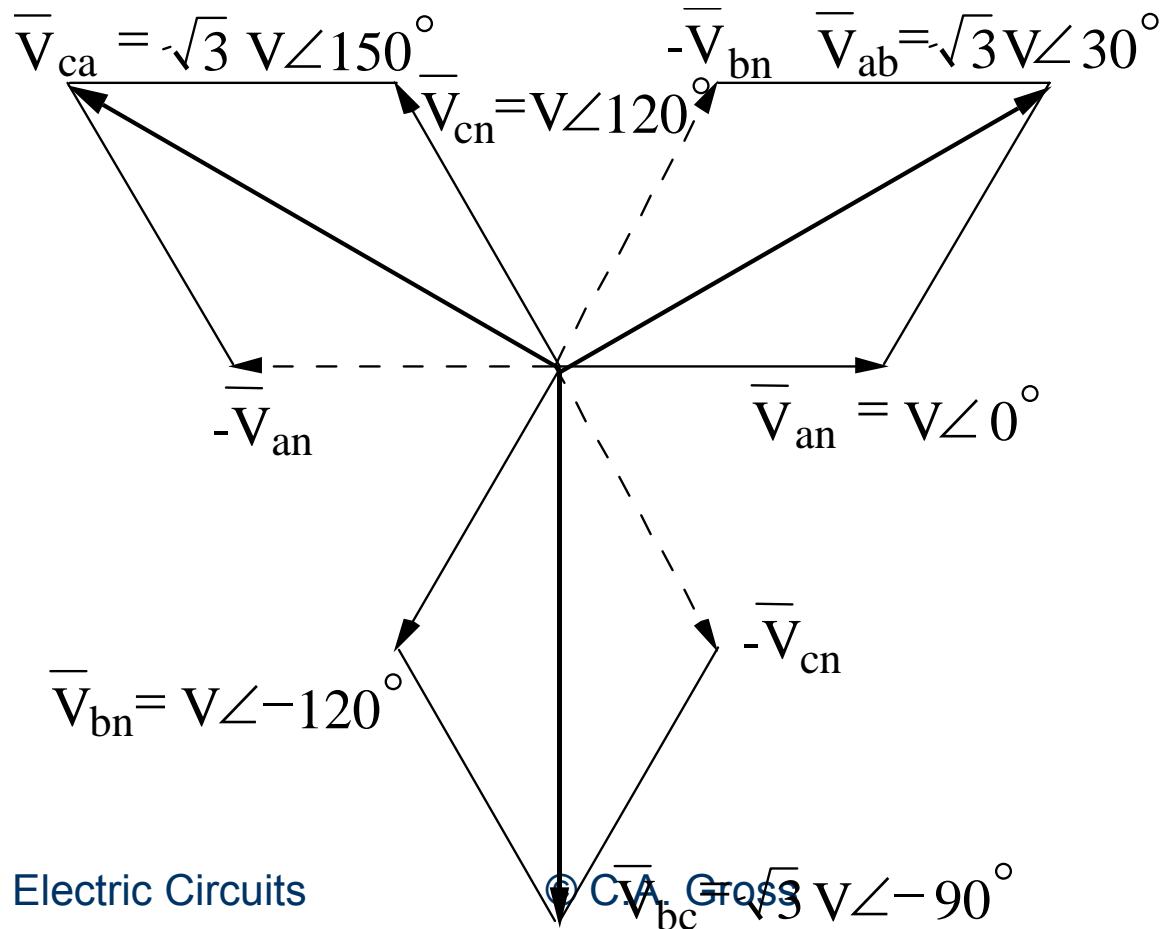

For our problem: $V_L = V_{ab} = 12.47 \text{ kV}$

$$V = \frac{V_L}{\sqrt{3}} = 7.2 \text{ kV}$$

$$\begin{aligned} \bar{V}_{an} &= 7.2 \angle 0^\circ \text{ kV} & \bar{V}_{ab} &= 12.47 \angle 30^\circ \text{ kV} \\ \bar{V}_{bn} &= 7.2 \angle -120^\circ \text{ kV} & \bar{V}_{bc} &= 12.47 \angle -90^\circ \text{ kV} \\ \bar{V}_{cn} &= 7.2 \angle +120^\circ \text{ kV} & \bar{V}_{ca} &= 12.47 \angle +150^\circ \text{ kV} \end{aligned}$$

assumes phase sequence abc and V_{an} as reference

b. Draw the Load power triangle


Consider the given load....

3ph-load of 3500 kVA @ pf = 0.7754 lag

$$\theta = \cos^{-1}(0.7754) = 39.2^\circ$$

$$P = S \cdot \cos(\theta) = 3500(0.7754) = 2714 \text{ kW}$$
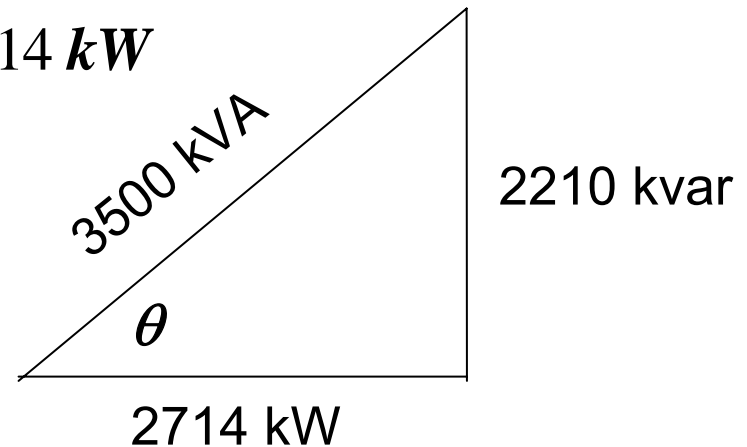
$$Q = S \cdot \sin(\theta) = 2210 \text{ k var}$$



c. Compute the load currents

$$I_a = \frac{S_a}{V_{an}} = \frac{S_a/3}{V_{an}} = \frac{3500/3}{7.2} = 162 \text{ A}$$


$$\bar{I}_a = 162 \angle -39.2^\circ \text{ A}$$

$$\bar{I}_b = 162 \angle (-39.2 - 120) = 162 \angle -159.2^\circ \text{ A}$$

$$\bar{I}_c = 162 \angle (-39.2 + 120) = 162 \angle 80.2^\circ \text{ A}$$

assumes phase sequence abc and V_{an} as reference

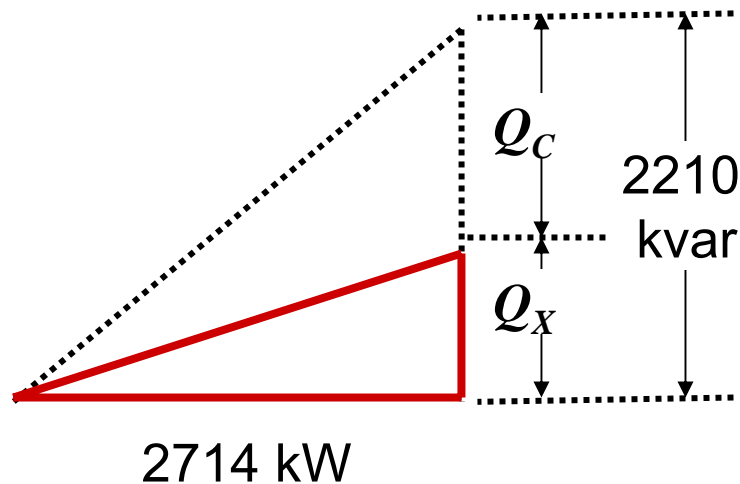d. Draw the corrected power triangle and determine the requisite Q_C



Load power triangle

The desired pf:


$$\theta = \cos^{-1}(0.93) = 21.6^\circ$$

$$\tan(21.6^\circ) = \frac{Q_X}{2714}$$

$$Q_X = 1073 \text{ kvar}$$

$$\begin{aligned} Q_C &= 2110 - Q_X \\ &= 1137 \text{ k var} \end{aligned}$$

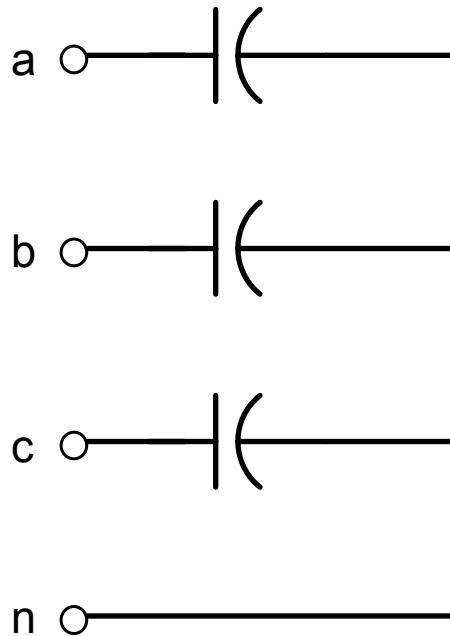e. If the capacitors are connected in wye, find each capacitance and draw the circuit.



$$Q_{an} = \frac{Q_C}{3} = \frac{1137}{3} = 379 \text{ kvar}$$


$$I_{an} = \frac{Q_{an}}{V_{an}} = \frac{379}{7.2} = 52.64 \text{ A}$$

$$Z_{an} = Z_Y = \frac{V_{an}}{I_{an}} = 136.8 \Omega$$

$$\bar{Z}_Y = -j136.8 \Omega$$

$$C_Y = \frac{1}{\omega Z_Y} = \frac{1}{0.377 \cdot 0.1368} = 19.39 \mu F$$

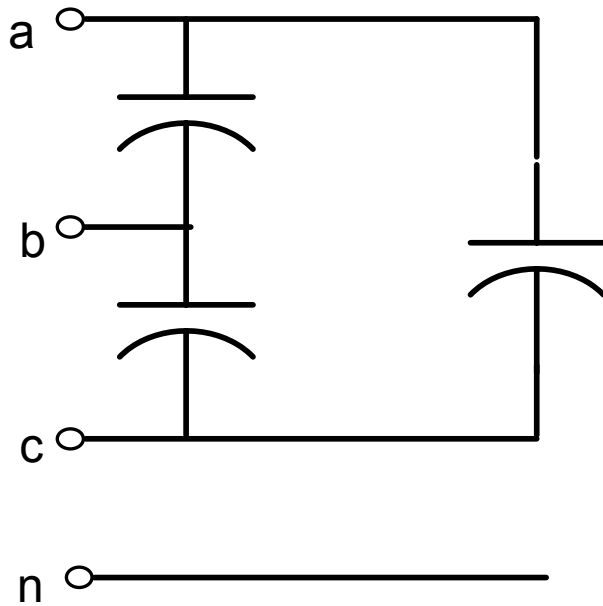f. If the capacitors are connected in delta, find each capacitance and draw the circuit.



$$Q_{ab} = \frac{Q_C}{3} = \frac{1137}{3} = 379 \text{ kvar}$$

$$I_{ab} = \frac{Q_{ab}}{V_{ab}} = \frac{379}{12.47} = 30.39 \text{ A}$$


$$Z_{ab} = Z_{\Delta} = \frac{V_{ab}}{I_{ab}} = 410.3 \Omega$$

$$\bar{Z}_{\Delta} = -j410.3 \Omega$$

$$C_{\Delta} = \frac{1}{\omega Z_{\Delta}} = \frac{1}{0.377 \cdot 0.4103} = 6.465 \mu F$$

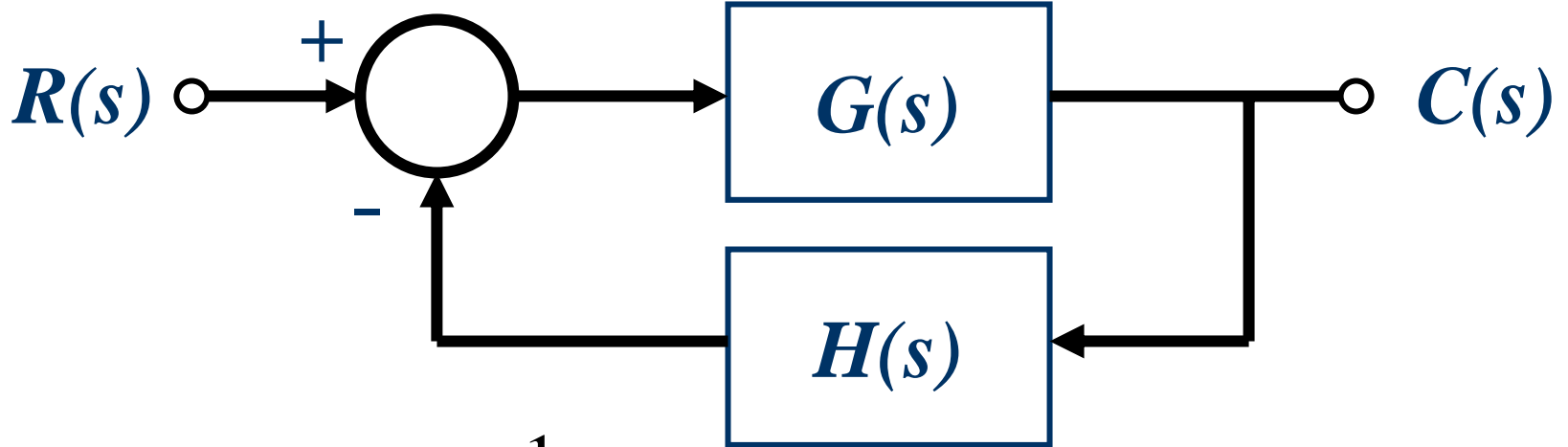5. Control

Given the following feedback control system:



$$G(s) = \frac{1}{(s - 1)(s + 4)}$$

$$H(s) = K$$

a. Write the closed loop transfer function in rational form

$$\frac{C}{R} = \frac{G}{1+GH} = \frac{\frac{1}{(s-1)(s+4)}}{1 + \frac{K}{(s-1)(s+4)}}$$

$$\frac{C}{R} = \frac{1}{(s-1)(s+4) + K} = \frac{1}{s^2 + 3s + (K-4)}$$

b. Write the characteristic equation

$$s^2 + 3s + (K - 4) = 0$$

c. What is the system order? 2


d. For $K = 0$, where are the poles located?

$$s^2 + 3s - 4 = (s - 1) \cdot (s + 4) = 0$$

$$s = +1; s = -4$$

e. For $K = 0$, is the system stable? NO

f. Sketch the root locus

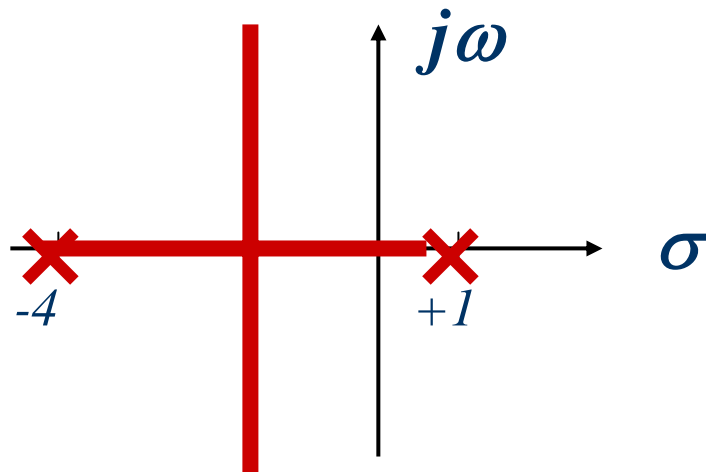

g. Find the range on K for system stability.

If $K = 4$:

$$s^2 + 3s + 0 = (s) \cdot (s + 3) = 0$$

Poles at $s = 0$; $s = -3$

Therefore for $K > 4$, poles are in LH s-plane and system is stable.

$$**$K \geq 4$**$$

h. Find K for critical damping

$$**CE** : \quad s^2 + 3s + (K - 4) = 0$$

$$\text{Solving the CE: } s = \frac{-3 \pm \sqrt{9 - 4(K - 4)}}{2}$$

Critical damping occurs when the poles are real and equal

$$\sqrt{9 - 4(K - 4)} = 0$$

$$K - 4 = 9/4;$$

$$K = 4 + 2.25 = 6.25$$

6. Signal Processing

*a. periodic time-domain functions have
continuous **discrete** frequency spectra.
(circle the correct adjective)*

*b. aperiodic time-domain functions have
continuous discrete frequency spectra.
(circle the correct adjective)*

c. Matching

Laplace Transform

d

Fourier Series

a

Inverse FT

e

Fourier Transform

c

Convolution integral

b

b.
$$y(t) = \int_{-\infty}^t x(\tau) \cdot h(t - \tau) \cdot d\tau$$

d.
$$X(s) = \int_0^{\infty} x(t) \cdot e^{-st} \cdot dt$$

a.
$$x(t) = \sum_{n=-N}^N \bar{D}_n \exp(jn\omega_0 t)$$

c.
$$\bar{X}(j\omega) = \int_{-\infty}^{\infty} x(t) \cdot e^{-j\omega t} \cdot dt$$

e.
$$x(t) = \frac{1}{2\pi} \int_{-\infty}^{\infty} \bar{X}(j\omega) \cdot e^{+j\omega t} \cdot d\omega$$

c. Matching

Z-Transform

d

Inverse ZT

a

Inverse DFT

e

DFT

c

Discrete Convolution

b

$$b. \quad y[k] = \sum_{n=-\infty}^k x[n] \cdot h[n - k]$$


$$d. \quad X(z) = \sum_{n=0}^{\infty} x[n] \cdot z^{-n}$$

$$a. \quad \bar{X}(j\Omega) = \sum_{n=-\infty}^{\infty} x[n] \cdot e^{-jn\Omega}$$


$$c. \quad \bar{X}_k = \sum_{n=0}^{N-1} x[n] \cdot e^{-j2\pi kn/N}$$

$$e. \quad x[n] = \frac{1}{N} \sum_{k=0}^{N-1} \bar{X}_k \cdot e^{+j2\pi kn/N}$$

7. Electronics

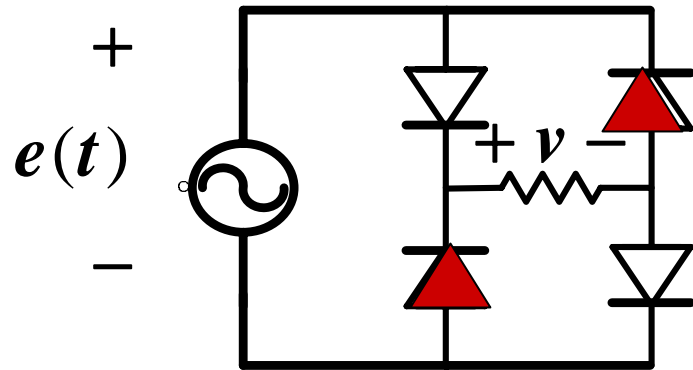



$$e(t) = 169.7 \cdot \sin(\omega t)$$

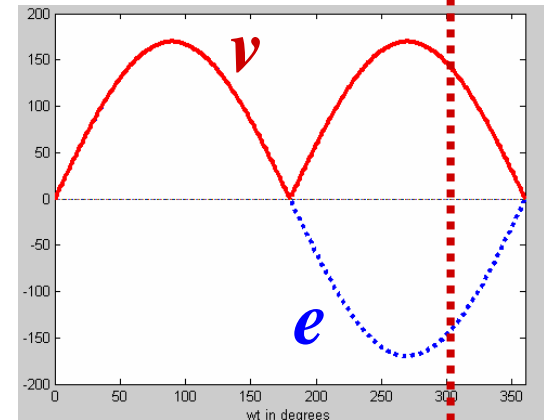

T


a. Darken the conducting diodes at time T

b. Given the "OP Amp" circuit

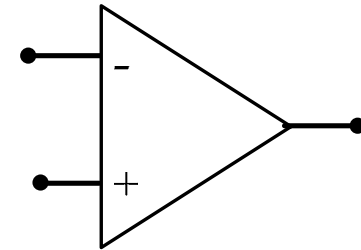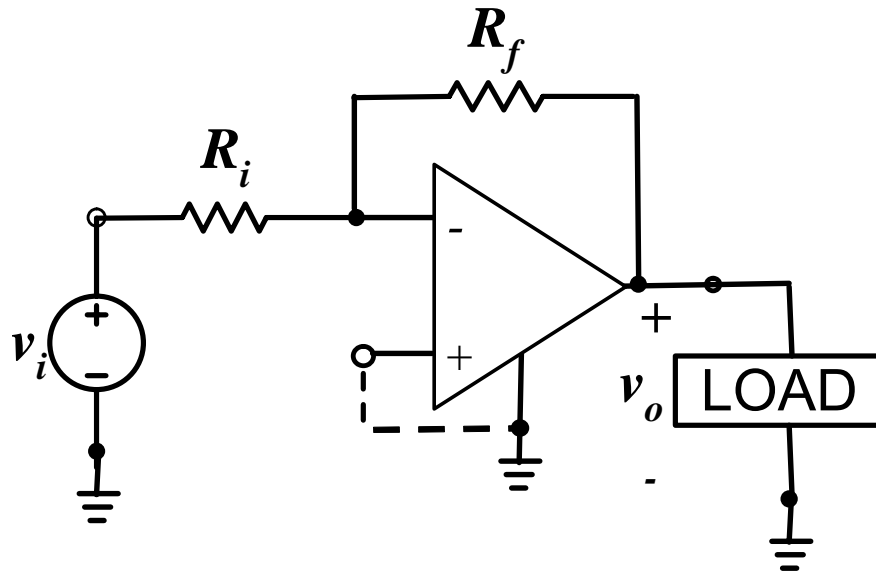

- Ideal OpAmp....***
- ***infinite input resistance***
 - ***zero input voltage***
 - ***infinite gain***
 - ***zero output resistance***

Find the output voltage.

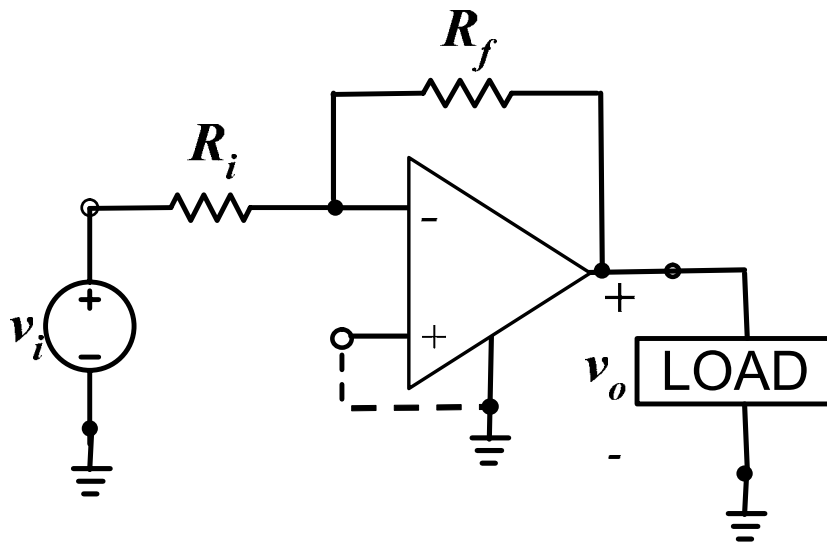

$$v_i = 5 \text{ V}$$

$$R_i = 10 \text{ k}\Omega$$


$$R_f = 50 \text{ k}\Omega$$

$$\text{KCL: } \frac{v_i}{R_i} + \frac{v_o}{R_f} = 0$$

$$v_o = -\left(\frac{R_f}{R_i}\right) \cdot v_i$$

$$v_o = -\left(\frac{50}{10}\right) \cdot 5 = -25 \text{ V}$$

c. Find the output voltage.

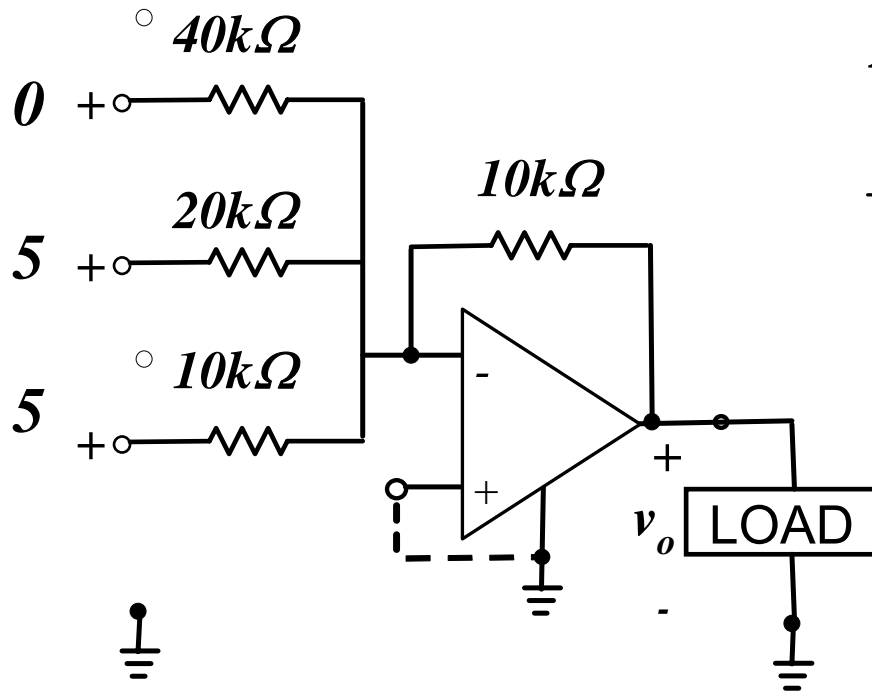


KCL:

$$\frac{v_1}{R_1} + \frac{v_2}{R_2} + \frac{v_3}{R_3} + \frac{v_0}{R_f} = 0$$

Solution:

"SUMMER"

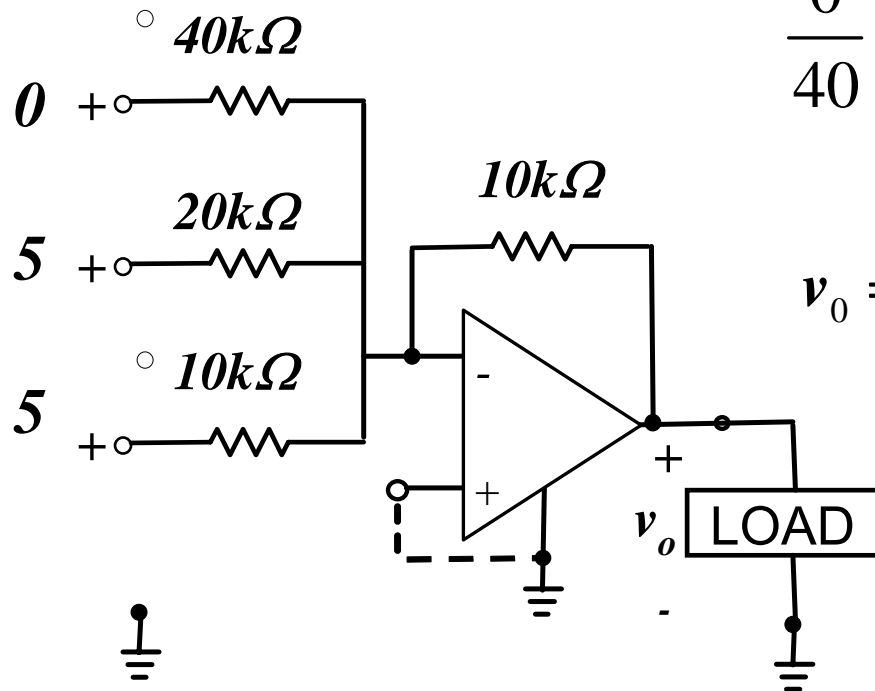

$$\frac{0}{40} + \frac{5}{20} + \frac{5}{10} + \frac{v_o}{10} = 0$$

$$v_o = -\left(\frac{10}{10}\right) \cdot 5 - \left(\frac{10}{20}\right) \cdot 5 - \left(\frac{10}{40}\right) \cdot 0$$

$$v_o = -7.5 \text{ V}$$

8. Digital Systems Logic Gates


AB	AND ($A \cdot B$)	NAND	OR	XOR	NOR	NOR
00	0					
01	0					
10	0					
11	1					

NO

FE: Electri

A	INV
0	1
1	0

INV





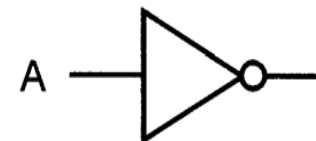


EE1- 54


8. Digital Systems

Logic Gates


A	B	AND	NAND	OR	NOR	XOR	XNOR
0	0	0	1	0	1	0	1
0	1	0	1	1	0	1	0
1	0	0	1	1	0	1	0
1	1	1	0	1	0	0	1

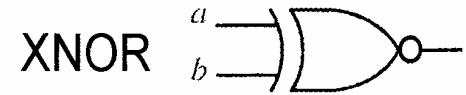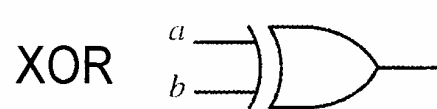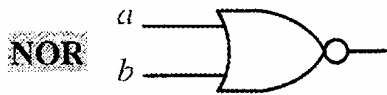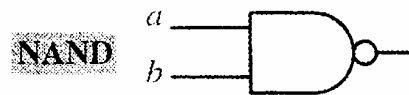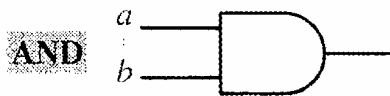

A	INV
0	1
1	0

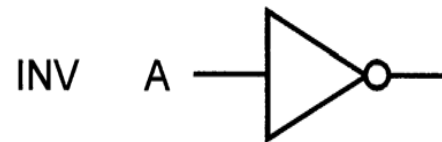

a. Complete the Truth Table

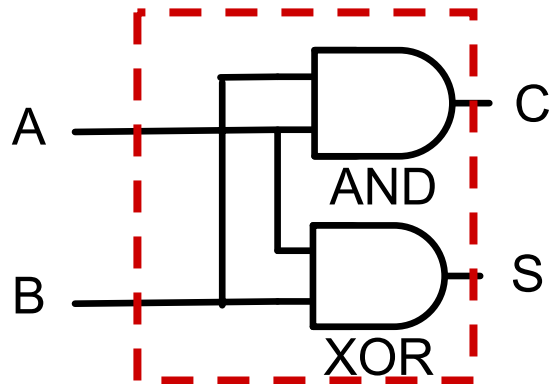

Half Adder (HA)

A	B	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

$$A + B = CS$$

$$0 + 0 = 00$$


$$0 + 1 = 01$$

$$1 + 0 = 01$$

$$1 + 1 = 10$$


b. Complete the indicated row in the TT

C_1	A_1	B_1	C_2	S_1
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

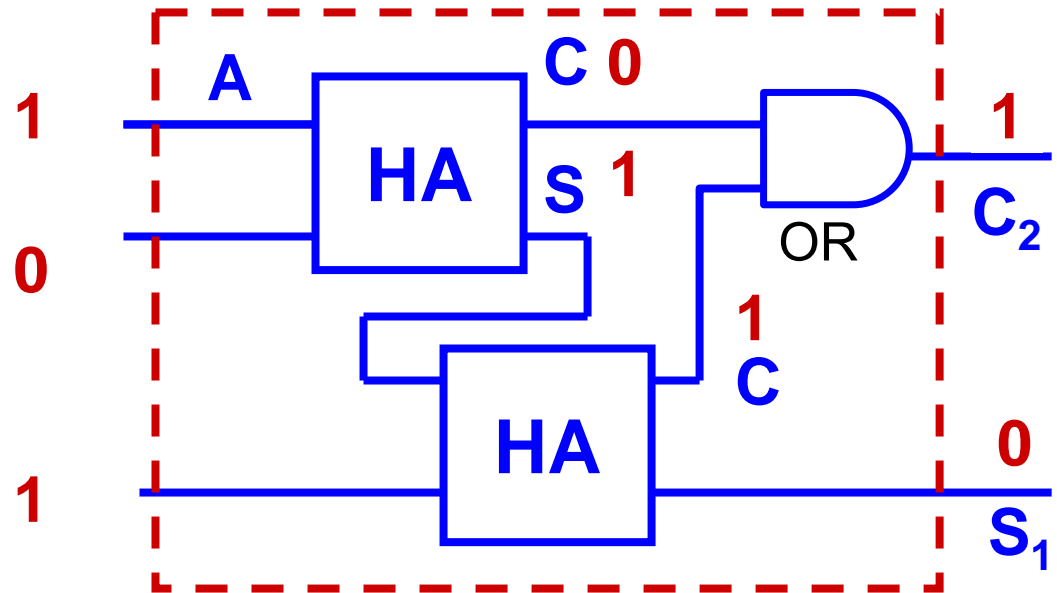

Full Adder (FA)

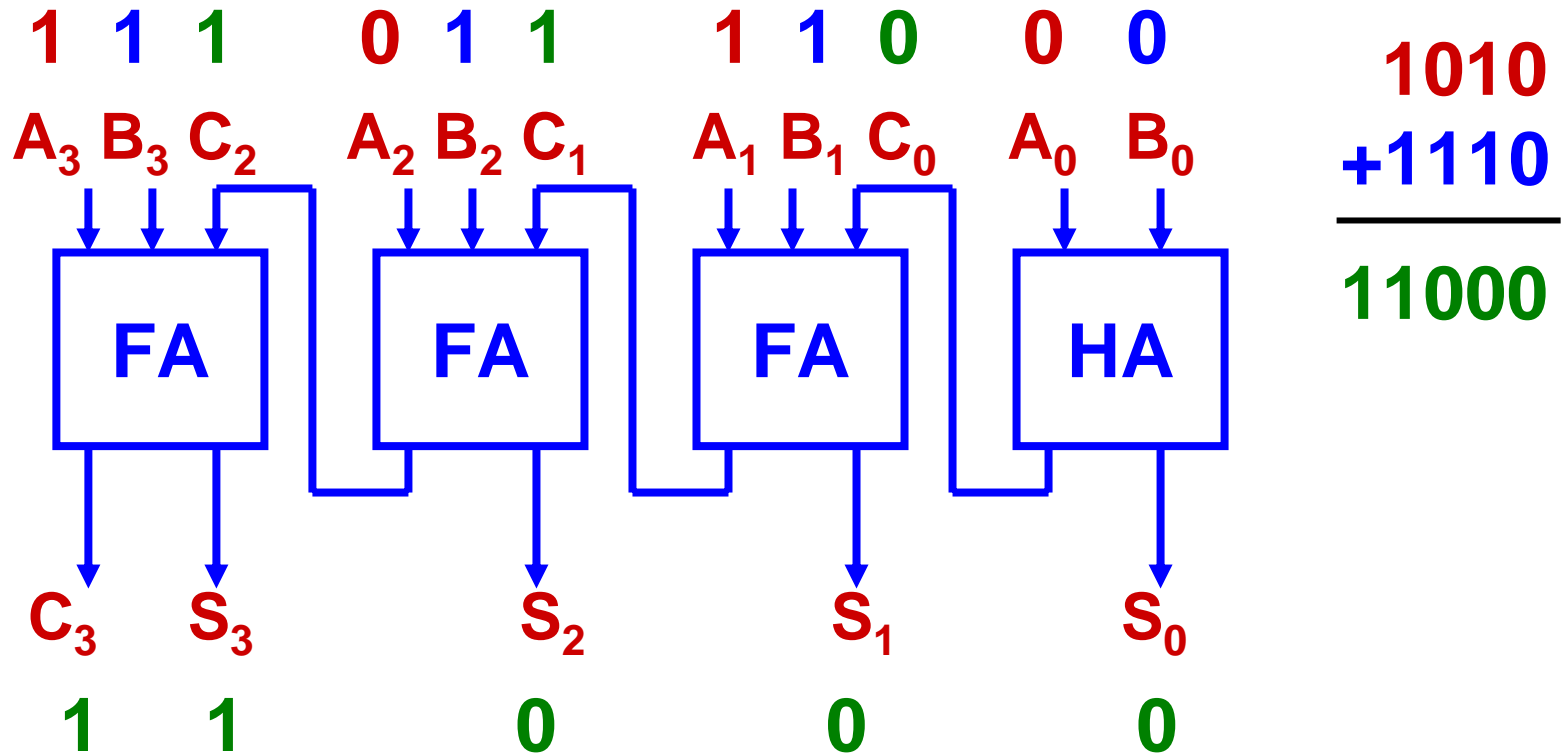c. Indicate the inputs and outputs to perform the given sum in a 4-bit adder



d. Design a D/A Converter to accommodate 3-bit digital inputs (5 volt logic)


Resolution: 3-bits
($2^3 = 8$ levels;
10 V scale)

Example...
Convert "110"
to analog

<i>Digital</i>	<i>Analog (V)</i>
000	0.00
001	1.25
010	2.50
011	3.75
100	5.00
101	6.25
110	7.50
111	8.75

Binary Word: ABC
(A msb; C lsb)

d. Finished Design

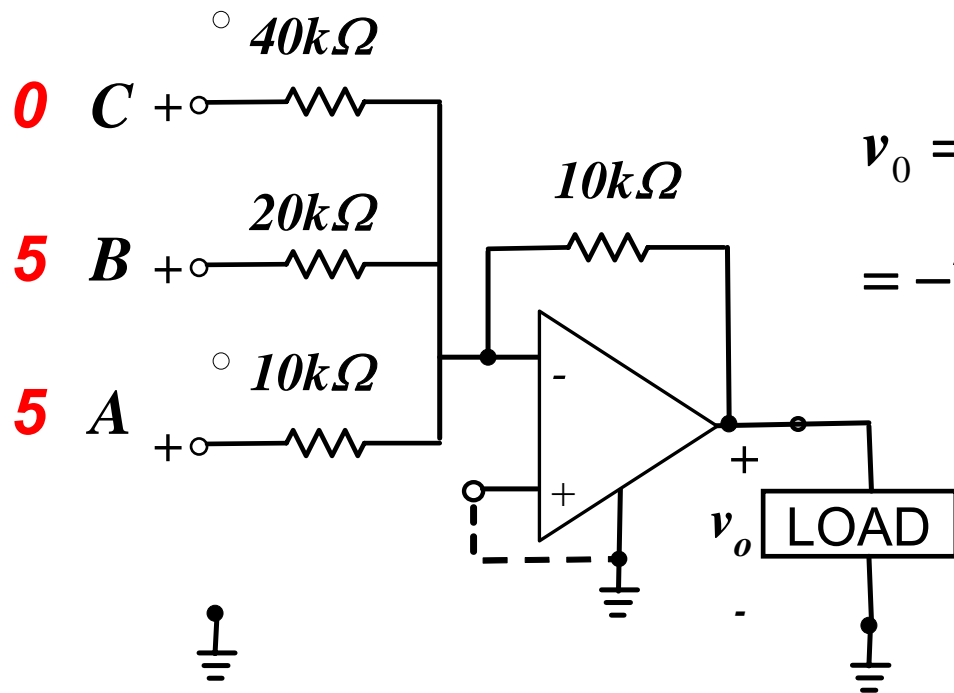

$$\begin{aligned} v_o &= -\frac{10}{10} \cdot 5 - \frac{10}{20} \cdot 5 - \frac{10}{40} \cdot 0 \\ &= -7.50 \end{aligned}$$

Good Luck on the Exam!

If I can help with any ECE material, come see me (7:30 - 11:00; 1:15 - 2:30)

*Charles A. Gross, Professor Emeritus
Electrical and Comp Engineering
Auburn University Broun 212
334.844.1812
gross@eng.auburn.edu*

Good Evening...