
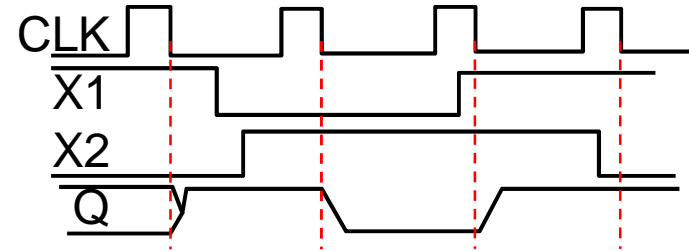


# Assignment #7 Solutions

**P6.9:**

J	K	Q <sup>+</sup>
0	0	Q
0	1	0
1	0	1
1	1	$\bar{Q}$

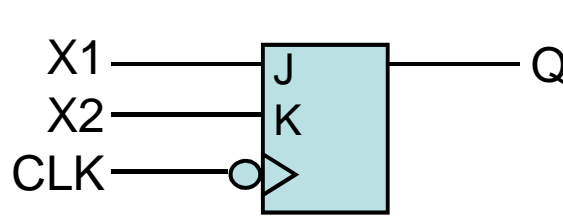

**P6.12:**

