

ELEC 2200 Digital Logic Circuits

Charles E. Stroud, Professor

Dept. of Electrical & Computer Engineering

Office: 325 Broun Hall

Email: cestroud@eng.auburn.edu

Text: Digital Logic Circuit Analysis & Design

Nelson, Nagle, Irwin & Carroll, Prentice Hall, '95


Class web page: www.eng.auburn.edu/~strouce

Some Basic Digital System Concepts

- Levels of design abstraction & hierarchy
 - System (behavioral) level – highest level
 - Register level – widely used for design in industry today
 - Gate level – level we will deal with most in this class
 - Transistor level – lowest level
- Top-down design
 - Begins at system level & moves toward transistor level
 - Typical way complex digital systems are designed in industry
 - CAD tools can synthesize lower levels of design abstraction from higher level descriptions
 - So what is the point of logic design?
 - CAD tools are not a magic wand, they don't design the circuit for you!

Example of Digital System Design



- The integrated circuit design process

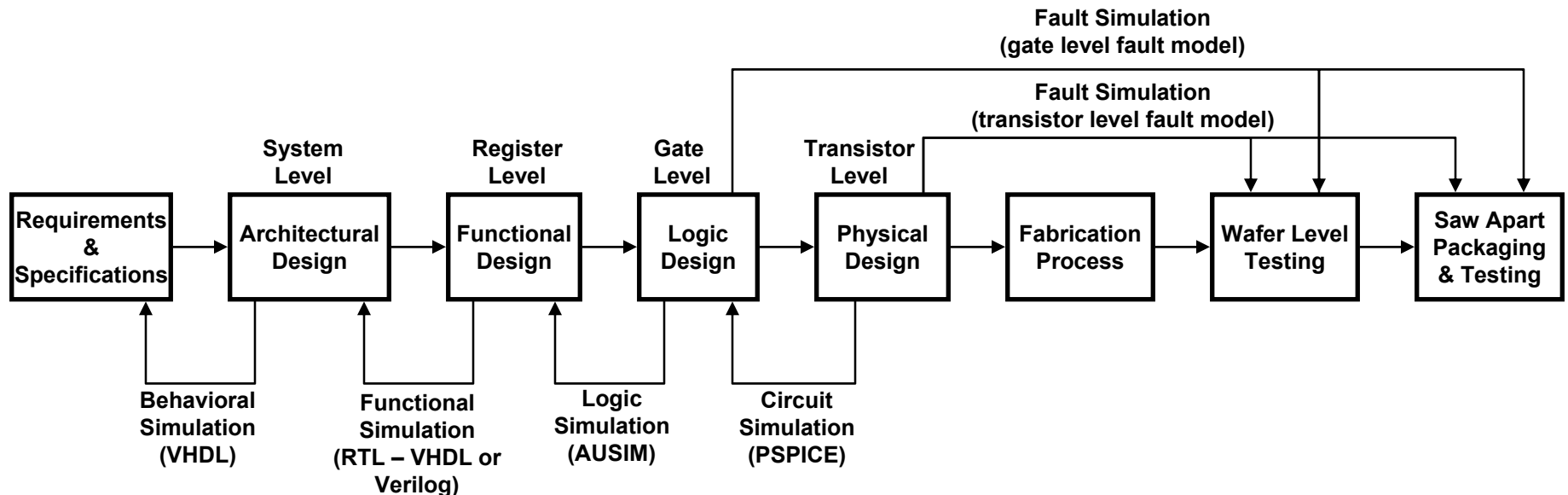

Hierarchical System Design

- Hierarchy is everywhere
 - Systems consist of units
 - Units consist of printed circuit boards (PCBs)
 - PCBs consist of integrated circuits (ICs)
 - ICs consist of logic gates
 - Logic gates consist of transistors
- Allows us to partition big designs into manageable components
- Once the circuit design works, why redesign it?
 - Instead, reuse it through hierarchical design
 - Reduces design time and design errors

Analog vs. Digital Systems

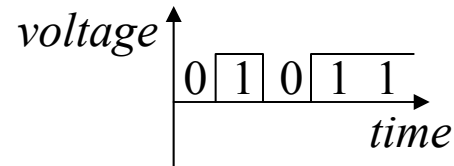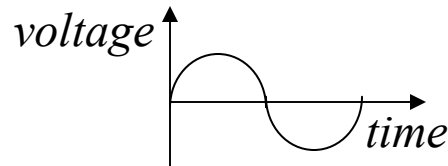

- Analog

- Continuous time-varying voltages and/or currents
- Basic elements of analog circuits:
 - Resistors
 - Capacitors
 - Inductors
 - Transistors

- Digital

- Discrete signals sampled in time
- Two possible values
 - 0V, low, false (logic 0)
 - 5V, high, true (logic 1)
- Basic elements of digital circuits:
 - Logic gates: AND, OR, NOT

Elementary Logic Gates




Name

Inverter
(NOT Gate)

AND Gate

OR Gate

Symbol

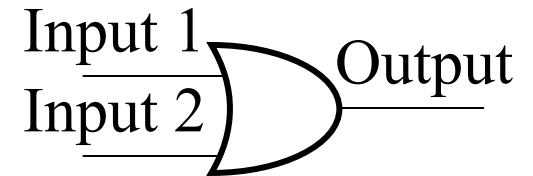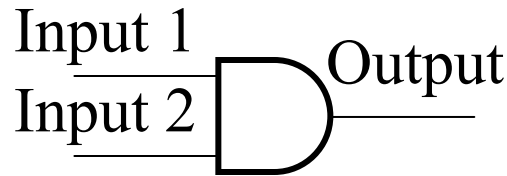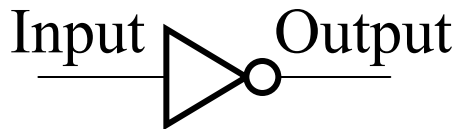

Truth Table

In	Out
0	1
1	0

In 1	In 2	Out
0	0	0
0	1	0
1	0	0
1	1	1

In 1	In 2	Out
0	0	0
0	1	1
1	0	1
1	1	1

Logic Equation

$$\text{Out} = \text{In}'$$

$$\text{Out} = \text{In1} \cdot \text{In2}$$


$$\text{Out} = \text{In1} + \text{In2}$$

Advantages of Digital Systems

- Reproducible results
- Relative ease of design
- Flexibility and functionality
- High speed
- Small size
- Low cost
- Low power
- Steadily advancing technology
- Programmable logic devices


Digital Systems

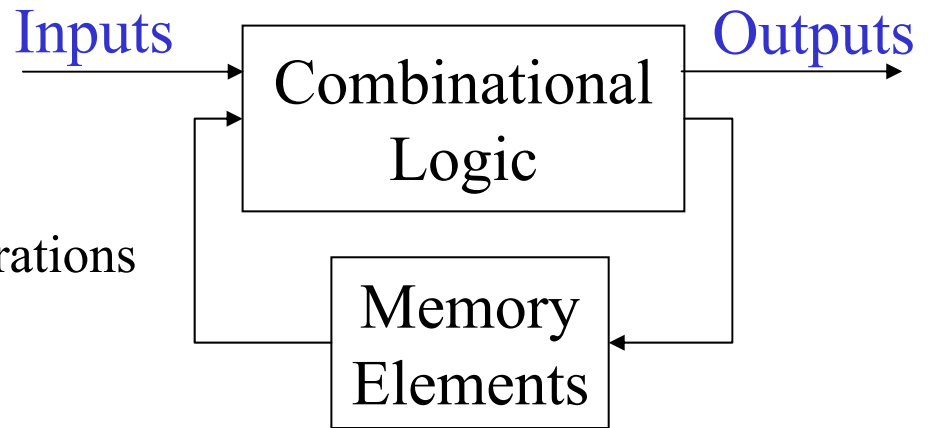- Most general model of a digital system
 - Often referred to as *General Sequential Logic*
 - aka *Huffman model*
 - Consists of:
 - Combinational logic
 - Performs logical operations
 - Memory elements
 - Stores data
 - These two items will be the focus of this course
 - Beginning with combinational logic




Stored Program Digital Computer

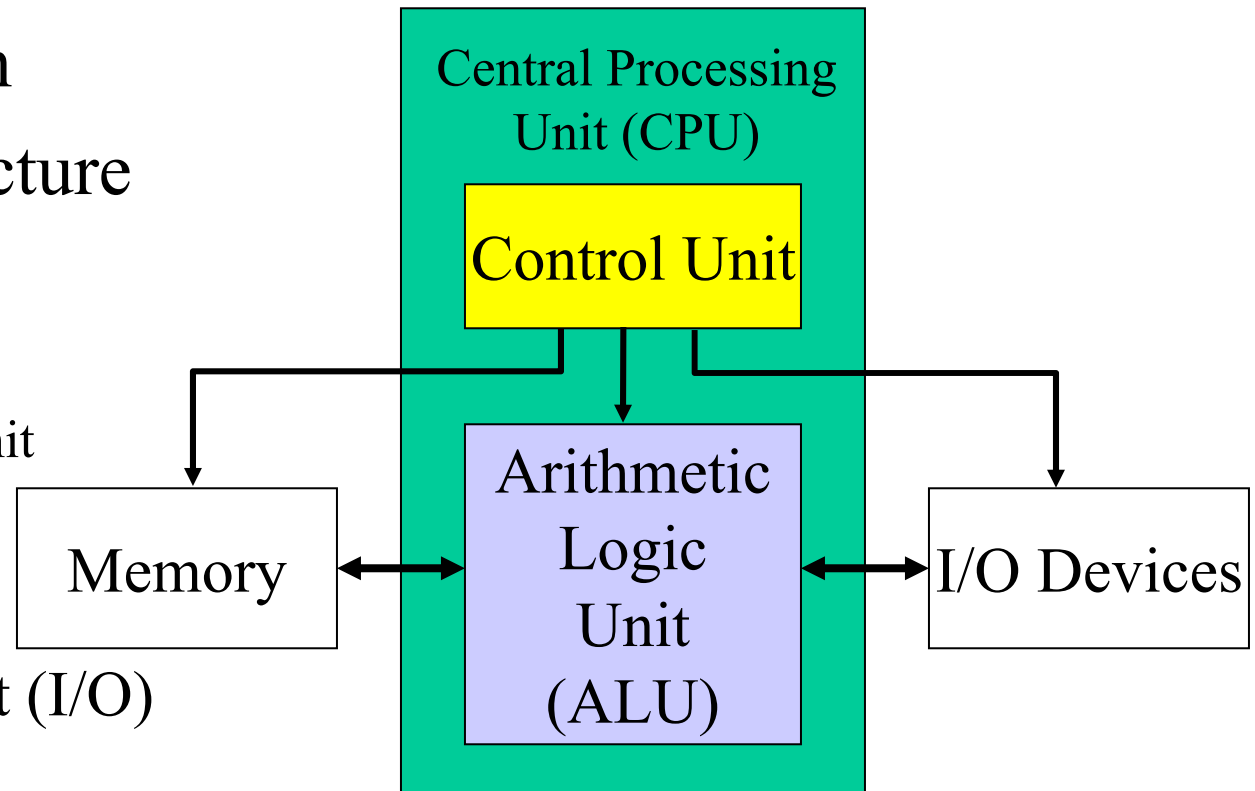- Good example of a digital system
- Basic architecture consists of:
 - CPU
 - Control Unit
 - ALU
 - Memory
 - Input/Output (I/O) Devices



Stored Program Digital Computer

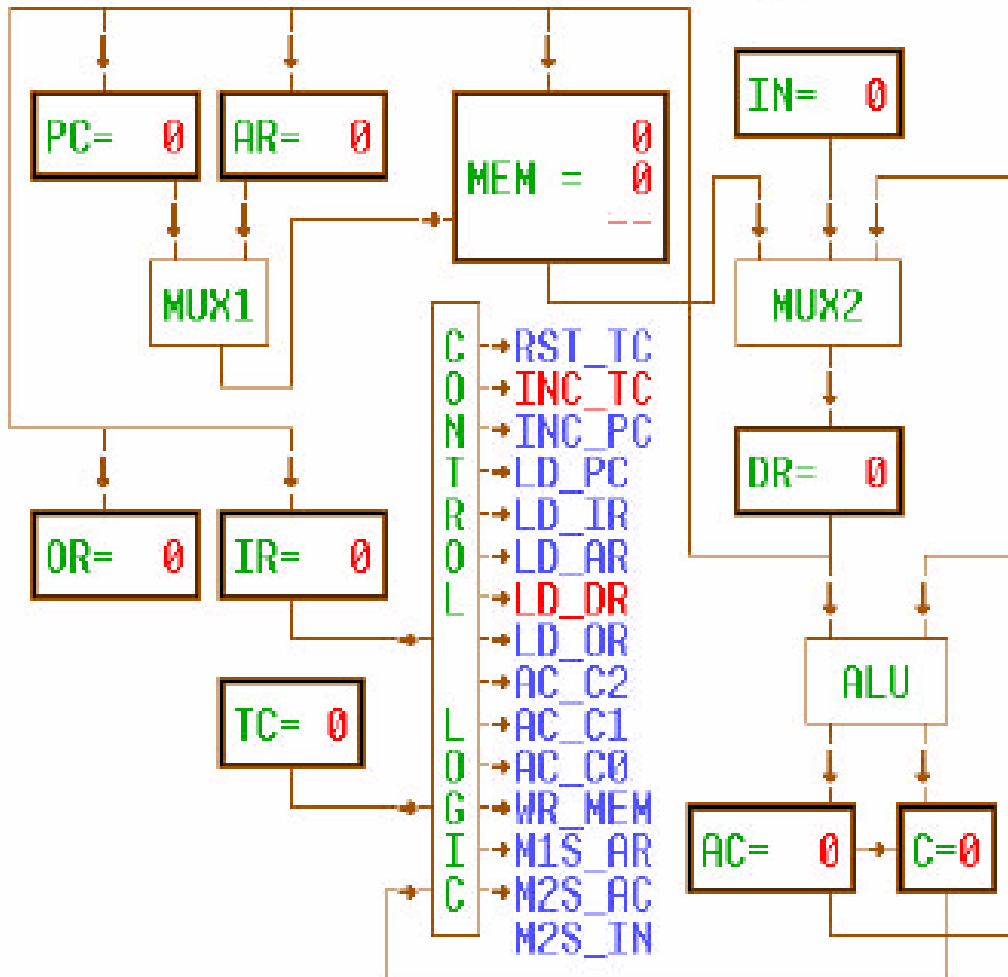

Memory:

Program Memory (MEM)

Data Register (DR)

I/O Devices:

Input Register (IN)

Output Register (OR)

Arithmetic-Logic Unit:

Arithmetic/Logic Unit (ALU)

Accumulator (AC)

ALU Carry Register (C)

Control Unit:

Program Counter (PC)


Address Register (AR)

Instruction Register (IR)

Timing Counter (TC)

Control Logic

Stored Program Digital Computer

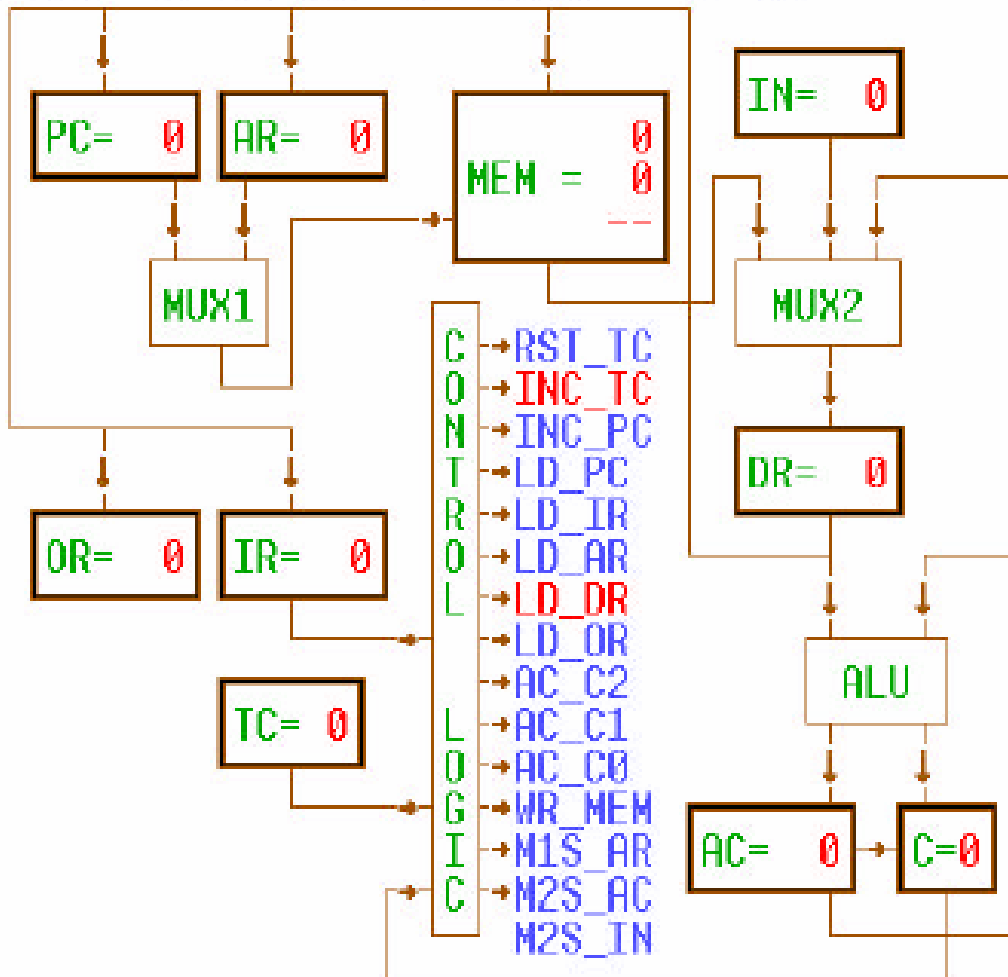

Sequential Logic:

- Program Memory (MEM)
- Program Counter (PC)
- Address Register (AR)
- Data Register (DR)
- Input Register (IN)
- Output Register (OR)
- Accumulator (AC)
- ALU Carry Register (C)
- Instruction Register (IR)
- Timing Counter (TC)

Combinational Logic:

- Control Logic
- Arithmetic/Logic Unit (ALU)
- Multiplexers 1&2 (MUX)

Digital Computer Basic Operation

- Consists of a series of instructions cycles, each consisting of:
 - Fetch
 - Fetch instruction from Program Memory (MEM) to Data Register (DR)
 - Decode
 - Pass instruction from DR to Instruction Register (IR) and decode using Control Logic
 - Execute
 - Perform operations decoded by Control Logic such as:
 - Get operands from MEM or Input Register (IN)
 - Arithmetic/logic operations
 - Store results in MEM or Output Register (OR)

