

## Introduction to Programmable Logic

Any combinational logic function can be expressed as:

1) Boolean Equations

$$X=A \oplus B$$

$$Y=A \bullet \overline{(B \bullet C)}$$

2) Truth Tables/Kmaps

<u>ABC</u>	<u>XY</u>	<u>ABC</u>	<u>XY</u>
0 0 0	00	0 0 x	00
0 0 1	00	0 1 x	10
0 1 0	10	1 0 x	11
0 1 1	10	1 1 0	01
1 0 0	11	1 1 1	00
1 0 1	11		
1 1 0	01		
1 1 1	00		

3) Sum-of-Products/Product-of-Sums

$$X=AB' + A'B$$

$$Y=AB' + AC'$$

4) Other representations as well

The first three representations above are important for implementing programmable logic which use:

1) ROMs – Read Only Memories

We can program a ROM (8 words by 2 bit/word), then use the address lines as the 3 input signals (A,B,C) and the ROM outputs as the output signals (X,Y)

2) RAMs – Random Access Memories

We can write the truth table into a RAM (8 words by 2 bit/word), then disable the WE and use the address lines as the 3 input signals (A,B,C) and the RAM outputs as the output signals (X,Y) – this is the now the same thing as the ROM except we can re-program the logic function by re-writing the RAM

3) PLAs – Programmable Logic Arrays

In the minimized truth table, there are only 3 words producing logic 1 for the output signals and the PLA allows implementing only those 3 words (and not the other 5)  $\Rightarrow$  smaller than ROM


## Introduction to Programmable Logic

Any sum-of-products can be implemented as a 2-level AND-OR or NAND-NAND logic function (assume 2-rail inputs: bit & bit-bar)  
 Any sum-of-products can also be implemented as a 2-level NOR-NOR logic function (assume 2-rail inputs) if we invert the inputs and the output.


$$X = AB' + A'B$$

$$Y = AB' + AC'$$

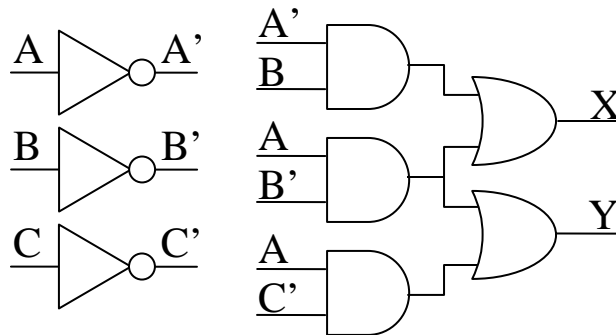
Note:  $AB'$  is a shared product term in all three implementations.



2-level AND-OR logic function

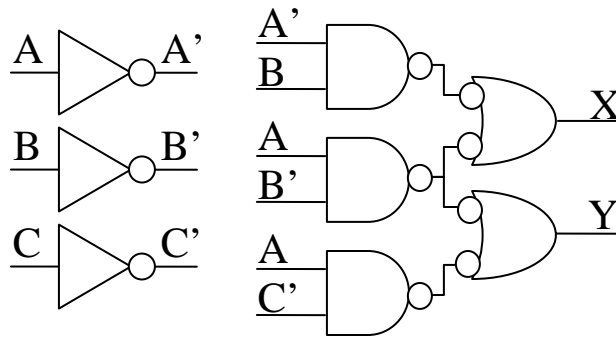


2-level NAND-NAND logic function

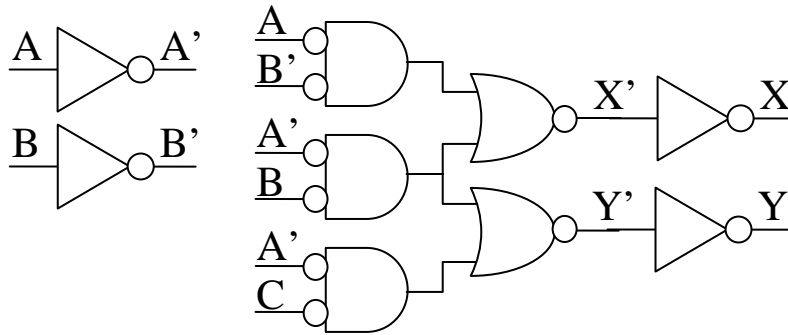


2-level NOR-NOR logic function
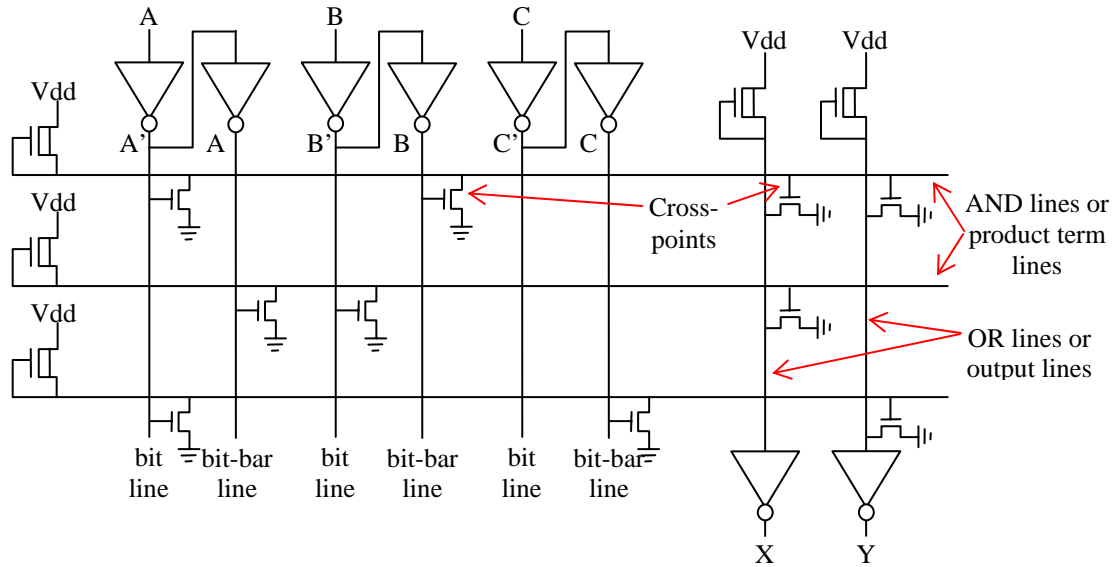
# Introduction to Programmable Logic

Programmable Logic Arrays (PLAs) take advantage of the NOR-NOR implementation of logic functions and the large fan-in limit of NMOS NOR gates.



Programmable Logic Array PLA

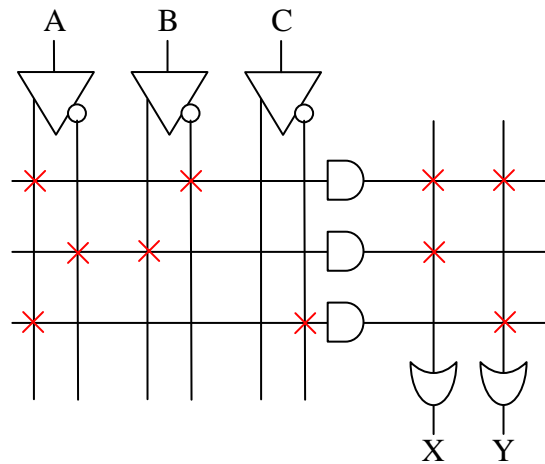


PLA Shorthand Notation

## Introduction to Programmable Logic

Programming technologies for Field Programmable Gate Arrays (FPGAs) and Complex Programmable Logic Devices (CPLDs):

1. Fuse/Anti-fuse
2. Floating Gate Technology
3. RAM

Consider a PLA cross-point

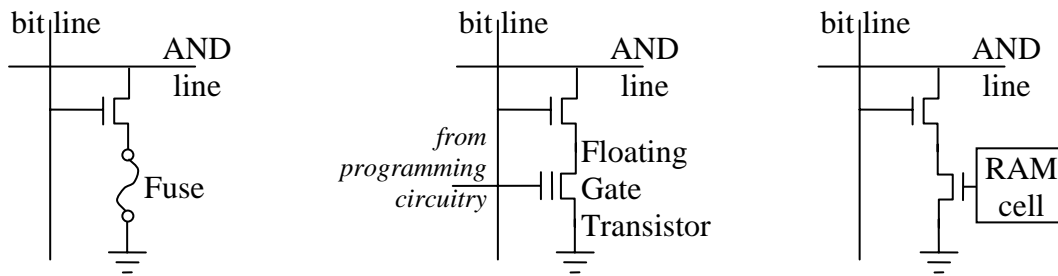

Floating gate technology includes:

1. UVEPROM (UV Erasable Programmable ROM)
2. EEPROM (Electrically Erasable Programmable ROM)
3. Flash Memory (like in memory keys)

Important Programming Technology Terms

OTP (one-time programmable) – characteristic of fuse/anti-fuse

ISP (in-system programmable) – some floating gate technologies are ISP

ISR (in-system re-programmable) – characteristic of RAM

OTP and floating gate technologies are non-volatile and logic will retain its configuration when powered down.

RAM is volatile and must be configured when power is turned on.