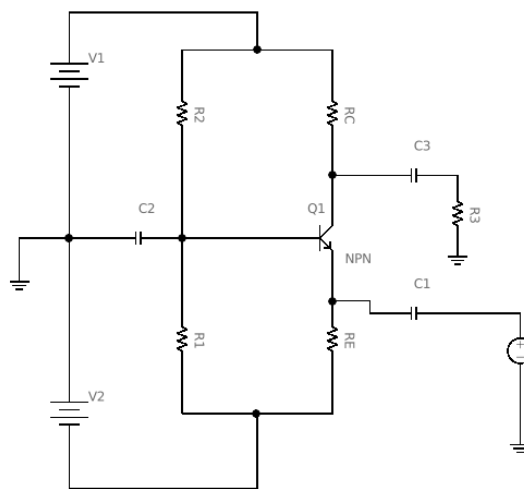


1. What are the definitions and equations of **Voltage Gain, Current Gain, Power Gain**.
2. What are the impedances of a capacitor, inductor, and resistor? What are the DC equivalent? What are the high frequency equivalent?
3. Know CC, CE, CB, CD, CG, CS amplifiers: what they look like, where the input comes in, where the output leaves, R_{in} , R_{out} , f_H , f_L , etc.
4. What is the Q-pt, r_m , r_o , r_π , μ_f , voltage gain, input and output resistance, and short circuit time constant f_L of the amplifier in Figure P13.11 (page 740) with the following parameters: $R_G = 121k\Omega$, $R_4 = 5.23k\Omega$, $R_3 = 20k\Omega$, $R_D = 6.04k\Omega$, $R_S = 4.75k\Omega$, $R_I = 1k\Omega$, $C_1 = 100pF$, $C_2 = 4.7\mu F$, $C_3 = 50pF$, $V_{CC} = 10V$, $V_{EE} = -10V$, $K'_n = 50\mu A/V^2$, $\frac{W}{L} = 10$, $V_{TN} = 1V$, $\lambda = 0$. What type of amplifier is this: common-collector, common-emitter, common-base? Is the amplifier inverting or non-inverting?
5. What is the Q-pt, r_m , r_o , r_π , μ_f , voltage gain, input and output resistance and short circuit time constant f_L , open circuit time constant f_H , and bandwidth of the amplifier below with the following parameters: $R_1 = 20k\Omega$, $R_2 = 6.04k\Omega$, $R_3 = 20k\Omega$, $R_C = 10k\Omega$, $R_E = 33.2k\Omega$, $C_1 = 33pF$, $C_2 = 0.20\mu F$, $C_3 = 820pF$, $C_\mu = 5.6pF$, $C_\pi = 8.2pF$, $V_1 = 9V$, $V_2 = 9V$. What type of amplifier is this: common-collector, common-emitter, common-base? Is the amplifier inverting or non-inverting?



6. What are the Q-pt, r_m , r_o , r_π , voltage gain, input and output resistance, short circuit time constant f_L : Q_1 's $\frac{W}{L} = 10$, $R_1 = R_5 = R_9 = 100k\Omega$, $R_2 = R_6 = R_{10} = 75k\Omega$, $R_3 = R_7 = R_{11} = 22.1k\Omega$, $R_4 = R_8 = R_{12} = 46k\Omega$, $R_{13} = 10k\Omega$, $V_{CC} = V_{EE} = 15V$, $C_1 = C_3 = C_6 = C_7 = 10\mu F$, $C_2 = 28\mu F$, $C_4 = 40\mu F$, $C_5 = 100\mu F$, $K'_n = 50\mu A/V^2$, $V_{TN} = 1V$, $\lambda = 0$. Is the overall amplifier inverting or non-inverting?

