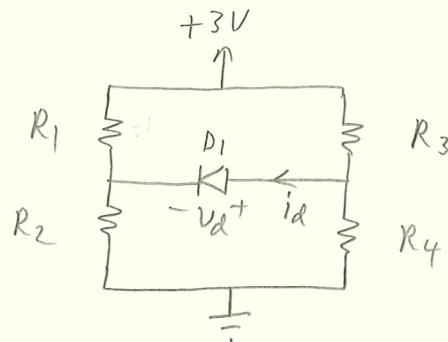


Due Wednesday 9/30/20

Problem 1

Find the Q-point for the diode using (a) the ideal diode model and (b) the CVD diode model with $V_{on} = 0.6V$




$$R_1 = 3\text{ k}\Omega, R_2 = R_3 = R_4 = 2\text{ k}\Omega$$


Problem 2


Find the Q-point for the diode circuits below using the ideal diode model:

(a)

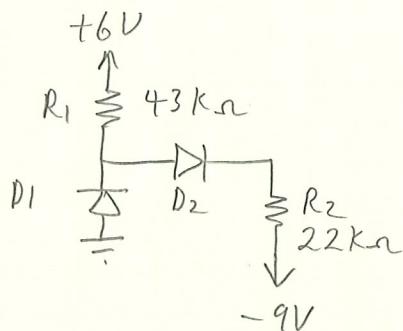

(b)

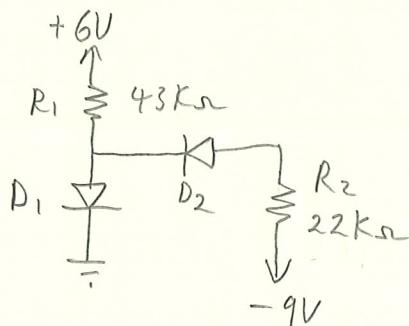

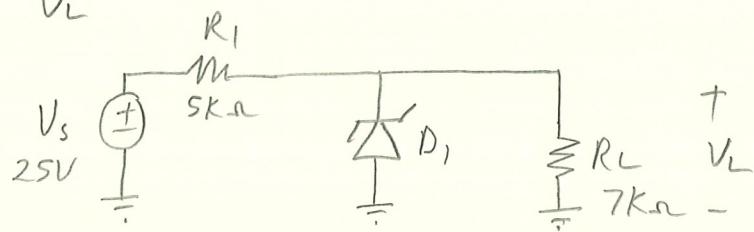Problem 3Find V_L 

- a. For $V_Z = 5V$, $R_Z = 0\Omega$
- b. For $V_Z = 5V$, $R_Z = 100\Omega$
- c. For $V_Z = 5V$, $R_Z = 0\Omega$: what is $R_{L_{min}}$?

Problem 4

What is f_T for an NMOS transistor with $L = 1\mu m$, $\mu_n = 1000 \text{ cm}^2/\text{Vs}$, $V_{DS} = 3.3V$, and $V_{TN} = 1V$?

Problem 5Find the Q-point for M_1 