

a. For each problem below, draw the CMOS circuit and size the transistors based on a CMOS inverter with $(\frac{w}{l})_n = \frac{2}{1}$ and $(\frac{w}{l})_p = \frac{5}{1}$.

$$1. Z = \overline{A + B + C}$$

$$2. Z = ABC$$

$$3. Z = \overline{A(B+C)}$$

$$4. Z = \overline{AB + CD}$$

$$5. Z = \overline{A + \overline{B}C}$$

b. For a 9 inverter ring oscillator, made with symmetrical inverters, what is the output frequency, when $R_{on} = 2500\Omega$ and $C = 1\text{pF}$?