

Key

Name:

Exam #1

ELEC 2210

Fri 10/2/20

I verify below by my signature that I received no assistance on this exam from another person:

Signature:

Problem 1: (15 points)

A pn junction diode is used in a circuit where i_D is 10 mA. If the circuit is operated at room temperature (20°C) and diode parameters are: $I_s = 0.1 \text{ fA}$ and $n = 1$, what is the voltage across the diode, v_D ?

$$i_D = I_s \left(e^{\frac{V_D}{V_T}} - 1 \right)$$




$$\frac{i_D}{I_s} + 1 = e^{\frac{V_D}{V_T}}$$

$$V_D = V_T \ln \left(\frac{i_D}{I_s} + 1 \right) = 0.025 \ln \left[\frac{10 \times 10^{-3}}{0.1 \times 10^{-15}} + 1 \right]$$

$$= 0.806 \text{ V}$$

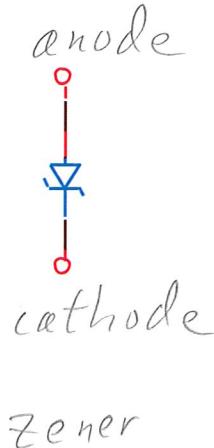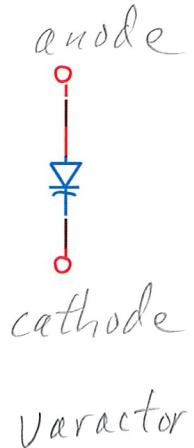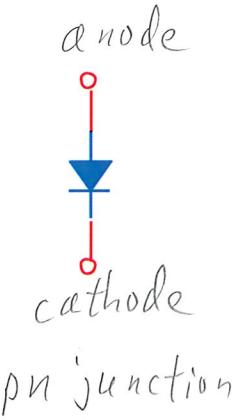Problem 2: (10 points)

Write the diode type below each symbol and label the terminals:



Match the question with an answer by writing the letter of the answer in the blank next to the question. No answer is used more than once. (30 points)

Questions


- 1) This is a common acceptor impurity for Si: I
- 2) What type of chemical bond does Si make with other Si atoms: C
- 3) N_D refers to: L
- 4) This is a reverse breakdown mechanism: J
- 5) How many possible operation states are there for a circuit with 3 diodes? B
- 6) This signal type has only 2 discrete levels: A
- 7) This is a unit of energy: H
- 8) Another name for the depletion layer: M
- 9) An acceptor impurity makes Si: G
- 10) A circuit for converting ac to pulsating dc: K
- 11) This is a common donor impurity for Si: P
- 12) This is a solid form of Si: D
- 13) This term relates electric field to carrier velocity: R
- 14) Another word for "pure": N
- 15) A type of diode that is made with a n-type Si to metal contact: O

Answers to choose from

- | | |
|-------------------|---------------------------------|
| A. Binary digital | J. Avalanche |
| B. Eight | K. Rectifier |
| C. Covalent | L. Donor impurity concentration |
| D. Amorphous | M. Space charge region |
| E. Twelve | N. Intrinsic |
| F. N-type | O. Schottky barrier |
| G. P-type | P. Phosphorous |
| H. Electron Volt | Q. Bandgap |
| I. Boron | R. Mobility |

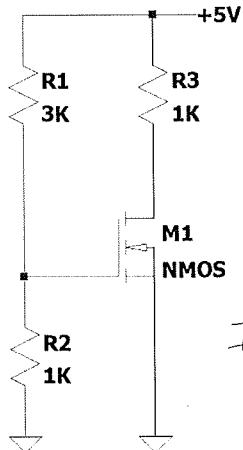Problem 3: (15 points)

For the circuit below, find the operating mode, I_D , V_{GS} , and V_D , for $K_n = 1 \times 10^{-3} \text{ A/V}^2$, $(W/L) = 10$, $V_{TN} = 1 \text{ V}$, and $\lambda = 0 \text{ V}^{-1}$.



$$V_Gs = \frac{5R_2}{R_1 + R_3} = \frac{5(1)}{(1+3)} = 1.25V$$

Assume Saturation mode

$$\begin{aligned} I_D &= \frac{1}{2} K_n \left(\frac{W}{L}\right) (V_{Gs} - V_{TN})^2 \\ &= \frac{1}{2} (1 \times 10^{-3})(10)(1.25 - 1)^2 \\ &= 312.5 \mu\text{A} \end{aligned}$$

$$V_D = 5 - I_D R_3 = 5 - (312.5 \times 10^{-6})(1000) = 4.69V$$


$$V_{DS} = V_D = 4.69V$$

$V_{DS} > V_{Gs} - V_{TN}$: in saturation mode


Q-point: $I_D = 312.5 \mu\text{A}$, $V_{GS} = 1.25V$, $V_{DS} = 4.69V$

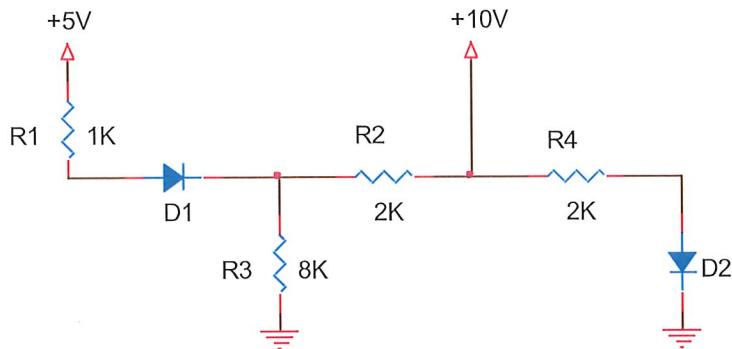Problem 4: (15 points)

What are the Q-points for the two diodes in the circuit below, using the ideal diode model?



Assume D_1 off and D_2 on

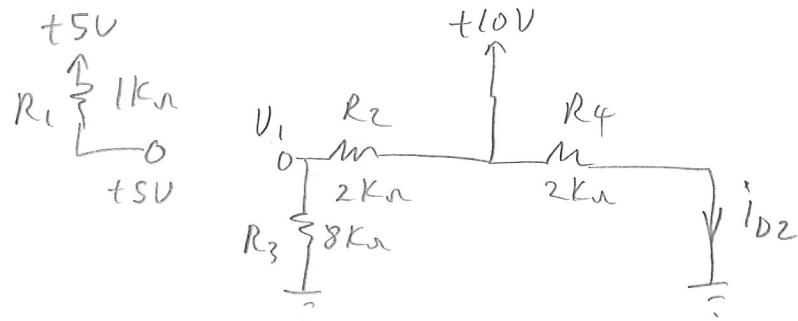

$$V_D1 = \frac{10(8)}{8+2} = 8V$$

$$V_{D1} = 5 - 8 = -3V \rightarrow D_1 \text{ is off}$$

$$I_{D2} = \frac{10}{2k} = 5mA \text{ if } D_2 \text{ is on}$$

Q-point: $D_1: (0A, -3V) \rightarrow \text{off}$

$D_2: (5mA, 0V) \rightarrow \text{on}$

Problem 5: (15 points)


What is f_T for an NMOS transistor with $L = 10 \mu\text{m}$, $\mu_N = 1100 \text{ cm}^2/\text{Vs}$, $V_{GS} = 4 \text{ V}$, and $V_{TN} = 1 \text{ V}$?

$$L = 10 \mu\text{m} = 10 \times 10^{-6} \text{ m} = 10 \times 10^{-4} \text{ cm}$$
$$f_T = \left(\frac{1}{2\pi}\right) \left(\frac{\mu_n}{L^2}\right) (V_{GS} - V_{TN})$$
$$= \left(\frac{1}{2\pi}\right) \left(\frac{1100}{(10 \times 10^{-4})^2}\right) (4 - 1)$$
$$= 525,2 \text{ MHz}$$

Bonus Problem (10 points)

What is the load voltage, V_L , for the circuit below, assuming that the filter only passes the dc voltage component? For D1, D2, D3 and D4, $V_{on} = 0.6 \text{ V}$. For D5, $V_z = 7 \text{ V}$ and $R_z = 100 \Omega$. The input voltage is 240 Vrms ac.


$$R_3 = R_1 + R_2 = 5 \text{ k}\Omega$$

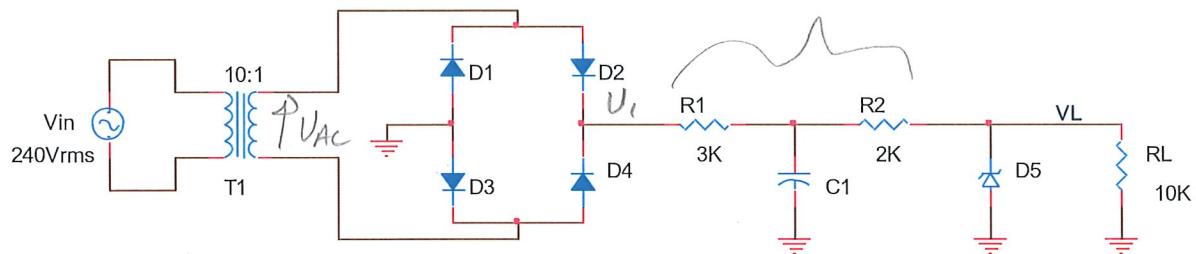

$$V_p = \sqrt{2} (240) = 339.41 \text{ V}$$


$$V_{AC} = \frac{V_p}{10} = 33.941 \text{ V}$$
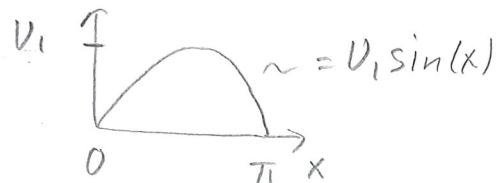
$$V_i = V_{AC} - 2(V_{on}) = 33.941 - 2(0.6) = 32.741 \text{ V}$$



$$V_{av} = V_{dc} = \frac{1}{\pi} \int_0^{\pi} V_i \sin(x) dx = \frac{V_i}{\pi} \left[-\cos(x) \right]_0^{\pi} = \frac{-V_i}{\pi} [-1 - 1] = \frac{2}{\pi} V_i$$
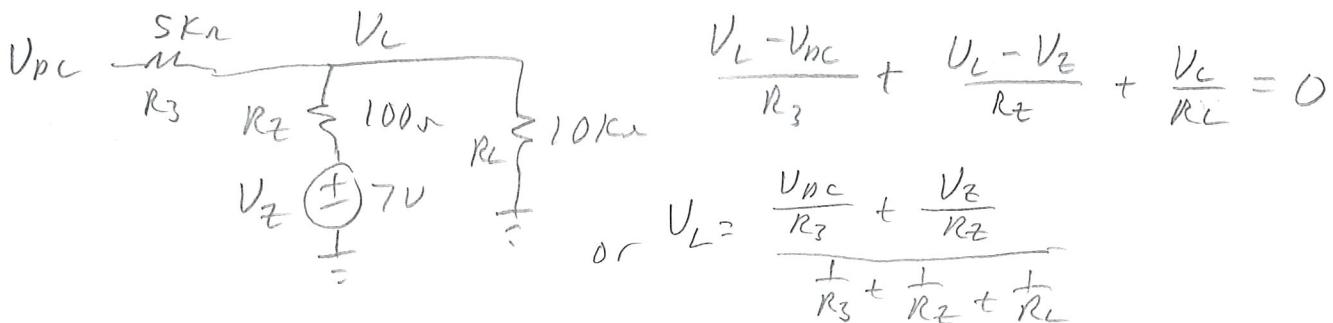
$$\therefore V_{dc} = \frac{2(32.741)}{\pi} = 20.841 \text{ V}$$



$$= \frac{\frac{20.841}{5000} + \frac{7}{100}}{\frac{1}{5000} + \frac{1}{100} + \frac{1}{10,000}}$$

$$= 7.20 \text{ V}$$

Blank sheet for Calculations