

Name:

Key

Exam #2

ELEC 2210

Wed 11/17/20

I verify below by my signature that I received no assistance on this exam from another person:

Signature:

Problem 1: (15 points)

What is the output frequency of a 7 inverter CMOS ring oscillator with a $R_{on} = 2.0 \text{ k}\Omega$ and $C = 1.1 \text{ pF}$ (5 points)?

$$f_{out} = \frac{1}{2N(2.4CR_{on})}$$

$$= \frac{1}{2(7)(2.4(1.1 \times 10^{-12})(2000))}$$

$$= 13.5 \text{ MHz}$$

Match the question with an answer by writing the letter of the answer in the blank next to the question. No answer is used more than once. (20 points)

Questions


- 1) This is parasitic-BJT event that is very bad for CMOS: I
- 2) A non-ideal effect in BJTs: P
- 3) This can be used to realize a mathematical function in a memory: E
- 4) A memory technology where UV light can be used to erase data: K
- 5) When current flows through a MOSFET that is off: L
- 6) This 2 transistor circuit can simplify the design of some logic gates: J
- 7) A CMOS inverter circuit with the input and output shorted can be used as a: B
- 8) A transistor made from two pn junctions connected back-to-back is a: C
- 9) This can be used to make a static memory cell: F
- 10) Unwanted variation in switching time: N

Answers to choose from

- | | |
|---------------------------------------|---------------------------------------|
| A. Thermal Noise | J. Transmission Gate |
| B. Voltage Reference | K. EPROM |
| C. BJT | L. Subthreshold Conduction |
| D. SRAM | M. MOSFET |
| E. Look-up Table | N. Jitter |
| F. Cross-coupled inverters | O. Transconductance |
| G. LED | P. Early Effect |
| H. Electron Volt | Q. Bandgap |
| I. Latchup | R. Mobility |

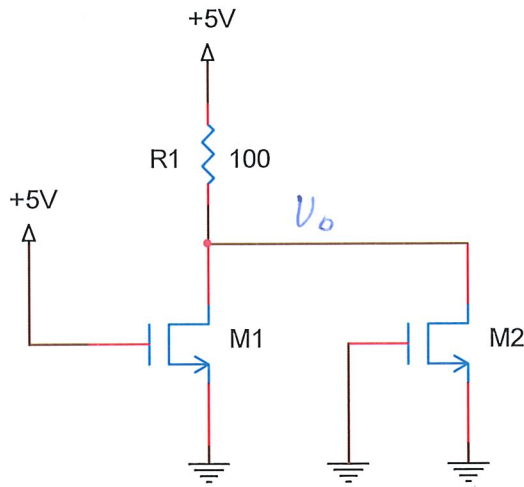Problem 3: (15 points)

Find the Q-points for M1 and M2 in the circuit below (I_D , V_{GS} , V_{DS}) AND operating mode, for $V_{TN} = 1$ V, $K_n = 1 \times 10^{-3}$ A/V², and $\lambda = 0$ V⁻¹.



Assume Saturation for m_1 ,

$$\therefore I_D = \frac{1}{2} K_n (V_{GS} - V_{TN})^2 = \frac{1}{2} (1 \times 10^{-3}) (5 - 1)^2 = 8 \times 10^{-3} \text{ A} = 8 \text{ mA}$$

$$V_D = 5 - 100(8 \times 10^{-3}) = 4.2 \text{ V} \approx V_{DS}$$

$$V_{GS} - V_{TN} = 5 - 1 = 4 \text{ V} \rightarrow V_{DS} > V_{GS} > V_{TN} \Rightarrow \therefore \text{Saturation}$$

$$M_2 \rightarrow V_{GS} = 0 \text{ V} \rightarrow \text{off}$$

$$m_1 \text{ Q-Point} : (I_D = 8 \text{ mA}, V_{GS} = 5 \text{ V}, V_{DS} = 4.2 \text{ V}) \rightarrow \text{Saturation}$$

$$m_2 \text{ Q-Point} : (I_D = 0 \text{ A}, V_{GS} = 0 \text{ V}, V_{DS} = 4.2 \text{ V}) \rightarrow \text{off}$$


Problem 4: (15 points)

What is R_{on} for M1 in problem 3?

$M_1 \rightarrow$ in saturation \Rightarrow cannot use $R_{on} = \frac{1}{K_n(V_{GS} - V_{TN})}$

$$\therefore R_{on} = \frac{V_{DS}}{I_D} = \frac{4.2}{8 \times 10^{-3}} = 525 \Omega$$

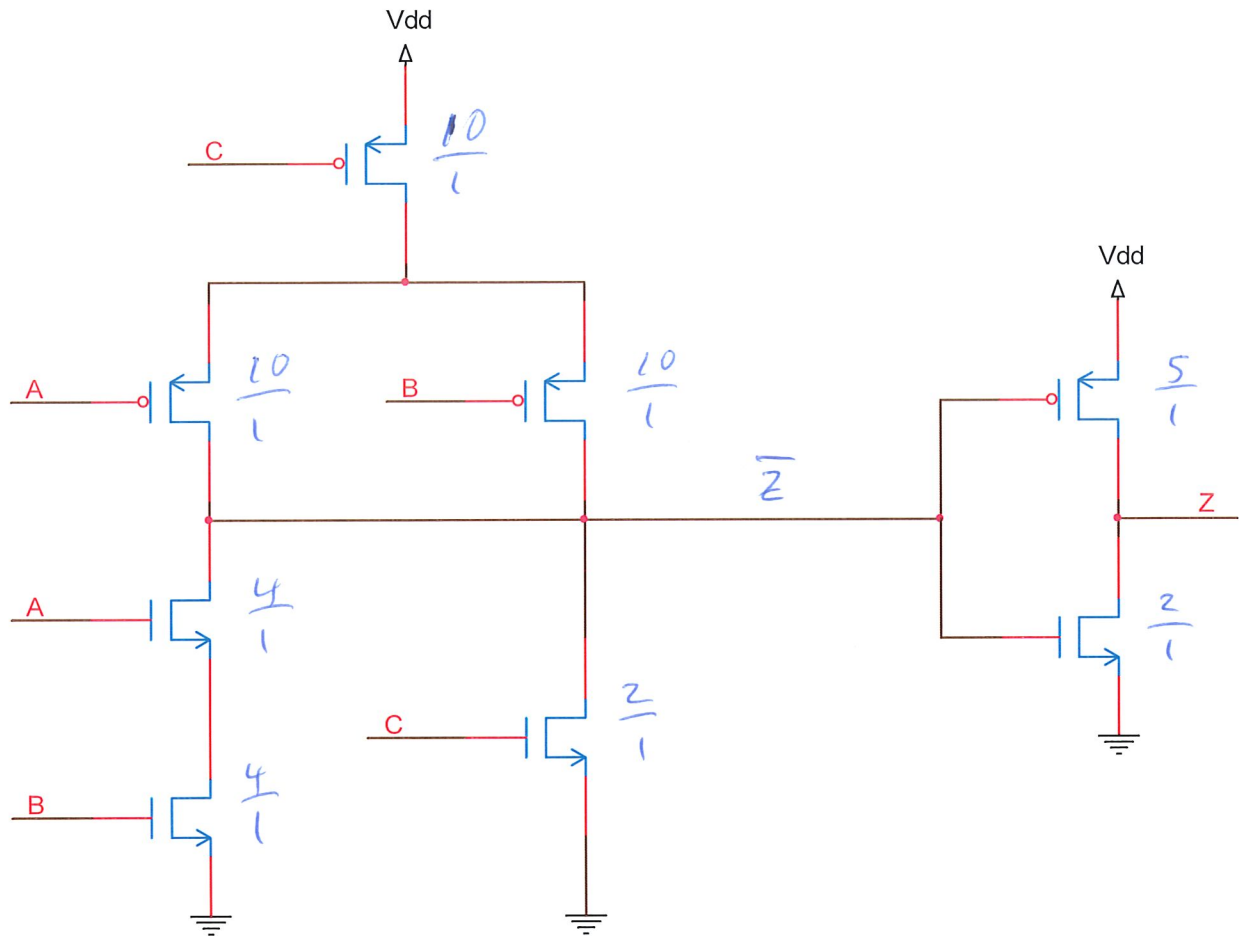Problem 5: Consider the CMOS logic circuit below:




a. Compared to a standard CMOS inverter with $\left(\frac{W}{L}\right)_n = \left(\frac{2}{1}\right)$ and $\left(\frac{W}{L}\right)_p = \left(\frac{5}{1}\right)$, write the optimum $\left(\frac{W}{L}\right)$ ratio next to each transistor in the circuit above **(10 points)**.

b. What is the Boolean expression for Z in the circuit above **(10 points)**?

$$Z = AB + C$$

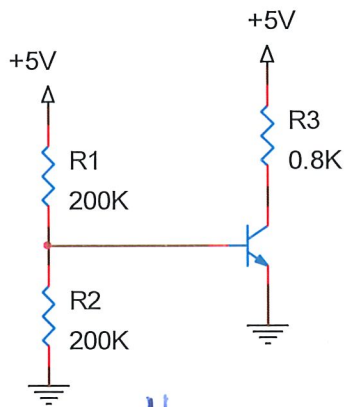
Problem 5: (15 points)

Find the BJT Q-Point, assuming Forward-Active Region of operation and $\beta_F = 100$.



$$V_{Th} = \frac{5(200)}{200+200} = 2.5V$$

$$R_{Th} = 200k // 200k = 100k\Omega$$

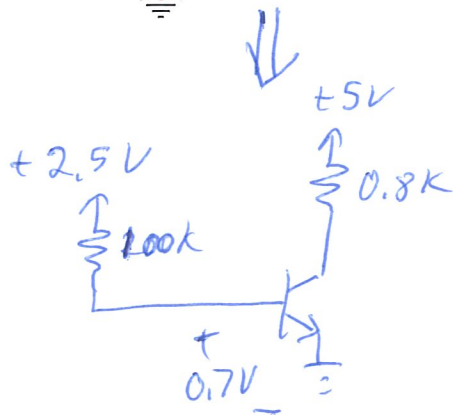

$$i_B = \frac{2.5 - 0.7}{100,000} = 18\mu A$$



$$\begin{aligned} i_C &= \beta i_B \\ &= 100(18\mu) \\ &= 1.8mA \end{aligned}$$

$$V_C = 5 - 800(1.8 \times 10^{-3}) = 3.56V = V_{CE}$$

$$Q\text{-Point} : (i_C = 1.8mA, V_{CE} = 3.56V)$$

Bonus Problem (10 points)

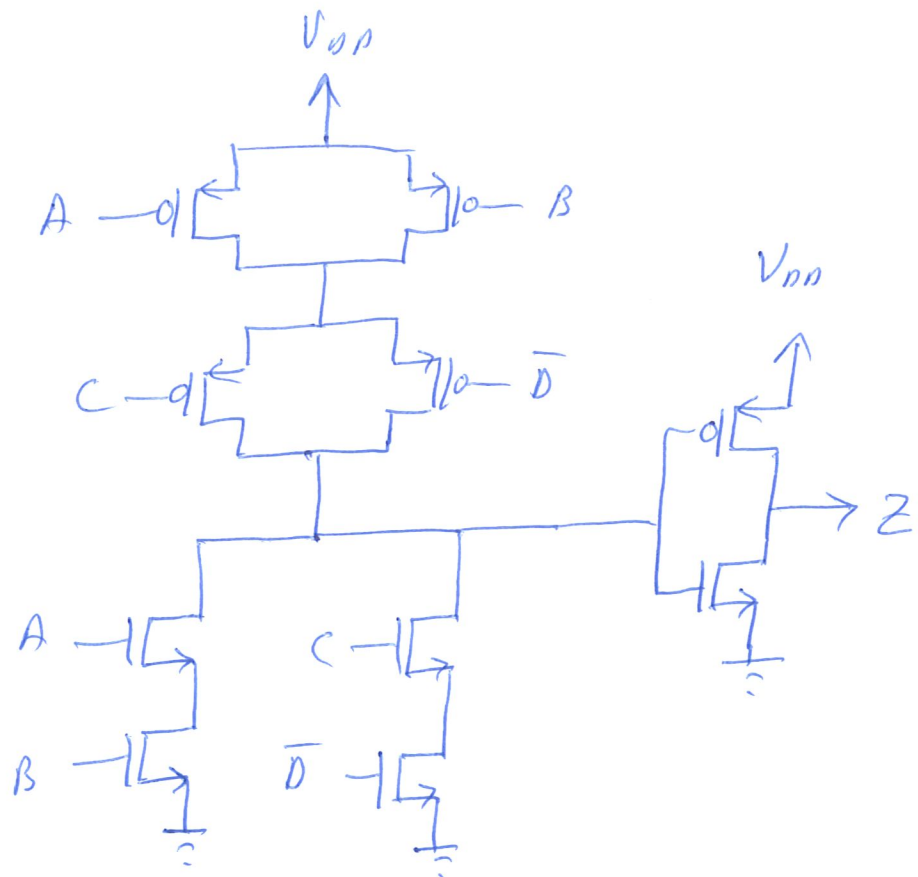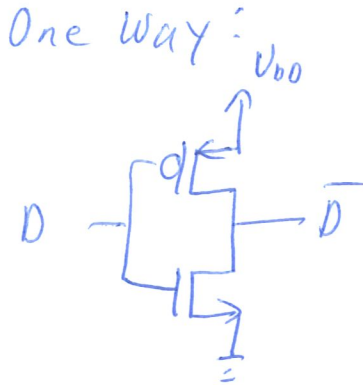Draw a CMOS logic circuit to realize this Boolean expression: $Z = AB + C\bar{D}$. Do not put (W/L) ratios, just draw the circuit.



Blank sheet for Calculations