

ELEC 7970

Homework 6

Due: Tuesday 3/21/23

Design and simulate a circuit that produces a 1 KHz 0 V – 5 V square wave. Show your schematic diagram (hand drawn is fine), simulation file, and time response for several cycles.