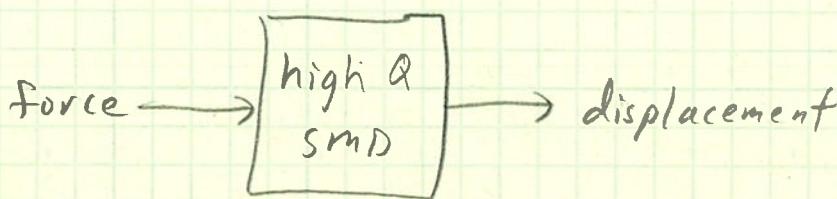



I. MEMS Resonators



at ω_d : displacement lags force by 90°

\therefore To make it self-resonate at ω_d , add 90° of additional phase delay and appropriate gain such that $AB = 1 \angle 0^\circ$ {positive feedback model} or $AB = 1 \angle -180^\circ$ {negative feedback model}

a. Example

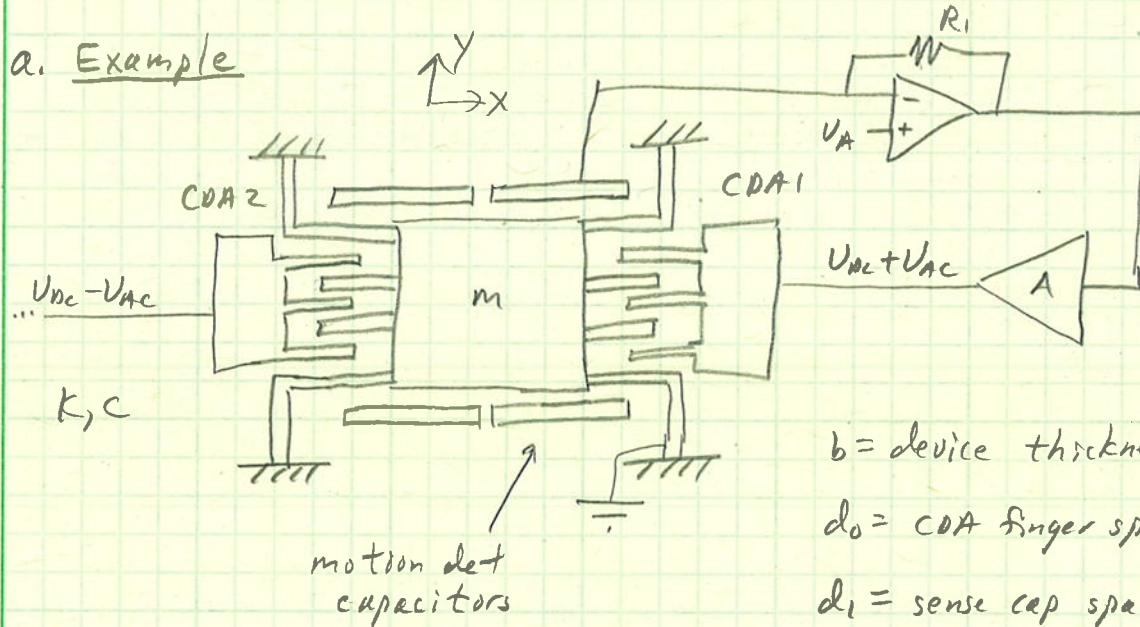

b = device thickness

d_0 = COA finger space width

d_1 = sense cap space width


l = sense cap nominal overlap

$$\text{Net force} = \frac{4n\beta \epsilon_0 Erb}{d_0} (V_{dc} V_{ac}) \sin(\omega_d t) = K_1 V_{ac} \sin(\omega_d t) = Ax \sin(\omega_d t)$$

$$\text{where } K = \frac{4n\beta \epsilon_0 Erb V_{dc}}{d_0}$$


$$\therefore x(t) = -\frac{Ax}{C \omega_d} \cos(\omega_d t) = -\frac{K_1 V_{ac}}{C \omega_d} \cos(\omega_d t)$$

Motion sense capacitor

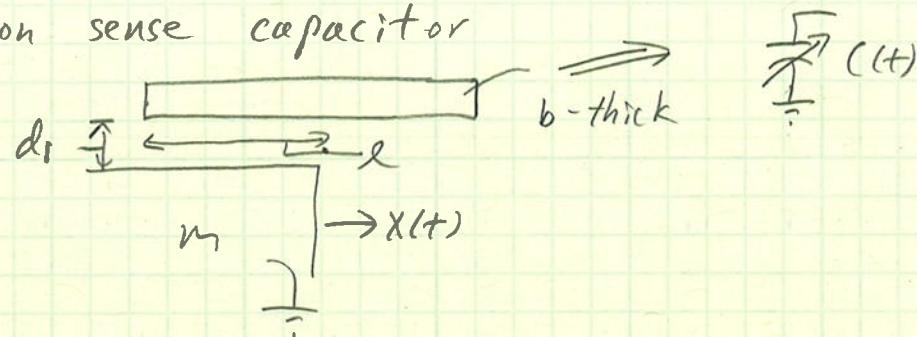

$$C(t) = \frac{\epsilon_0 \epsilon_r b}{d_1} (l + x(t)) = \frac{\epsilon_0 \epsilon_r b}{d_1} \left(l - \frac{k_1 V_{AC}}{c \omega d} \cos(\omega t) \right)$$

Using a TIA

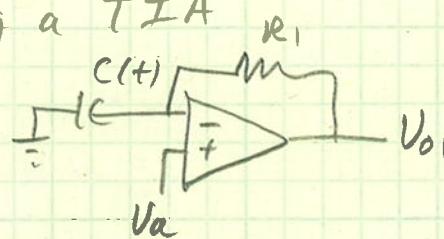

$V_A = \text{DC voltage}$

$$V_{o1} = V_a + V_a R_i \frac{dc}{dt}$$

$$= V_a + \frac{V_a R_i \epsilon_0 \epsilon_r b}{d_1} \left(0 + \frac{k_1 V_{AC}}{c} \sin(\omega t) \right)$$

$$= V_a + \frac{V_a R_i \epsilon_0 \epsilon_r b k_1 V_{AC}}{d_1 c} \sin(\omega t)$$

V_{o1} is in phase with Net force $\rightarrow |AB| = 0^\circ$ at $\omega = \omega_d$

\therefore remove V_a and amplify with a gain, G


$$\therefore |AB| = I = \frac{G V_a R_i \epsilon_0 \epsilon_r b 4 n \beta \epsilon_0 \epsilon_r b V_{pc}}{d_1 c d_0}$$

$$\therefore G = \frac{d_1 c d_0}{V_a \epsilon_0^2 \epsilon_r^2 b^2 4 n \beta V_{pc} R_i} = G_{\text{optimum}}$$

If $G < G_{\text{optimum}}$ \rightarrow motion dies out

If $G > G_{\text{optimum}}$ \rightarrow mass crashes into frame and probably breaks
or motion is distorted

\therefore AGC is needed

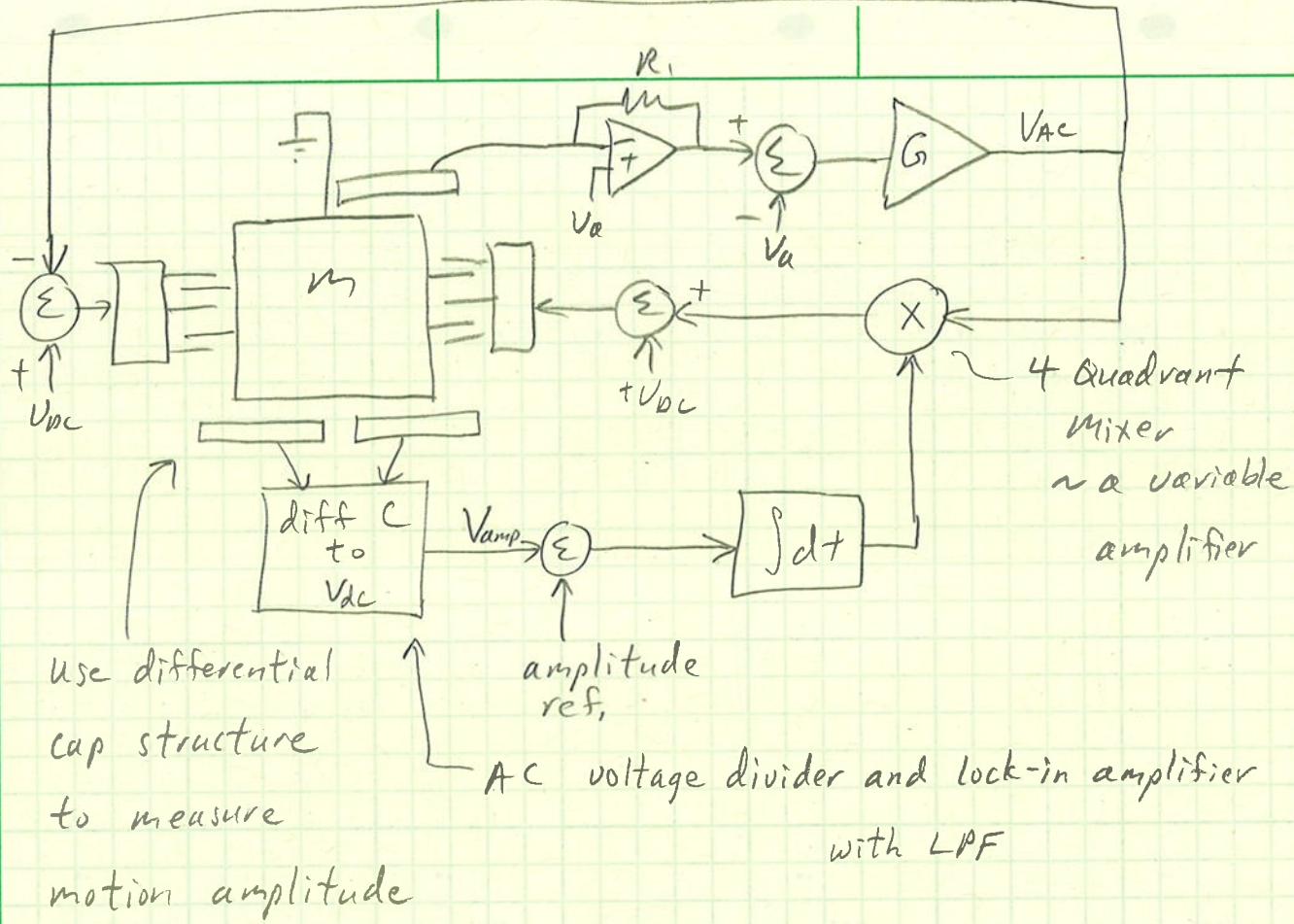

b. Other Configurations + Notes

- ① RC stage(s) used to produce 90° phase delay instead of TIA → differentiator {noisy}
- ② Piezoresistors {Wheatstone Bridge} used to detect displacement instead of capacitors
- ③ MEMS resonators → relatively low frequency, could possibly perform signal processing steps digitally using A/D, microcontroller, D/A and simple fixed gain amplifier
- ④ Non-idealities in components (MEMS device, op amps, etc.) should be considered
- ⑤ Check stability of the control loops