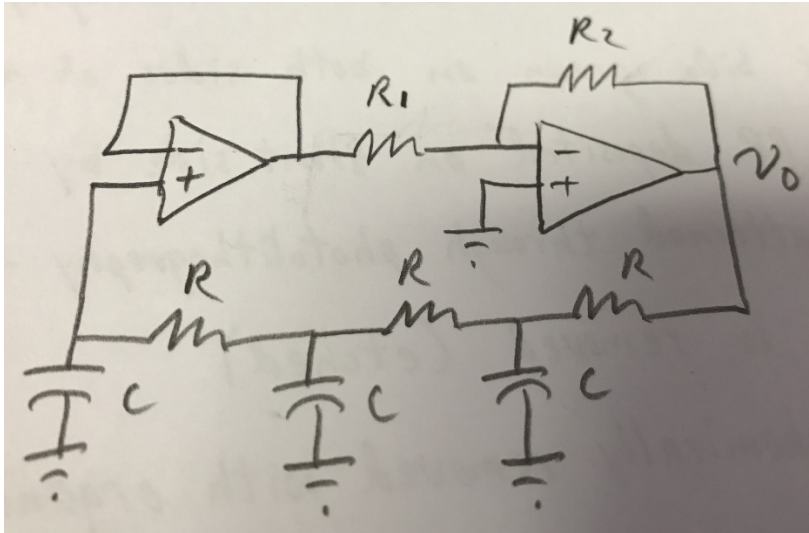


Thursday 2/2/23

b. RC : CR transformation phase shift oscillator

Here, the R's and C's have been interchanged compared to the earlier phase shift oscillator circuit.

The voltage follower buffer (a second op amp) is needed to prevent loading of the CR ladder circuit.




$$A(j\omega)\beta(j\omega) = \frac{-\frac{R_2}{R_1}}{(sCR)^3 + 5(sCR)^2 + 6sCR + 1}$$

$$\text{Consider: } A(j\omega)\beta(j\omega) \Big|_{\omega = \frac{\sqrt{6}}{RC}} = \frac{-\frac{R_2}{R_1}}{-j6\sqrt{6}-30+j6\sqrt{6}+1} = \frac{\frac{R_2}{R_1}}{-29}$$

Therefore for oscillation: $\omega = \frac{\sqrt{6}}{RC}$ and $\frac{R_2}{R_1} = 29$

c. Buffered RC phase delay oscillator

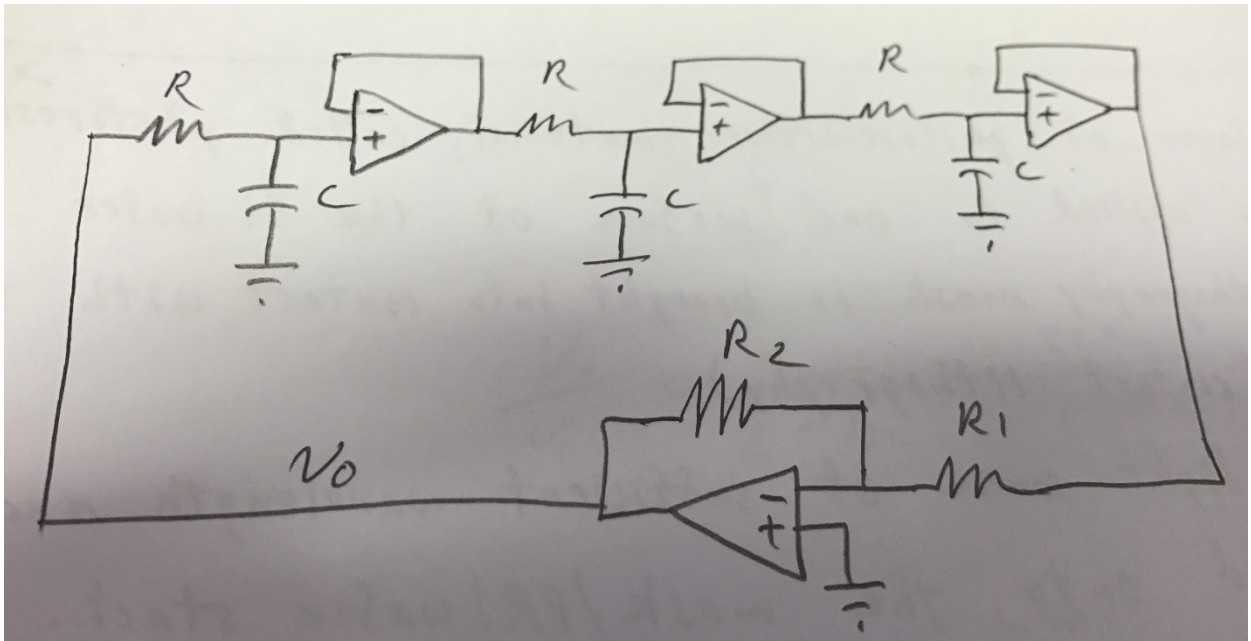

Easy to build with a quad op amp package.

Each buffered RC stage must provide -60° phase delay at the oscillation frequency:

$$G_{RC} = \frac{1}{1 + j\omega RC}$$

$$\phi = -\tan^{-1}(\omega RC) = -60^\circ \text{ per stage}$$

$$\text{Therefore: } \omega = \frac{\sqrt{3}}{RC}$$


$$\text{Per RC stage: } |G_{RC}| = \frac{1}{\sqrt{1+(\omega RC)^2}} = \frac{1}{2}$$

$$\text{Therefore, for all 3 RC stages: } |G| = \frac{1}{8}$$

Therefore $A(j\omega)$ to satisfy the BSC for oscillation has a gain of 8.

A gain of 8 is much less restrictive on op amp BW than a gain of 29!

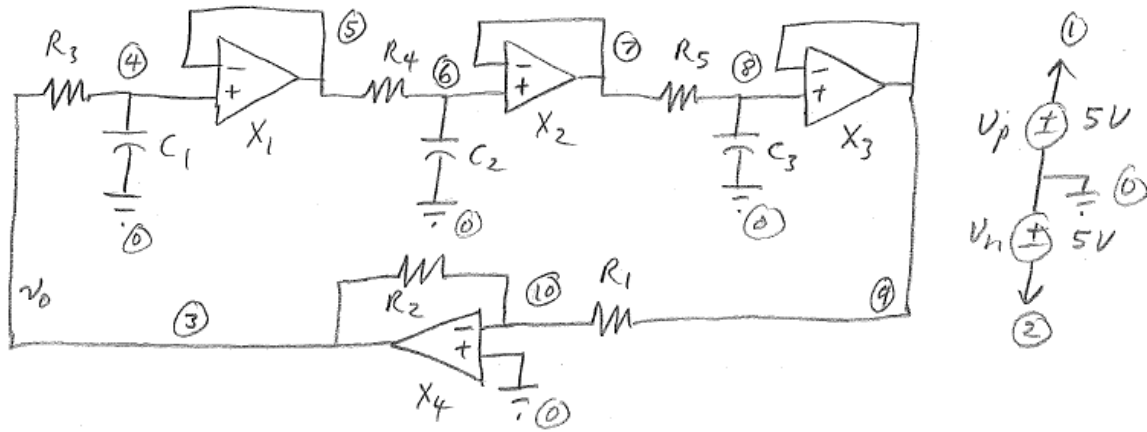The circuit does require 4 op amps though.



op amp: ADI AD8610

select $f = 1\text{kHz}$, $R_3 = R_4 = R_5 = 1\text{k}\Omega$


$$C = \frac{\sqrt{3}}{2\pi R f} \approx 0.276\mu\text{F} = C_1 = C_2 = C_3$$

let $R_1 = 1\text{k}\Omega$, $R_2 = 8\text{k}\Omega$


Pspice simulation result: no oscillation

\therefore set $R_2 = 9\text{k}\Omega \rightarrow$ now it oscillates


$$f_0 \approx 1000\text{Hz}$$

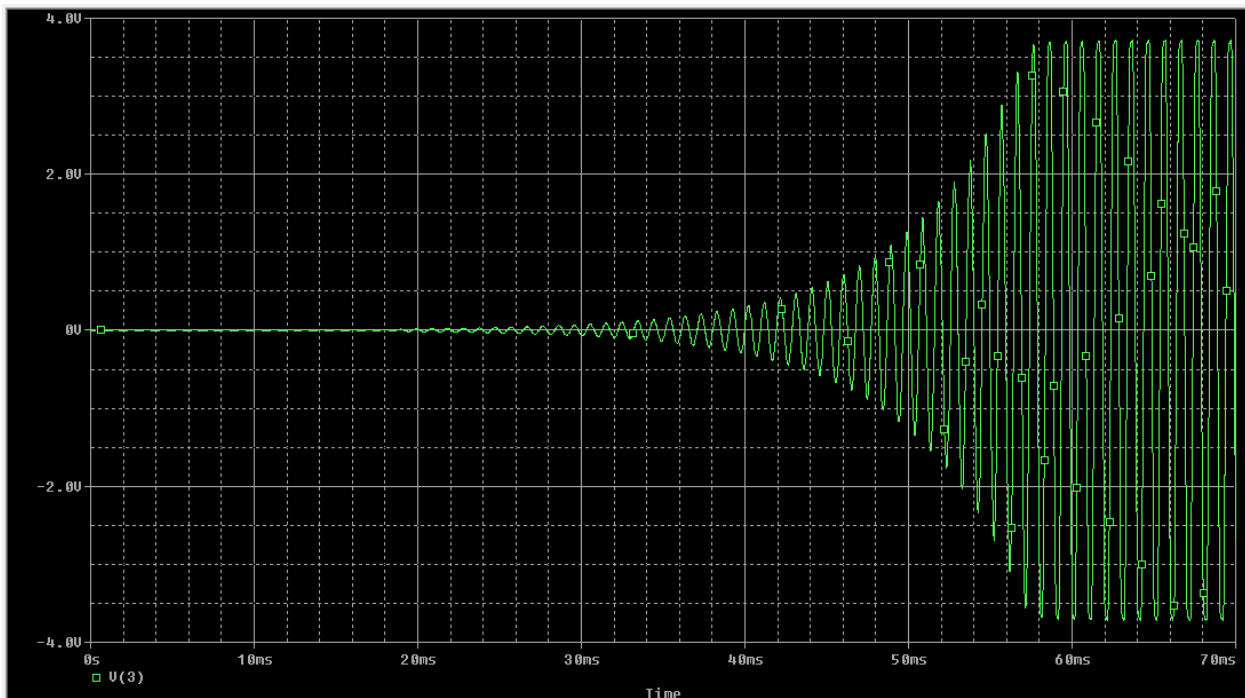

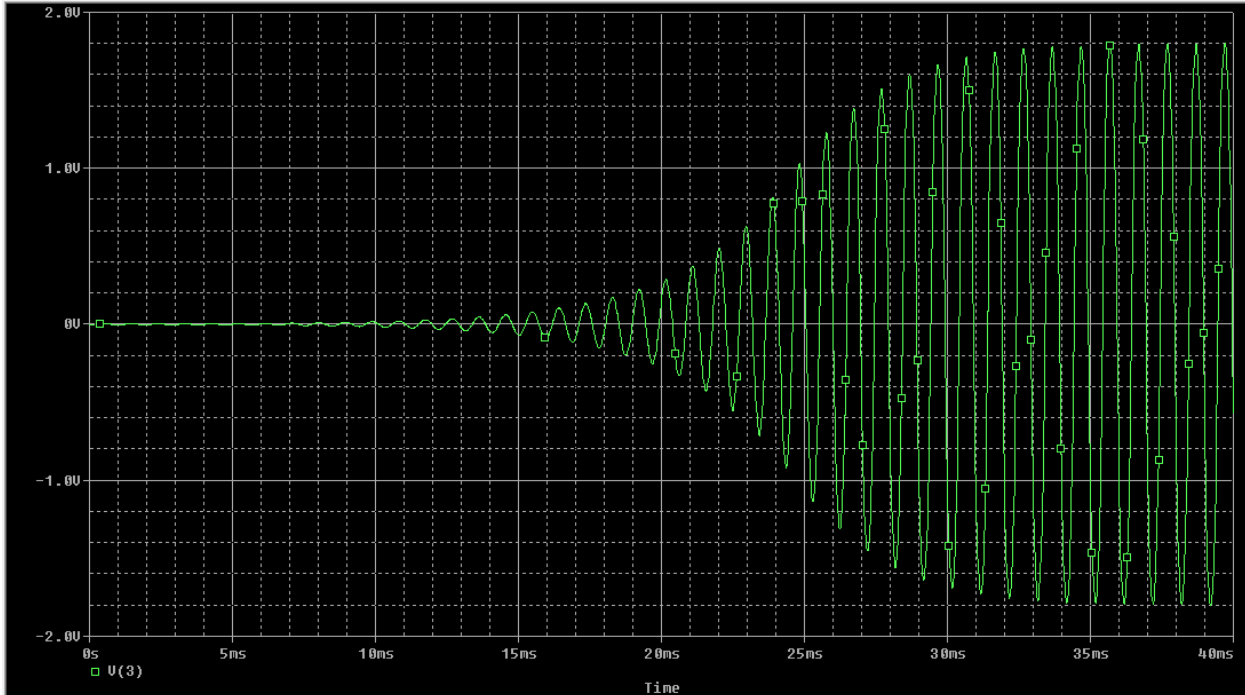AGC: R_2 replaced with a 10 k Ω pot, two 0.5V Schottky diodes connected between the wiper and one end, in opposite directions. The pot is set with 5 k Ω on each side of the wiper:



Close up:

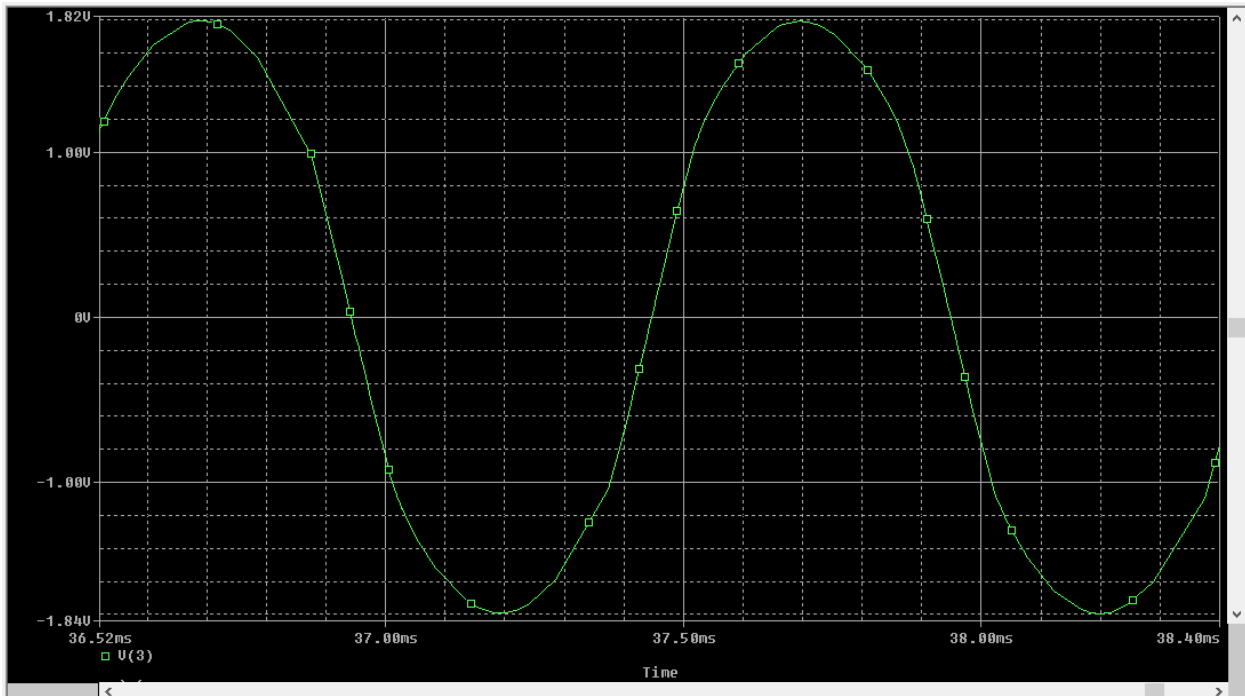

d. Buffered RC phase delay oscillator with four RC stages

This circuit requires 5 op amps.

Each buffered RC stage must provide -45° phase delay at the oscillation frequency:

$$G_{RC} = \frac{1}{1 + j\omega RC}$$

$$\phi = -\tan^{-1}(\omega RC) = -45^\circ$$


$$\text{Therefore: } \omega = \frac{1}{RC}$$

$$\text{Per RC stage: } |G_{RC}| = \frac{1}{\sqrt{1+(\omega RC)^2}} = \frac{1}{\sqrt{2}}$$

$$\text{Therefore, for all 4 RC stages: } |G| = \frac{1}{4}$$

Therefore $A(j\omega)$ to satisfy the BSC for oscillation has a gain of 4.

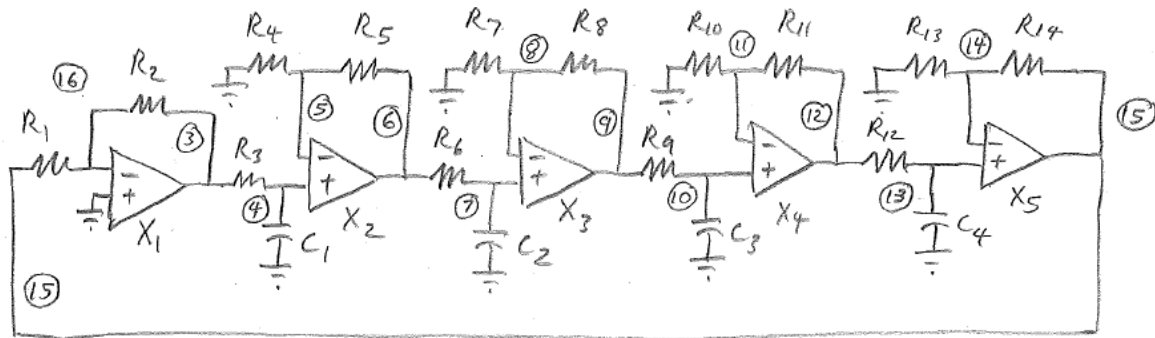Advantage to this circuit: two sinusoids 90° apart are available from the circuit, which are needed for quadrature signal processing applications.



$$1 + \frac{R_5}{R_4} = \sqrt{2} = 1.414 : R_4 = 10k\Omega \text{ and } R_5 = 4140\Omega$$

$$R_4 = R_7 = R_{10} = R_{13} \text{ and } R_5 = R_8 = R_{11} = R_{14}$$

$$\text{desire } f = 1\text{KHz} : f = \frac{1}{2\pi RC} \rightarrow C = \frac{1}{2\pi Rf} = \frac{1}{2\pi(1000)(1000)} = 159.16\text{nF}$$

$$R_3 = R_6 = R_9 = R_{12} = 1k\Omega$$


$$C_1 = C_2 = C_3 = C_4 = 159.16\text{nF}$$

$$\text{Let } R_1 = R_2 = 10k\Omega \rightarrow AC(j\omega) = -1$$



Result : no significant oscillation

set $R_2 = 15k\Omega \rightarrow$ good oscillation

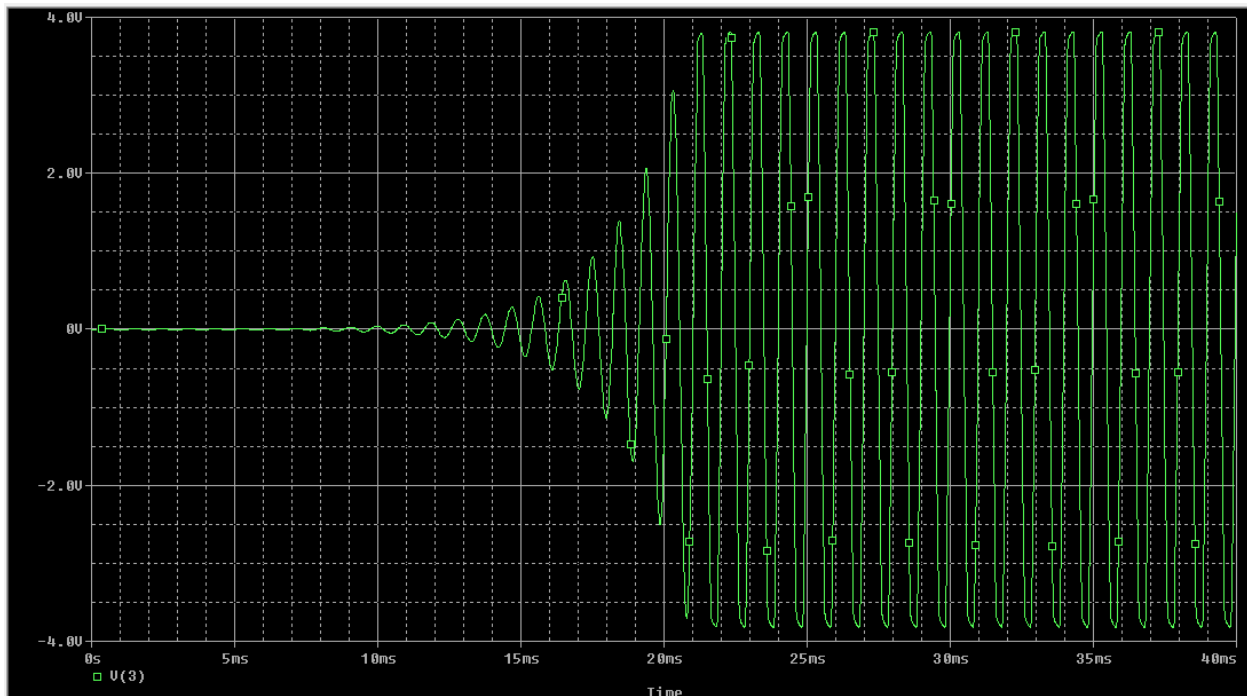
measured oscillation frequency $\approx 1\text{KHz}$



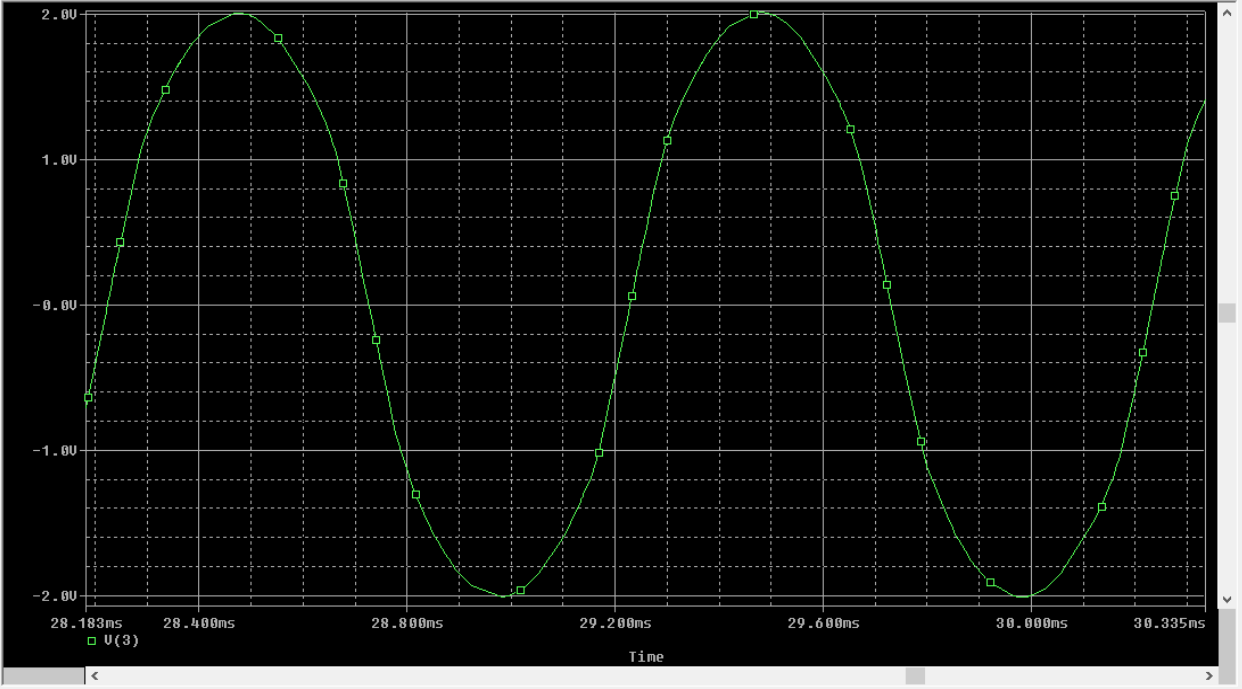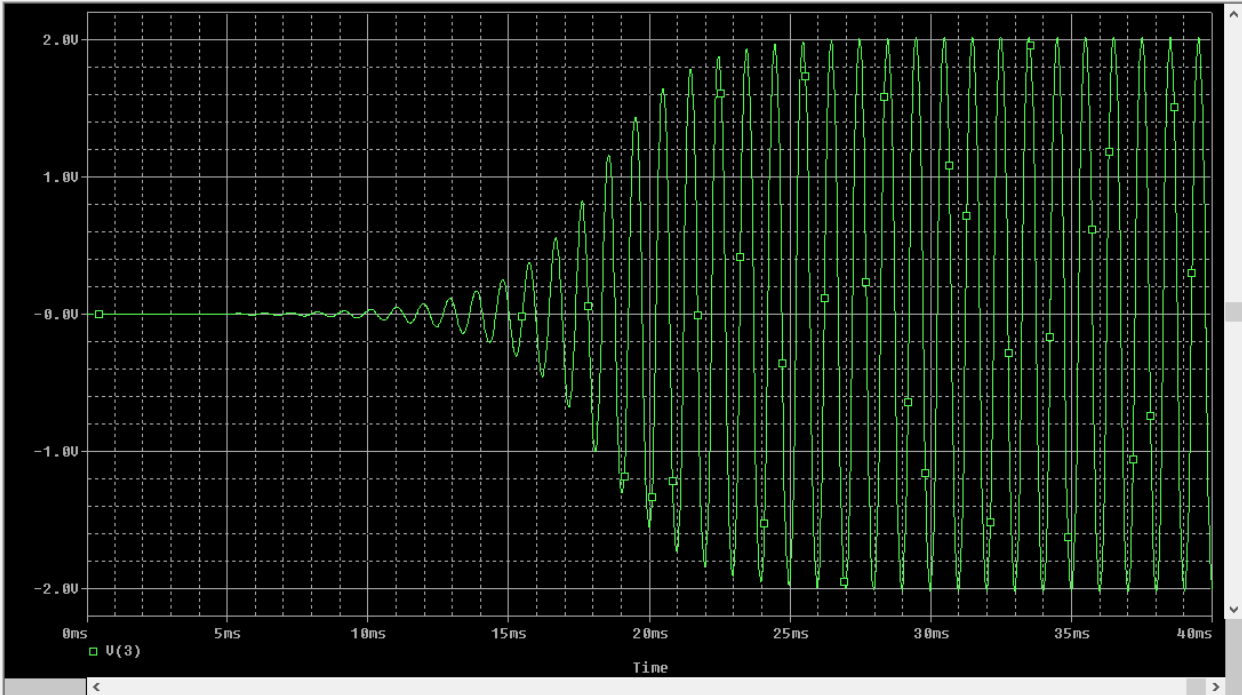Replacing R_2 with 13 k Ω pot and two Schottky diodes between the wiper and node 3, with 6.4 k Ω between the diodes results in a sinewave with an amplitude of approximately 2V:



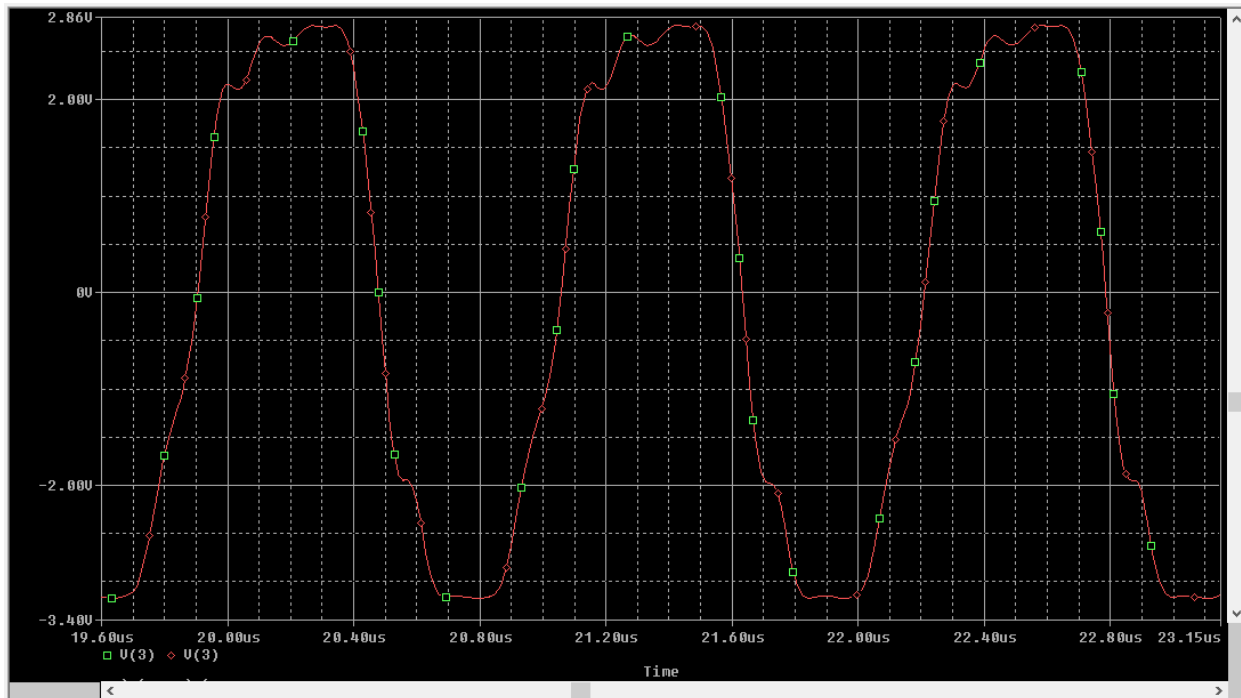How high in frequency can this oscillator go? All C's were replaced with 159.16pF, which should result in a 999,969 Hz (almost 1 MHz) sinewave.



The distorted sinewave has a fundamental frequency of approximately 950 KHz. The oscillator used the 25 MHz GBW product AD8610 op amp for all op amps. The distortion might also be due to the AGC diodes.