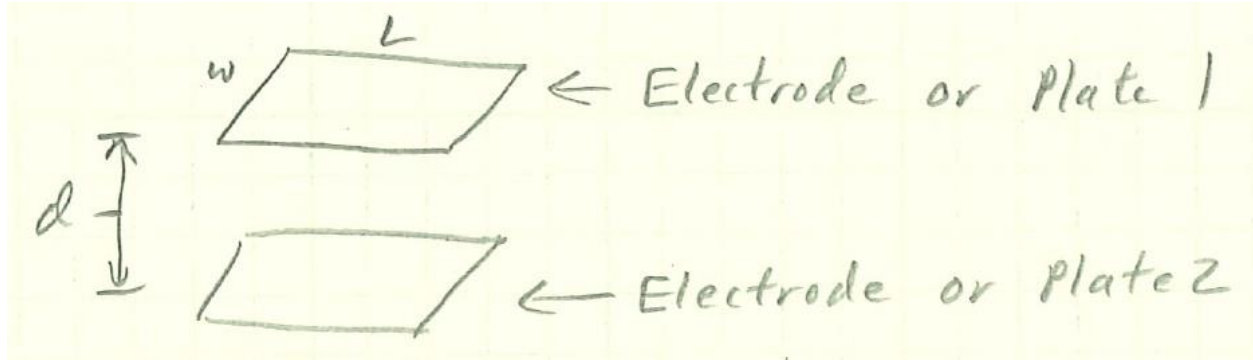


Capacitive Sensing

1. Simple Parallel Plate Capacitor



d is the electrode separation distance.

For $A \gg d^2$: fringing effects can be ignored and $C = \frac{\epsilon_0 \epsilon_r A}{d}$

where: ϵ_0 = permittivity of free space = 8.854 pF/m

ϵ_r = relative permittivity of the dielectric material between the electrodes


For a vacuum $\epsilon_r = 1$, and for most gases: $\epsilon_r \approx 1$

A = electrode overlapping surface area = wL here

Ways to detect with a capacitive sensor (non-fringing sensor):

- 1) Change the dielectric material, i.e. change $\epsilon_r \rightarrow$ this can be difficult to do.
- 2) Change the electrode separation distance \rightarrow easy to do.

Consider this simple MEMS accelerometer:

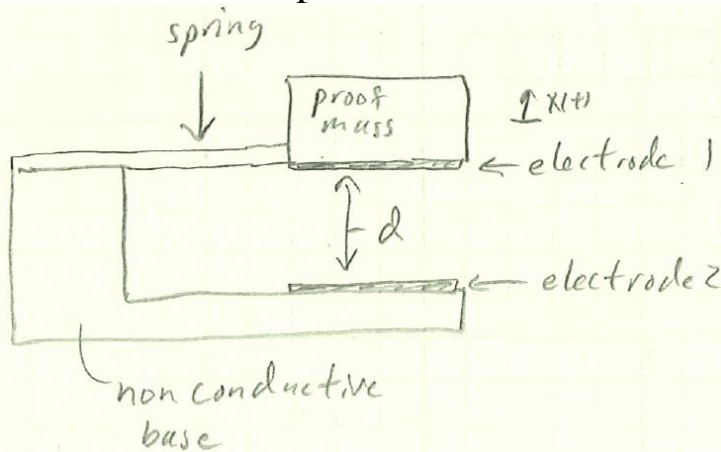


$$C = \frac{\epsilon_0 \epsilon_r A}{d_0 + x(t)}$$

where d_0 is d when $x(t) = 0$ ("at rest" condition)

3) Change the electrode overlap area \rightarrow easy to do.

Consider this MEMS accelerometer

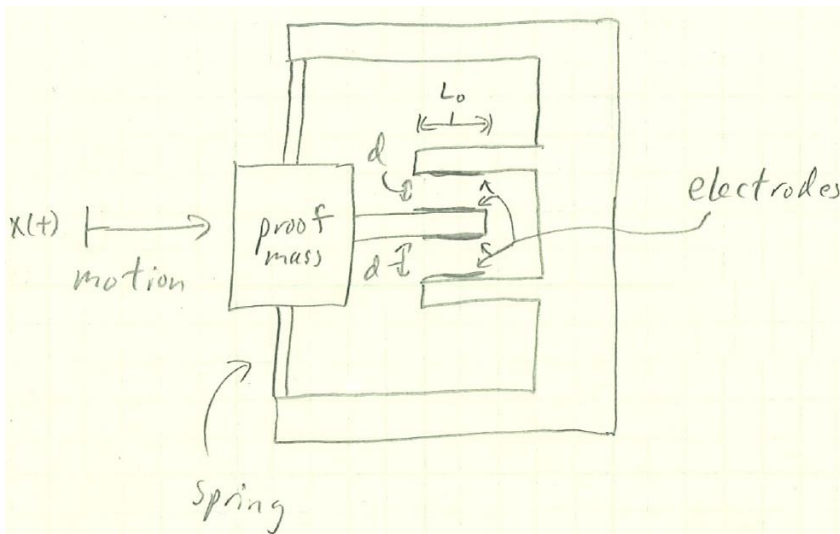

d , w , and ϵ_r are constants here.

$$L(t) = L_0 + x(t)$$

$$\therefore C(t) = \frac{\epsilon_0 \epsilon_r w L(t)}{d} = \frac{\epsilon_0 \epsilon_r w}{d} (L_0 + x(t))$$

2. Typical Capacitor Sizes in MEMS


For a parallel plate capacitor: let $w = 50 \mu\text{m}$, $L = 100 \mu\text{m}$, $d = 10 \mu\text{m}$, and $\epsilon_r = 1$

$$\therefore C = \frac{(8.854)(50 \times 10^{-6})(100 \times 10^{-6})}{10 \times 10^{-6}} = 0.004427 \text{ pF} = 4.427 \text{ fF}$$

1 fF = 1×10^{-15} F ! \rightarrow a very small capacitance!

Consider that a 10% change in C is only 0.4427 fF!

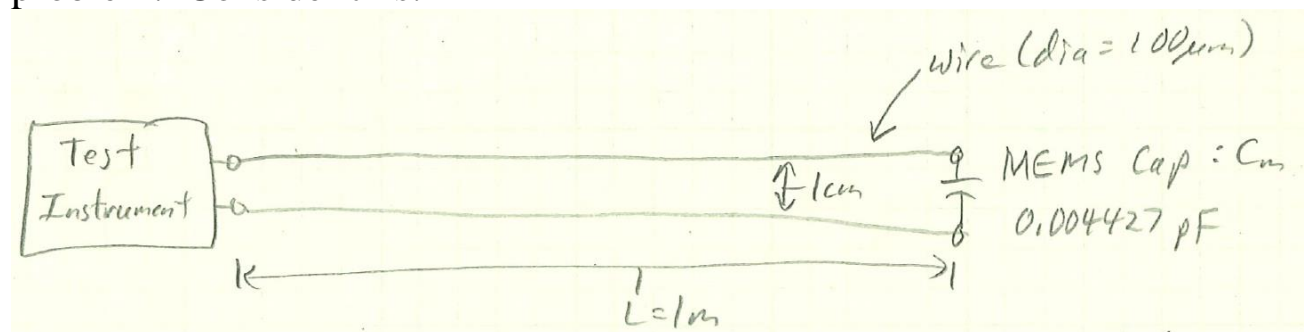
With sensor capacitances this small, stray capacitance can be a big problem. Consider this:



$$\text{For the cable: } C_L \approx \frac{(8.854)(100 \times 10^{-6})(1)}{0.01} = 0.08854 \text{ pF}$$

Observe that: $\frac{C_L}{C_m} = 20 \rightarrow C_L = 20C_m!$ or $C_L = 200\Delta C_m |_{10\% \Delta}$


Instrumentation model:

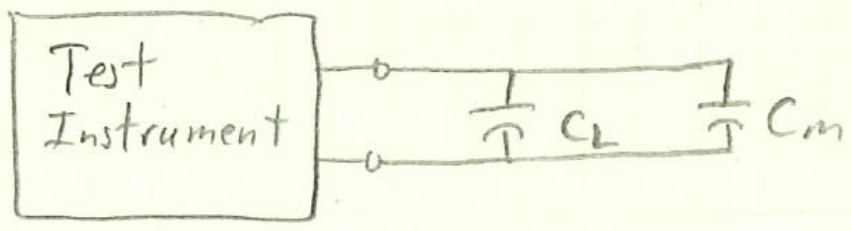

C_m adds with C_L . Therefore, you need to locate the interface circuitry as close to the MEMS capacitor as possible, such as on the same chip.

Note: stray capacitance can also be an issue on the MEMS chip between different microstructures.

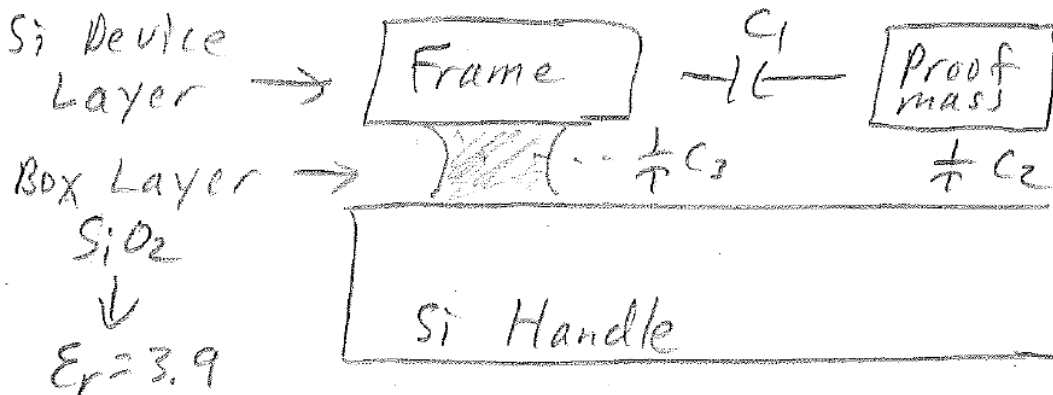Example: A cross-section of an SOI MEMS device:



C_1 → desired capacitance between two microstructures

C_2 → stray capacitance in air ($\epsilon_r \sim 1$)

C_3 → stray capacitance in SiO₂ ($\epsilon_r = 3.9$)

So, C_2 and C_3 may not be able to be ignored, depending on the design, particularly with a typical Box Layer thickness of 0.5 μm to 1 μm .

3. Capacitor Interface Circuitry: Oscillator


Consider C: $q = CV$ and $\dot{q} = \dot{C}V + \dot{V}C = i(t)$

In most EE application: $\dot{C} = 0 \rightarrow i(t) = C \frac{dV}{dt}$


However, with capacitive sensors, $\dot{C} \neq 0$ usually

So, how then do you measure C(t)???

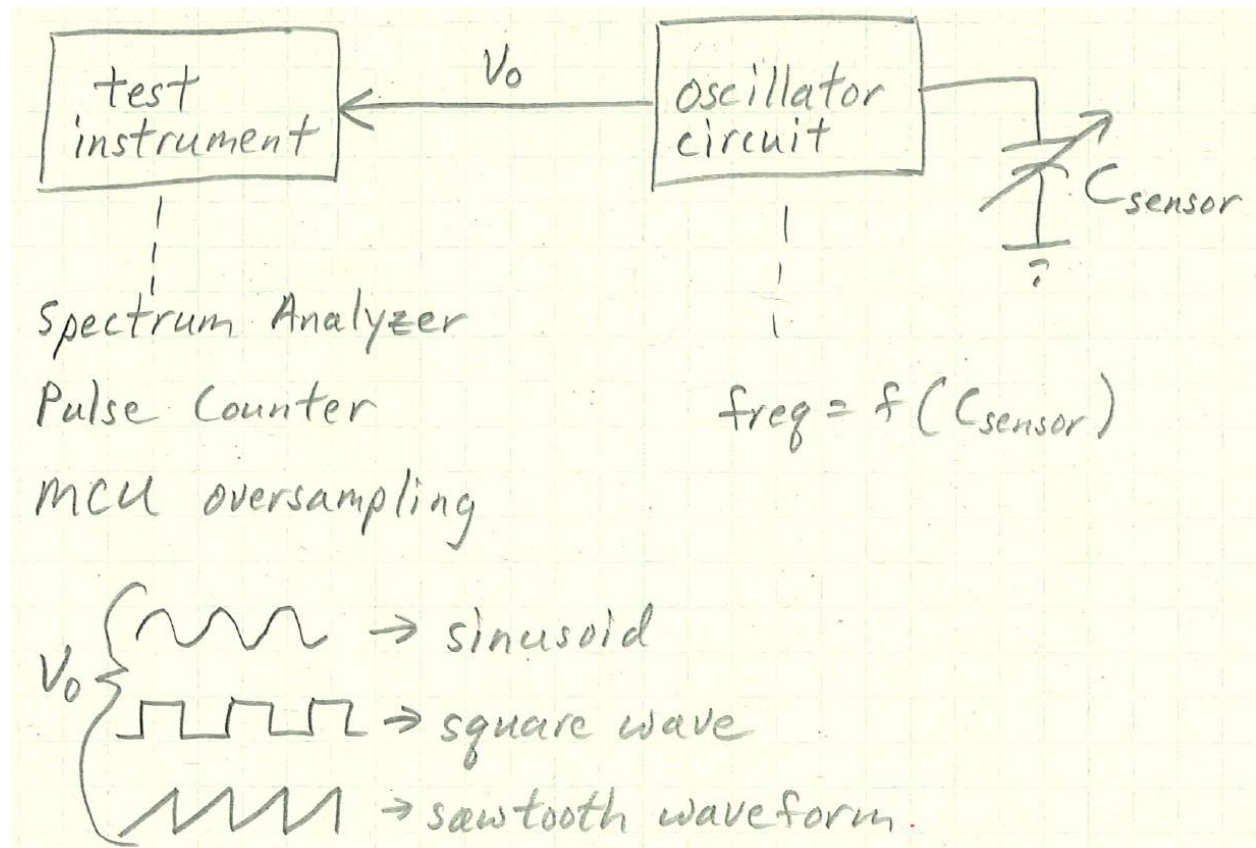One technique is to place C(t) in an oscillator circuit where $\text{freq} = f(C)$:



Consider a simple CMOS ring oscillator:

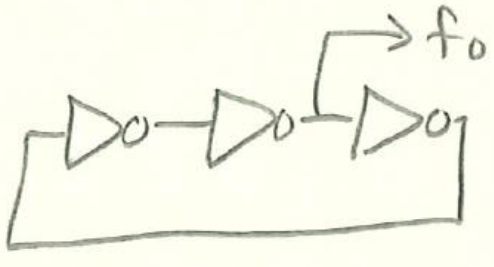

It is a closed chain of an odd number of inverter stages \rightarrow unstable


Let τ_d = propagation delay per inverter

N = number of inverters

It takes two complete cycles for two state changes (1 period)

$$\text{Therefore: } f = \frac{1}{2\tau_d N}$$

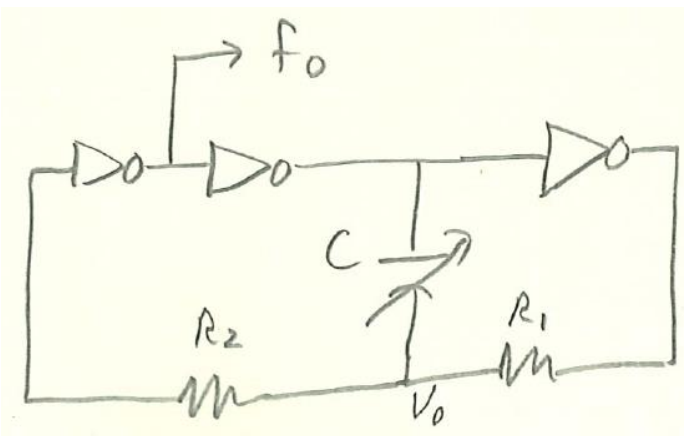Although this oscillator circuit is not useful for a capacitive sensor interface circuit, consider this related circuit:



This oscillator circuit is called a relaxation oscillator, and it is based on an RC time constant that controls when a state change occurs in the unstable chain of CMOS inverters.

Circuit analysis:

Assume: (1) $R_1 = R_2 = R$


(2) $C \gg$ input capacitance on an inverter

(3) The inverter trip voltage: $V_{tr} = \frac{V_{dd}}{2}$

Therefore, when V_o crosses V_{tr} , the system changes state.


The RC time constant determines the output frequency, f_o , let's see how:

Examine the circuit with $V_{dd} = 5V$:

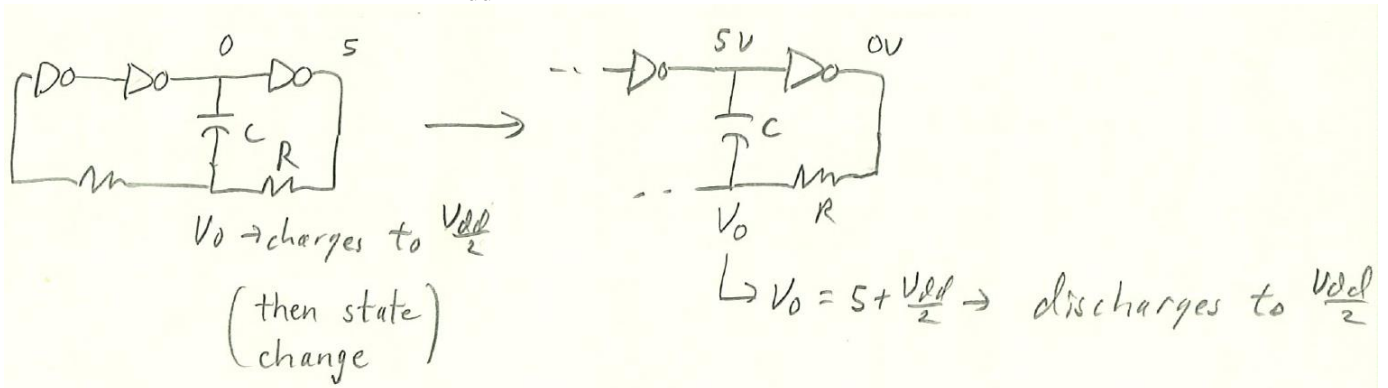

With $V_{dd} = 5V$: $V_{tr} = 2.5V$

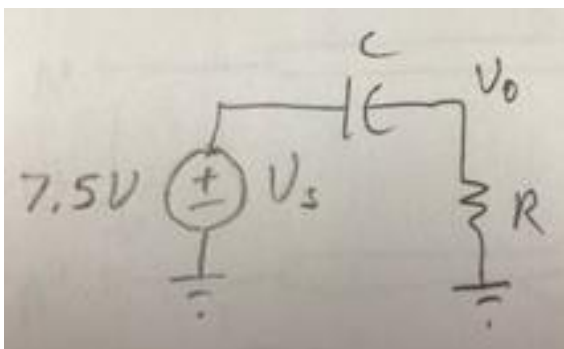At switching time, we have this circuit model:



With this model, C is fully discharged initially and $v_o = 7.5\text{V}$. We want to find t for $v_o = 2.5\text{V}$.

$$\frac{V_o}{V_s} = \frac{R}{R + \frac{1}{sC}} = \frac{s}{s + \frac{1}{RC}}$$

$$V_s(s) = \frac{7.5}{s}$$

$$V_o(s) = V_s(s) \left(\frac{s}{s + \frac{1}{RC}} \right) = \frac{7.5}{s + \frac{1}{RC}}$$

$$v_o(t) = 7.5e^{-\frac{t}{RC}}$$

We want to evaluate t when $v_o(t) = 2.5\text{ V}$

$$2.5 = 7.5e^{-\frac{t}{RC}}$$

$$\text{Solving for t: } t = -RC \ln \left(\frac{2.5}{7.5} \right) = 1.0986RC$$

For the square wave output: $T = 2t$ and $f = 1/T$, and $f = \frac{0.455}{RC}$

For an actual circuit, the equation for f will be slightly different due to the analysis assumptions. But for low frequency square waves (less than about 1 MHz), it should be close. This also works for fixed C: R-sensor.

For the case where $C = \frac{\epsilon_o \epsilon_r A}{d} = \frac{\epsilon_o \epsilon_r A}{x(t)} \rightarrow$ plate separation C sensor,

$$f = \frac{0.455}{RC} = \frac{0.455x(t)}{R\epsilon_o \epsilon_r A} \rightarrow \text{therefore } f \propto x(t)$$