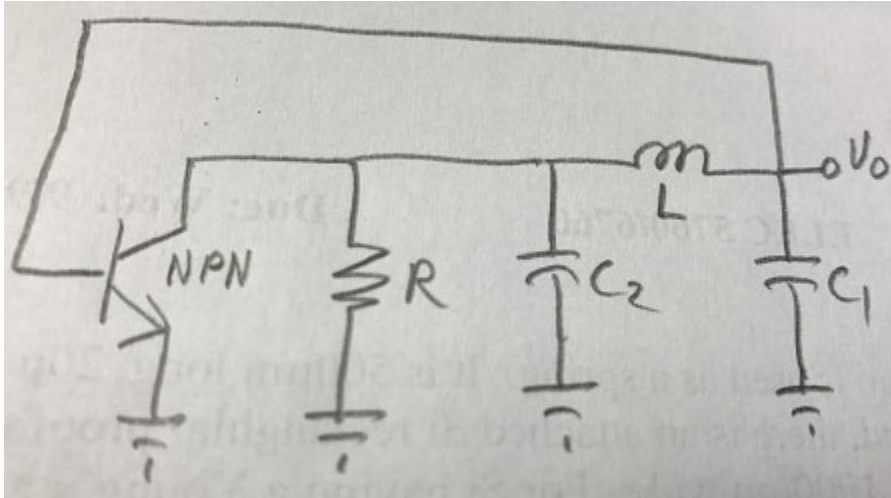


Tuesday 9/23/25


## Simplified Circuit Analysis of BJT Colpitts and Hartley Oscillators

### a. Colpitts Oscillator




Notice that the biasing resistors are not shown in this simplistic circuit.

Simplistic Small signal model:

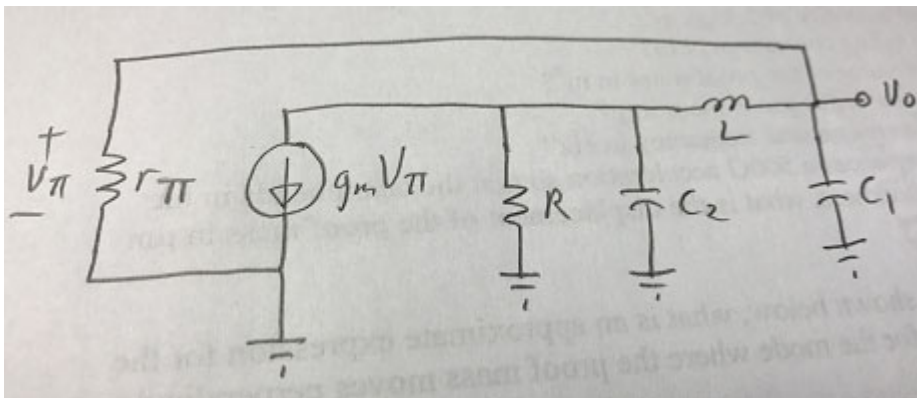

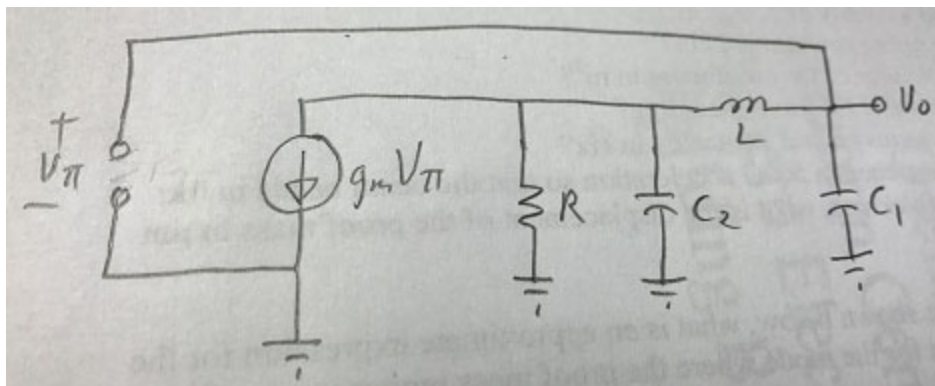
Let's further simplify by assuming that  $r_\pi$  is so large that we can approximate  $r_\pi$  as an open circuit:



Here,  $V_\pi = V_o$

To evaluate the conditions for which the circuit will oscillate, one approach is to break the circuit at the  $v_\pi$  positive terminal, and evaluate  $T(s)$  for the condition that  $T(j\omega) = 1|_{0^\circ}$ , modelled as a positive feedback oscillator.

Therefore, define the circuit as:

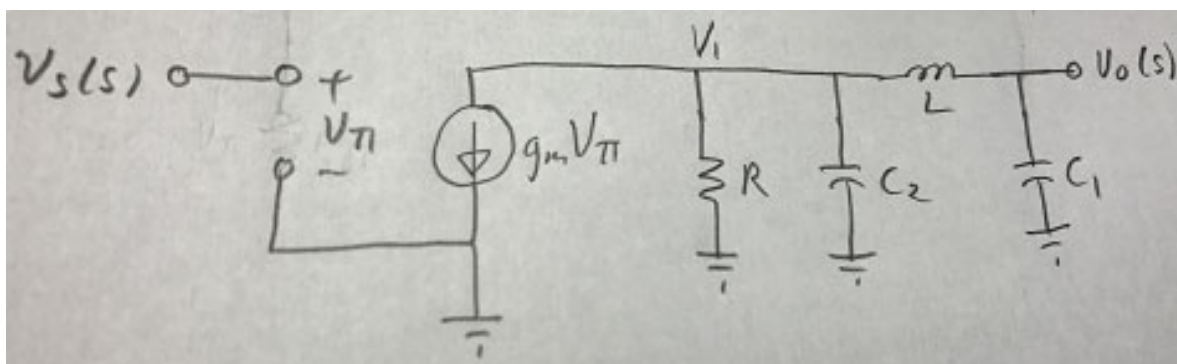

$$T(s) = \frac{V_{out}}{V_{in}}(s) = \frac{V_o}{V_s}(s)$$

$$V_o \left( sC_1 + \frac{1}{sL} \right) - V_1 \left( \frac{1}{sL} \right) = 0$$

$$V_o(s^2 LC_1 + 1) = V_1 \quad (1)$$

$$V_1 \left( \frac{1}{R} + sC_2 + \frac{1}{sL} \right) - V_o \left( \frac{1}{sL} \right) = -g_m V_\pi = -g_m V_s$$

$$V_1 \left( \frac{sL}{R} + s^2 LC_2 + 1 \right) - V_o = -g_m sL V_s \quad (2)$$

(1)→(2)

$$V_o (s^2 LC_1 + 1) \left( \frac{sL}{R} + s^2 LC_2 + 1 \right) - V_o = -g_m sL V_s$$


Then calculate  $T(s)$  and  $T(j\omega)$

For oscillation: find the constraints so that  $T(j\omega) = 1|0^\circ$ .

Obviously, there are  $s^4$  terms, making this a 4<sup>th</sup> order system.

Much arithmetic will be required to obtain  $T(j\omega) = 1|0^\circ$ .

Another approach may be simpler.

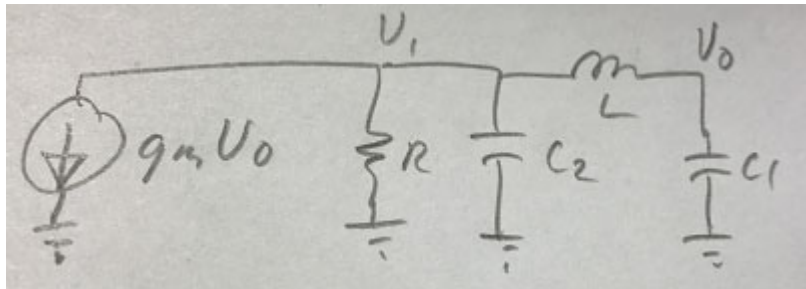

From this tank circuit configuration, we know that:  $\omega_o = \sqrt{\frac{C_1 + C_2}{LC_1 C_2}}$

For oscillation, the energy supplied by  $g_m V_o$  must be equal to or greater than the energy dissipated by R:

$$E|_{g_m V_o} \geq E|_R$$

$$V_o \left( sC_1 + \frac{1}{sL} \right) - V_1 \left( \frac{1}{sL} \right) = 0$$

$$V_o(s^2LC_1 + 1) = V_1$$

$$E|_{g_m V_o} = (-g_m V_o) V_1 t$$

$$E|_{g_m V_o} = -\frac{g_m V_1^2 t}{1 + s^2 LC_1}$$

$$E|_{g_m V_o} = -\frac{g_m V_1^2 t}{1 - \omega^2 LC_1} \rightarrow \text{evaluate at } \omega = \omega_o$$

$$E|_{g_m V_o} = -\frac{g_m V_1^2 t}{1 - \frac{C_1 + C_2}{C_2}}$$

$$E|_{g_m V_o} = -\frac{g_m V_1^2 t}{-\frac{C_1}{C_2}}$$

$$E|_{g_m V_o} = \frac{g_m V_1^2 t C_2}{C_1}$$

$$E|_R = \frac{V_1^2}{R} t$$

Therefore:

$$\frac{g_m V_1^2 t C_2}{C_1} \geq \frac{V_1^2}{R} t$$


$$\frac{g_m C_2}{C_1} \geq \frac{1}{R}$$

$$g_m R \geq \frac{C_1}{C_2}$$


This is the condition for oscillation.

This makes sense because an  $R \rightarrow \infty$   $\Omega$  is the condition here for a lossless system.

## b. Hartley Oscillator

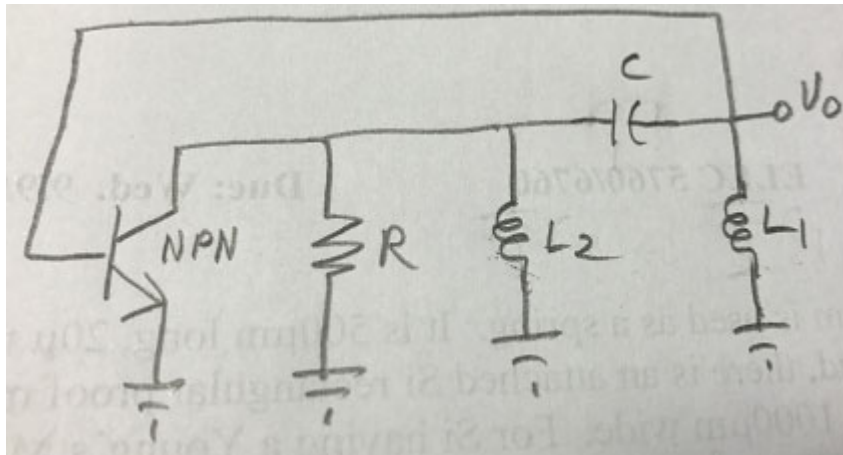

Simplified small signal model:

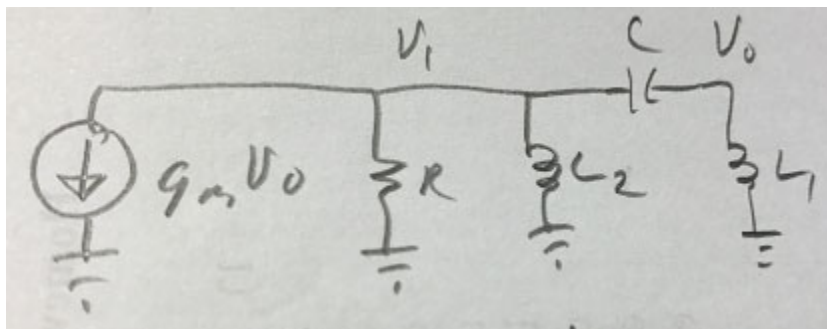

Here, the tank circuit has  $\omega_o = \frac{1}{\sqrt{C(L_1+L_2)}}$

$$V_o \left( \frac{1}{sL_1} + sC \right) - V_1(sC) = 0$$

$$V_o(1 + s^2LC_1) = V_1s^2LC_1$$

Using the energy balance relationship:

$$E|_{g_m V_o} \geq E|_R$$

$$E|_{g_m V_o} = (-g_m V_o)V_1 t$$

$$E|_{g_m V_o} = -\frac{g_m V_1^2 t s^2 C L_1}{1 + s^2 C L_1}$$

$$E|_{g_m V_o} = \frac{g_m V_1^2 t \omega^2 C L_1}{1 - \omega^2 C L_1} \rightarrow \text{evaluate at } \omega = \omega_o$$

$$E|_{g_m V_o} = \frac{(g_m V_1^2 t) \frac{L_1}{L_1 + L_2}}{1 - \frac{L_1}{L_1 + L_2}}$$

$$E|_{g_m V_o} = \frac{(g_m V_1^2 t) L_1}{L_1 + L_2 - L_1}$$

$$E|_{g_m V_o} = \frac{(g_m V_1^2 t) L_1}{L_2}$$

$$E|_R = \frac{V_1^2}{R} t$$

$$\frac{(g_m V_1^2 t) L_1}{L_2} \geq \frac{V_1^2}{R} t$$


$$\frac{g_m L_1}{L_2} \geq \frac{1}{R}$$

$$g_m R \geq \frac{L_2}{L_1}$$

This is the condition for oscillation.

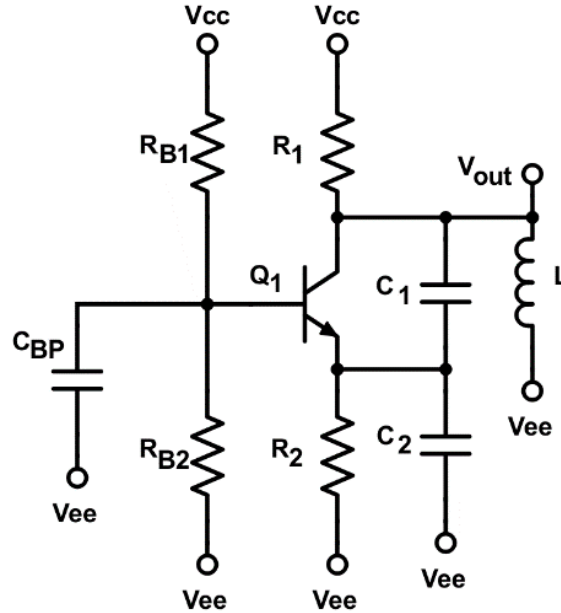c. A more thorough analysis of a BJT Colpitts oscillator

Consider the schematic diagram of this NPN BJT Colpitts oscillator:



$C_{BP}$  is a bypass capacitor (assume an open for DC analysis and a short for small signal AC analysis)

$R_{B1}$  and  $R_{B2}$  set the bias point for the transistor. First perform a DC analysis of the BJT operating mode and calculate a value for  $I_c$ . Then calculate values for  $g_m$  and  $r_\pi$ .


$$g_m = \frac{I_c}{V_t},$$

where  $V_t$  is the thermal voltage (known for the operating temperature).

$$r_\pi = \frac{\beta}{g_m}$$

where  $\beta$  is the common emitter current gain (known for the BJT).

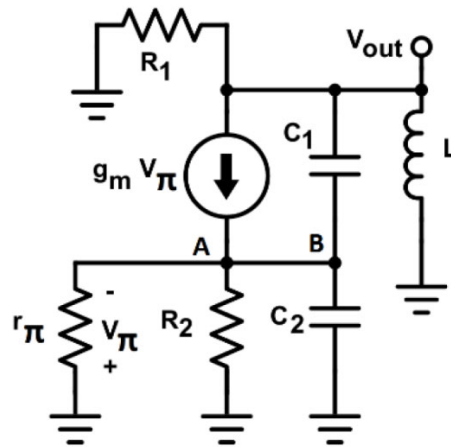Then perform a small signal analysis using hybrid-pi small signal model for the BJT.



We will break the loop between nodes A and B to calculate the loop gain, AB. The BSC is satisfied when:

$$A \cdot B = 1 \angle 0^\circ ,$$

and the circuit will have negative damping when:


$$|A \cdot B| > 1 .$$

After breaking the loop, node A will be the input and node B will be the output. Node B will need to include the impedance looking into Node A, and we will call this impedance  $R_A$ , where  $R_A$  is calculated to be:

$$R_A = \frac{1}{\frac{1}{r_\pi} + \frac{1}{R_2} + g_m} .$$



Therefore, the circuit model becomes:

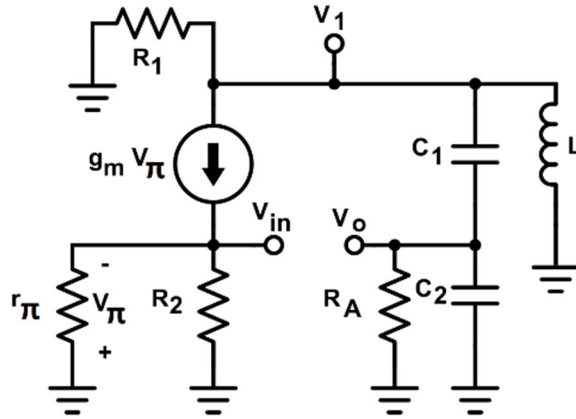

The three voltage nodes,  $V_{in}$ ,  $V_o$ , and  $V_1$ , are used to calculate the loop gain,  $AB$ .  $A$  is therefore defined as:

$$A = \frac{V_1}{V_{in}} = \frac{g_m}{\frac{1}{R_1} + \frac{1}{4R_A}} .$$

In order to define  $B$ , the two capacitors,  $C_1$  and  $C_2$ , with  $C_1$  equal to  $C_2$ , are assumed to approximately act as a voltage divider between the voltage nodes  $V_1$  and  $V_o$  at the tank circuit's natural frequency, yielding an equation for  $B$  of:

$$B = \frac{V_o}{V_1} = \frac{C_1}{C_1 + C_2} = \frac{1}{2} .$$


Combining the equations for  $A$ ,  $B$  and  $R_A$  results in:

$$AB = \frac{g_m R_1}{2 \left[ 1 + \frac{R_1}{4} \left( \frac{1}{r_{\pi}} + \frac{1}{R_2} + g_m \right) \right]} .$$

As long as  $AB > 1$ , oscillations will grow in amplitude.

## Other Transistor Oscillators


### a. Phase Shift Oscillator

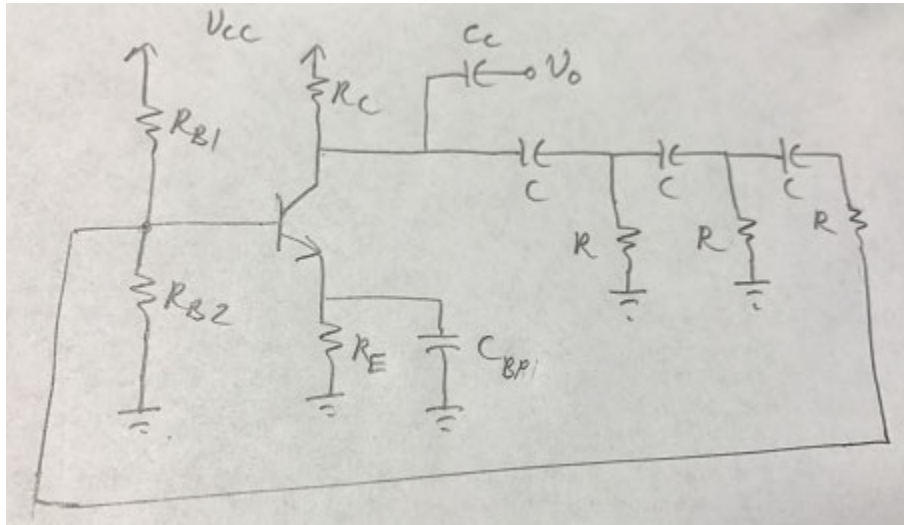

This circuit uses a common emitter (large negative gain) amplifier. The oscillator uses negative feedback to satisfy the BSC:  $1|_{-180^\circ}$ .


$C_{BP}$  is a large capacitance bypass capacitor.  $C_C$  is a large capacitance coupling capacitor.  $R_{B1}$ ,  $R_{B2}$ ,  $R_C$  and  $R_E$  bias the transistor and determine the amplifier's gain.

### b. Wien Bridge Oscillator

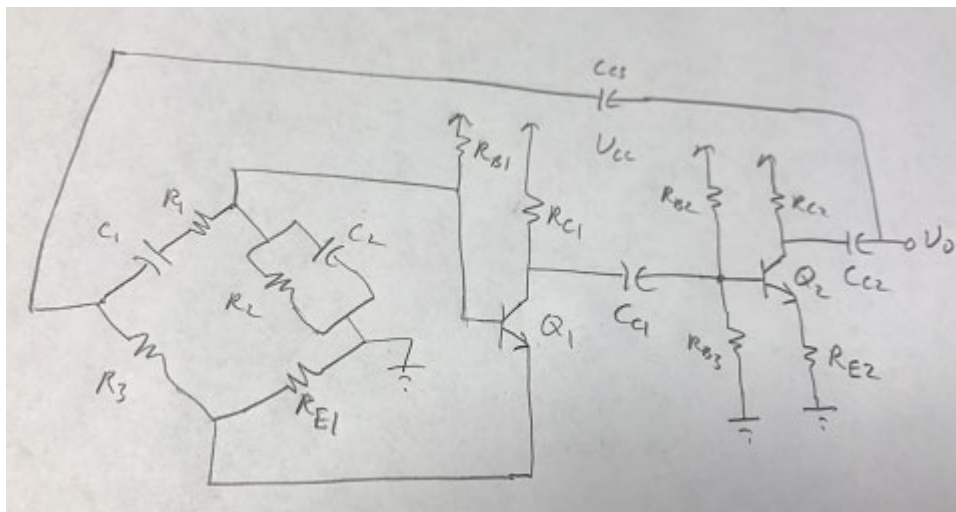


This circuit uses a two stage amplifier (two negative gain common emitter amplifiers) to achieve a positive gain for the Wein bridge oscillator.

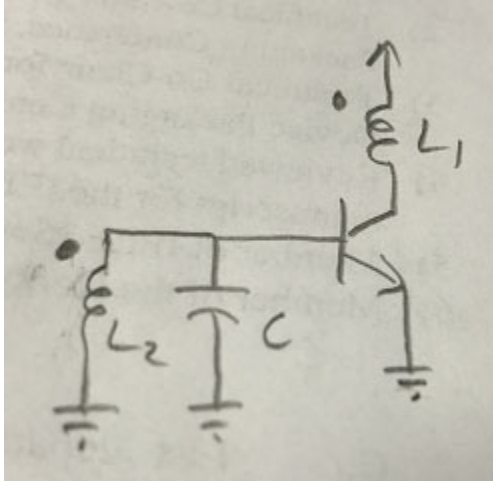c. Armstrong (1912 – U.S) or Meissner (1913 - Austria) Oscillator



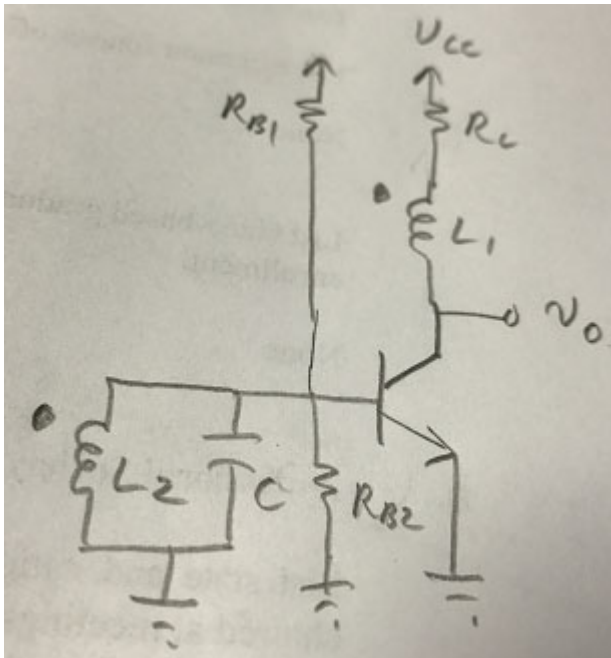Without biasing resistors shown. The transformer provides feedback from the output of the common emitter amplifier back around to the base. A transformer can easily provide a  $180^\circ$  phase shift. Transformer's inductance with  $C$  determines the oscillation frequency.



Same oscillator with possible biasing resistors shown.