

- 1) A MEMS device consists of a proof mass attached to a frame with a suspension system. The bottom of the proof mass is 1 mm by 1 mm in size and serves as an electrode. Another electrode of the same size is located 2 μm beneath it. If the proof mass can move up and down $\pm 1 \mu\text{m}$ from its nominal distance to the bottom electrodes, calculate the nominal, maximum and minimum capacitance between the two electrodes. Assume that the device is in a vacuum.
- 2) A certain MEMS capacitance has a rest (i.e. nominal) value of 3 pF, a minimum value of 2 pF and a maximum value of 5 pF. Place it in a charge amplifier circuit that has an input voltage of 10 V and a feedback capacitor (C_2) of 10 pF. Calculate the amplifier output voltage (at the end of the ϕ_2 cycle) for the nominal, minimum and maximum capacitance values.
- 3) For the MEMS capacitance in (2) place it in a 5 V CMOS relaxation oscillator circuit with both resistors being 100 k Ω . What is the output frequency for C_{\min} , C_{nom} and C_{\max} ?
- 4) If two MEMS capacitances from (2) are placed in a capacitive AC voltage divider to realize a differential capacitive sensor configuration, with the input voltage having an amplitude of 10 V, what is the output voltage amplitude for each case?
- 5) If the MEMS capacitance from (2) is placed in a switched-capacitor circuit that is switched at 250 kHz, what is the value of the equivalent resistance for the nominal, minimum and maximum capacitance values?
- 6) If the MEMS device in (2) is placed in an RC phase delay circuit, where $R = 250 \text{ k}\Omega$, what is the phase delay in μs for the nominal, minimum and maximum capacitance values?
- 7) Your resistive sensor measures a conductance of 100 μS in an aqueous solution at 10 $^\circ\text{C}$. If your sensor's cell constant is 10 m, what the EC at 25 $^\circ\text{C}$, using a temperature compensation factor of 0.02 / $^\circ\text{C}$?