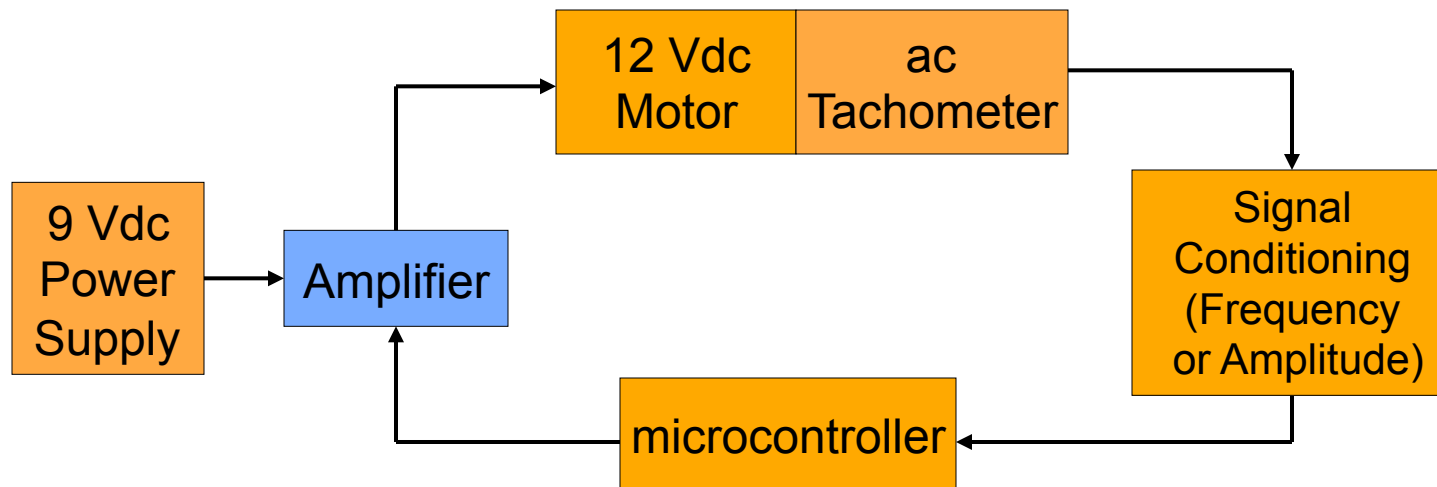

Lab 8. Speed Control of a Dc motor

The Motor Drive

Motor Speed Control Project

1. Generate PWM waveform
2. **Amplify** the waveform to drive the motor
3. Measure tachometer signal (motor speed)
4. Find parameters of a motor model
5. Control motor speed with a computer algorithm



Buehler 12 volt permanent-magnet dc motor with tachometer output

Electrical Connections


yellow/green -- tachometer
output

blue/red -- motor winding

*Note: Tachometer wires may not
have two colors on some units.*




Exploded view

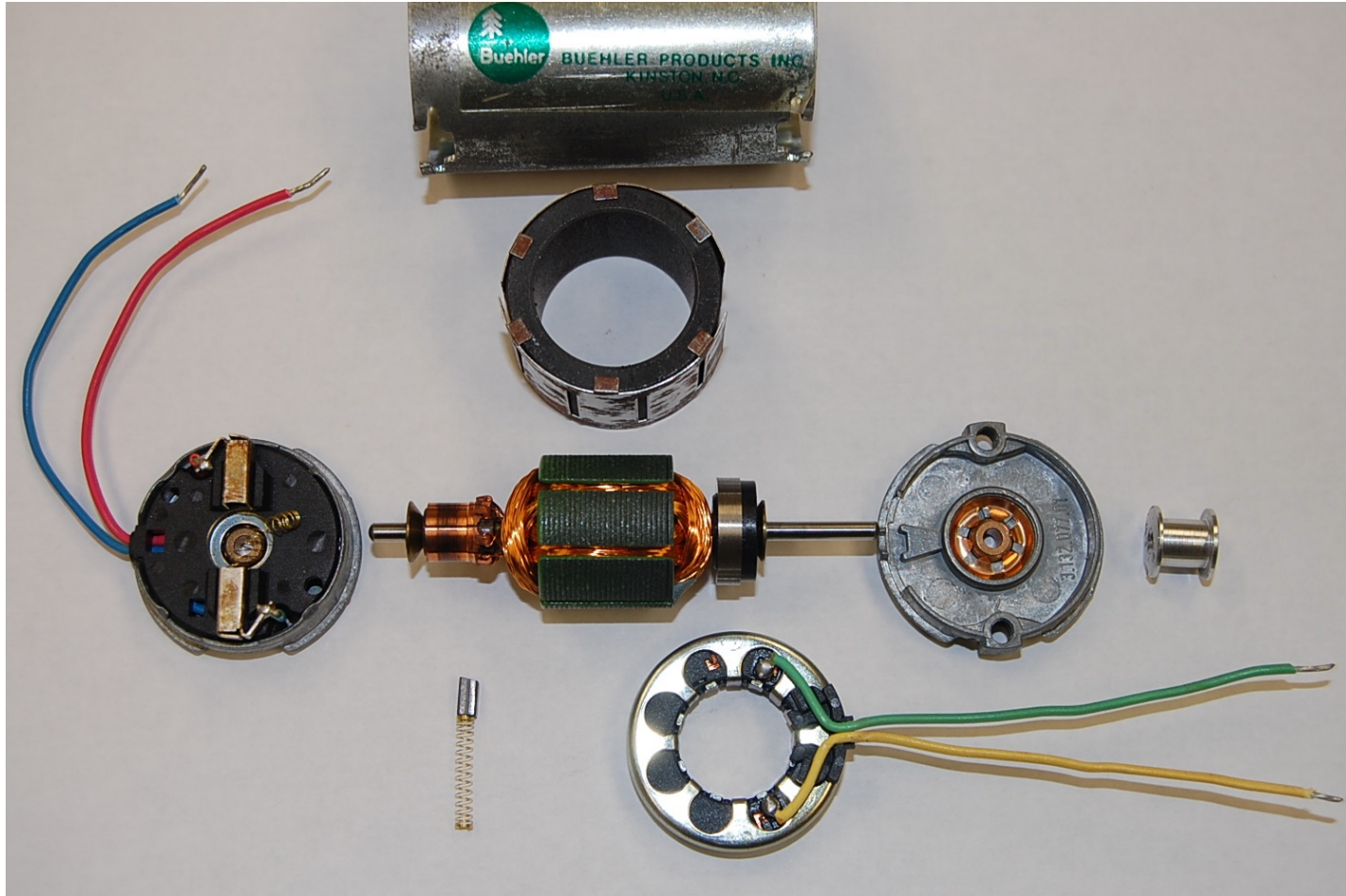


Some questions

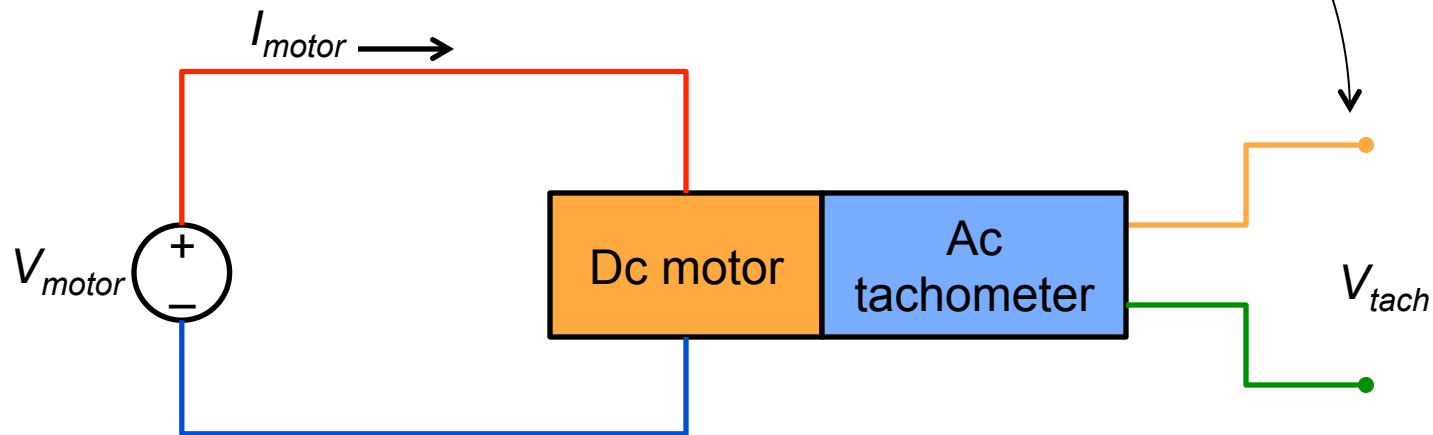- Required power? $P = V_{motor} \times I_{motor}$
- Ac tachometer signal behavior?




Set up an experiment

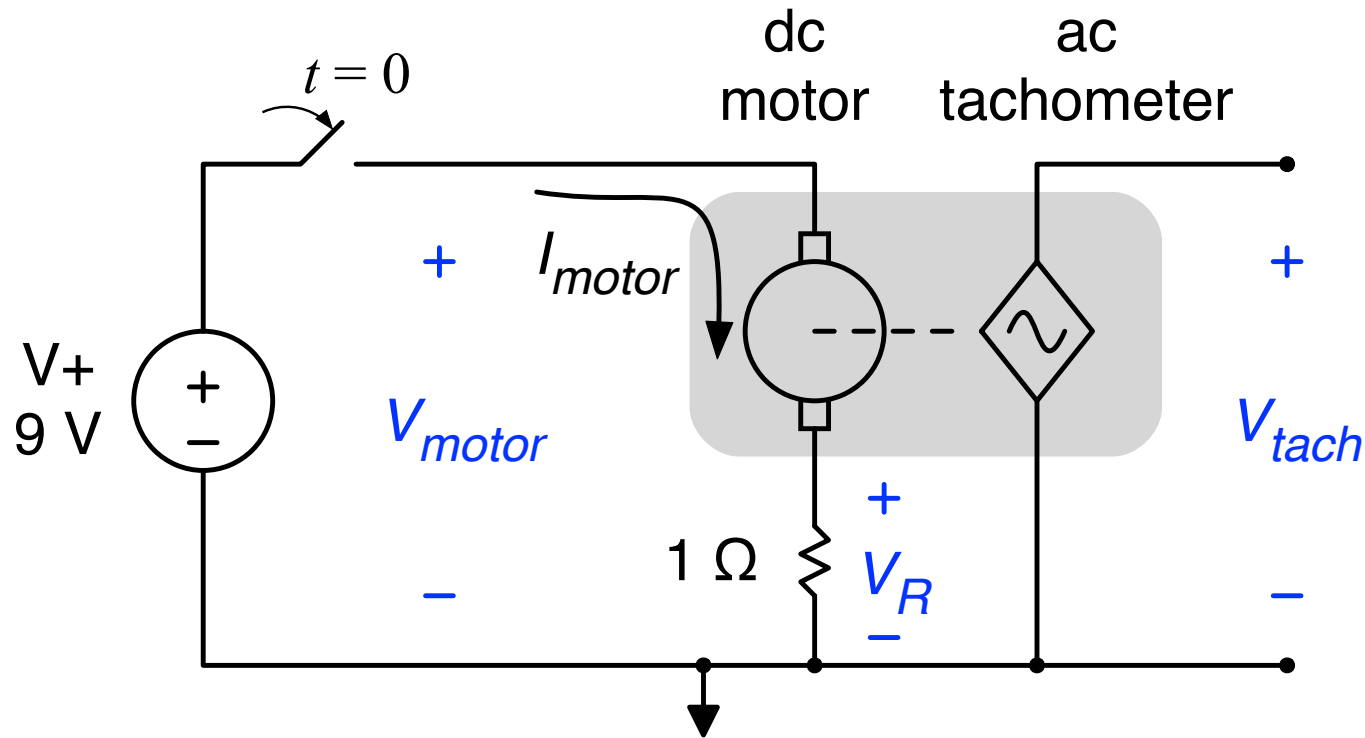

- Measure V_{motor} , V_R , and V_{tach}
- $I_{motor} = V_R$ (because $R = 1 \Omega$)

Experimental results

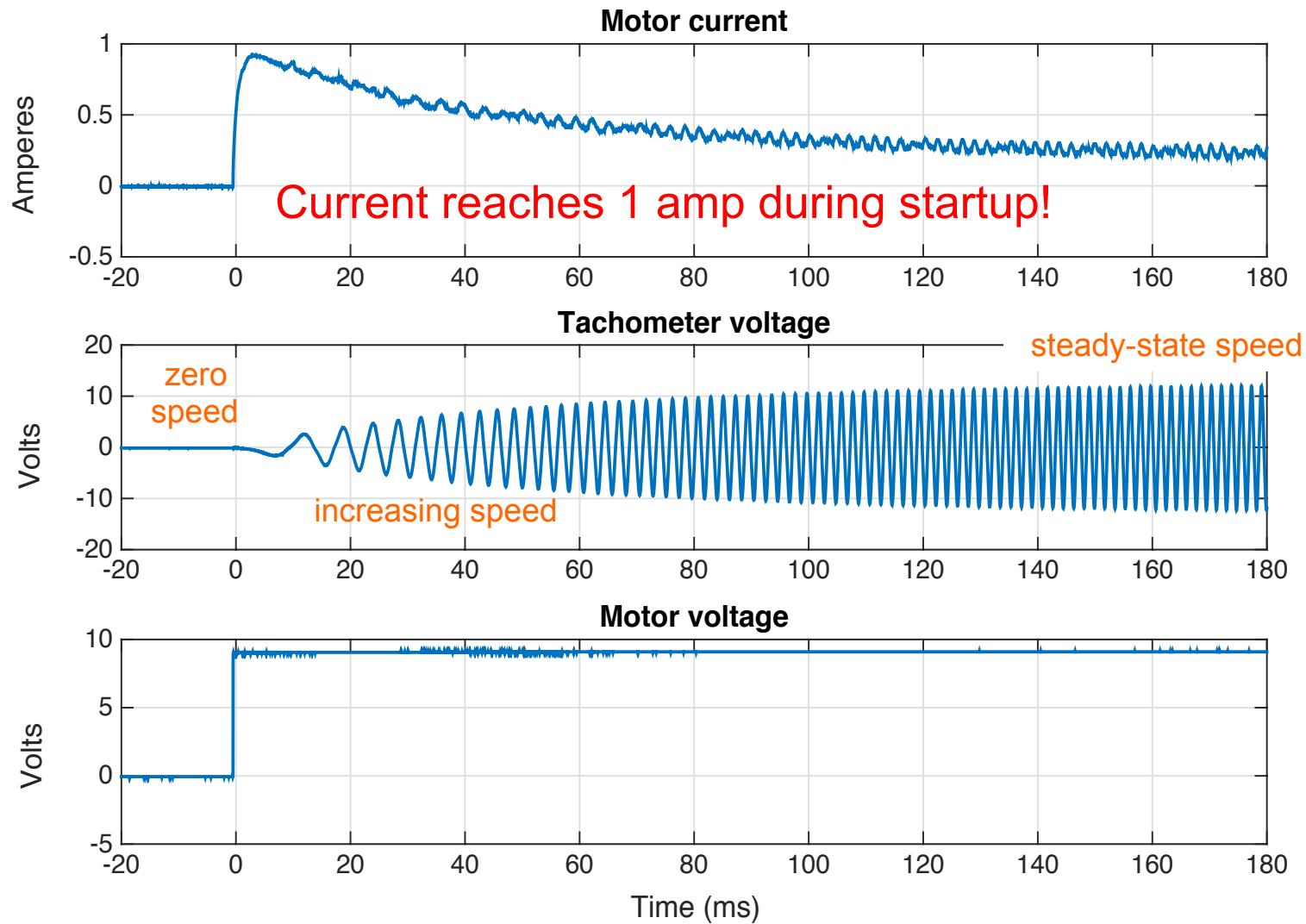


Some observations

- V_{tach} amplitude grows with motor speed
- V_{tach} frequency also grows with speed
- Initial current I_{motor} peaks around 1 A
- Steady state I_{motor} is approx. 250 mA

Why does the process behave this way?

Some analytical modeling...

Motor electro-mechanical models

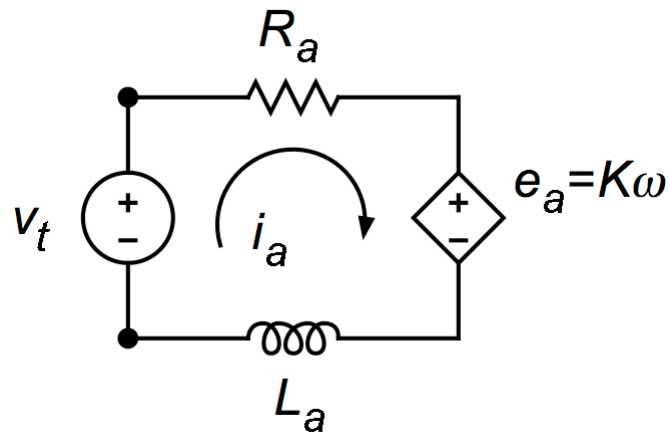


R_a – armature winding resistance

L_a – armature winding inductance

i_a – armature current

V_t – motor terminal voltage

e_a – back emf

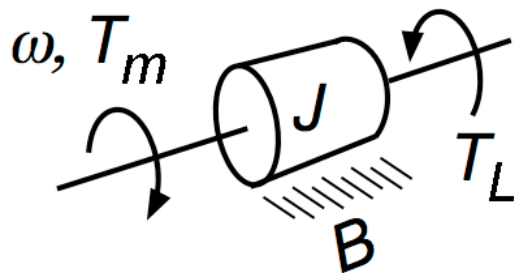

T_m – developed torque


T_L – torque needed for load

ω – rotational speed

B – friction coefficient

J – moment of inertia

Motor electrical dynamics

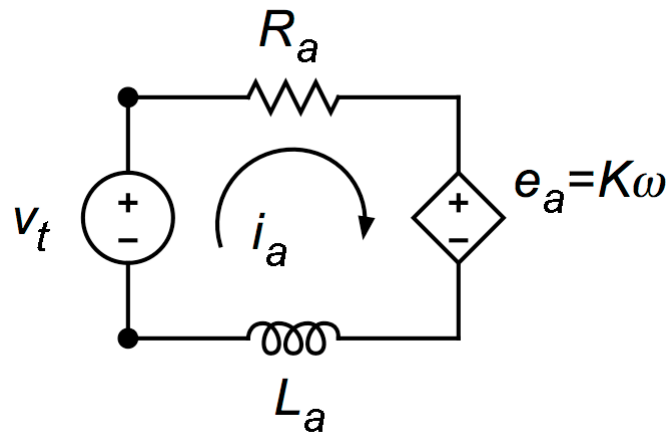


$$v_t = R_a \cdot i_a + L \frac{di_a}{dt} + e_a$$

$$e_a = K\omega_m$$

e_a = “back emf” (electromotive force)
generated within armature windings


Note: Emf $e_a = 0$ at standstill, and increases linearly with motor speed. Current i_a is high at low speed.

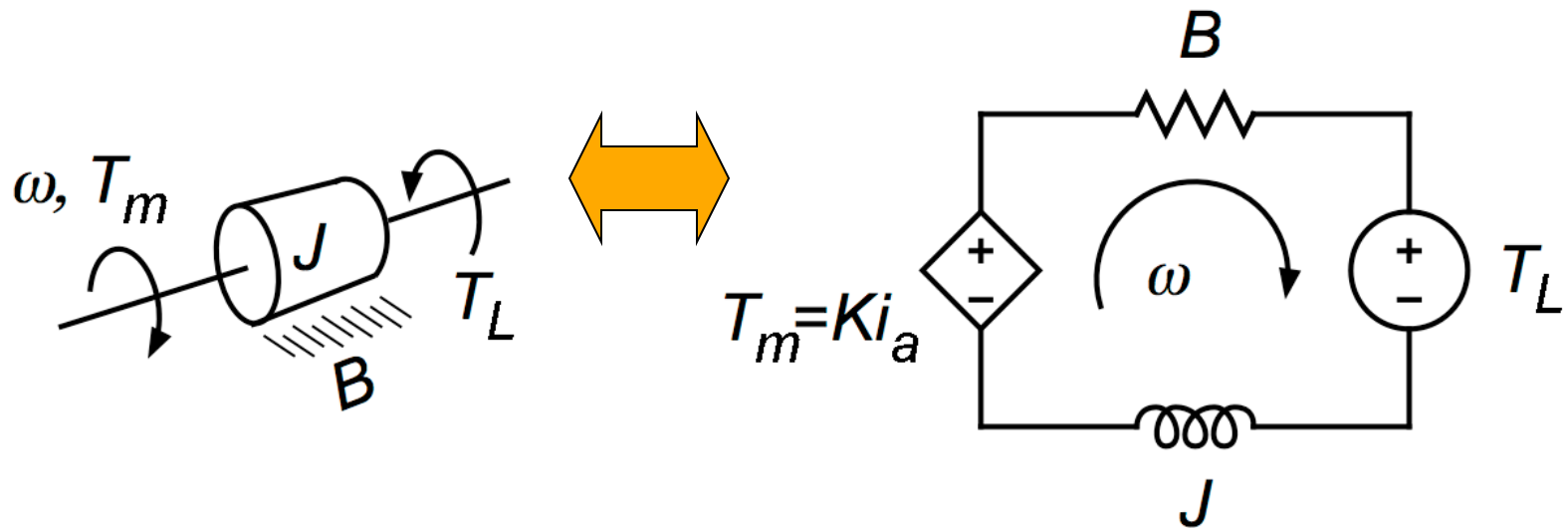Mechanical dynamics analogous to electrical circuits!



Equations for these systems
have similar form.

Motor mechanical dynamics

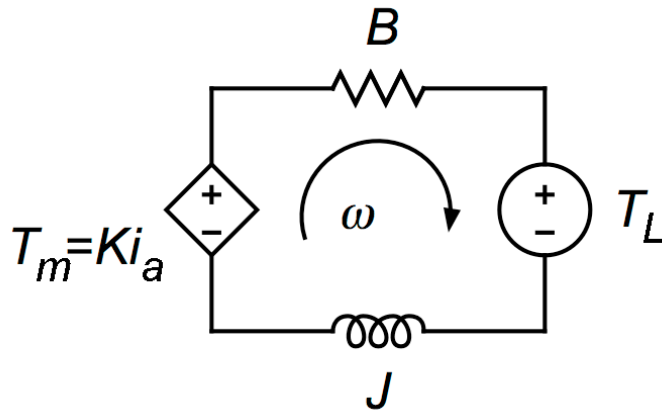

$$T_m = J \cdot \frac{d\omega}{dt} + B \cdot \omega + T_L$$

$$T_m = K \cdot i_a$$

T_m = developed torque increases with current

J = motor moment of inertia

B = motor friction coefficient

ω = angular velocity of the motor

T_L = torque required to drive the load

Laplace transformed equations

- Electrical

$$V_t(s) = R_a \cdot I_a(s) + L_a \cdot sI_a(s) + K \cdot \Omega(s)$$

- Mechanical

$$K \cdot I_a(s) = J \cdot s\Omega(s) + B \cdot \Omega(s) + T_L(s)$$

Steady state analysis ($s=0$)

- Electrical steady state

$$V_t = R_a \cdot I_a + K \cdot \Omega$$

- Mechanical steady state

$$K \cdot I_a = B \cdot \Omega + T_L$$


- Solve for speed

$$\Omega = -\frac{R_a}{R_a B_m + K^2} \cdot T_L + \frac{K}{R_a B_m + K^2} \cdot V_t$$

Motor speed vs. load torque

- Speed is related to load torque and terminal voltage
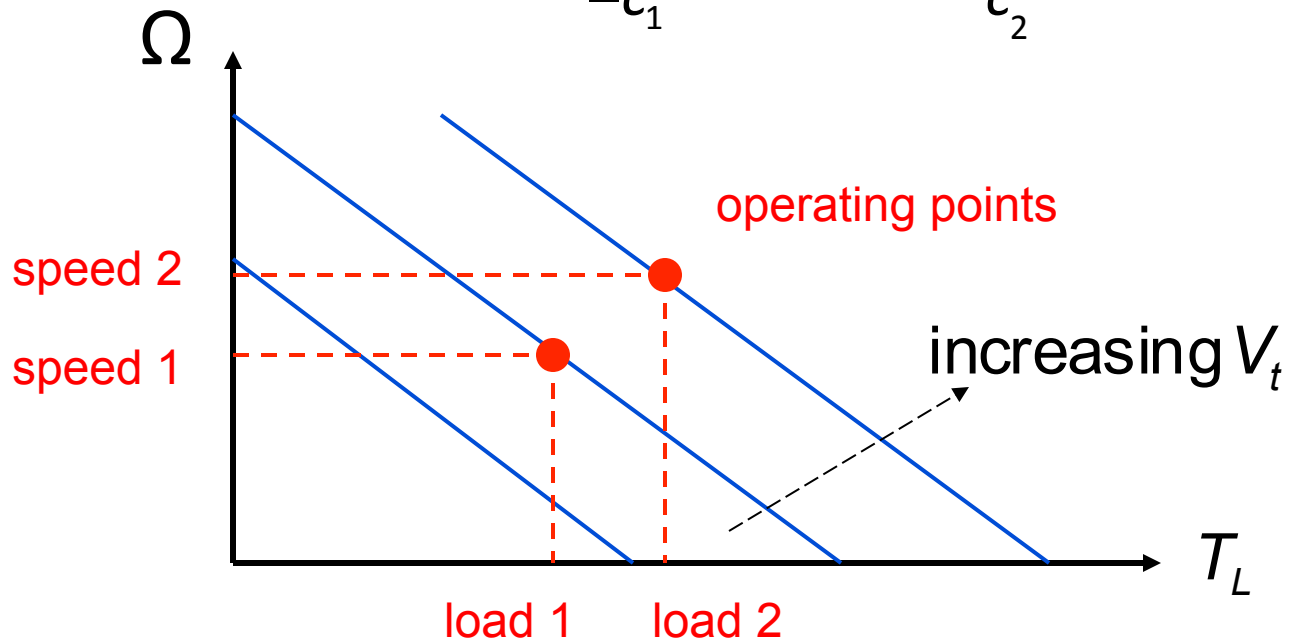
$$\Omega = -\underbrace{\frac{R_a}{R_a B_m + K^2}}_{-C_1} \cdot T_L + \underbrace{\frac{K}{R_a B_m + K^2}}_{C_2} \cdot V_t$$



What we now know:

- For a given load, motor speed is proportional to voltage applied to its terminals
- Use of a PWM signal allows the **average** voltage of the signal to be varied by varying duty cycle




$$V_{avg} = V_{digital} \left(\frac{T1}{T1 + T2} \right)$$

T1 = "ON" time
T2 = "OFF" time

- We have a 12 Vdc motor (max. terminal voltage is 12 Vdc)
 - A 3 volt signal will be insufficient to produce full speed, PLUS ...
 - Motor may draw 1 **A** of current, whereas microcontroller output pins can typically supply only **milliamperes**

Idea: Use a single transistor switch to
amplify the digital PWM signal
to drive the motor

Basic transistor switch

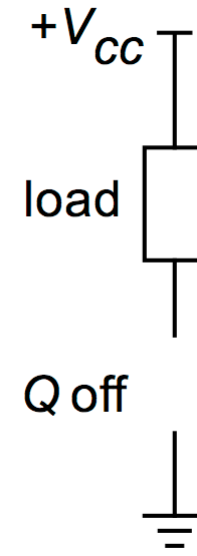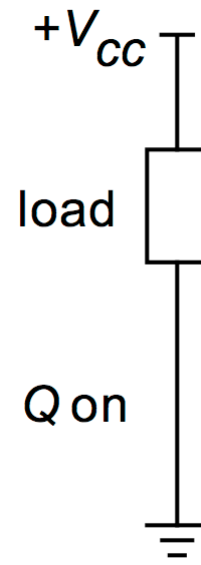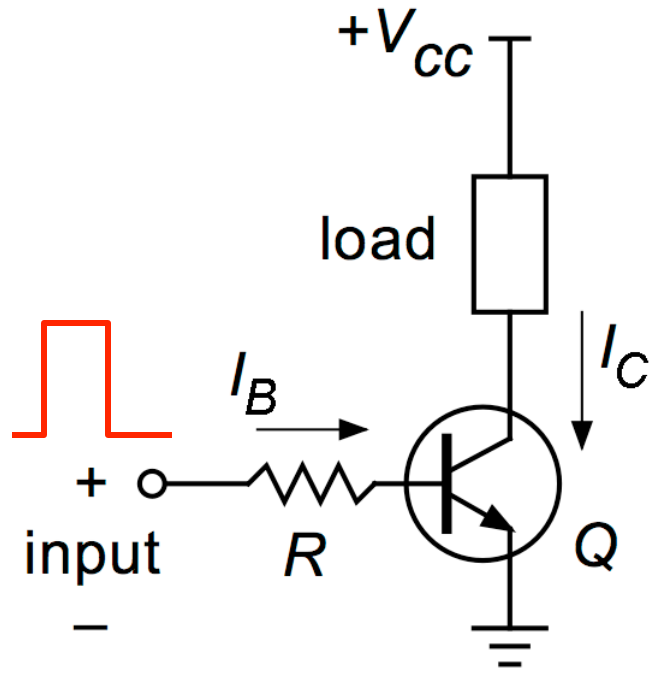


(ideal models)

Switching an inductive load (motor winding)

- Inductor voltage-current law:

$$V_L(t) = L \frac{di_C}{dt}$$

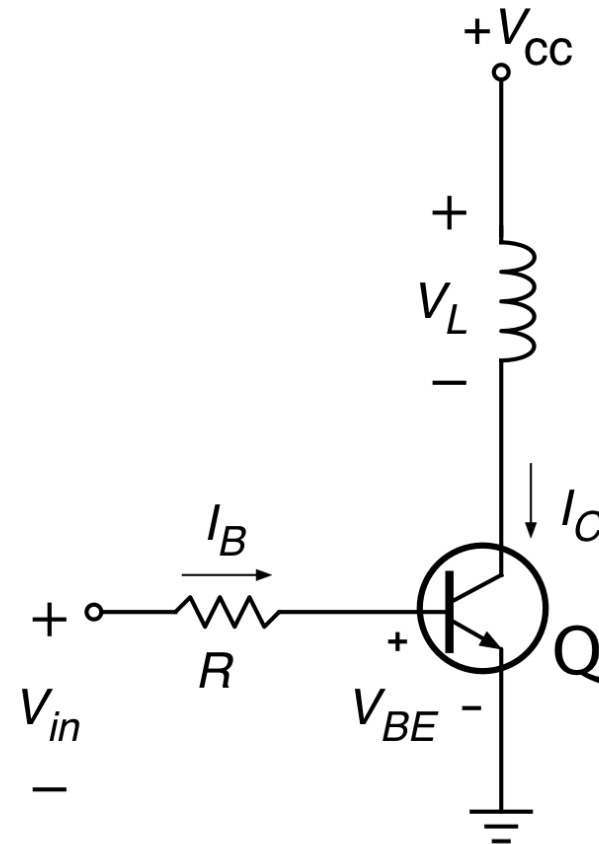
- As current i_C is switching off,
 - di_C/dt is large and negative
 - Inductor voltage V_L is large and negative
 - Collector voltage $> V_{CC}$
- **Q may be destroyed!**




Switching an inductive load (need to protect switch Q)

- Use anti-parallel diode **D!!!**

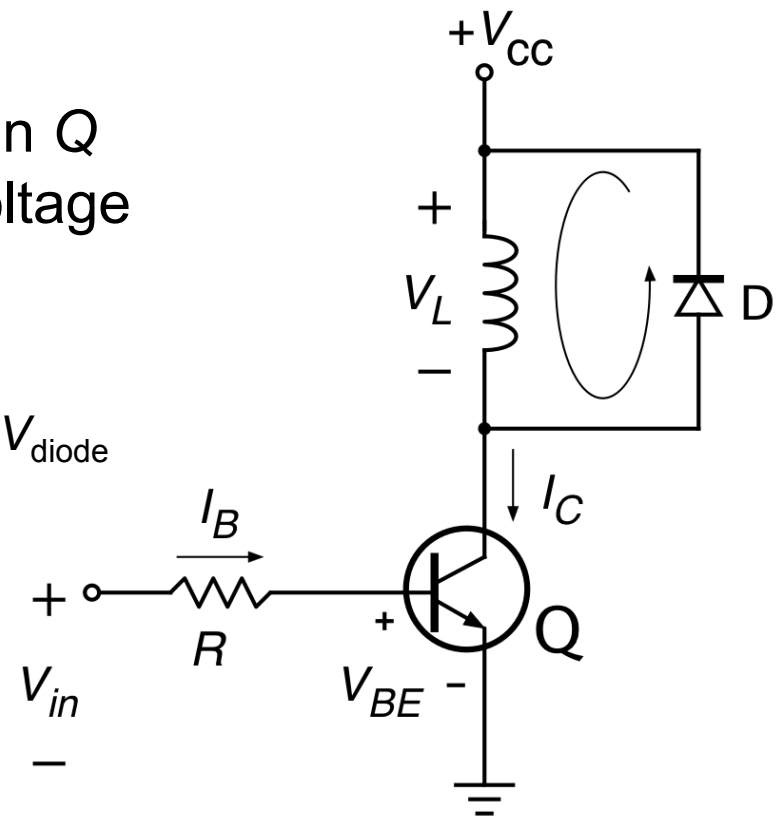- reverse biased when Q is ON
- gives alternate current path when Q switches OFF (when inductor voltage becomes negative)
- protects Q
 - Collector voltage is clamped to $V_{cc} + V_{diode}$
- a.k.a. *freewheeling* diode



Drive design practical model

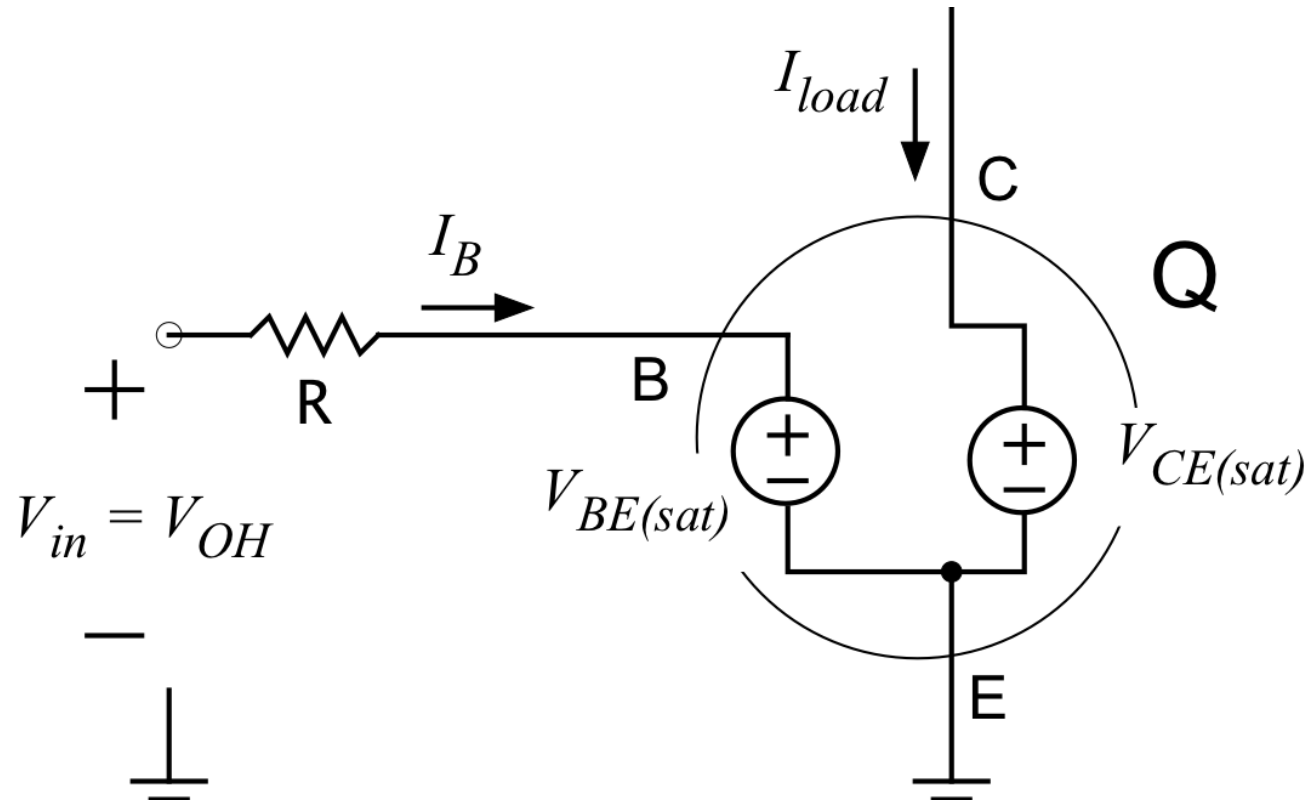

Drive design considerations

- Maximum load current, I_{LOAD}
 - Transistor characteristics
 - current gain, h_{FE}
 - voltage $V_{BE(sat)}$ in saturation mode
 - Microcontroller limitations
 - digital pin output voltage (high), V_{OH}
 - digital pin output current, $I_{IO} \approx 20 \text{ mA (max)}$
-

Design equations

- Constraints for base current in the ON state

$$I_{IO} > I_B \gg \frac{I_{LOAD}}{h_{FE}}$$


- Calculate base series resistance, R

$$R = \frac{V_{OH} - V_{BE(sat)}}{I_B}$$

EE Board variable power supply


Positive Supply
VP+ output voltage & current limit

VP+ ON

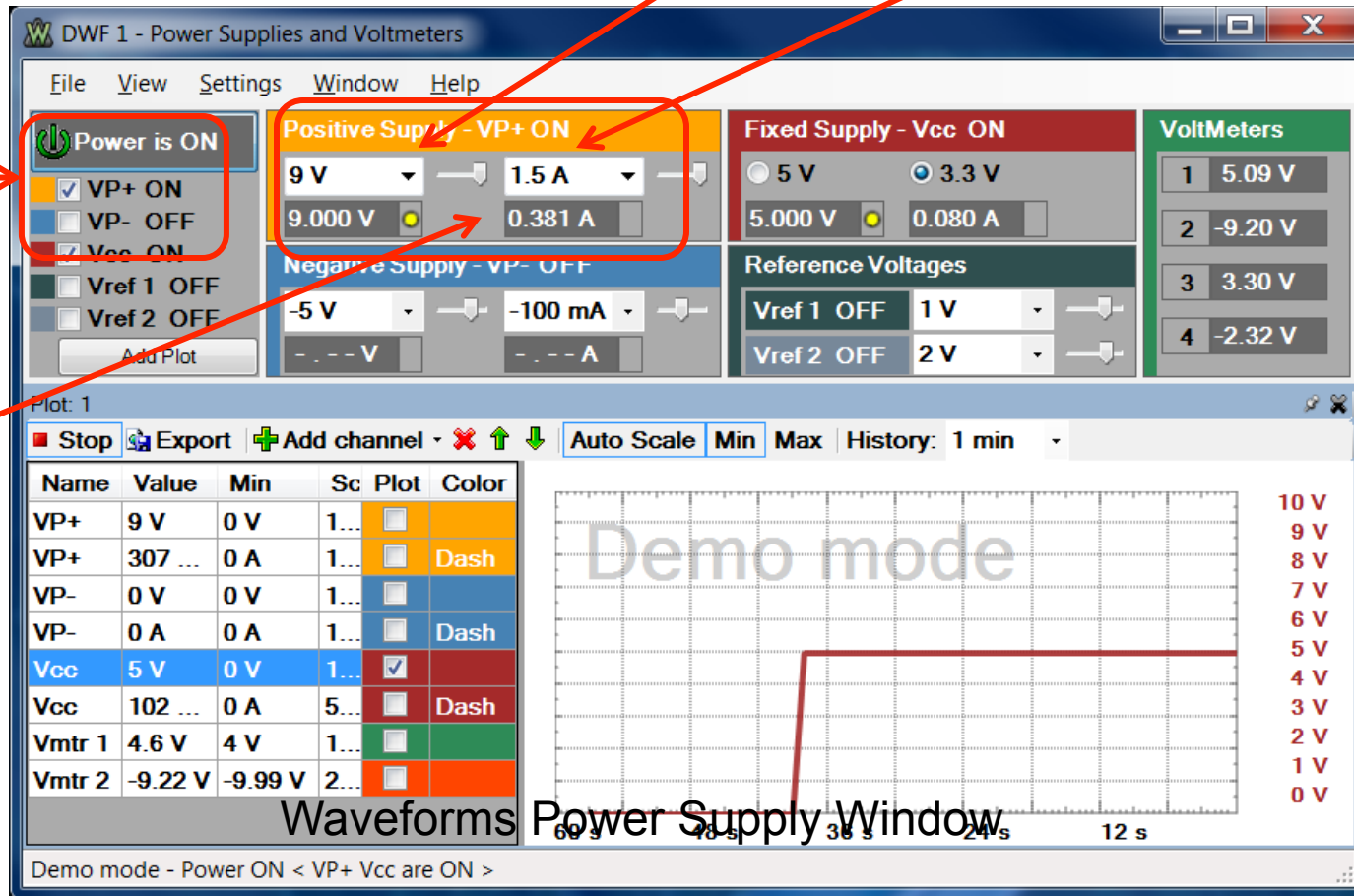

Actual
VP+
Current

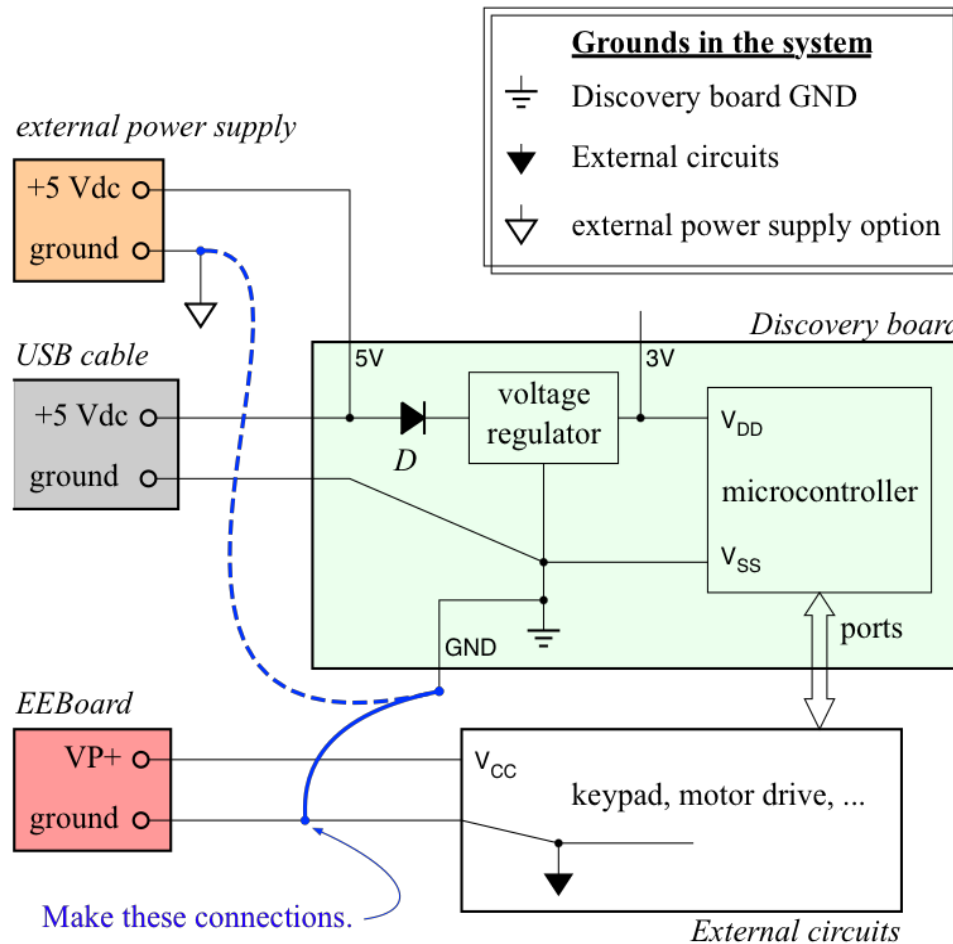Connect grounds of multiple power supplies



Lab procedure

- Verify proper PWM signal generation
 - Study amplifier behavior
 - Measure V_{in} , V_{BE} , V_{CE}
 - Compare to theoretical assumptions
 - Study motor behavior
 - Measure tachometer output (yellow/green leads)
 - Plot motor speed vs. PWM signal duty cycle
 - Repeat for several PWM signal frequencies
 - Analyze data and discuss results
-

Choice of devices

- Transistor (Q)
 - 2N3904 is cheap but under-rated for current
 - 2N2222 has higher current rating
 - Both may be destroyed if motor is stalled
 - Diode (D)
 - 1N4001 is a rectifier diode: a bit slow, has large diameter leads
 - 1N4148 (or 1N914) is a switching diode: faster, but has low current rating (but is not expensive)
-

2N2222 NPN transistor data

Source: Fairchild Semiconductor

Absolute Maximum Ratings

Symbol	Parameter	Value	Unit
V_{CEO}	Collector-emitter voltage (base open)	40	V
V_{CBO}	Collector-base voltage (emitter open)	75	V
V_{EBO}	Emitter-base voltage (collector open)	6	V
I_C	Collector current	1	A

Electrical Characteristics

Symbol	Parameter	Conditions	min	max	Unit
h_{FE}	Dc current gain	$I_C = 150 \text{ mA}, V_{CE} = 1 \text{ V}$	50		
$V_{CE(sat)}$	Collector-emitter saturation voltage	$I_C = 150 \text{ mA}, I_B = 15 \text{ mA}$		0.3	V
$V_{BE(sat)}$	Base-emitter saturation voltage	$I_C = 150 \text{ mA}, I_B = 15 \text{ mA}$	0.6	1.2	V

2N3904 NPN transistor data

Source: Fairchild Semiconductor

Absolute Maximum Ratings

Symbol	Parameter	Value	Unit
V_{CEO}	Collector-emitter voltage (base open)	40	V
V_{CBO}	Collector-base voltage (emitter open)	60	V
V_{EBO}	Emitter-base voltage (collector open)	6	V
I_C	Collector current	200	mA

Electrical Characteristics

Symbol	Parameter	Conditions	min	max	Unit
h_{FE}	Dc current gain	$I_C = 100 \text{ mA}, V_{CE} = 1 \text{ V}$	30		
$V_{CE(sat)}$	Collector-emitter saturation voltage	$I_C = 50 \text{ mA}, I_B = 5 \text{ mA}$		0.3	V
$V_{BE(sat)}$	Base-emitter saturation voltage	$I_C = 150 \text{ mA}, I_B = 5 \text{ mA}$		0.95	V

1N4148 switching diode data

Source: Fairchild Semiconductor

Absolute Maximum Ratings

Symbol	Parameter	Value	Unit
V_{RRM}	Maximum repetitive reverse voltage	100	V
I_O	Average rectified forward current	200	mA
I_F	Dc forward current	300	mA
I_C	Collector current	200	mA

Electrical Characteristics

Symbol	Parameter	Conditions	min	max	Unit
V_F	Forward voltage	$I_F = 100 \text{ mA}$		1	V
I_R	Reverse leakage	$V_R = 20 \text{ V}$		0.025	μA
t_{rr}	Reverse recovery time	$I_F = 10 \text{ mA}$, $V_R = 6 \text{ V}$, $I_{rr} = 1 \text{ mA}$, $R_L = 100 \text{ ohm}$		4	ns