


Programmable Logic Devices

Roth Text: Chapter 3 (sections 3.1-3.3)

Nelson Text: Chapter 5 (combinational)

Chapter 11 (sequential)

Programmable logic taxonomy

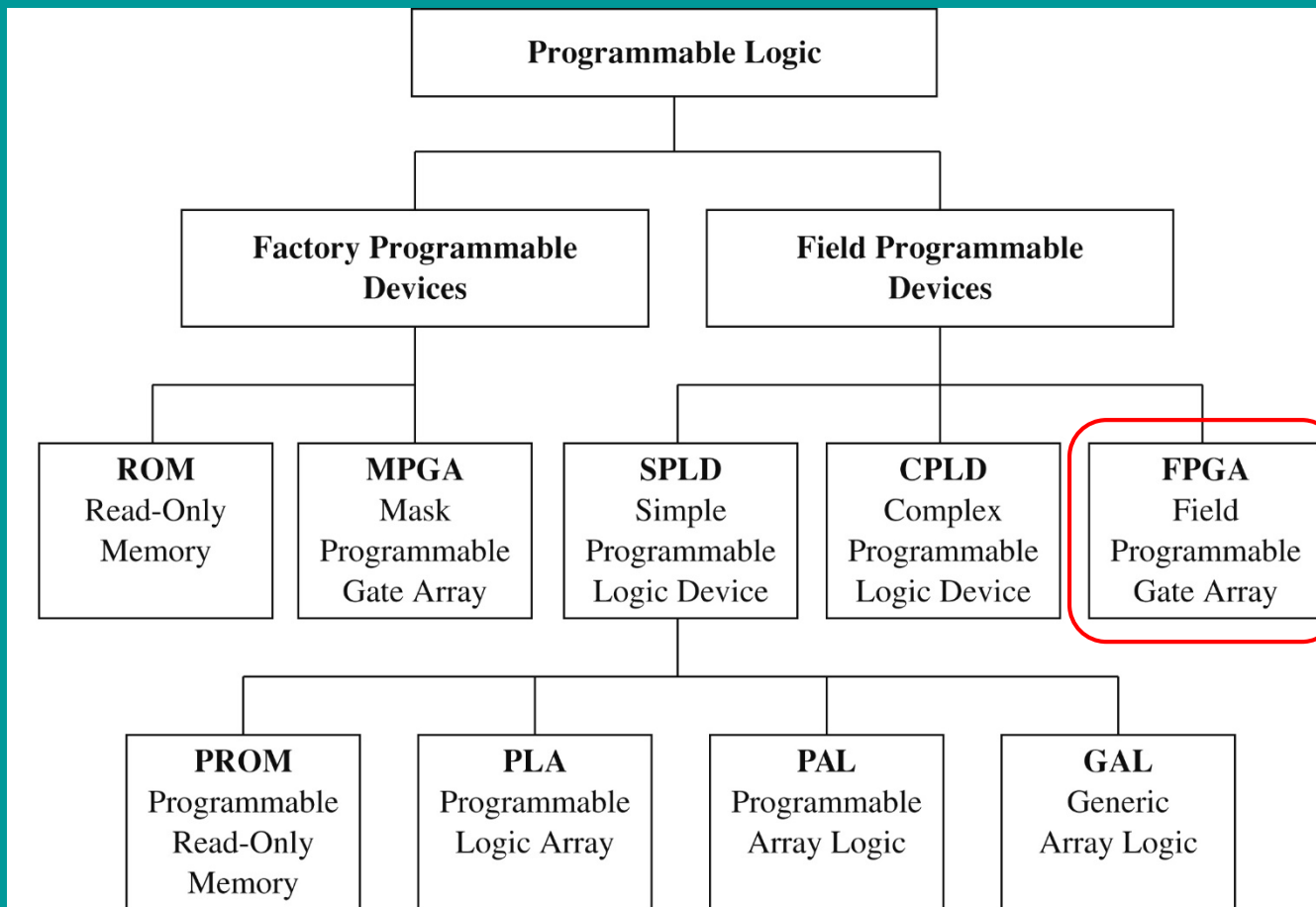

Lab
Device

**TABLE 3-1:
A Comparison of
Programmable
Devices**

| | SPLD | CPLD | FPGA |
|--------------------------------|--|---|--|
| Density | Low Few hundred gates | Low to Medium 500 to 12,000 gates | Medium to High 3,000 to 5,000,000 gates |
| Timing | Predictable | Predictable | Unpredictable |
| Cost | Low | Low to Medium | Medium to High |
| Major Vendors | Lattice Semiconductor Cypress AMD | Xilinx Altera | Xilinx Altera Lattice Semiconductor Actel |
| Example Device Families | Lattice Semiconductor GAL16LV8 GAL22V10 Cypress PALCE16V8 AMD 22V10 | Xilinx CoolRunner XC9500 Altera MAX | Xilinx Virtex Spartan Altera Stratix Lattice Mach ECP Actel Accelerator |

History of Programmable Logic

- Programmable Logic Arrays ~ 1970
 - Incorporated in VLSI devices
 - Can implement any set of SOP logic equations
 - Outputs can share common product terms
- Programmable Logic Devices ~ 1980
 - MMI Programmable Array Logic (PAL)
 - 16L8 – combinational logic only
 - 8 outputs with 7 programmable PTs of 16 input variables
 - 16R8 – sequential logic only
 - 8 registered outputs with 8 programmable PTs of 16 input variables
 - Lattice 16V8
 - 8 outputs with 8 programmable PTs of 16 input variables
 - Each output programmable to use or bypass flip-flop
 - Complex PLDs – arrays of PLDs with routing network
- Field Programmable Gate Arrays ~ 1985
 - Xilinx Logic Cell Array (LCA)
- CPLD & FPGA architectures became similar ~ 2000
 - Incorporation of RAMs and other specialized cores
 - Programmable system-on-chips

Programming Technologies


- PLAs were mask programmable
- PALs used fuses for programming
- Early PLDs & CPLDs used floating gate technology
 - Erasable Programmable Read Only Memory (EPROM)
 - Ultra-violet erasable (UVEPROM)
 - Electrically erasable (EEPROM)
 - Flash memory came later and was used for CPLDs
- FPGAs used RAM for programming
- Later trends
 - Fuses were replaced with anti-fuses
 - Better reliability
 - Large CPLDs went to RAM-based programming

Programming Technologies

- PLAs were mask programmable
- PALs used fuses for programming
- Early PLDs & CPLDs used floating gate technology
 - Erasable Programmable Read Only Memory (EPROM)
 - Ultra-violet erasable (UVEPROM)
 - Electrically erasable (EEPROM)
 - Flash memory came later and was used for CPLDs
- FPGAs used RAM for programming
- Later trends
 - Fuses were replaced with anti-fuses
 - Better reliability
 - Large CPLDs went to RAM-based programming

Programming Technologies

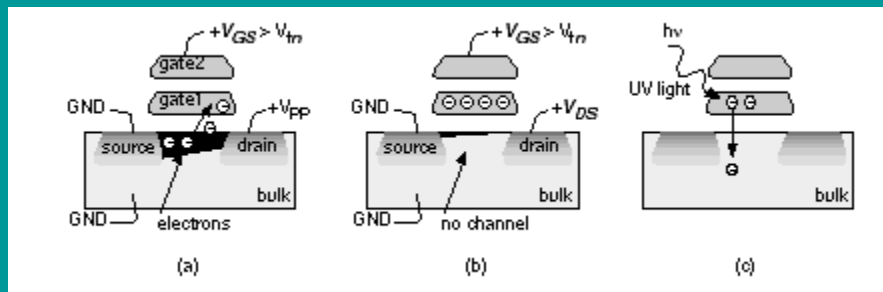
- Floating gate technologies
 - Non-volatile but re-usable
 - UV EPROM, EEPROM, and flash memory
 - In-System Programmable (ISP)
 - EEPROM and flash memory
 - In-System Re-programmable (ISR)
 - Flash memory



EPROM transistor – Programming voltage forces charge into floating gate.
(trapped until given energy to escape)
[Altera EPLDs, Xilinx EPLDs]

Programming Technologies

 - Fuse/anti-fuse
 - Non-volatile but not re-usable
 - One Time Programmable (OTP)




Antifuse - Open until programming current melts dielectric (one time only)

[Actel PLICE[©]]

Programming Technologies

■ RAM

 
- Volatile – must configure after power-up
- In-System Re-programmable (ISR)
- Run-Time Reconfiguration (RTR)
 - dynamic reconfiguration while system is operating



SRAM cell

Logic functions in read-only memory (ROM)

FIGURE 3-2:
An 8-Word \times 4-Bit
ROM

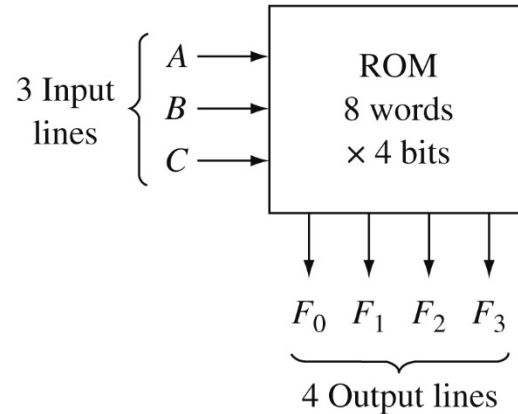


(a) Block diagram

| <i>A</i> | <i>B</i> | <i>C</i> | <i>F</i> ₀ | <i>F</i> ₁ | <i>F</i> ₂ | <i>F</i> ₃ |
|----------|----------|----------|-----------------------|-----------------------|-----------------------|-----------------------|
| 0 | 0 | 0 | 1 | 0 | 1 | 0 |
| 0 | 0 | 1 | 1 | 0 | 1 | 0 |
| 0 | 1 | 0 | 0 | 1 | 1 | 1 |
| 0 | 1 | 1 | 0 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 | 1 | 0 | 0 |
| 1 | 0 | 1 | 0 | 0 | 0 | 1 |
| 1 | 1 | 0 | 1 | 1 | 1 | 1 |
| 1 | 1 | 1 | 0 | 1 | 0 | 1 |

Typical data
stored in ROM
(2^3 words of
4 bits each)

(b) Truth table for ROM


FIGURE 3-3:
Read-Only Memory
with n Inputs and
 m Outputs

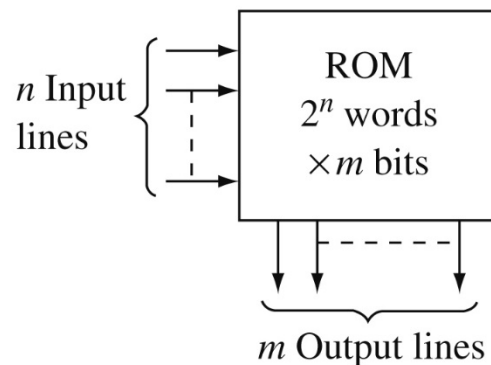

| n Input Variables | m Output Variables |
|------------------------|-------------------------|
| 00...00 | 100...110 |
| 00...01 | 010...111 |
| 00...10 | 101...101 |
| 00...11 | 110...010 |
| \vdots | \vdots |
| 11...00 | 001...011 |
| 11...01 | 110...110 |
| 11...10 | 011...000 |
| 11...11 | 111...101 |

Typical data
array stored
in ROM
(2^n words of
 m bits each)

FIGURE 3-4: Block Diagram and Truth Table of a 2-Bit Adder

 

| X_1 | X_0 | Y_1 | Y_0 | S_2 | S_1 | S_0 |
|-------|-------|-------|-------|-------|-------|-------|
| 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 0 | 1 | 0 | 0 | 1 |
| 0 | 0 | 1 | 0 | 0 | 1 | 0 |
| 0 | 0 | 1 | 1 | 0 | 1 | 1 |
| 0 | 1 | 0 | 0 | 0 | 0 | 1 |
| 0 | 1 | 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 | 0 | 1 | 1 |
| 0 | 1 | 1 | 1 | 1 | 0 | 0 |
| 1 | 0 | 0 | 0 | 0 | 1 | 0 |
| 1 | 0 | 0 | 1 | 0 | 1 | 1 |
| 1 | 0 | 1 | 0 | 1 | 0 | 0 |
| 1 | 0 | 1 | 1 | 1 | 0 | 1 |
| 1 | 1 | 0 | 0 | 0 | 1 | 1 |
| 1 | 1 | 0 | 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 0 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 | 1 | 1 | 0 |

FIGURE 3-5: ROM Implementation of a 2-Bit Full Adder

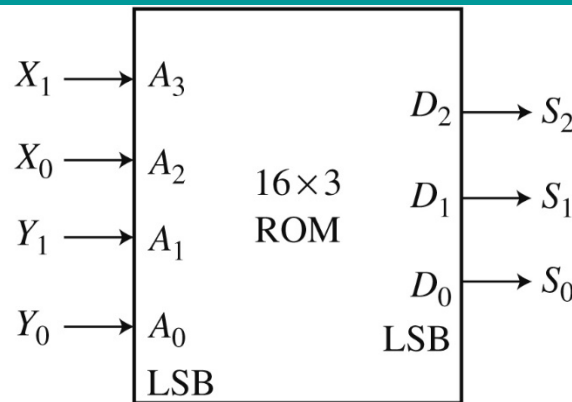


FIGURE 3-6: 8-to-3 Priority Encoder


 


FIGURE 3-7:
State Table for a
Sequential Circuit

| PS | NS | | Z | |
|-------|-------|-------|-----|-----|
| | X=0 | X=1 | X=0 | X=1 |
| S_0 | S_1 | S_2 | 1 | 0 |
| S_1 | S_3 | S_4 | 1 | 0 |
| S_2 | S_4 | S_4 | 0 | 1 |
| S_3 | S_5 | S_5 | 0 | 1 |
| S_4 | S_5 | S_6 | 1 | 0 |
| S_5 | S_0 | S_0 | 0 | 1 |
| S_6 | S_0 | — | 1 | — |

FIGURE 3-8:
Realization of a
Mealy Sequential
Circuit with a ROM

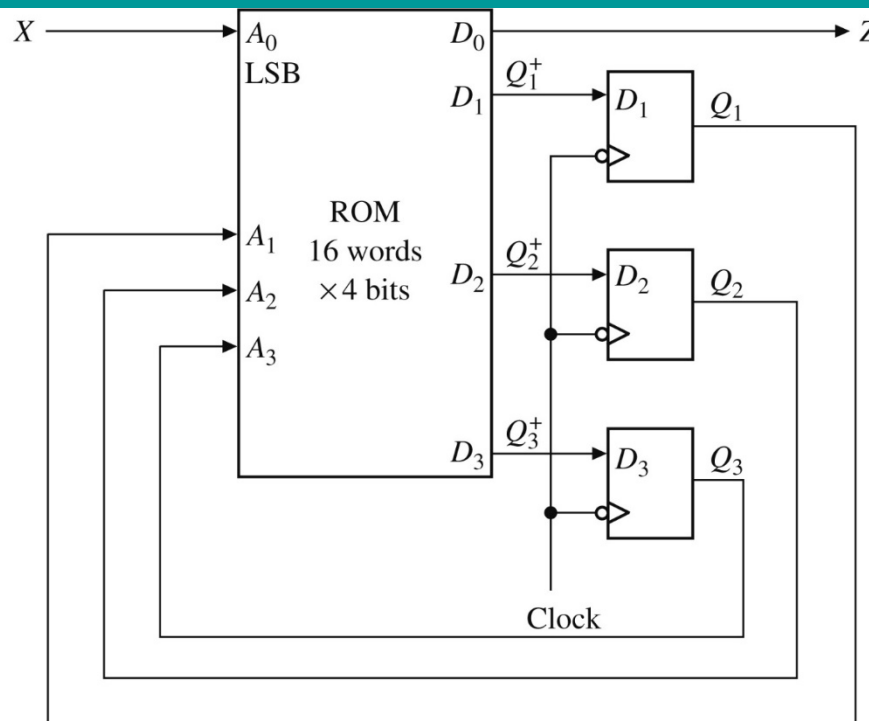


*ROM on
next slide*

| TABLE 3-2: ROM Truth Table | Q_3 | Q_2 | Q_1 | X | Q_3^+ | Q_2^+ | Q_1^+ | Z |
|---------------------------------------|-------|-------|-------|-----|---------|---------|---------|-----|
| | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 1 |
| | 0 | 0 | 0 | 1 | 0 | 1 | 0 | 0 |
| | 0 | 0 | 1 | 0 | 0 | 1 | 1 | 1 |
| | 0 | 0 | 1 | 1 | 1 | 0 | 0 | 0 |
| | 0 | 1 | 0 | 0 | 1 | 0 | 0 | 0 |
| | 0 | 1 | 0 | 1 | 1 | 0 | 0 | 1 |
| | 0 | 1 | 1 | 0 | 1 | 0 | 1 | 0 |
| | 0 | 1 | 1 | 1 | 1 | 0 | 1 | 1 |
| | 1 | 0 | 0 | 0 | 1 | 0 | 1 | 1 |
| | 1 | 0 | 0 | 1 | 1 | 1 | 0 | 0 |
| | 1 | 0 | 1 | 0 | 0 | 0 | 0 | 0 |
| | 1 | 0 | 1 | 1 | 0 | 0 | 0 | 1 |
| | 1 | 1 | 0 | 0 | 0 | 0 | 0 | 1 |
| | 1 | 1 | 0 | 1 | 0 | 0 | 0 | 0 |
| | 1 | 1 | 1 | 0 | 0 | 0 | 0 | 0 |
| | 1 | 1 | 1 | 1 | 0 | 0 | 0 | 0 |

Programmable logic array structure

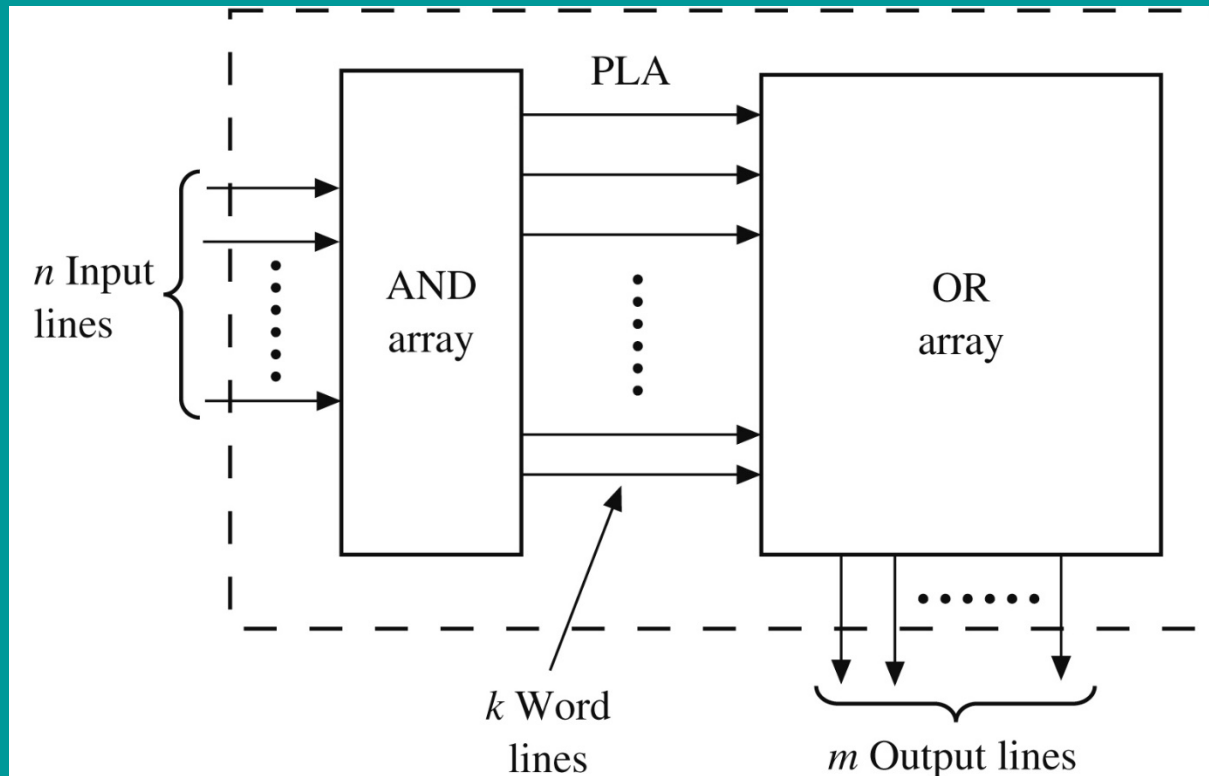
Implement sum of products logic expressions



Each one
"product"
of the inputs

Each one "sum"
of the products

NOR function in programmable logic

 

$X_i = 0$ turns transistor OFF (transistor = open circuit)

$X_i = 1$ turns transistor ON (transistor shorts Z to ground/0)

+V pulls Z up to 1 if not shorted to ground

Truth Table:


| <u>X1</u> | <u>X2</u> | <u>Z</u> | |
|-----------|-----------|----------|--|
| 0 | 0 | 1 | - both transistors OFF/Z pulled up to +V |
| 0 | 1 | 0 | - transistor 2 ON/shorts Z to ground |
| 1 | 0 | 0 | - transistor 1 ON/shorts Z to ground |
| 1 | 1 | 0 | - both transistors ON/short Z to ground |

Manipulate sum of products form to use NOR-NOR structures



PLA implements SOP forms

$$F_0 = \bar{A}\bar{B} + A\bar{C}$$

FIGURE 3-13:
Conversion of
NOR-NOR to
AND-OR

 


Equivalent
AND-OR form

  


Inputs and complements typically provided in PLA

Compact representation of product

 


PLA with 3 inputs/5 products/4 sums

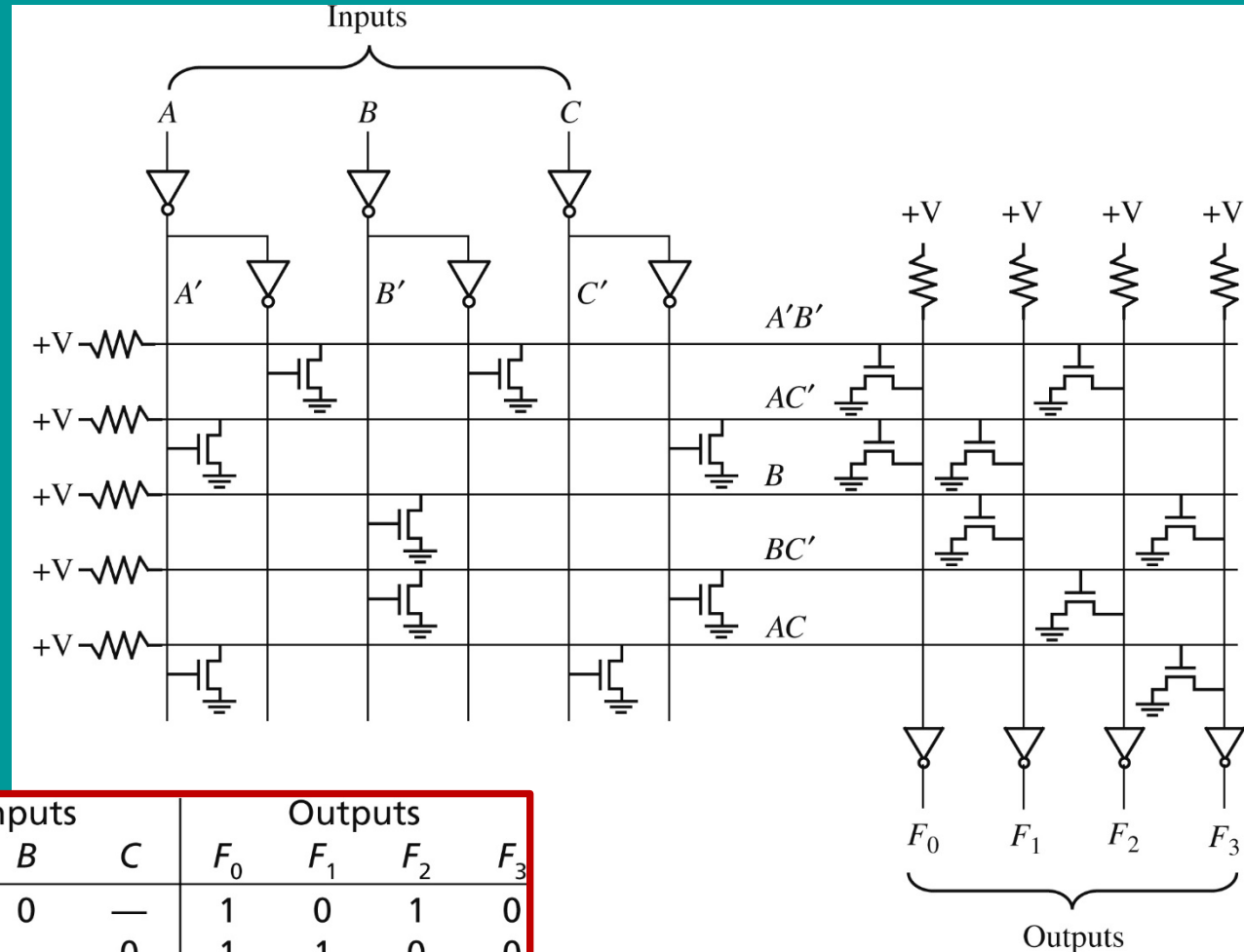

| Product Term | Inputs | | | Outputs | | | |
|--------------|--------|---|---|----------------|----------------|----------------|----------------|
| | A | B | C | F ₀ | F ₁ | F ₂ | F ₃ |
| A'B' | 0 | 0 | — | 1 | 0 | 1 | 0 |
| AC' | 1 | — | 0 | 1 | 1 | 0 | 0 |
| B | — | 1 | — | 0 | 1 | 0 | 1 |
| BC' | — | 1 | 0 | 0 | 0 | 1 | 0 |
| AC | 1 | — | 1 | 0 | 0 | 1 | 1 |

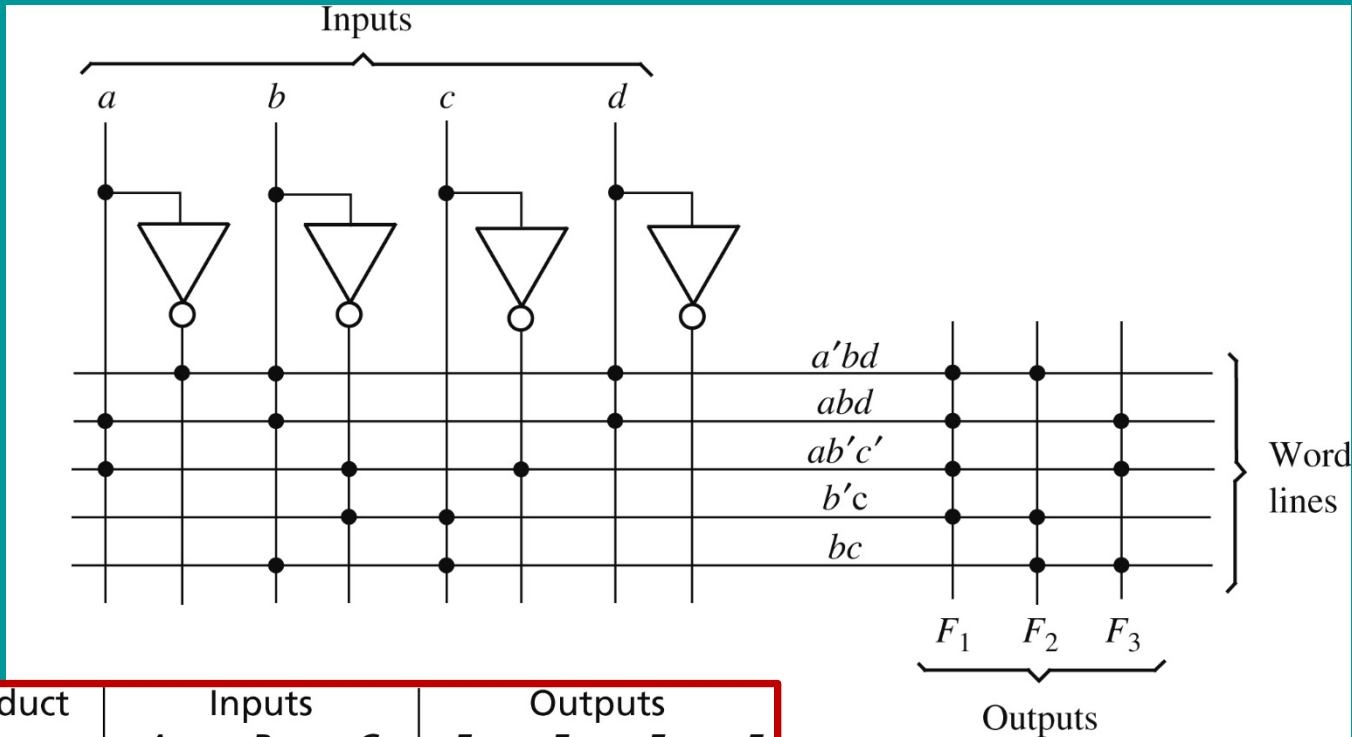Compact representation of previous PLA circuit




| Product Term | Inputs | | | Outputs | | | |
|--------------|--------|---|---|----------------|----------------|----------------|----------------|
| | A | B | C | F ₀ | F ₁ | F ₂ | F ₃ |
| A'B' | 0 | 0 | — | 1 | 0 | 1 | 0 |
| AC' | 1 | — | 0 | 1 | 1 | 0 | 0 |
| B | — | 1 | — | 0 | 1 | 0 | 1 |
| BC' | — | 1 | 0 | 0 | 0 | 1 | 0 |
| AC | 1 | — | 1 | 0 | 0 | 1 | 1 |

PLDs

| TABLE 3-4: Reduced PLA Table | a | b | c | d | F_1 | F_2 | F_3 |
|---------------------------------|-----|-----|-----|-----|-------|-------|-------|
| | 0 | 1 | — | 1 | 1 | 1 | 0 |
| | 1 | 1 | — | 1 | 1 | 0 | 1 |
| | 1 | 0 | 0 | — | 1 | 0 | 1 |
| | — | 0 | 1 | — | 1 | 1 | 0 |
| | — | 1 | 1 | — | 0 | 1 | 1 |

FIGURE 3-15:
PLA Realization of
Equations (3-4)

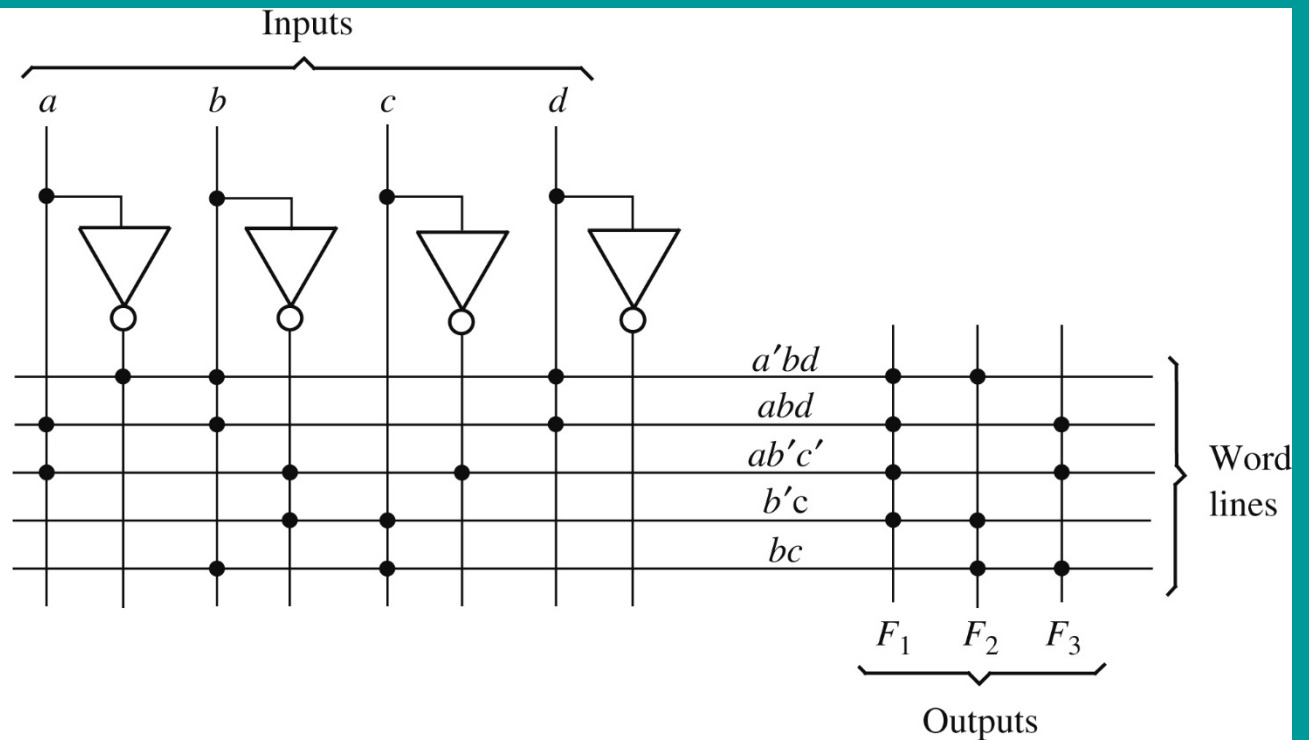

Sequential circuit implementation


BCD to Excess-3 Converter

TABLE 3-5:
PLA Table


| Product Term | Q_1 | Q_2 | Q_3 | X | Q_1^+ | Q_2^+ | Q_3^+ | Z |
|---------------|-------|-------|-------|-----|---------|---------|---------|-----|
| Q_2' | — | 0 | — | — | 1 | 0 | 0 | 0 |
| Q_1 | 1 | — | — | — | 0 | 1 | 0 | 0 |
| $Q_1 Q_2 Q_3$ | 1 | 1 | 1 | — | 0 | 0 | 1 | 0 |
| $Q_1 Q_3' X'$ | 1 | — | 0 | 0 | 0 | 0 | 1 | 0 |
| $Q_1' Q_2' X$ | 0 | 0 | — | 1 | 0 | 0 | 1 | 0 |
| $Q_3' X'$ | — | — | 0 | 0 | 0 | 0 | 0 | 1 |
| $Q_3 X$ | — | — | 1 | 1 | 0 | 0 | 0 | 1 |

Programmable Array Logic (PAL)

FIGURE 3-16:
PAL Segment

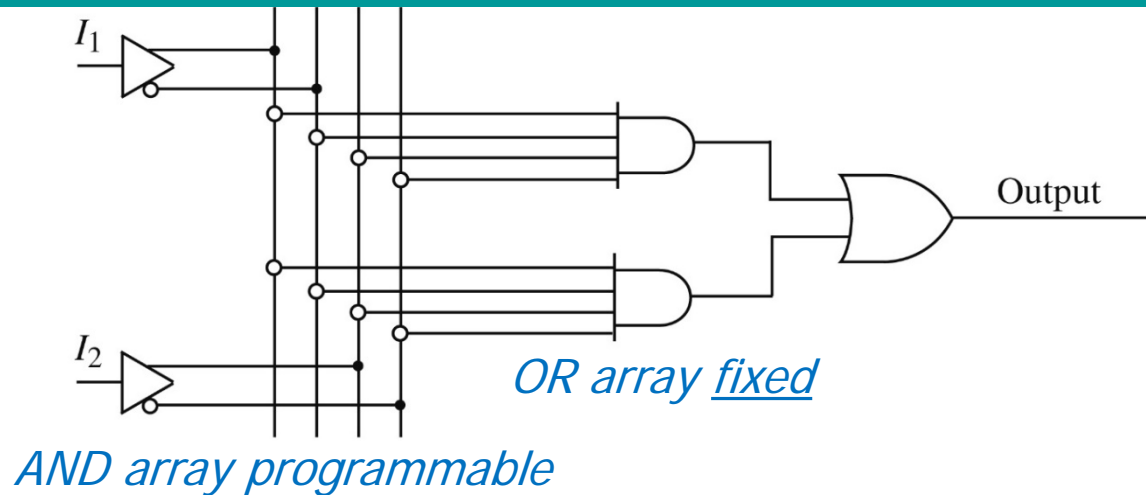


(a) Unprogrammed

 

(b) Programmed

Full adder with a PAL


FIGURE 3-17:
Implementation of
a Full Adder Using
a PAL

 

PALs


16L8 – combinational logic

 - 10 to 16 inputs, each with true and complement signal
- 2 to 8 outputs, each with
 - 7 product terms can AND any of up to 16 inputs or their complements
 - Tri-state control product term for inverting output buffer
 - When output in tri-state, I/O pin can be used as input
 - High impedance output with no signal driven




Sequential PAL

FIGURE 3-18:
Segment of a
Sequential PAL

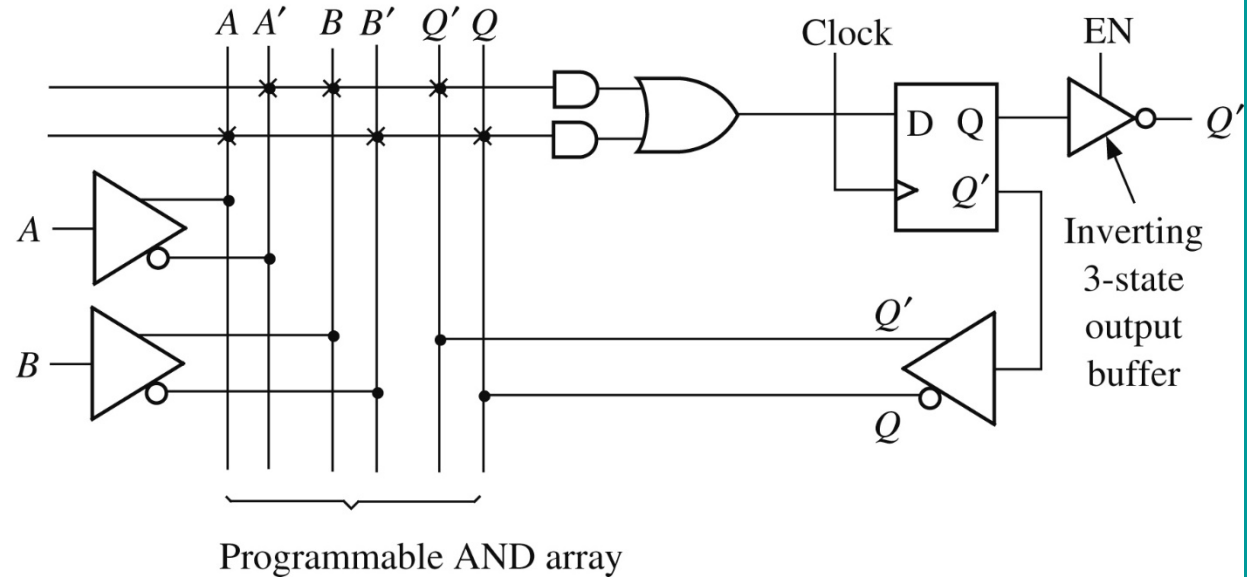


Sequential circuit with a PAL

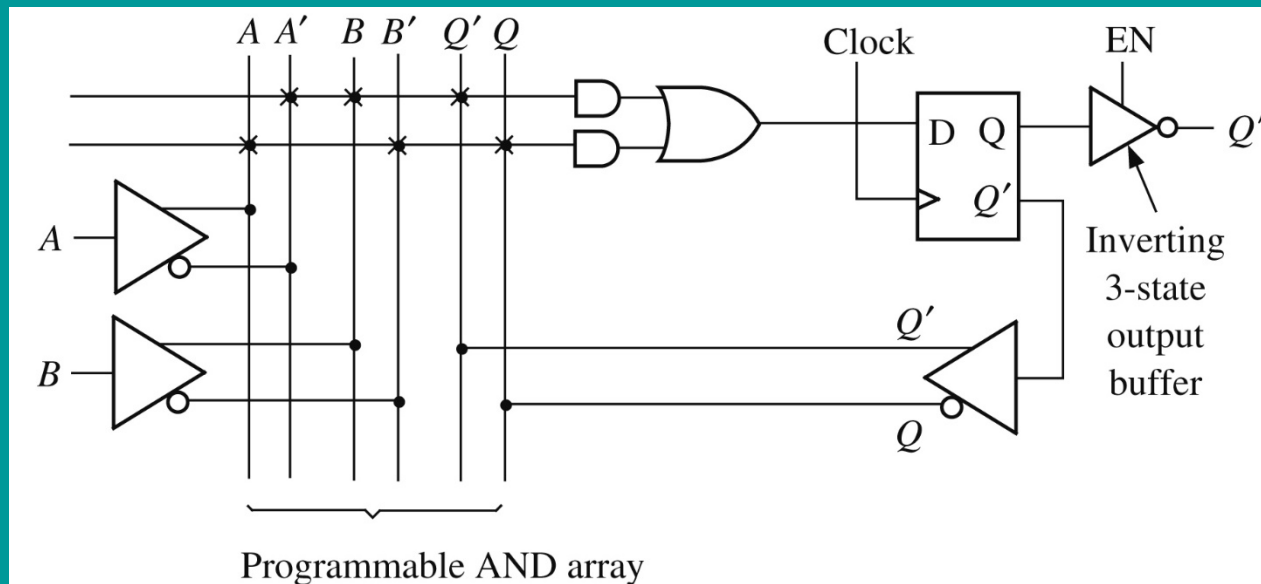

PALS


16R8 – sequential logic

 - 8 inputs, each with true & complement
- 8 outputs, each with
 - D flip-flop
 - With feedback for FSMs
 - 8 product terms that can AND any of:
 - 8 inputs or their complements
 - 8 feedbacks or their complements from D flip-flops
- One clock for all FFs
- One tri-state control for all outputs



PLD Basic Structure

 - Programmable product terms (AND plane)
 - AND gates can connect to any input/FF bit or bit-bar
- Fixed OR plane determine maximum # PTs
- Programmable macrocell
 - XOR gate selects SOP or POS for fewer PTs
 - FF for sequential logic or bypass for combinational logic
 - Feedback current state into array for FSM design



PLDs

22V10 replaced all PALs

- Combinational and/or sequential logic
 - Macrocell program bits C0, C1
- Up to 22 inputs w/complement
- Up to 10 outputs, each with
 - Macrocell
 - 8-16 product terms
 - Tri-state control product term
- Global
 - preset & clear PTs
 - clock



 
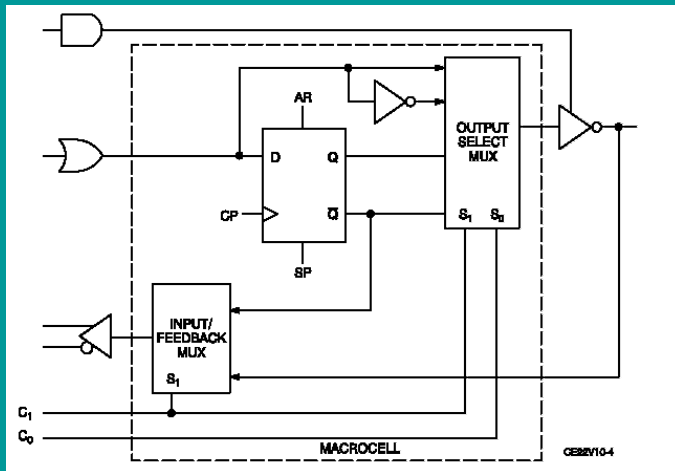


FIGURE 3-20: PLD Output Macrocell of 22V10

of 22V10

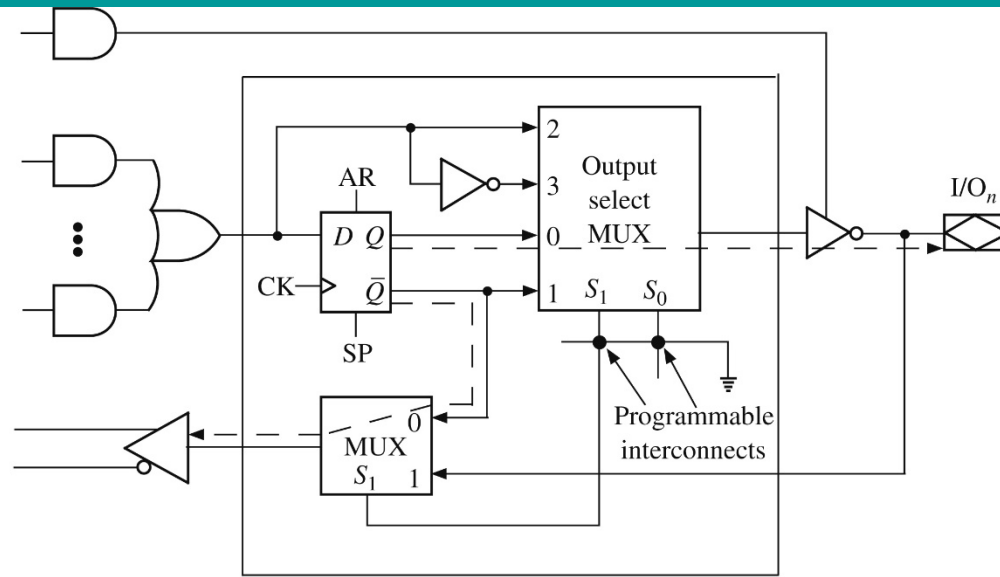

(a) Paths with $S_1 = S_0 = 0$

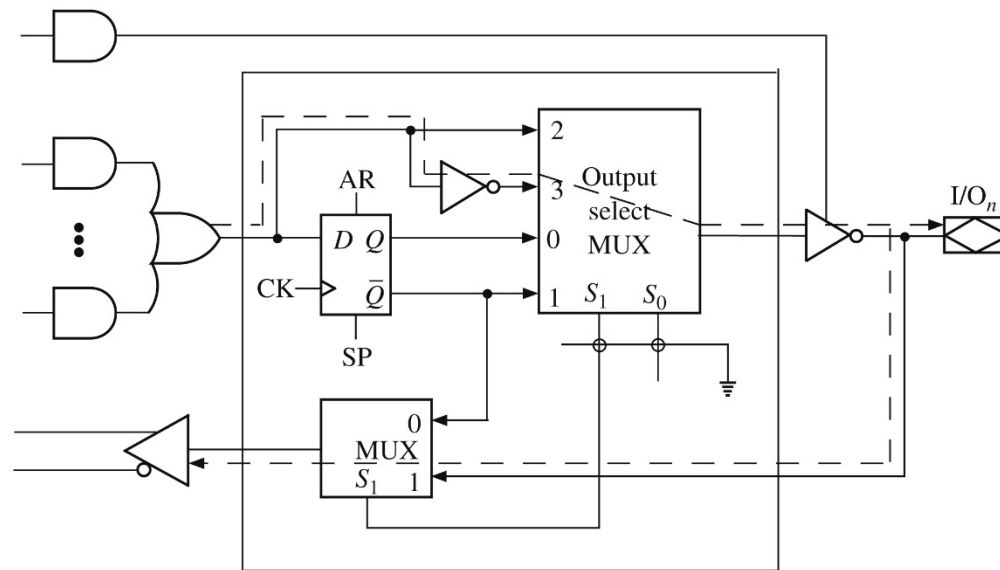

(b) Paths with $S_1 = S_0 = 1$

CPLD implementation of a Mealy machine

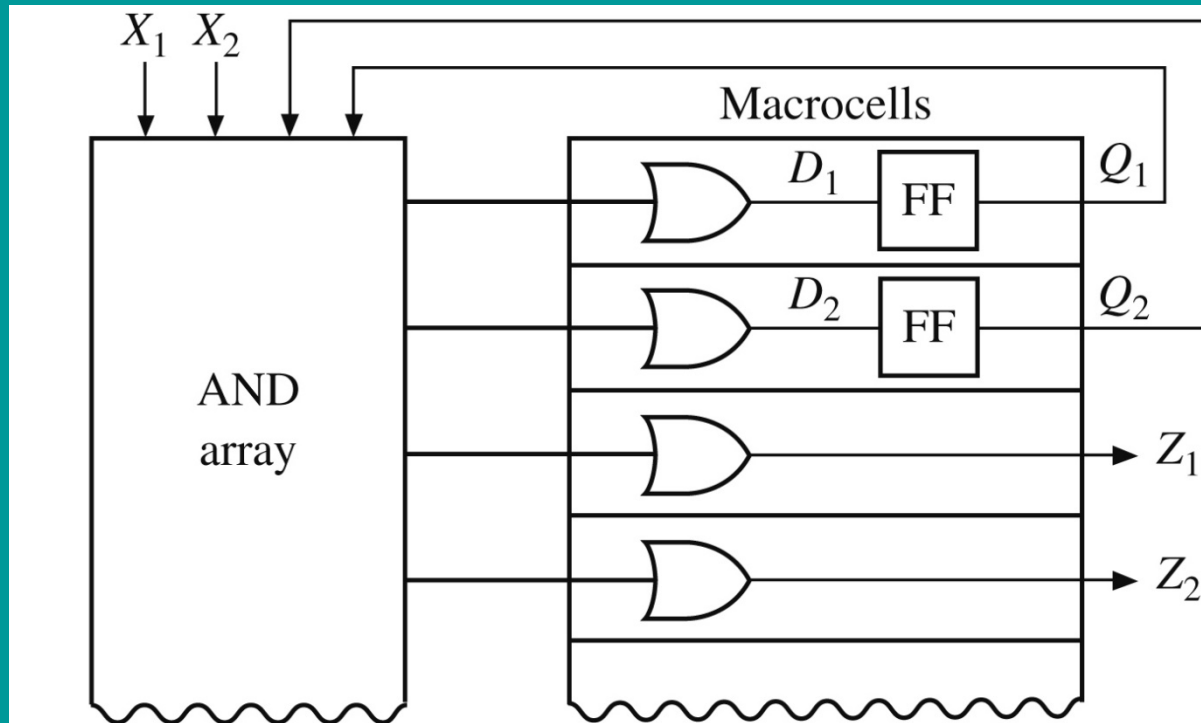


FIGURE 3-24: N-Bit Parallel Adder with Accumulator


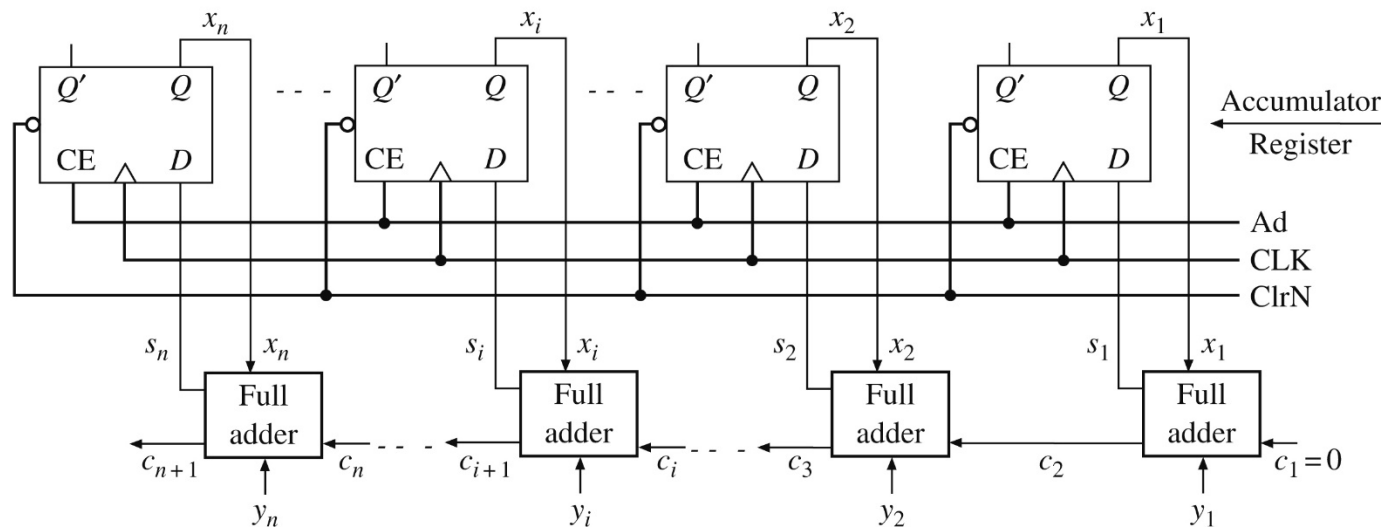


FIGURE 3-25: CPLD Implementation of a Parallel Adder with Accumulator

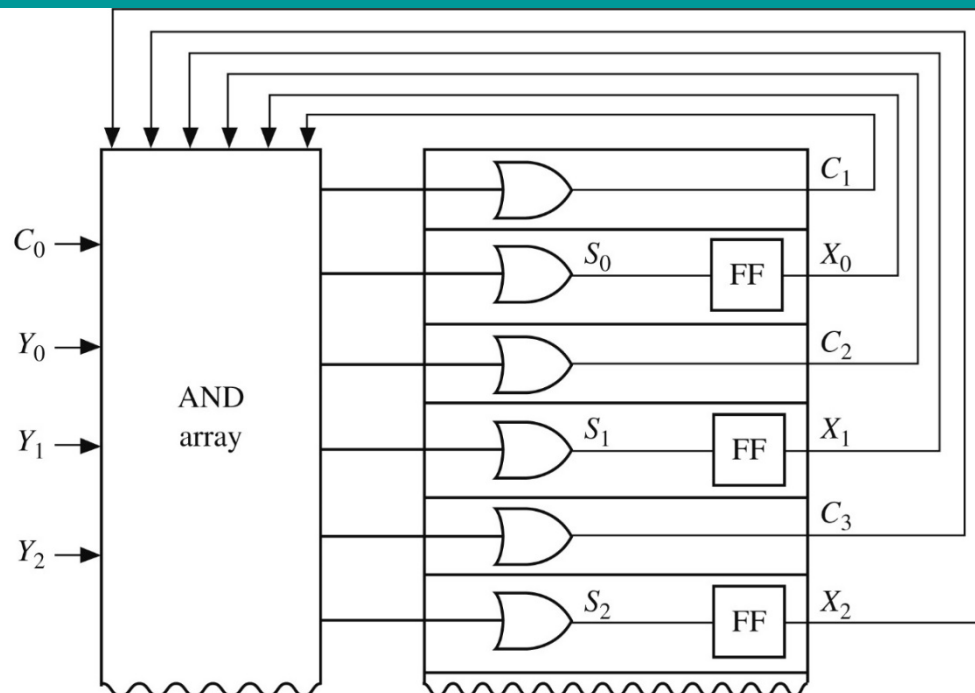

Complex PLDs (CPLDs)

- An array of PLDs
 - Global routing resources for connections
 - PLDs to other PLDs
 - PLDs to/from I/O pins
- Example: Cypress 39K
 - Each Logic Block (LB) similar to a 22V10
 - Each cluster of 8 LBs has two 8K RAMs & one 4K dual-port RAM/FIFO
 - Programmable Interconnect Modules (PIMs) provide interconnections
 - Array of up to 24 clusters with global routing

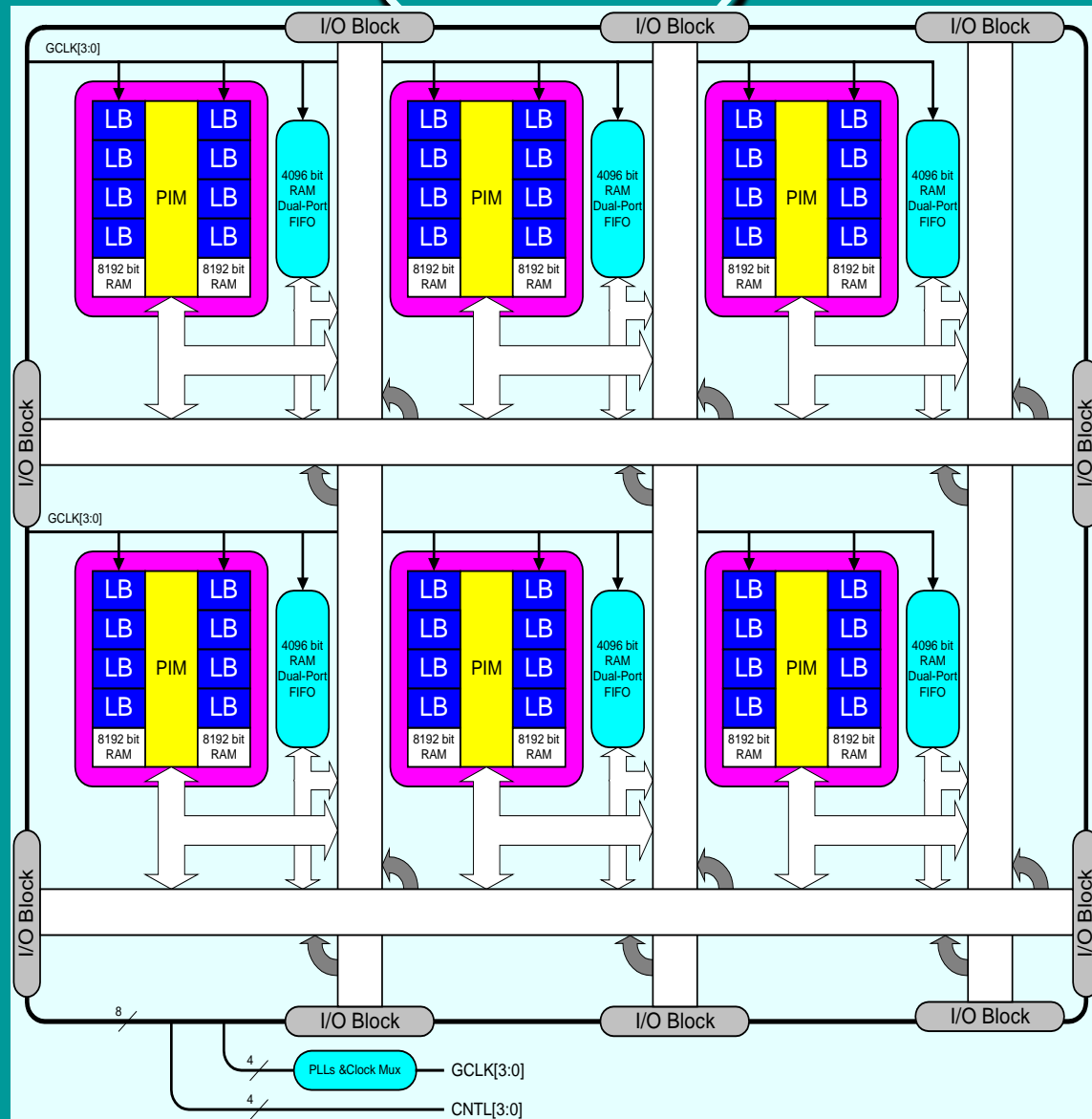


FIGURE 3-21: Architecture of Xilinx CoolRunner XCR3064XL CPLD



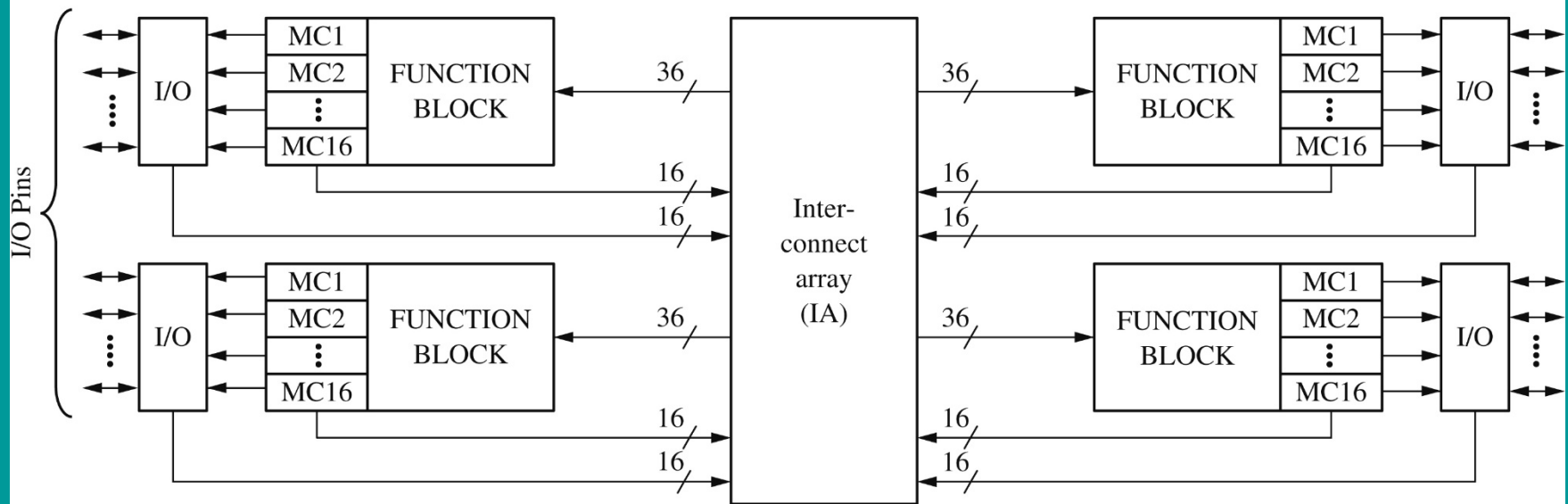


FIGURE 3-22: CPLD Function Block and Macrocell (Simplified Version of XCR3064XL)

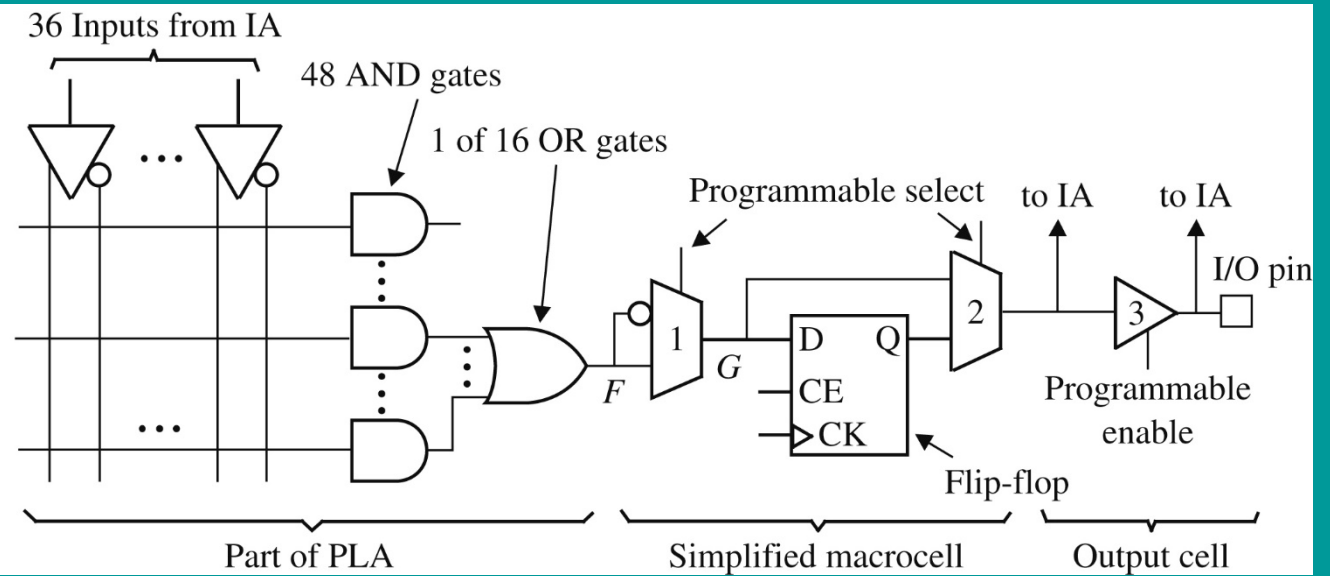

Altera MAX architecture (PAL-based logic modules)

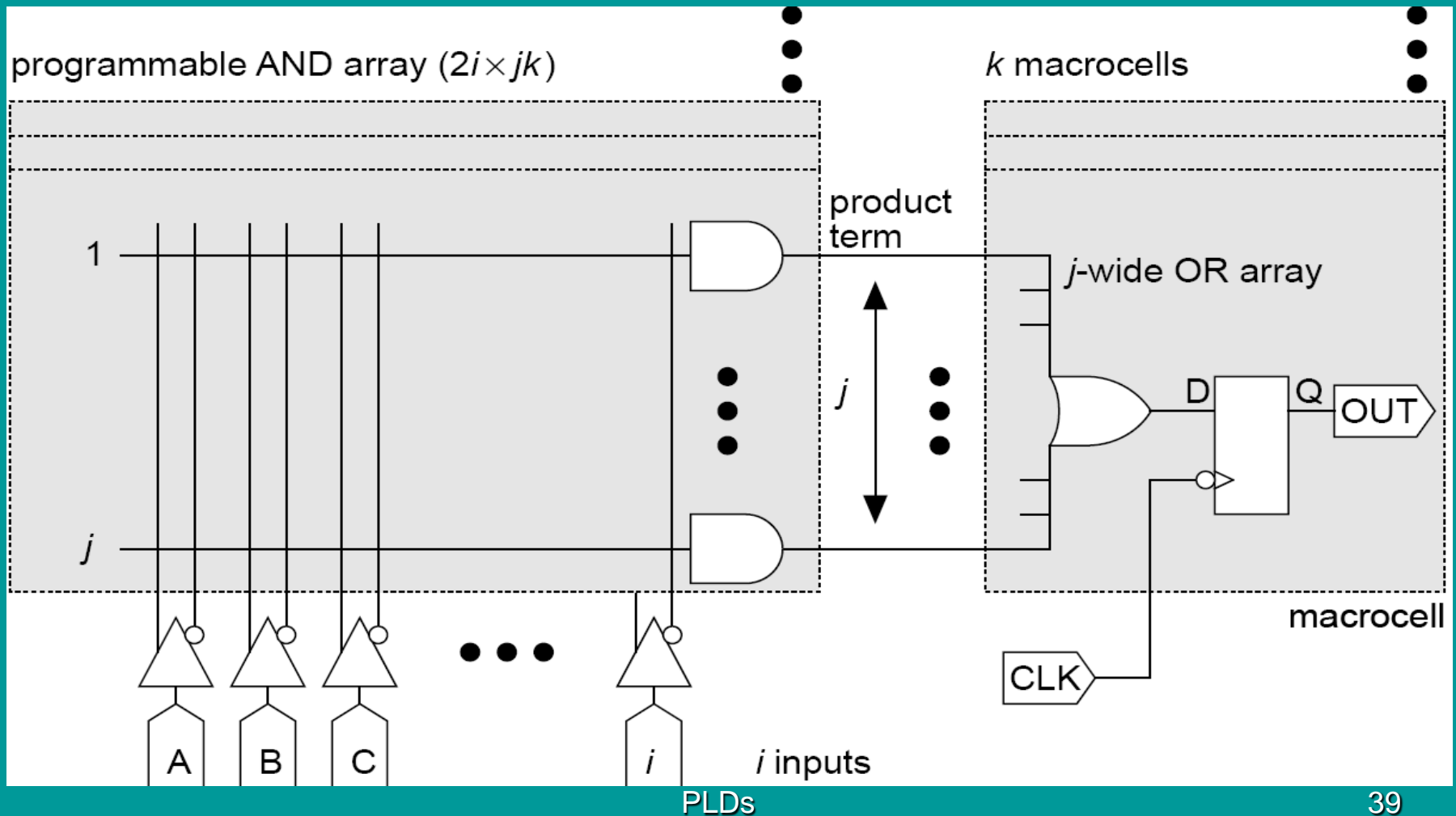

**TABLE 3-6:
Major CPLDs and
their Approximate
Capacity**

| Vendor | CPLD family | Gate Count |
|-----------------------|---------------------------|----------------------------|
| Xilinx | CoolRunner-II | 750 to 12K |
| | CoolRunner XPLA3 | 750 to 12K |
| | XC9500XV | 800 to 6400 |
| | XC9500 | 800 to 6400 |
| | XC9500XL | 800 to 6400 |
| Atmel | CPLD ATF15 | 750 to 3000 usable gates |
| | CPLD-2 22V10 | 500 usable gates |
| Cypress | Delta39K | 30K to 200K |
| | Flash370i | 800 to 3200 |
| | Quantum38K | 30K to 100K |
| | Ultra37000 | 960 to 7700 |
| | MAX340 high-density EPLDs | 600 to 3750 |
| Lattice Semiconductor | ispXPLD 5000MX | 75K to 300K |
| | ispMACH 4000B/C/V/Z | 640 to 10,240 |
| Altera | MAX II | 240 to 2210 logic elements |
| | MAX3000 | 600 to 10K usable gates |
| | MAX7000 | 600 to 10K usable gates |