

# Faults, Testing & Test Generation

Smith Text: Chapter 14.1, 14.3, 14.4


Mentor Graphics/Tessent:

“Scan and ATPG Process Guide”

“ATPG and Failure Diagnosis Tools Reference Manual”

(access via “mgcdocs”)

# ASIC Design Flow

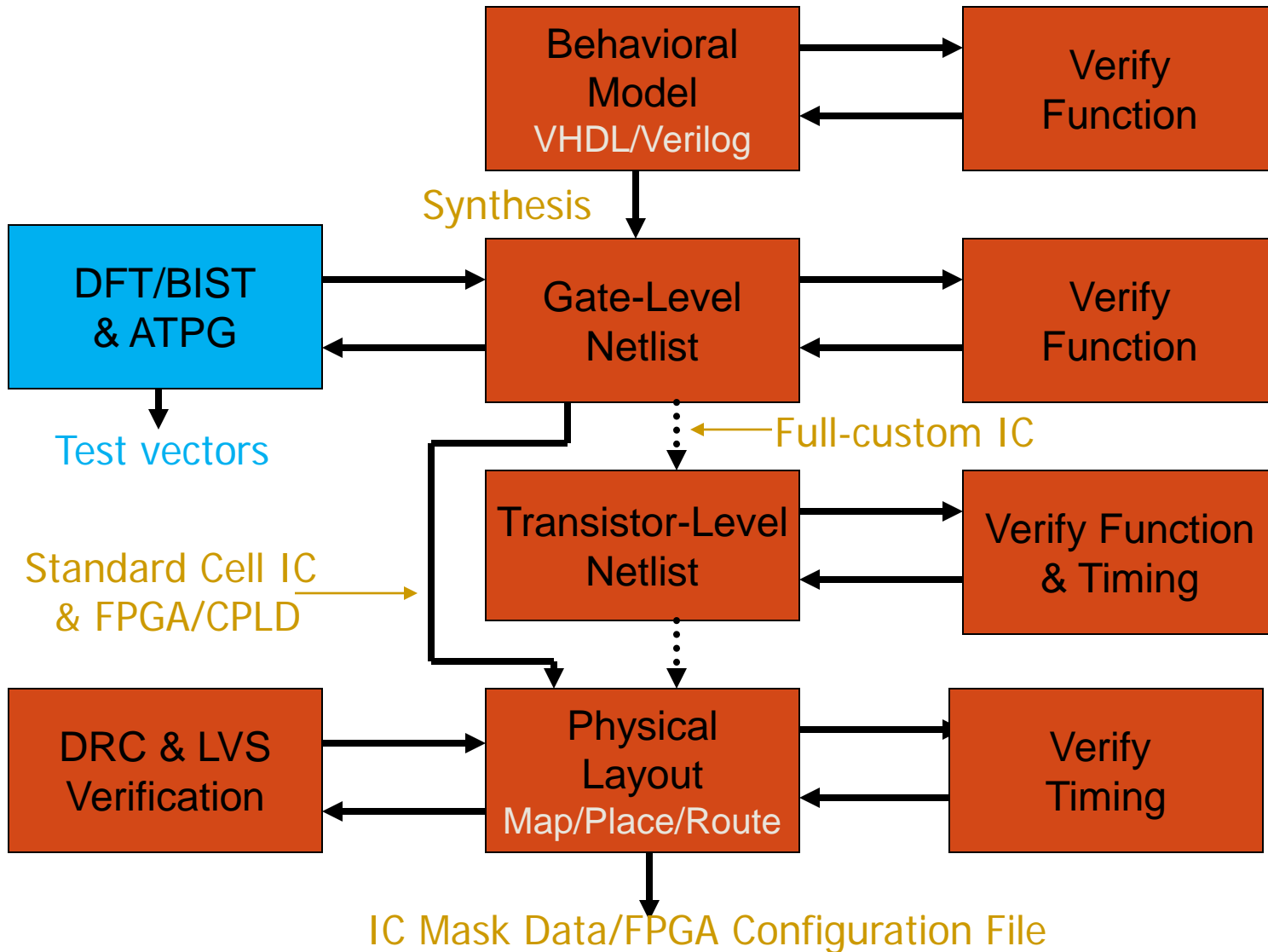

# Importance of test (Ch. 14.1)

ASIC defect level	Defective ASICs	Total PCB repair cost	Total system repair cost
5%	5000	\$1 million	\$5 million
1%	1000	\$200,000	\$1 million
0.1%	100	\$20,000	\$100,000
0.01%	10	\$2,000	\$10,000


Parts shipped: 100,000 @ part cost = \$10

PCB cost: \$200, System cost: \$5,000, 100,000 systems shipped

System repair/replace cost: \$10,000


Q: What would it cost to reduce defect density from 5% to 1% ?

# Top-down test design flow

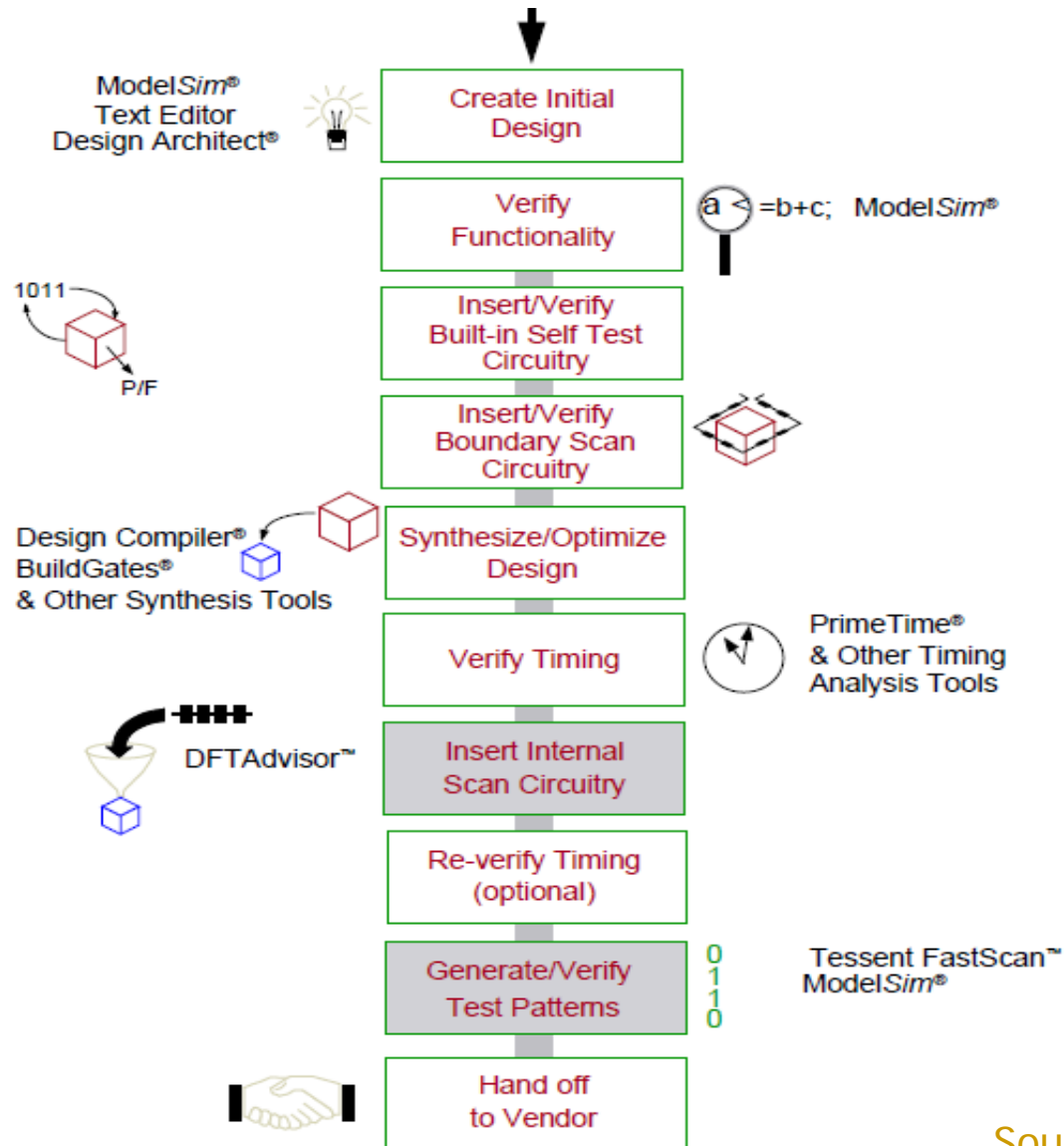

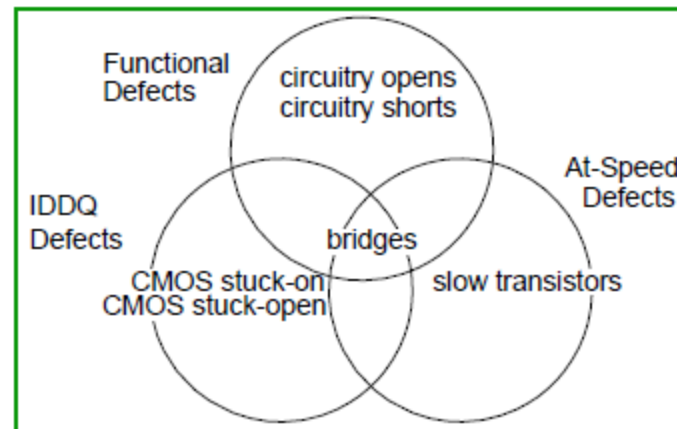
# Fault models *(supported by FastScan)*

- Map physical fault to a “logical” fault, i.e. faults that change the logic function of the circuit
  - Stuck-at: net effectively stuck at a logic 0/1
  - Bridging: value on one net affects another net
- “Parametric” faults alter physical properties other than logic function
  - Delay
  - Transition
  - IDDQ
  - Voltage level
  - Signal strength




# Defects and physical faults

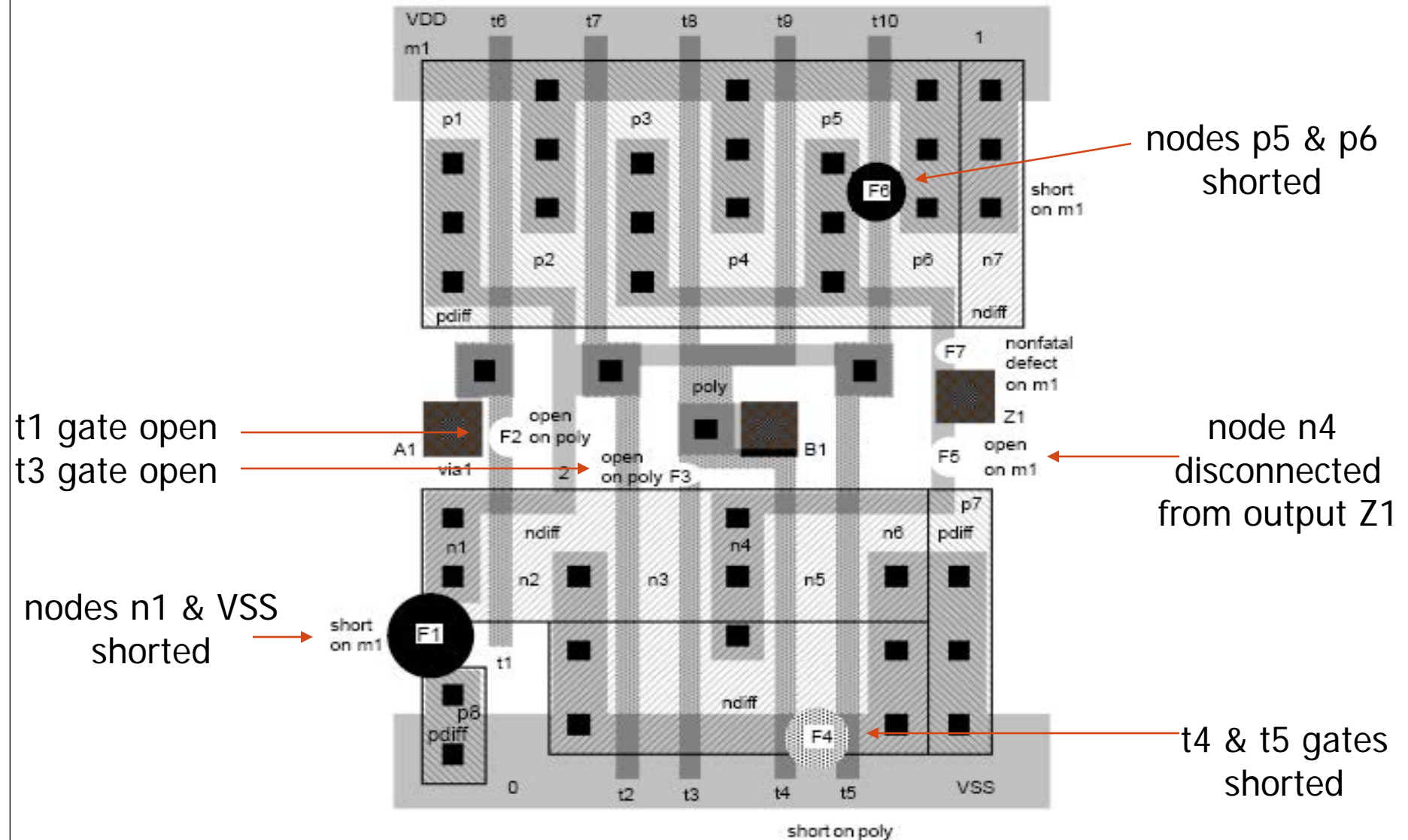


Smith Text: Figure 14.11

# Defects translated to logical faults

(defects from previous slide)

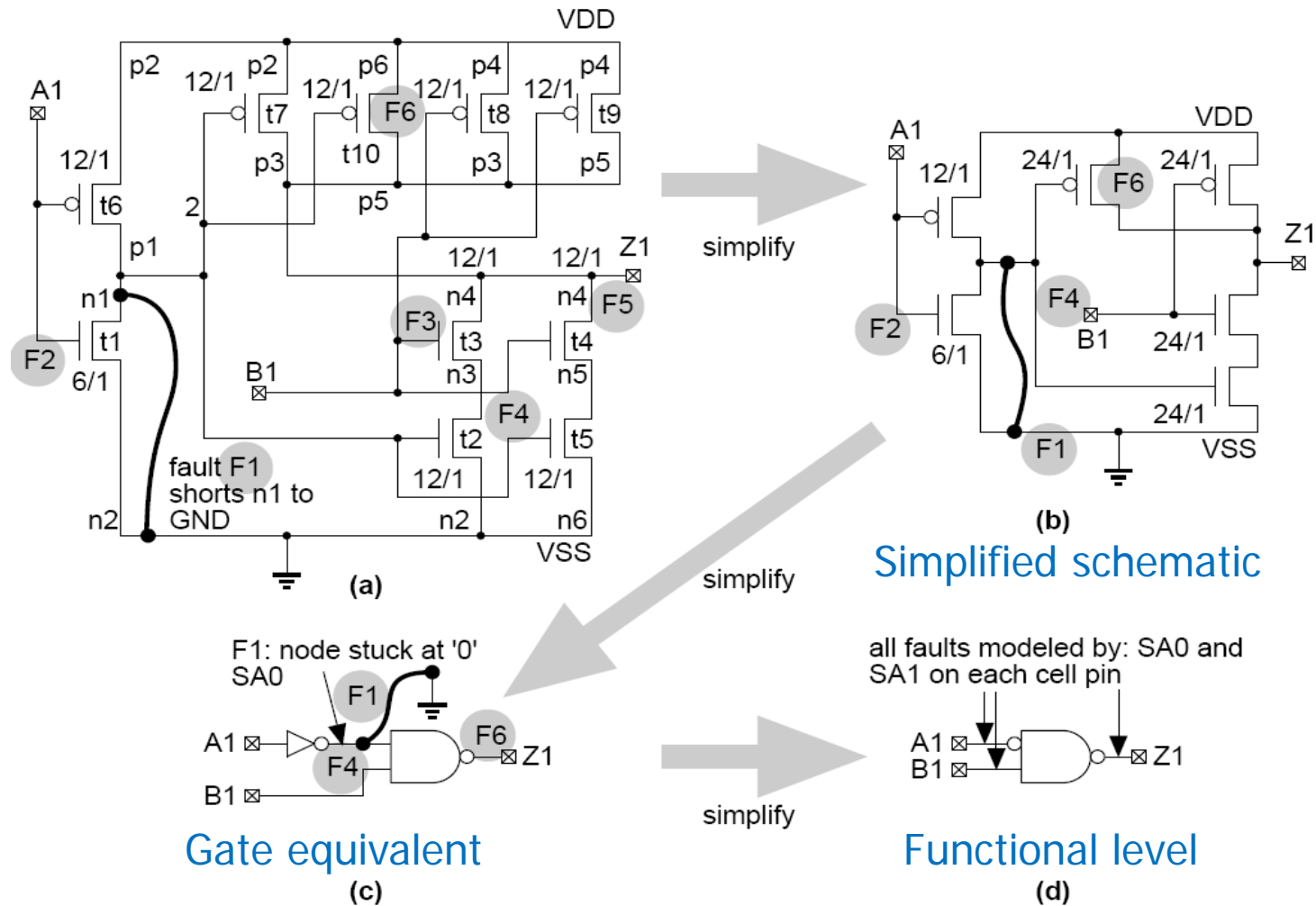

# Stuck-at faults

 


Fault	Test (A,B)	Y(good)	Y(faulty)	Resulting function
A/0	11	1	0	Y=0
A/1	01	0	1	Y=B
B/0	11	1	0	Y=0
B/1	10	0	1	Y=A
Y/0	11	1	0	Y=0
Y/1	01,10,00	0	1	Y=1

# Fault collapsing

- Fault A equivalent to fault B if every test for A is also a test for B and vice versa
  - Faults are indistinguishable
  - Group equivalent faults into a fault-equivalence class (FEC)
  - *Only one fault from a FEC needs to be tested*
- Fault A dominates fault B if any test for B also detects A, but only some of A tests detect B
  - *Need only test dominated fault B*  
(guarantees A tested also)

# Fault collapsing example

 

$A/0 = B/0 = Y/0$  (remove  $B/0, Y/0$ )

$A/1$  dominates  $Y/1$  (remove  $Y/1$ )


$B/1$  dominates  $Y/1$  (remove  $Y/1$ )

*Collapsed fault set =  $\{A/0, A/1, B/1\}$*

*Min test set =  $\{11, 01, 10\}$*

Fault	Test (A,B)	Y(good)	Y(faulty)	Collapsing
A/0	11	1	0	A/0 equiv to B/0, Y/0
A/1	01	0	1	A/1 dom by Y/1
B/0	11	1	0	B/0 equiv to A/0, Y/0
B/1	10	0	1	B/1 dom by Y/1
Y/0	11	1	0	Y/0 equiv to A/0, B/0
Y/1	01,10,00	0	1	Y/1 dom A/1, B/1

# Fault collapsing example

 

## Equivalence classes:

{A/0, B1/0, G/1} – keep G/1

{B2/0, C/0, F/1} – keep F/1

{G/0, K/0, Y/0} – keep G/0

{D2/0, E/0, J/1, H/1, K/1, F/0, D1/0} – keep F/0

## Fault dominance: (remove dominated)

A/1 -> G/0

B1/1 -> G/0

B2/1 -> F/0

C/1 -> H/0

D2/1 -> J/0

E/1 -> J/0

F/1 -> H/0

D1/1 -> H/0

H/0 -> K/0

J/0 -> K/0

G/1 -> Y/1


K/1 -> Y/1

Collapsed fault set = {A/1, B1/1, B2/1, C/1, D1/1, D2/1, E/1, G/1, F/1, K/1}

# Test generation: D Algorithm

- Select a fault on net N (ex. sa0)
- Produce an error at N (ex. N=1)
  - “D” denotes expected 1, actual 0 values
  - “D\*” denotes expected 0, actual 1 values
- Propagate D condition to primary output
  - Set gate inputs to propage D
- “Justify” D condition from primary inputs
  - Set gate inputs to create D condition

# D Algorithm – tabular method

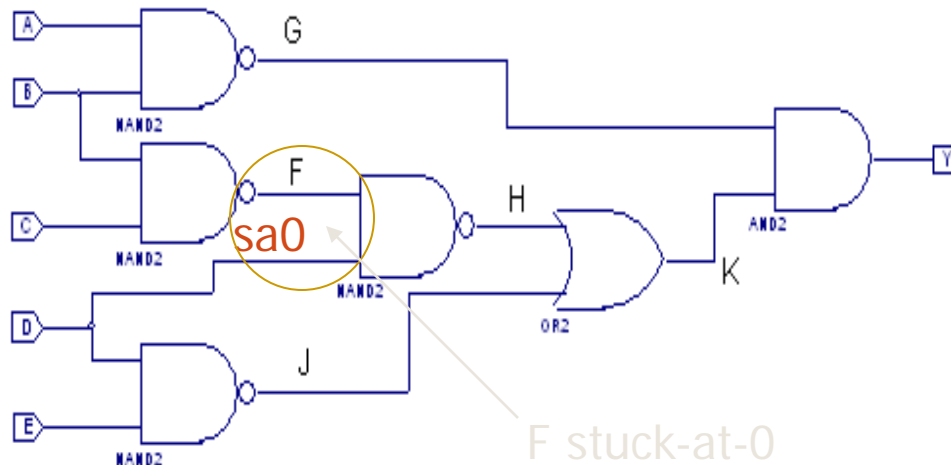


Step	A	B	C	D	E	F	G	H	J	K	Y
control						D					
observe				1		D		D*			
observe				1		D		D*	0	D*	
observe				1		D	1	D*	0	D*	D*
Consistency - J				1	1	D	1	D*	0	D*	D*
Consistency - G	x	0		1	1	D	1	D*	0	D*	D*
Consistency - F	x	0	x	1	1	D	1	D*	0	D*	D*

Test vectors:  $ABCDE = \{-0-11, 0-011\} = \{00011, 10011, 00111, 10111, 01011\}$

# Generate and verify a test set

- Collapse the fault set
  - minimize fault set required for 100% fault coverage  
“coverage” =  $(\# \text{ faults detected}) / (\# \text{ possible faults})$
- Automatic test pattern generation (ATPG)
  - apply D algorithm or other method to derive test patterns for all faults in the collapsed fault set
  - “random patterns” detect many faults – use deterministic method to detect the others (*FastScan*)
- Fault simulation
  - verify fault coverage of test patterns
  - simulate fault, apply test pattern, and observe output  
fault detected if output different from expected value
  - repeat for each fault & test pattern combination

# ATPG flow

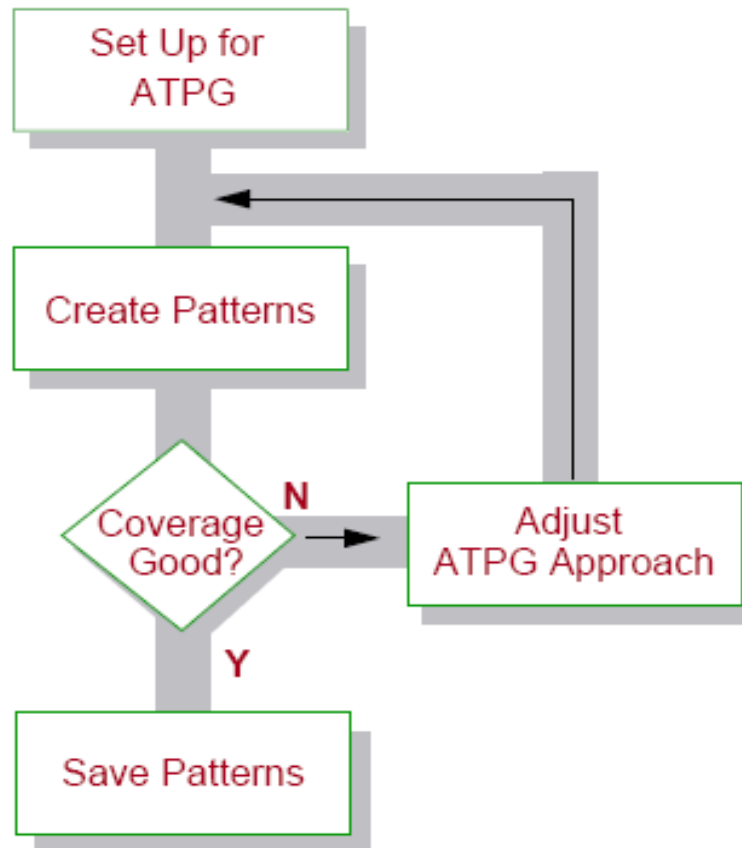


# Mentor Graphics “Tessent” *FastScan*

- Perform design for testability (DFT), ATPG, and fault simulation
  - **FastScan:** full-scan designs
    - Legacy: FlexTest: non-scan through full-scan designs*
- Typical flow:
  1. **Implement DFT**
  2. **Generate test patterns (ATPG)**
  3. **Verify fault coverage of patterns through fault simulation**
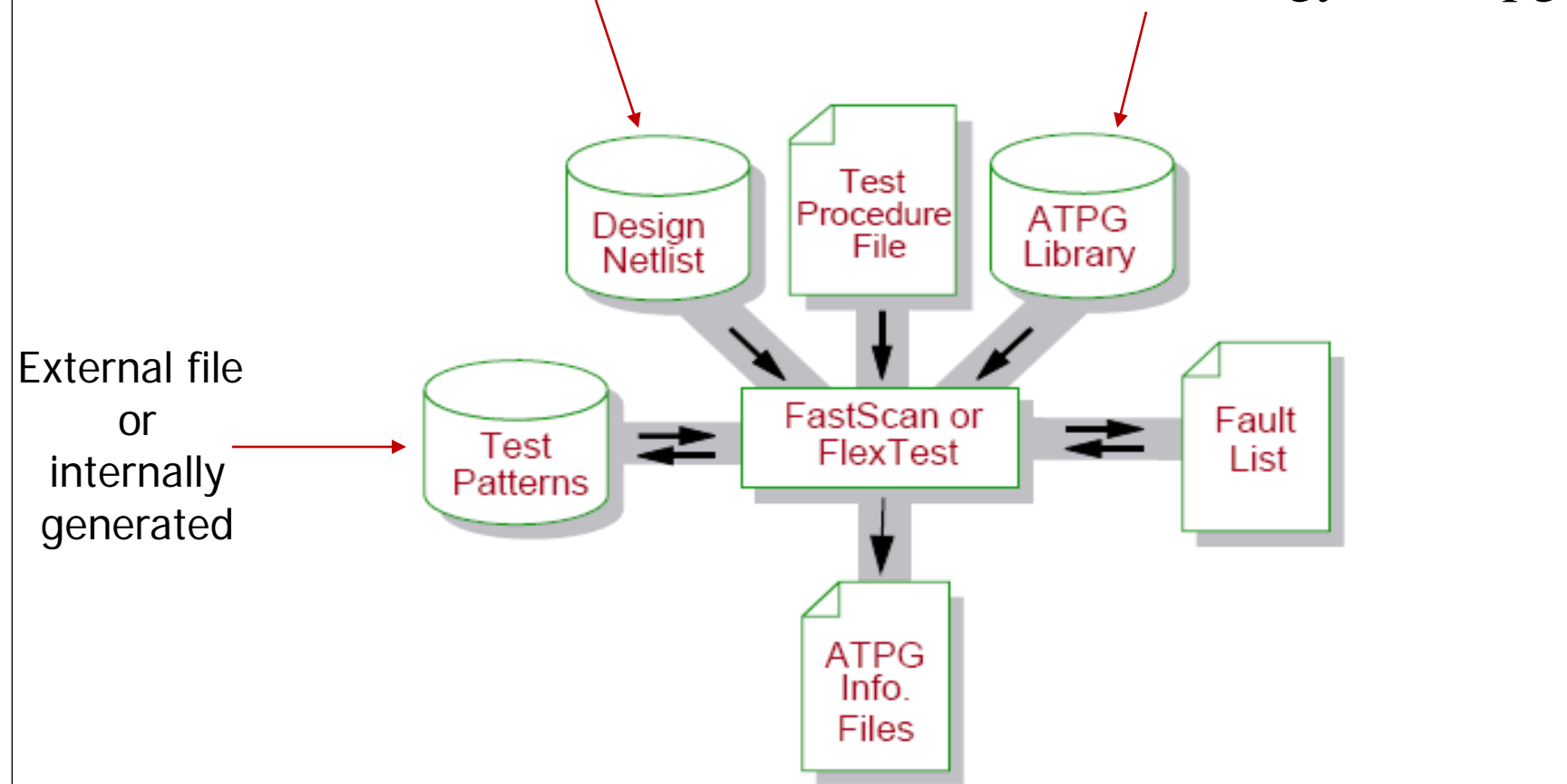
# FastScan inputs & outputs

file.v  
(from Leonardo)      \$ADK/technology/adk.atpg




# FastScan Flow

Setup mode

Flatten model,  
Study circuit,  
Perform DRC

Enter:  
Good/ATPG/Fault  
mode

Save patterns &  
fault lists

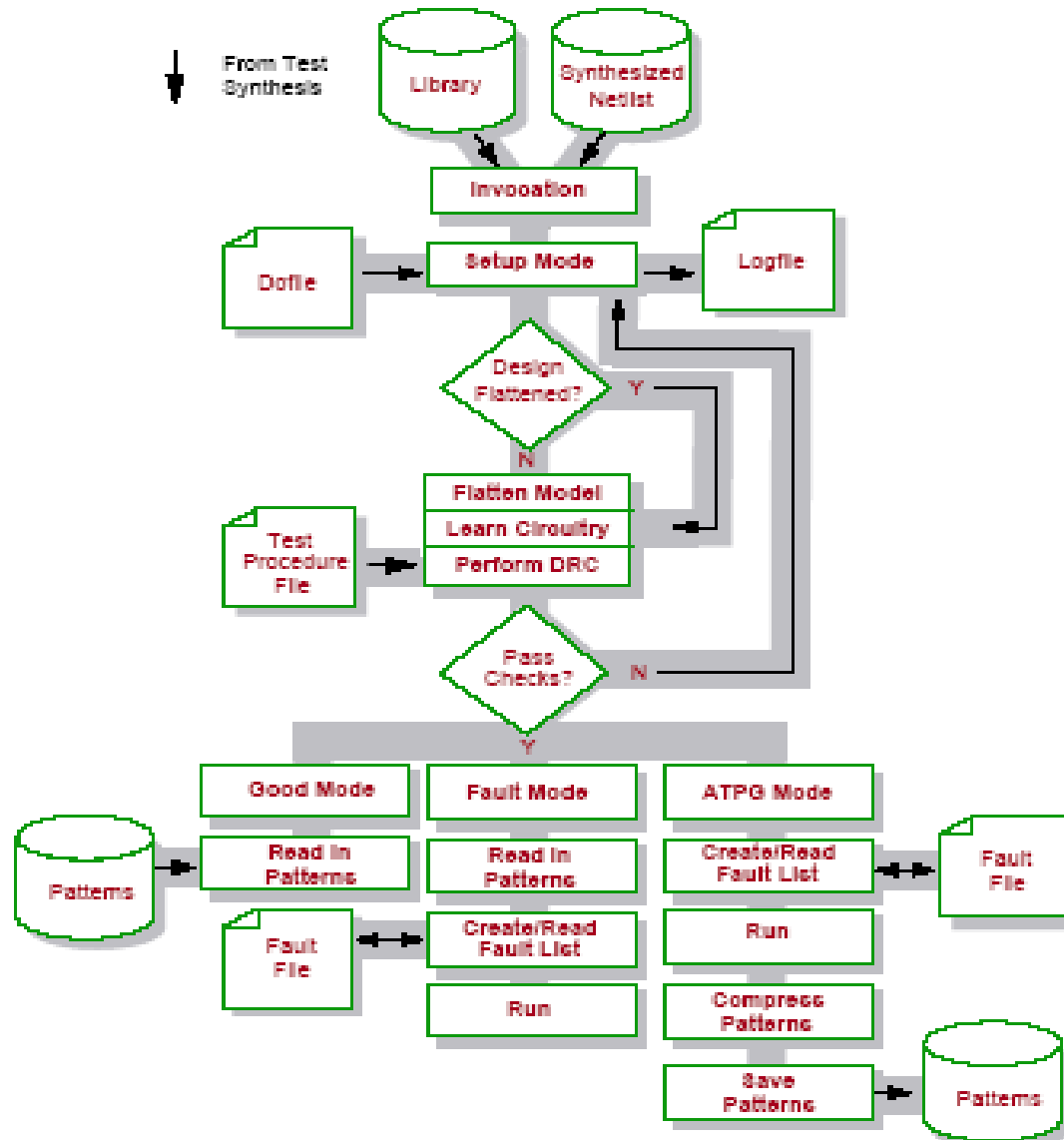

# Invoking FastScan

Command> `fastscan testckt.v -lib $ADK/technology/adk.atpg`


↑  
Verilog  
Netlist

↑  
ATPG Library

`-DOFile dofile_name`

↑  
Execute commands  
From "do file"
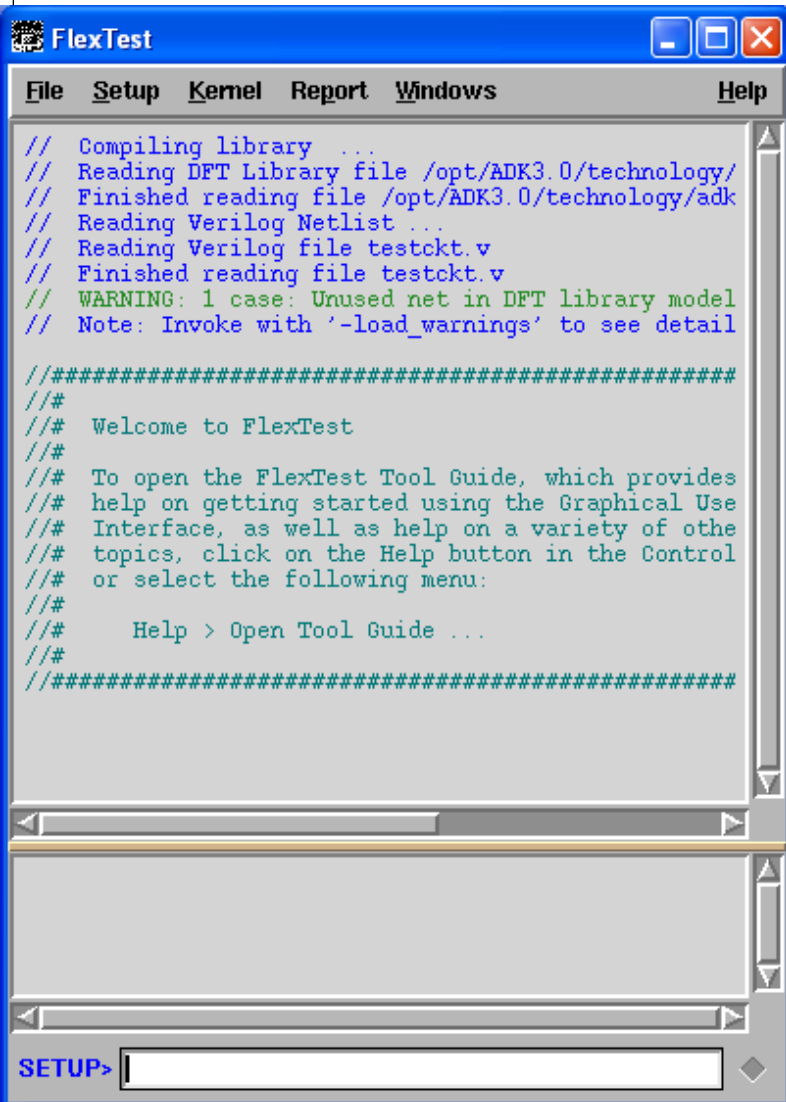
# “Legacy” FlexTest/FastScan control panel




```
FlexTest
File Setup Kernel Report Windows Help

// Compiling library ...
// Reading DFT Library file /opt/ADK3.0/technology/
// Finished reading file /opt/ADK3.0/technology/adk
// Reading Verilog Netlist ...
// Reading Verilog file testckt.v
// Finished reading file testckt.v
// WARNING: 1 case: Unused net in DFT library model
// Note: Invoke with '-load_warnings' to see detail

#####
//#
//# Welcome to FlexTest
//#
//# To open the FlexTest Tool Guide, which provides
//# help on getting started using the Graphical Use
//# Interface, as well as help on a variety of othe
//# topics, click on the Help button in the Control
//# or select the following menu:
//#
//# Help > Open Tool Guide ...
//#
#####

SETUP>
```

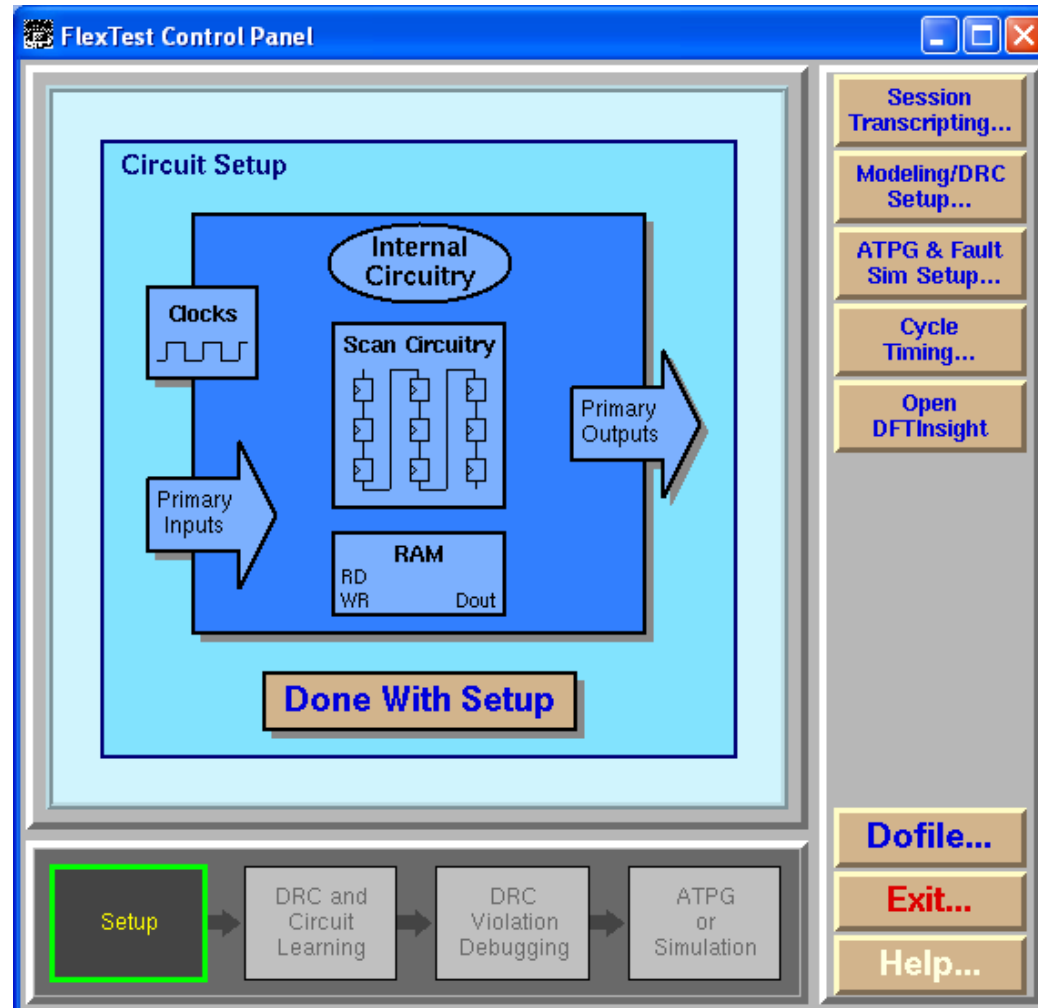


# “Legacy” FlexTest ATPG control panel

1. Select faults to be tested

3. Run the ATPG and fault simulation

4. Report results

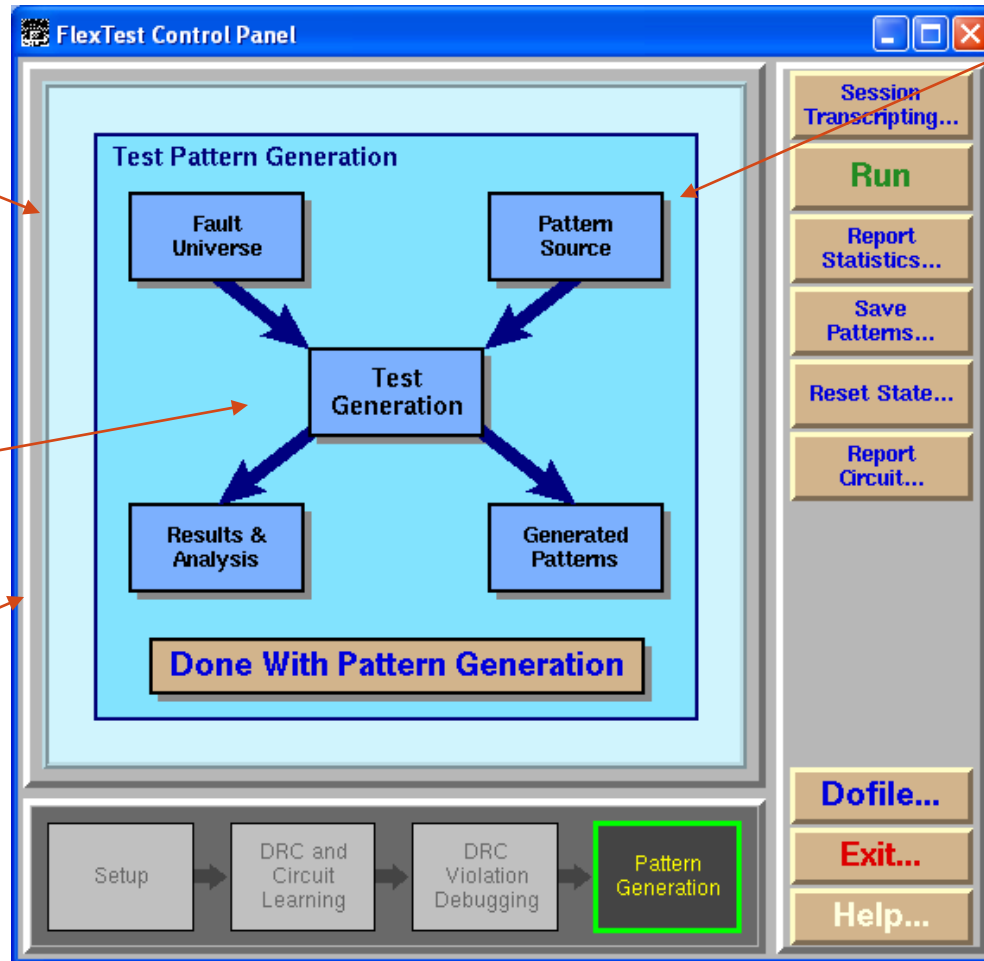

2. Select auto test patterns or external test file

# Design rule checks

Check for design issues that affect testability

Example: synchronous circuit DRC:

- System has a minimum number of clocks—optimally only one.
- Register all design inputs and account for metastability.
  - Treat metastability time as another delay in the path.
  - If the propagation delay plus the metastability time is less than the clock period, the system is synchronous.
  - If it is greater than or equal to the clock period, add an extra flip-flop to ensure the proper data enters the circuit.
- No combinational logic drives flip flop set/reset/clock inputs.
- No asynchronous signals set or reset the flip-flops.
- Buffers or other delay elements do not delay clock signals.
- Do not use logic to delay signals.
- Do not assume logic delays are longer than routing delays.

# Select fault types/models

- *set fault type Stuck* (default)
  - Fault model to be used for ATPG
  - Also: Iddq, Toggle, Transition, Path\_delay, Bridge
  - Can specify “multiple detection” # to require multiple detections of each fault
- *add faults -all*
  - add faults to current fault list, discarding all patterns and setting all faults to undetected
  - options for each fault model (ex. *Stuck\_at 01* or *1* or *0*)
- *load faults file* - load fault list from file
- *write faults file* – write fault list to file
- *report faults* – print list of modeled faults

# Select the test pattern source

- *set pattern source Internal*
  - Generate and use ATPG patterns
- *set pattern source External filename*
  - Load and use patterns from file
- *set pattern source Random*
  - Generate and use random patterns
- *set pattern source Bist*
  - BIST circuit generates patterns


# FastScan simulation modes

- Good – verify the simulation model
  - Use ATPG algorithm to generate test patterns
  - Apply patterns and capture outputs without simulating faults
  - Produces expected output for each test pattern
- Fault – determine fault coverage of a set of patterns
  - User provides a set of test patterns and fault list
  - Perform fault simulation using these patterns and faults to determine coverage
- ATPG -
  - Use ATPG algorithms to generate test patterns for given faults
  - Perform fault simulation using generated patterns to determine coverage of the ATPG-produced test set

# Fault simulation with external file selected as “Pattern Source” (“Table Pattern” option)

// FastScan test pattern file – define inputs

PI A  
PI B  
PI C  
PI D  
PI E  
PO Y

 


// test patterns – bits in above order

000100  
010000  
011111  
100111  
100010

Note: These were “random” patterns
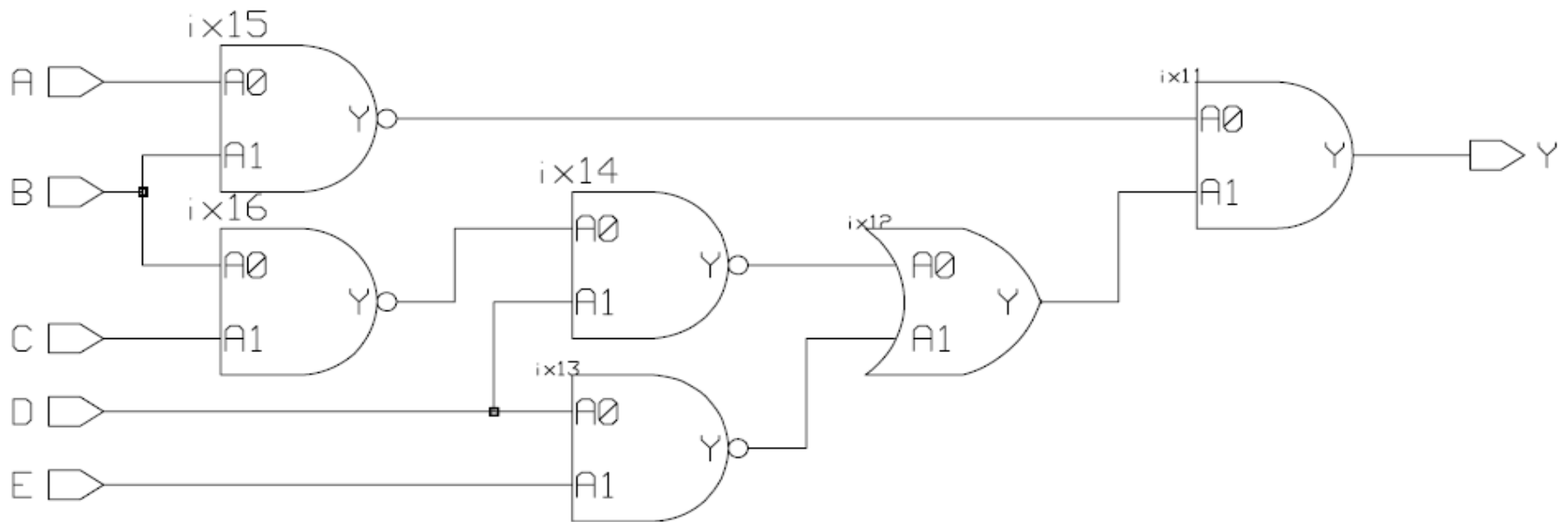
# Example circuit (Design Architect)

Net names appear in FastScan report on next page



# FastScan fault simulation results

1	RE	/ix14/A1	0	DS	/ix16/Y	0	DS	/ix12/A1
1	RE	/ix13/A0	0	DS	/ix14/A1	0	DS	/ix13/Y
1	DS	/ix15/A1	1	DS	/Y	0	DS	/Y
1	DS	/B	1	DS	/ix11/Y	0	DS	/ix11/Y
1	DS	/D	0	DS	/B	0	DS	/ix11/A0
0	DS	/D	1	DS	/ix14/A0	0	DS	/ix15/Y
1	DS	/ix11/A1	1	DS	/ix16/Y	0	DS	/ix11/A1
1	DS	/ix12/Y	0	DS	/ix16/A1	0	DS	/ix12/Y
1	DS	/ix12/A1	0	DS	/C	1	UO	/ix16/A1
1	DS	/ix13/Y	0	DS	/ix16/A0	1	UO	/C
0	DS	/ix13/A1	0	DS	/ix12/A0	1	UO	/ix16/A0
0	DS	/E	0	DS	/ix14/Y	1	UC	/ix11/A0
0	DS	/ix13/A0	1	DS	/ix15/A0	1	UC	/ix15/Y
1	DS	/ix12/A0	1	DS	/A	0	UC	/ix15/A0
1	DS	/ix14/Y	1	DS	/ix13/A1	0	UC	/A
0	DS	/ix14/A0	1	DS	/E	0	UC	/ix15/A1

Test coverage = 38 detected/48 faults = 79%


DS – fault detected in simulation

RE – redundant fault

UO – unobserved fault

UC – uncontrolled fault
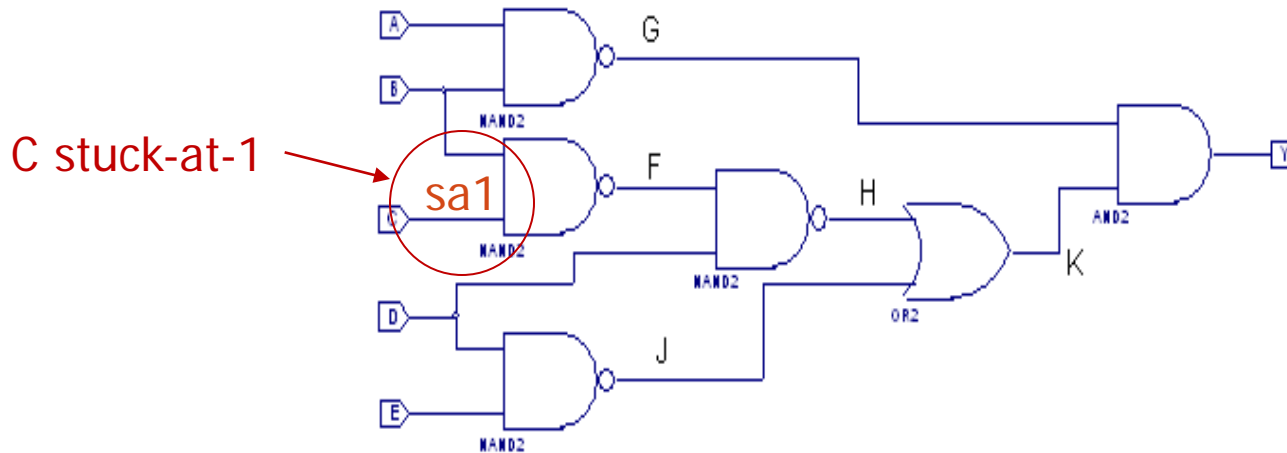
# Design individual tests for UC/UO faults



Step	A	B	C	D	E	F	G	H	J	K	Y
control			D*								
observe		1	D*			D					
observe				1		D		D*			
observe								D*	0	D*	
observe							1			D*	D*
Consistency - J				1	1				0		
Consistency - G	0	x					1				
Final values	0	x	D*	1	1	D	1	D*	0	D*	D*

Test vector: ABCDE = {01011} – Raised fault coverage to 80%

# Fault Simulation (Chap. 14.4)

- Deliberately induce faults to determine what happens to circuit operation
- Access limited to primary inputs (PIs) & primary outputs (POs)
- Apply pattern to PIs at start of test cycle
- At end of test cycle, compare POs to expected values
- Fault detected if POs differ from correct values
- Fault coverage = detected faults / modeled faults

# Fault simulation types

- Serial – simulate two copies of circuit
  - One good circuit
  - One with a single fault injected
  - Repeat for each possible faulty circuit (slow)
- Parallel – simulate N copies of the circuit in parallel
  - N-bit data word holds values of a given signal line in each copy
- Concurrent – Simulate the good circuit, and then only those parts affected by each fault
  - Different faults affect different parts of the circuit
  - Simulate those faults concurrently

# Fault simulation types (continued)

- Deterministic fault simulation:
  - Determine which faults are detected by a test set (as in serial, parallel & concurrent)
- Probabilistic fault simulation:
  - Simulate a subset of faults and extrapolate coverage from the sample
- Statistical fault simulation:
  - Predict coverage from fault-free simulation, based on ability to control/observe nodes