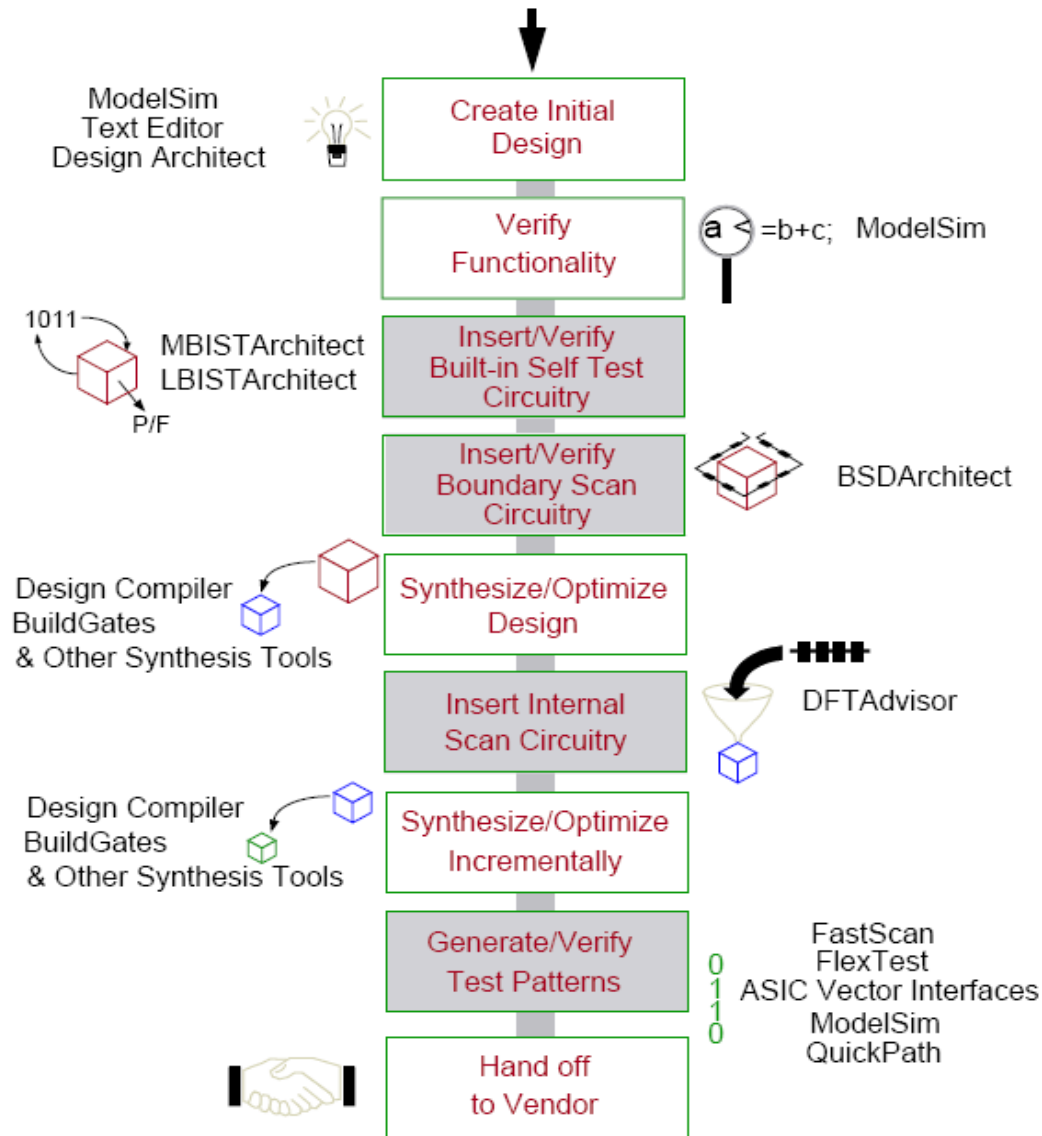


Built-In Self Test

Smith Text: Chapter 14.7


Top-down test design flow




Built-In Self-Test (BIST)

- Structured-test techniques for logic circuits to improve access to internal signals from primary inputs/outputs
- BIST procedure:
 - generate a test pattern
 - apply the pattern to “circuit under test” (CUT)
 - check the response
 - repeat for each test pattern
- Most BIST approaches use pseudo-random test vectors

Logic BIST architecture

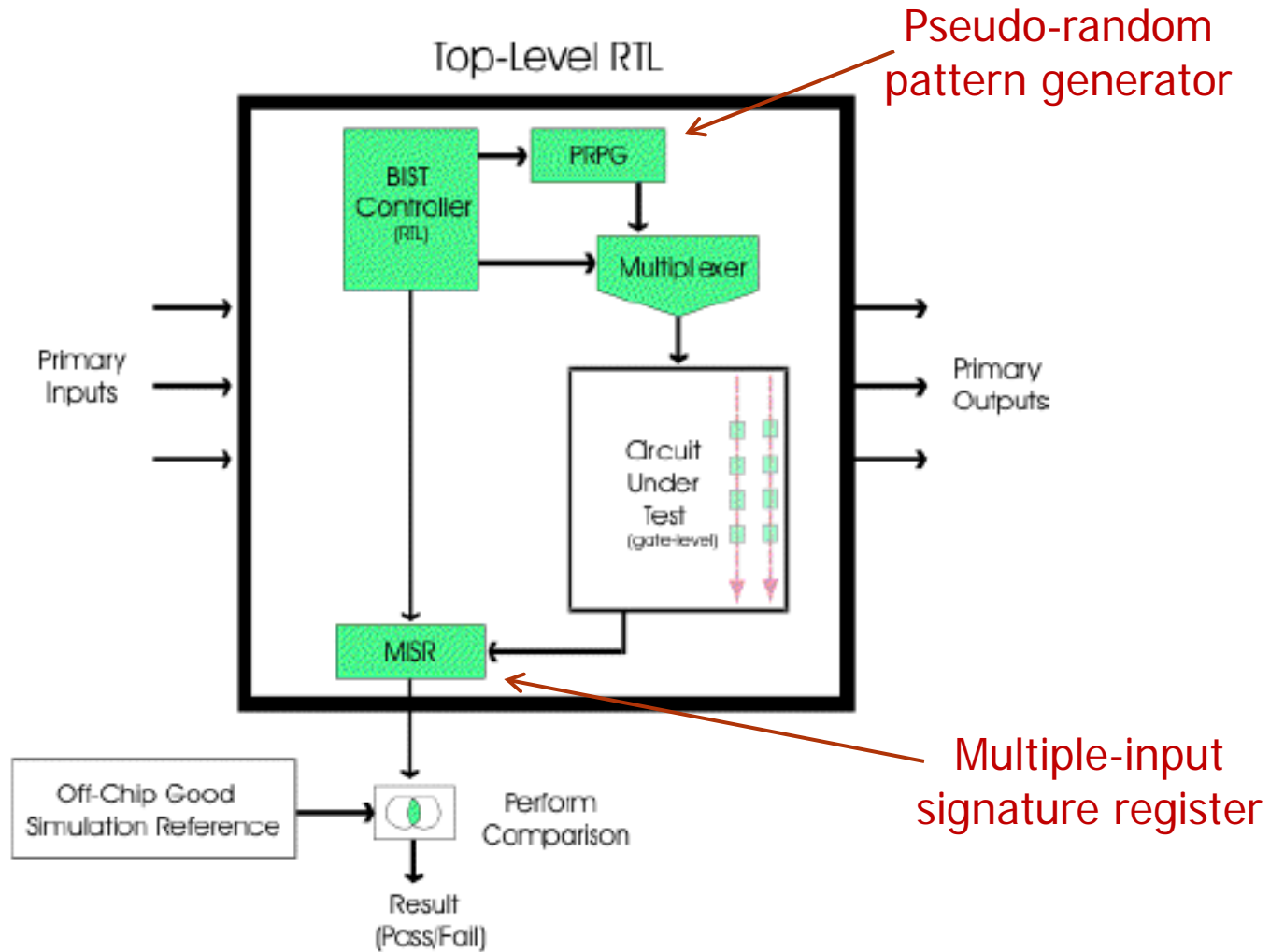


Logic BIST general architecture

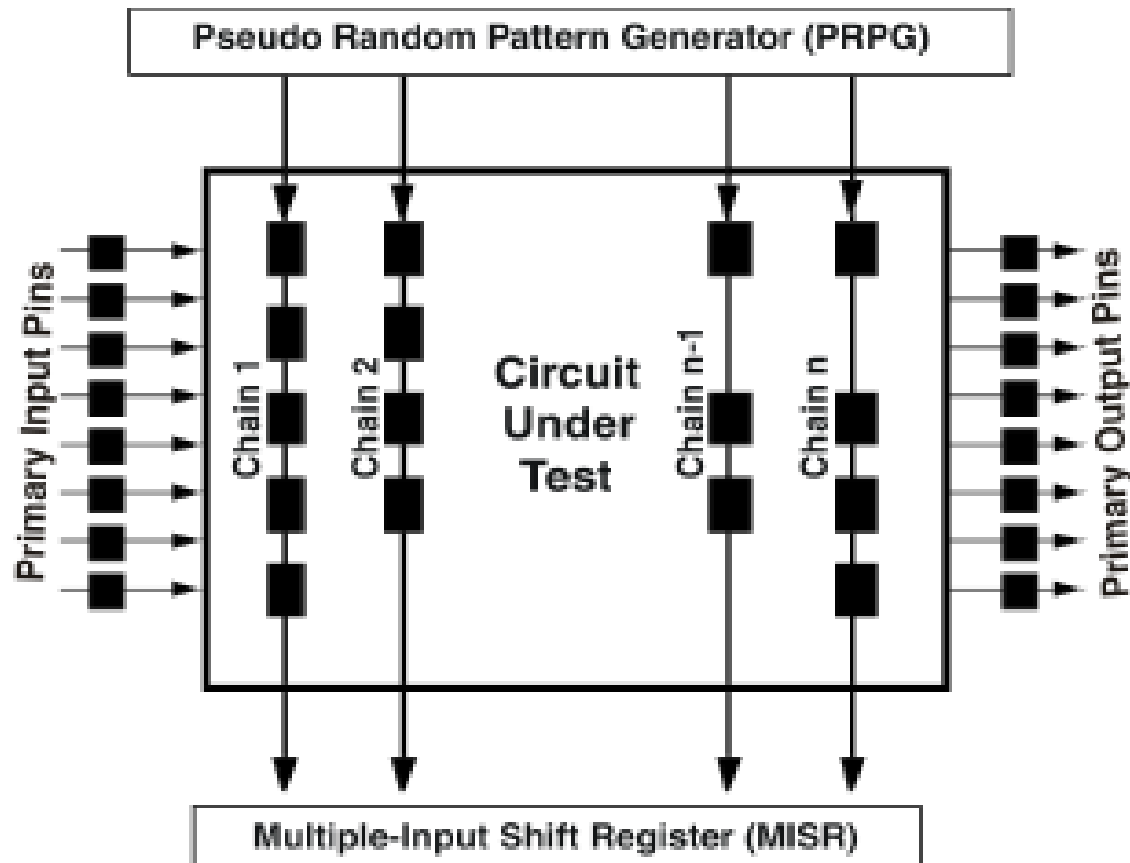

Memory BIST architecture

BIST controller generates & applies patterns

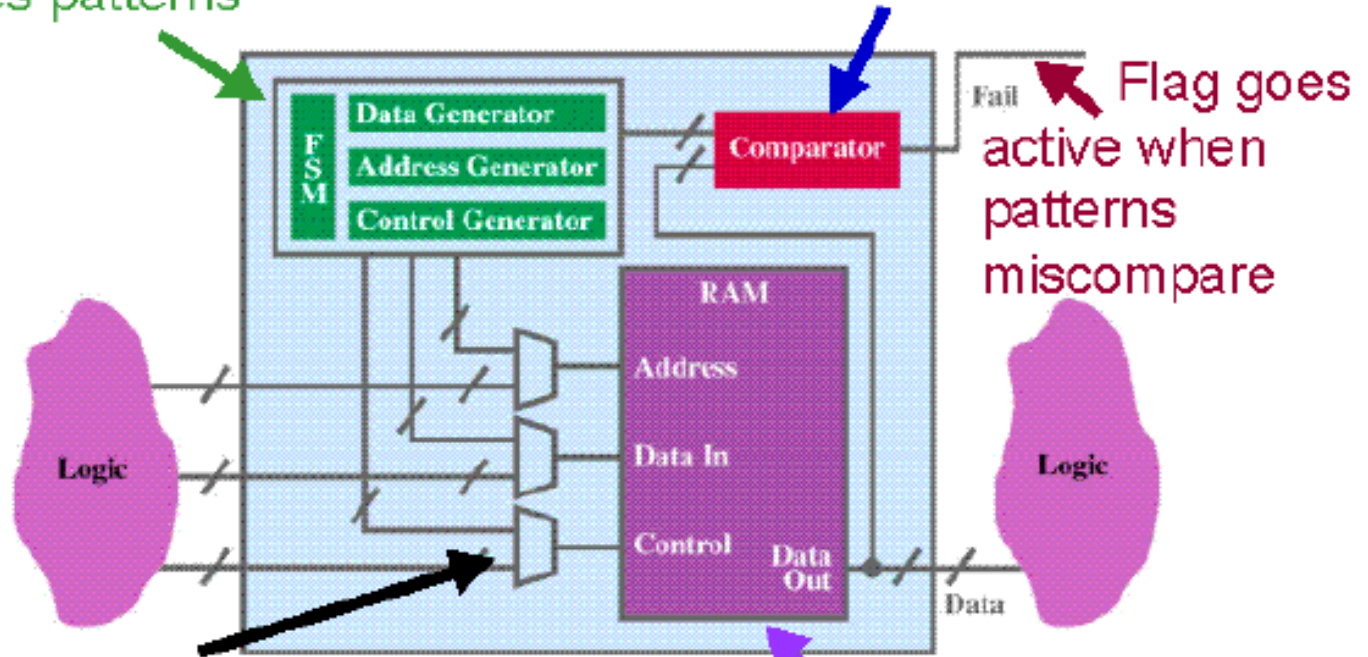Comparator compares patterns applied to/read from memory




Flag goes active when patterns mismatch

Multiplexers select between system and test data


Memory with BIST

LBIST Process Flow

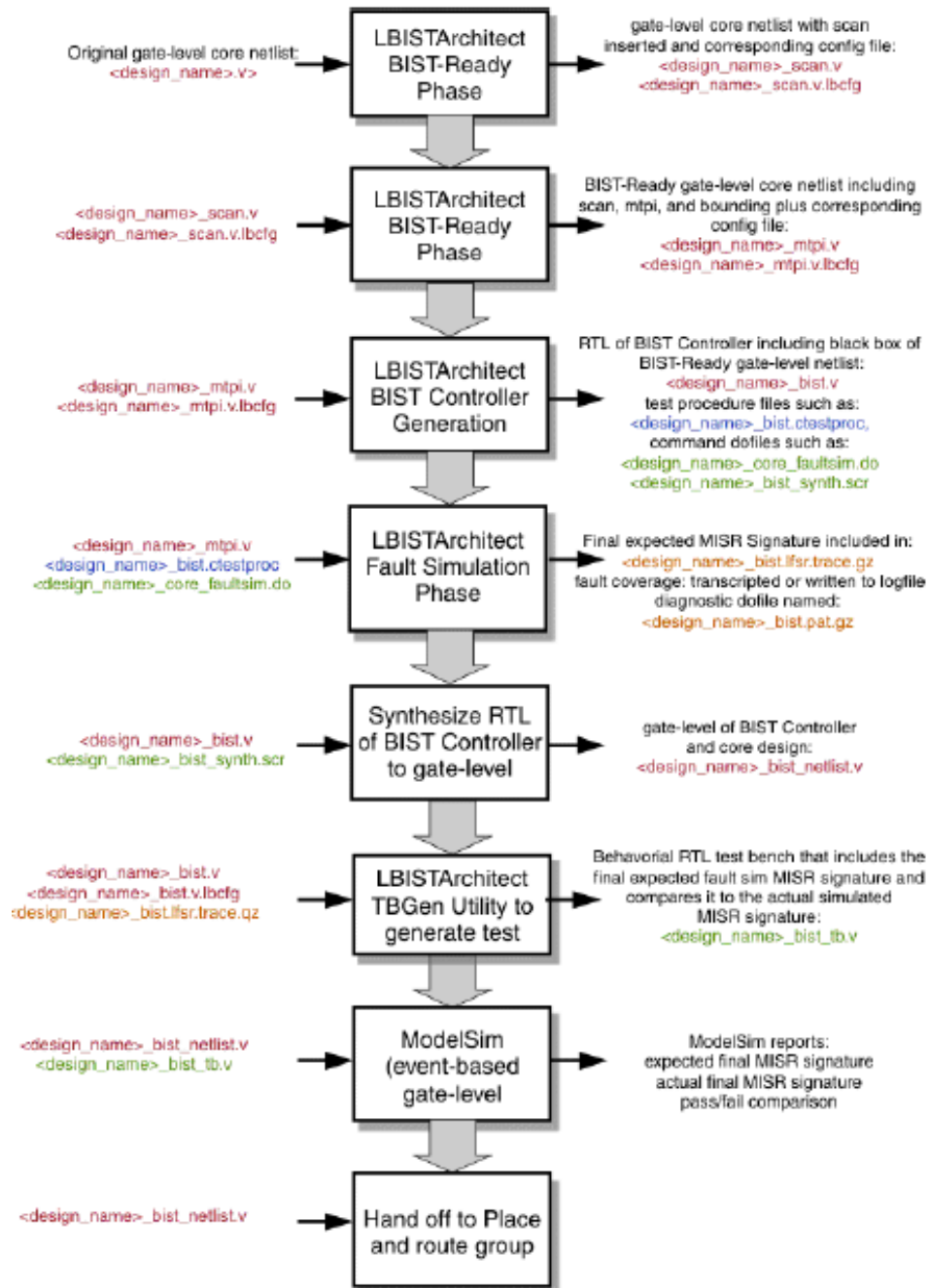


Linear Feedback Shift Register (LFSR)

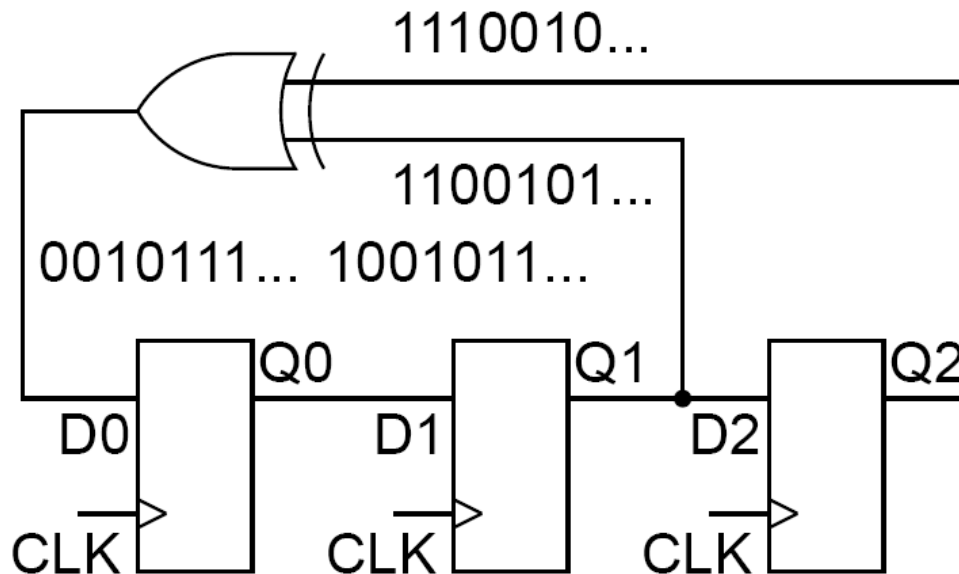- Produce pseudorandom binary sequences (PRBS)
- Implement with shift register and XOR gates
- Selection of feedback points allows n-bit register to produce a PRBS of length $2^n - 1$



LFSR produces
pattern:
7,3,1,4,2,5,6
(PRBS length 7)


4-stage LFSR with one tap point

 

<u>State</u>	<u>Pattern</u>	<u>State</u>	<u>Pattern</u>
0	1000	8	1101
1	1100	9	0110
2	1110	10	0011
3	1111	11	1001
4	0111	12	0100
5	1011	13	0010
6	0101	14	0001
7	1010	15	1000

Serial Input Signature Register (SISR)

 - Use an LFSR to compact serial input data into an n-bit “signature”
- For sufficiently large n, two different sequences producing the same signature is unlikely
- Good circuit has a unique signature




Initialize LFSR
to '000' via RES.

Signature formed
via shift & add

BIST Example (Fig. 14.25)

Pattern generator


Signature analyzer

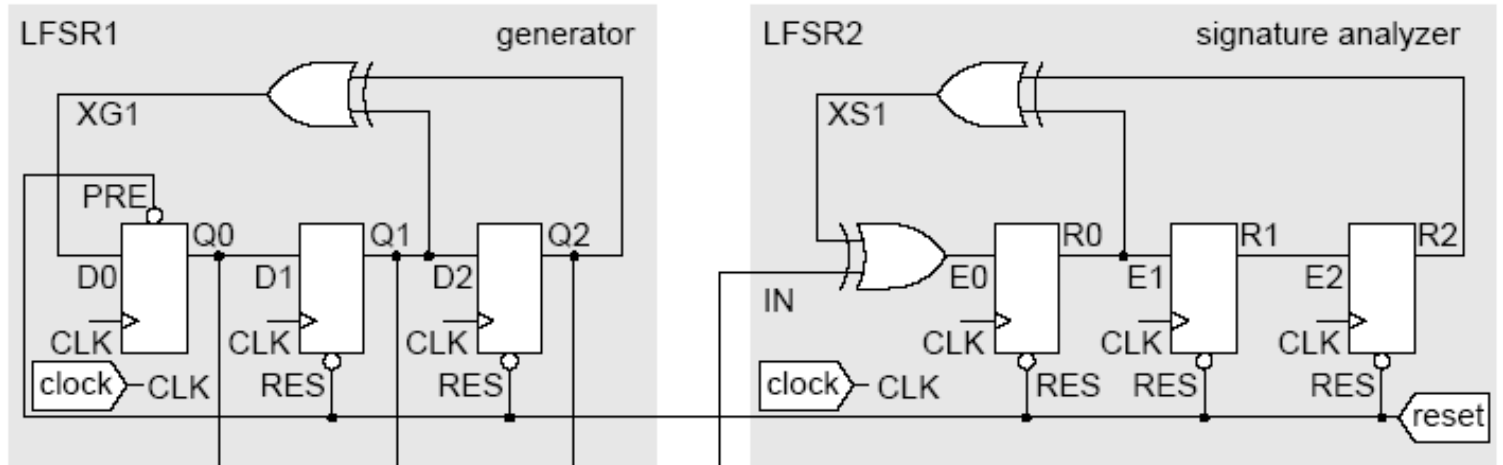

Generated test patterns

good	1011100	0101110	0010111
bad	1011100	0101110	0010111

01001100	00111110	00011111	00001111
01011100	00111000	00011100	00001110

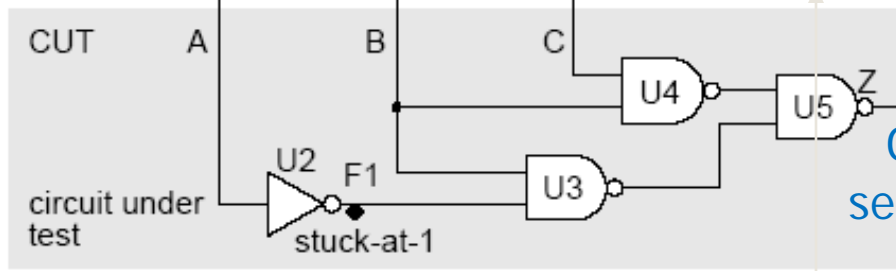

Output sequences

signatures:
 good = hex 3 = 011
 R0 = 0, R1 = 1, R2 = 1
 bad (F1) = hex 0 = 000
 R0 = 0, R1 = 0, R2 = 0

Circuit under test

Signatures

Aliasing

- Good and bad circuits might produce the same signature (“aliasing”) – masking errors
- Previous example:
 - 7-bit sequence applied to signature analyzer
 - $2^7 = 128$ possible patterns
 - 3-bit signature register: $2^3 = 8$ possible signatures
 - $128/8 = 16$ streams can produce the good signature: 1 corresponds to good circuit, 15 to faulty circuits
(assume all bit streams equally likely)
 - $128-1 = 127$ streams correspond to bad circuits
 - $15/127 = 11.8\%$ of bad bit streams produce the good signature, and therefore will be undetected
(Probability of missing a bad circuit = 11.8%)

Aliasing – Error Probability

- Given test sequence length L & signature register length R
- Probability of aliasing is:

- For $L \gg R$:

$$p = \frac{2^{L-R} - 1}{2^L - 1}$$

- Use long sequences to minimize aliasing

$$p \approx 2^{-R}$$

LFSR Theory (chap 14.7.5)

- Operation based on polynomials and Galois-field theory used in coding
- Each LFSR has a “characteristic polynomial”
 - Called a “primitive polynomial” if it generates a maximum-length PRBS
 - General form: $P(x) = c_0 \oplus c_1x^1 \oplus \dots \oplus c_nx^n$
 c_k always 0 or 1, $\oplus = \text{xor}$
 - Reciprocal of $P(x)$ is also primitive:
 $P^*(x) = x^n P(x^{-1})$
- LFSR can be constructed from $P(x)$ or $P^*(x)$


Primitive polynomial examples

- $P(x) = 1 \oplus x^1 \oplus x^3$
 - Order: $n = 3$
 - Coefficients: $c_0=1, c_1=1, c_2=0, c_3=1$
 - LFSR feedback taps: $s = 0, 1, 3$
(non-zero coefficients)

- $P^*(x) = 1 \oplus x^2 \oplus x^3$

“Type 1” LFSR schematic
 
$$P(x) = 1 \oplus c_1x \oplus \dots \oplus c_{n-1}x^{n-1} \oplus x^n$$




$$\text{or } P^*(x) = 1 \oplus c_{n-1}x \oplus \dots \oplus c_1x^{n-1} \oplus x^n$$

If $c_k=1$ add feedback connection & xor gate in position k


Four LFSR structures for every primitive polynomial

Type 1

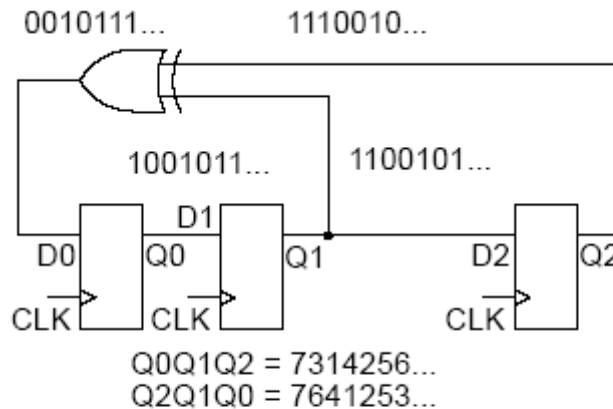- external XOR
- easy to build from existing registers
- Q outputs delayed by 1 clock (test seq's are correlated)




Type 1, $P^*(x)$ (a)

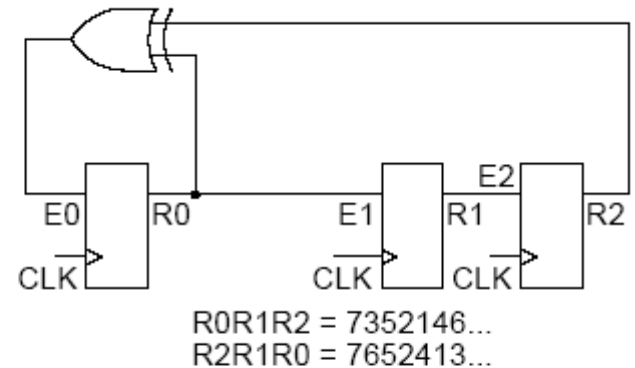


Type 1, $P(x)$ (b)

Type 2

 - internal XOR
- fewer series XORs (faster)
- outputs not correlated
- usually used for BIST



Type 2, $P(x)$ (c)

 

Type 2, $P^*(x)$ (d)

$$P(x) = 1 \oplus x \oplus x^3$$

$$P^*(x) = 1 \oplus x^2 \oplus x^3$$

Common LFSR Configurations

Table 2-1. Common LFSR Configuration

LFSR Length	Primitive Polynomial	Tap Points (“in”/Type2)	Tap Points (“out”/Type1)
8-bits	$x^8+x^4+x^3+x^2+1$	6, 5, 4	4, 3, 2
16-bits	$x^{16}+x^5+x^4+x^3+1$	13, 12, 11	5, 4, 3
24-bits	$x^{24}+x^7+x^2+x+1$	23, 22, 17	7, 2, 1
32-bits	$x^{32}+x^{22}+x^2+x+1$	31, 30, 10	22, 2, 1


Source: Mentor Graphics “LBISTArchitect Process Guide”

Also see Figure 14.27 and Table 14.11 in the Smith Text

Multiple-Input Signature Register (MISR)

- Reduce test logic by using multiple bit streams to create a signature
- BILBO (built-in logic block observer) – uses MISR as *both* PRBS generator and signature register

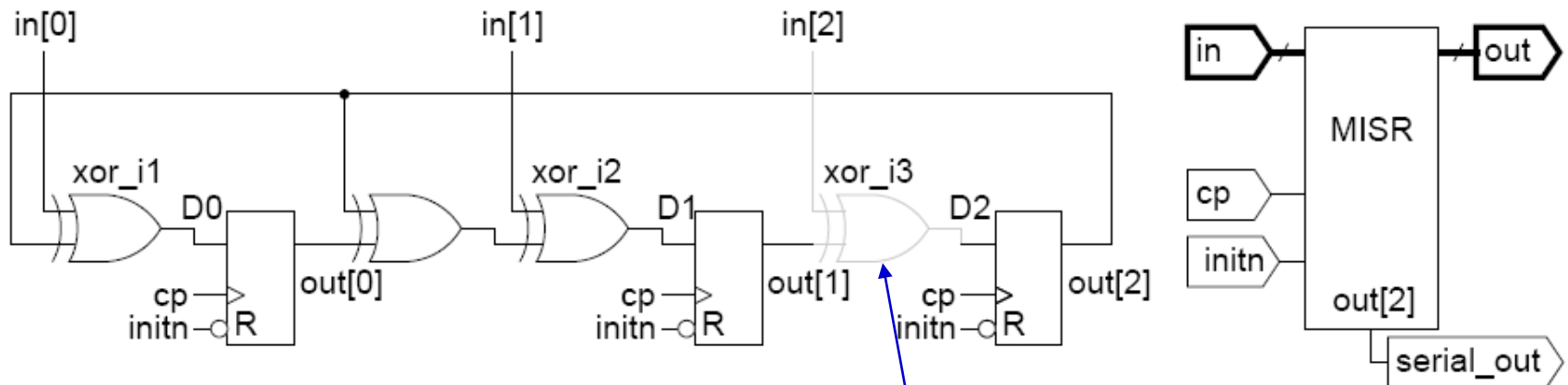Example: MISR from Type 2 LFSR with $P^*(x) = 1 \oplus x^2 \oplus x^3$




omit xor_i3 if only 2 outputs to test


Mentor Graphics Tools

- LBISTArchitect
 - logic BIST design & insertion
 - Reference: “LBISTArchitect Process Guide”
- MBISTArchitect
 - memory BIST design & insertion


Architecture produced by LBISTArchitect

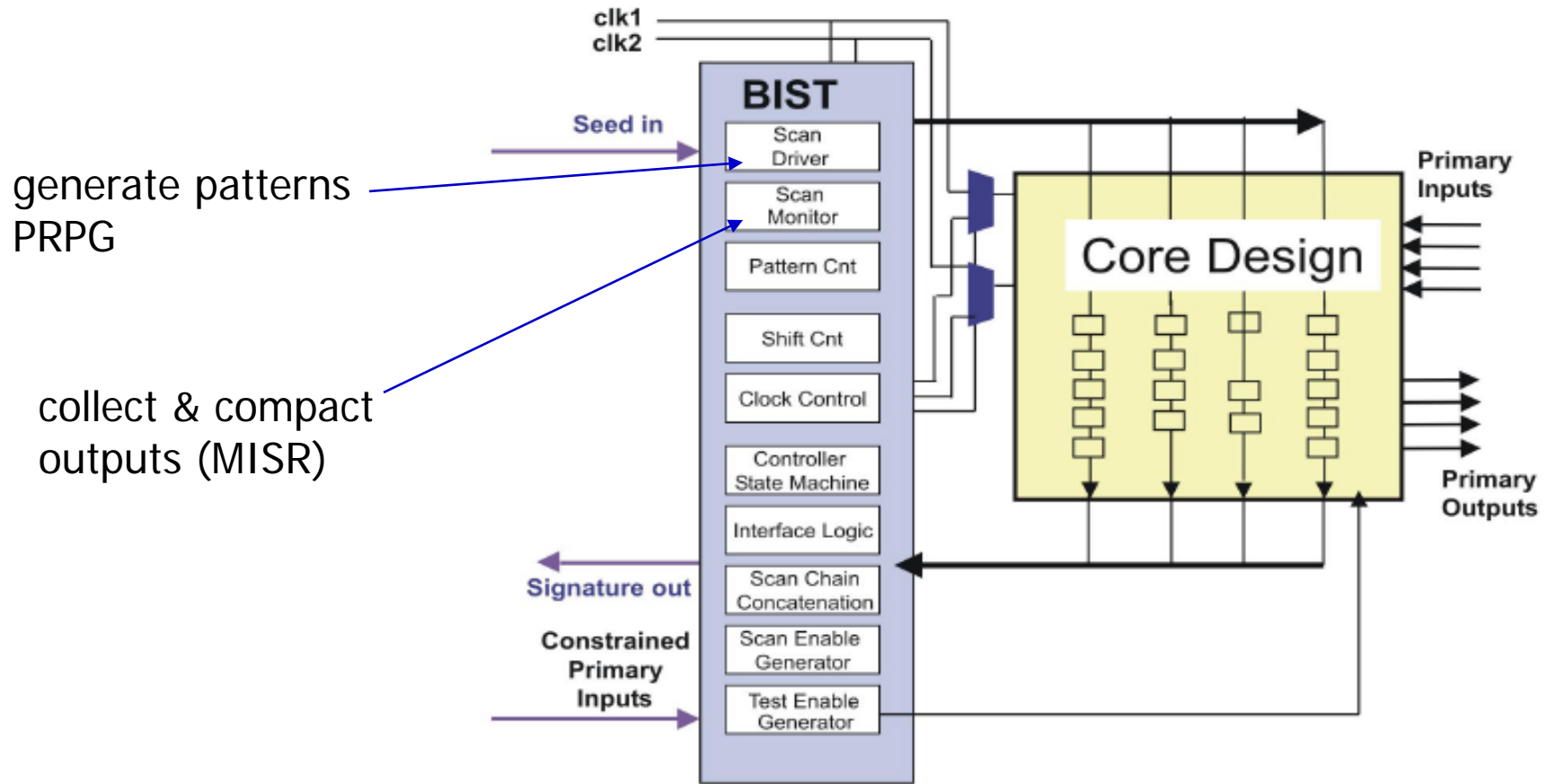

Logic BIST design flow

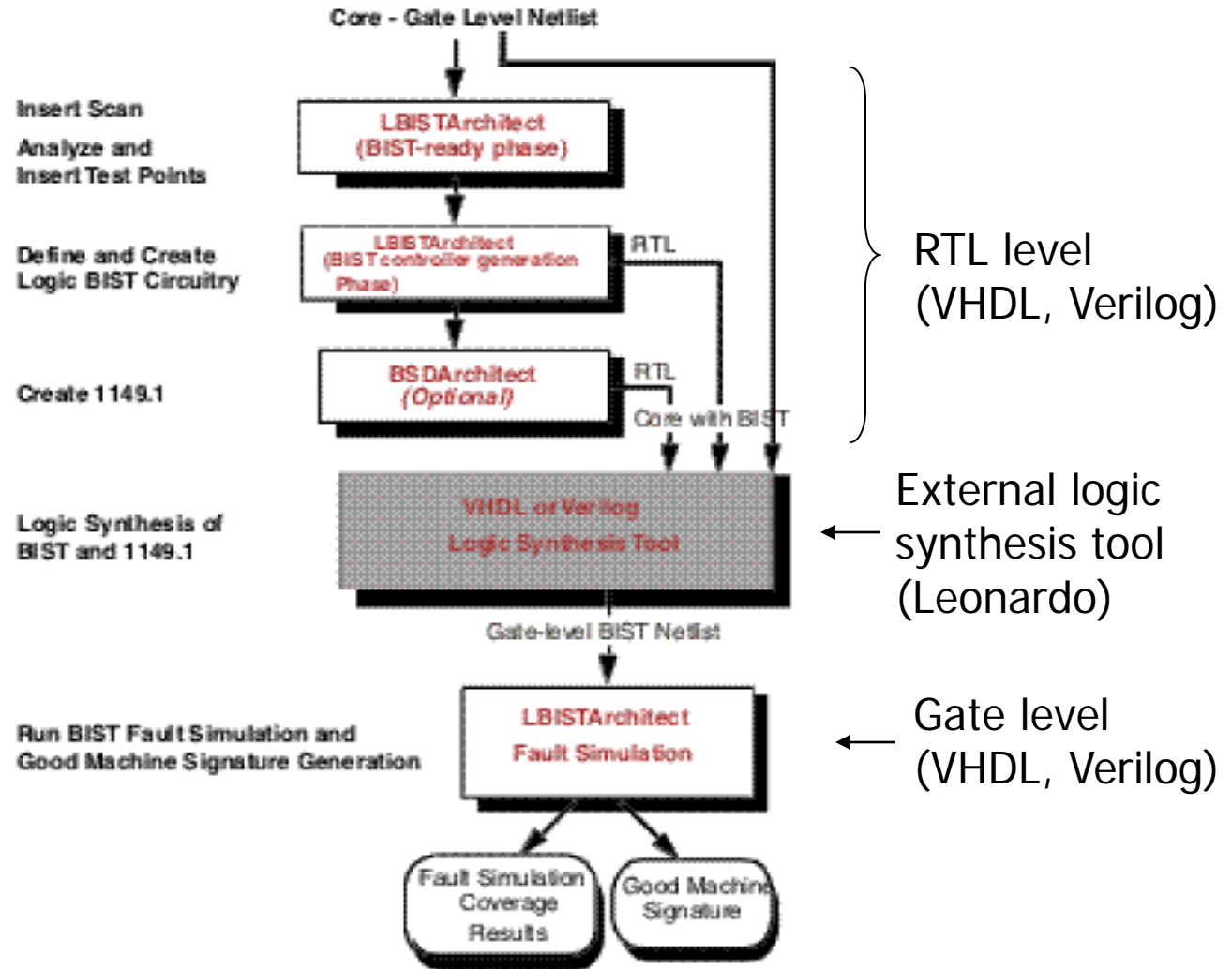


Logic BIST Flow

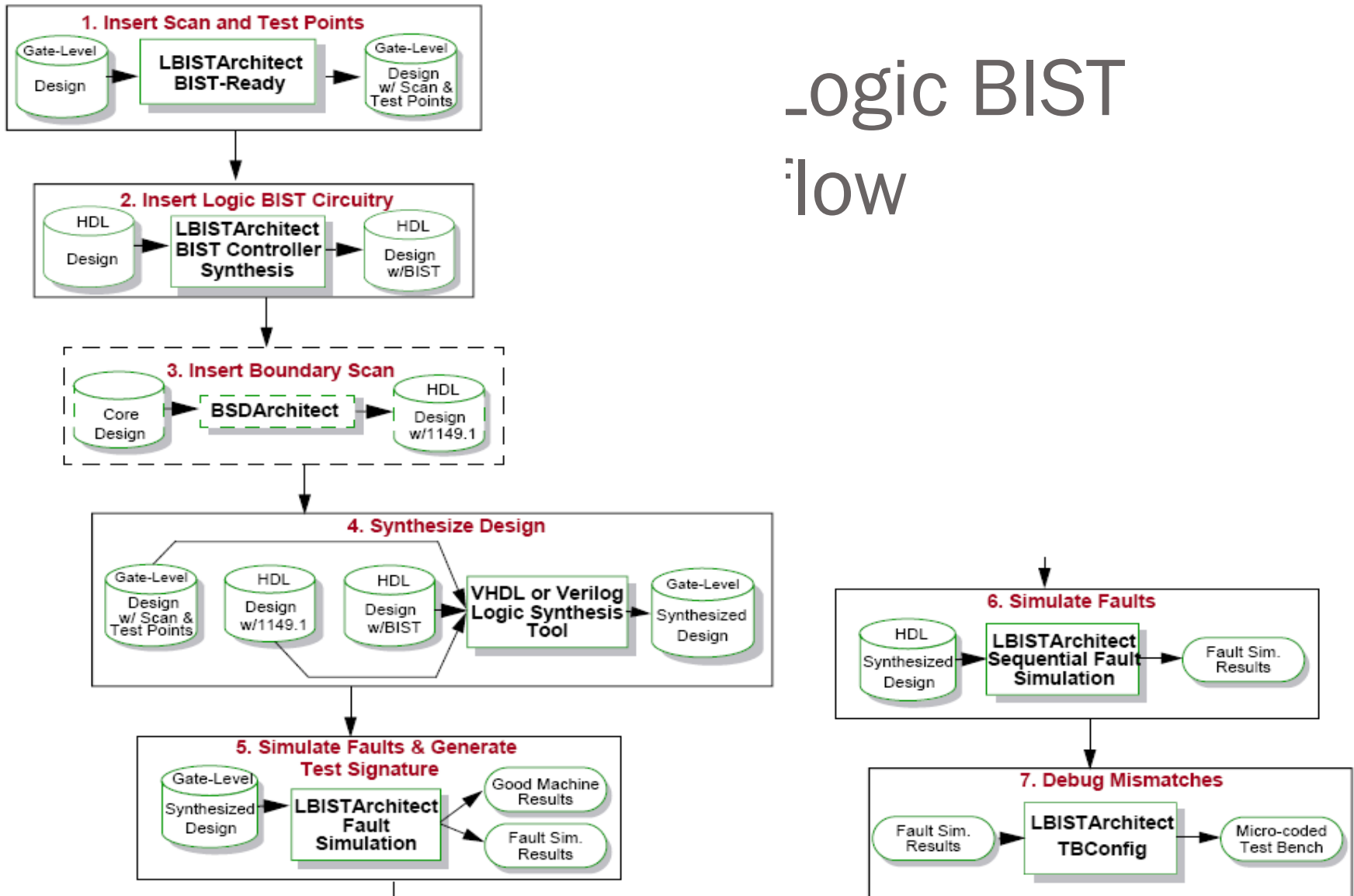

Source: Mentor Graphics "LBISTArchitect Process Guide"

Logic BIST insertion flow

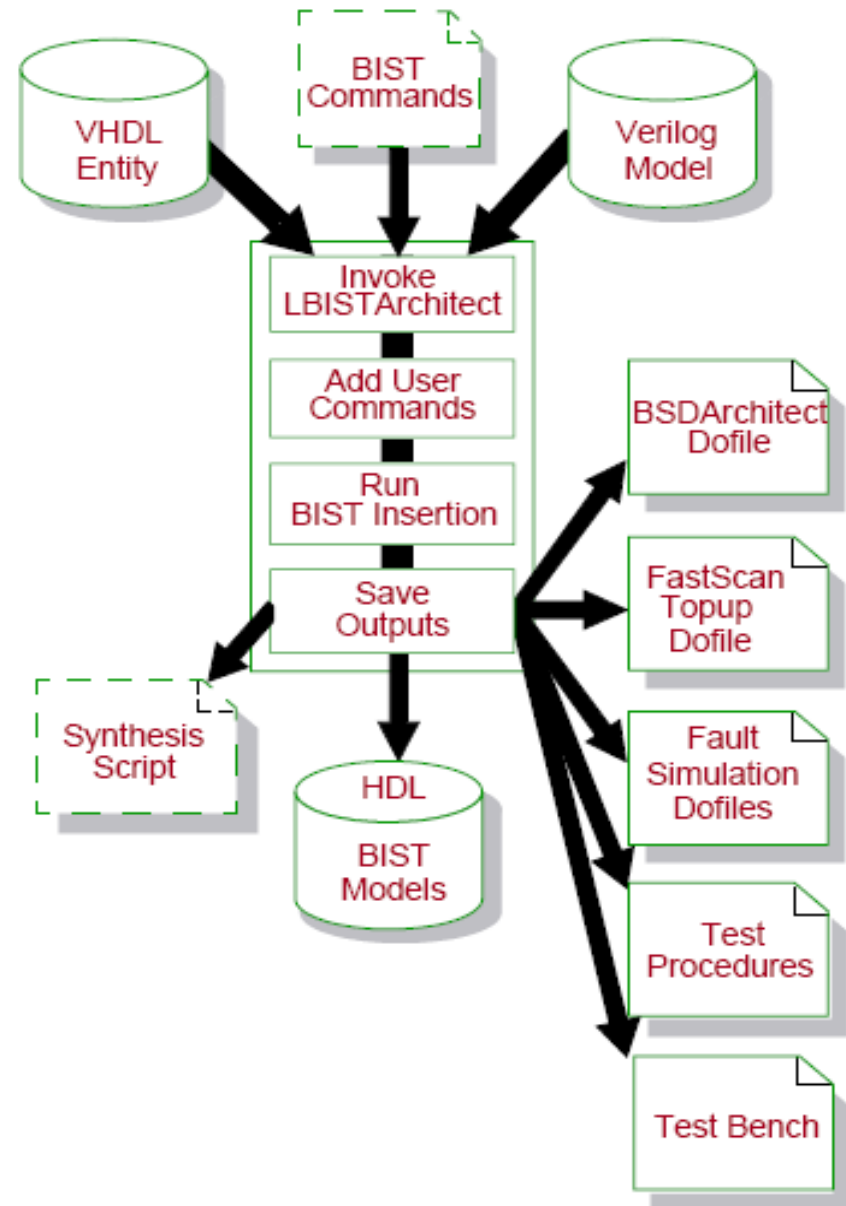

Logic BIST design phases

- BIST-Ready:
 - check design for testability
 - insert scan circuits & test points
- BIST Controller Generation:
 - produce synthesizable RTL model (VHDL, Verilog)
 - includes scan driver/PRPG, scan monitor/MISR
- Boundary Scan Insertion (optional)
 - BSDarchitect can tie 1149.1 to logic BIST
 - inserts boundary scan ckts & TAP controller

LOGIC BIST design phases (2)

- Fault simulation & signature generation
 - determine fault coverage of BIST patterns
 - generate signature of “good circuit”
- Sequential fault simulation (optional)
 - determine fault coverage of BIST hardware
- BIST verification (optional)
 - generate test bench for full simulation
- Manufacturing diagnostics (optional)
 - generate info to assist in fault diagnosis

BIST-ready phase: test point insertion

- Add control test points to gain access to inputs of difficult-to-test gates
- Add observe test points to gain access to outputs of difficult-to-test gates
- MTPI: Multiphase Test Point Insertion
 - break test into phases (ex. 256 patterns each)
 - activate only test points used in a phase
 - add points to improve detection of faults not detected in previous test phases

MTPI Example

Table 2-2. Four-Phase Test Point Control Activity

Phase	Patterns	Activity
0	1—256	No active TP controls
1	257—512	1st TP control active
2	513—768	2nd TP control active
3	769—1024	3rd TP control active

