

# VHDL Modeling for Synthesis

Combinational Logic Circuits

# VHDL synthesis references

---

- ▶ “**LeonardoSpectrum** HDL Synthesis Manual”
  - ▶ Access from Leonardo “Help” menu or
  - ▶ mgcdocs \_bk\_leospec.pdf
  
- ▶ **Smith Text: Chapter 12**
  - ▶ VHDL and Verilog synthesis examples
  - ▶ **Synopsys Design Compiler (DC)** used for book examples
  - ▶ **Synopsys DesignVision** is the GUI interface to DC



# Common types of synthesized circuits

---

- ▶ **Combinational logic circuits** (12.6.2 – 12.6.5)
  - ▶ random logic (12.6.2)
  - ▶ multiplexers (12.6.3)
  - ▶ decoders (12.6.4)
- ▶ **Arithmetic functions** (12.6.5, 12.6.9, 12.6.10)
- ▶ **Sequential logic (registers)** (12.6.6)
  - ▶ synchronous & asynchronous inputs
- ▶ **Shift registers** (12.6.8)
- ▶ **Finite state machines** (12.7, 12.7.2)
- ▶ **Memory synthesis** (12.8, 12.8.2)



# Combinational logic

---

-- Specify behavior via concurrent signal assignments

entity Gates is

port (a, b, c: in BIT; d: out BIT);

end Gates;

architecture behavior of Gates is

signal e: BIT;

Begin

-- concurrent signal assignment statements

e <= (a and b) xor (not c); -- synthesize gate-level ckt

d <= a nor b and (not e); -- in target technology

end;

---



# VHDL “Process” Construct

---

- ▶ Allows conventional programming language methods to describe circuit behavior
- ▶ Supported language constructs (“sequential statements”) – **only allowed within a process:**
  - ▶ variable assignment
  - ▶ if-then-else (elsif)
  - ▶ case statement
  - ▶ while (condition) loop
  - ▶ for (range) loop



# Process Format

---

```
[label:] process (sensitivity list)  
    declarations  
begin  
    sequential statements  
end process;
```

- ▶ Process statements executed once at start of simulation
- ▶ Process halts at “end” until an event occurs on a signal in the “sensitivity list”



# Combinational logic via process

---

-- All signals referenced in process must be in the sensitivity list.

entity And\_Good is

port (a, b: in BIT; c: out BIT);

end And\_Good;

architecture Synthesis\_Good of And\_Good is

begin

process (a,b) -- gate sensitive to events on (a, b)

begin

c <= a and b; -- c updated on a or b “events”

end process;

end;



# Combinational logic via process

---

-- This example produces unexpected results.

```
entity And_Bad is
```

```
    port (a, b: in BIT; c: out BIT);
```

```
end And_Bad;
```

```
architecture Synthesis_Bad of And_Bad is
```

```
begin
```

```
    process (a)          -- this should be process (a, b)
```

```
    begin
```

```
        c <= a and b; -- will not react to changes in b
```

```
    end process;
```

```
end Synthesis_Bad;
```

-- synthesis tool may generate a flip flop, triggered by signal a

---




# Structural architecture example (no “behavior” specified)

---

architecture structure of full\_add1 is

```
component xor      -- declare component to be used
    port (x,y: in bit;
          z: out bit);
end component;
for all: xor use entity work.xor(eqns); -- if multiple arch's
signal x1: bit;      -- signal internal to this component
begin
    G1: xor port map (a, b, x1);      -- instantiate 1st xor gate
    G2: xor port map (x1, cin, sum); -- instantiate 2nd xor gate
    ...add circuit for carry output...
end;
```

 

# Half adder “structural” architecture

---

architecture Netlist of Half\_Adder is

-- declare all components to be used

component MyXor -- component with formals

port (A\_Xor,B\_Xor : in BIT; Z\_Xor : out BIT);

end component;

component MyAnd -- component with formals

port (A\_And,B\_And : in BIT; Z\_And : out BIT);

end component;

begin

-- instantiate components:

Xor1: MyXor port map (X, Y, Sum); -- instance with actuals

And1: MyAnd port map (X, Y, Cout); -- instance with actuals

end;

---



# Cells defined in an ASIC vendor library

---

## -- AND2 Cell

entity AndGate is

```
    port (Ain_1, Ain_2 : in BIT; A_out : out BIT); -- formals
```

end;

architecture Simple of AndGate is

begin

```
    Aout <= Ain_1 and Ain_2;
```

end;

## -- XOR2 Cell

entity XorGate is

```
    port (Xin_1, Xin_2 : in BIT; Xout : out BIT); -- formals
```

end;

architecture Simple of XorGate is

begin

```
    Xout <= Xin_1 xor Xin_2;
```

end;

File adk.vhd contains  
models of all ADK  
standard cells.



# Associating signals with formal ports

---

```
component AndGate port
    (Ain_1,Ain_2 : in BIT;      -- formal parameters
     Aout : out BIT);
end component;
```

-- positional association:

```
A1:AndGate port map (X,Y,Z1);
```

-- named association:

```
A2:AndGate port map (Ain_2=>Y, Aout=>Z2, Ain_1=>X);
```

-- both (positional must begin from leftmost formal):

```
A3:AndGate port map (X, Aout => Z3, Ain_2 => Y);
```

---




# Example: D flip-flop

---

entity DFF is

```
port (Preset: in bit;  
      Clear: in bit;  
      Clock: in bit;  
      Data: in bit;  
      Q: out bit;  
      Qbar: out bit);
```

```
end DFF;
```

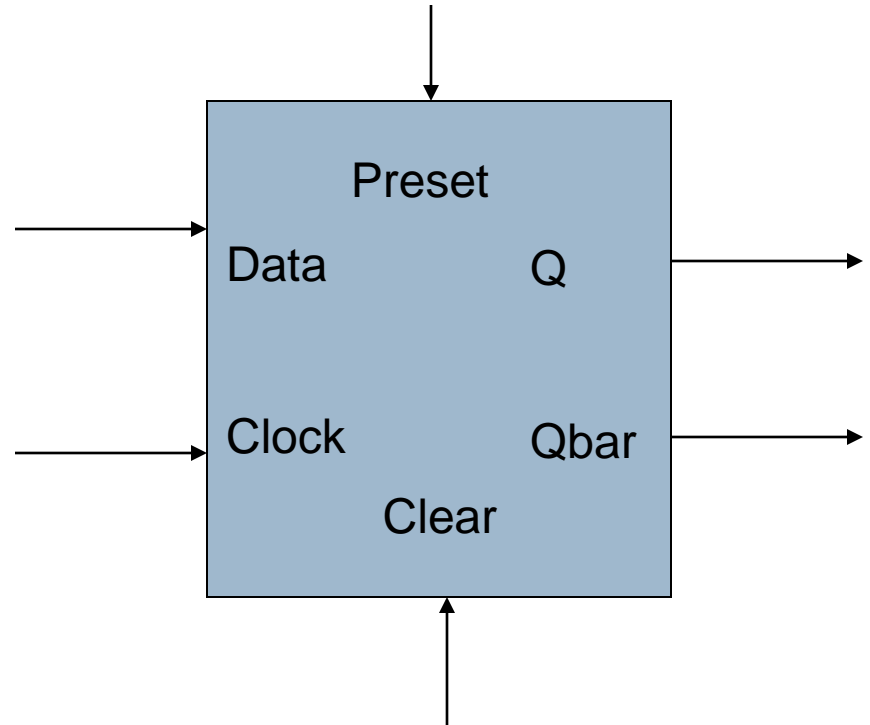

# 7474 D flip-flop equations

---

architecture eqns of DFF is

signal A,B,C,D: bit;

signal QInt, QBarInt: bit;

begin

A <= not (Preset and D and B) after 1 ns;

B <= not (A and Clear and Clock) after 1 ns;

C <= not (B and Clock and D) after 1 ns;

D <= not (C and Clear and Data) after 1 ns;

Qint <= not (Preset and B and QbarInt) after 1 ns;

QBarInt <= not (QInt and Clear and C) after 1 ns;

Q <= QInt;           -- Can drive but not read "outs"

QBar <= QBarInt;   -- Can read & drive "internals"

end;

---




# 4-bit Register (Structural Model)

---

entity Register4 is

```
port ( D: in bit_vector(0 to 3);  
      Q: out bit_vector(0 to 3);  
      Clk: in bit;  
      Clr: in bit;  
      Pre: in bit);
```

end Register4;

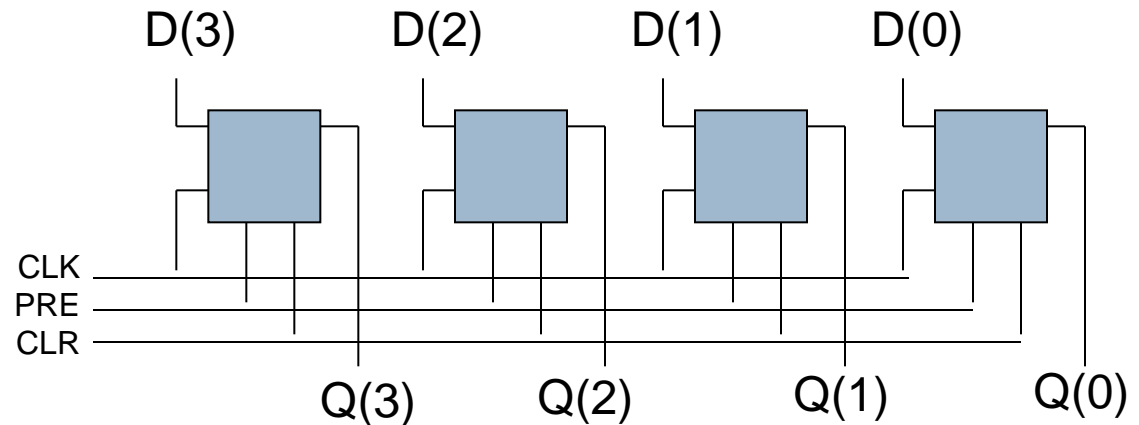

# Register Structure

---

architecture structure of Register4 is

```
component DFF          -- declare library component to be used
  port (Preset: in bit;
        Clear: in bit;
        Clock: in bit;
        Data: in bit;
        Q: out bit;
        Qbar: out bit);
end component;
signal Qbar: bit_vector(0 to 3); -- dummy for unused FF outputs
begin
  -- Signals connect to ports in order listed above
  F3: DFF port map (Pre, Clr, Clk, D(3), Q(3), Qbar(3));
  F2: DFF port map (Pre, Clr, Clk, D(2), Q(2), Qbar(2));
  F1: DFF port map (Pre, Clr, Clk, D(1), Q(1), Qbar(1));
  F0: DFF port map (Pre, Clr, Clk, D(0), Q(0), Qbar(0));
end;
```

---



# Short cut – “generate” statement

---

```
for k in 0 to 3 generate
```

```
    F: DFF port map (Pre, Clr, Clk, D(k), Q(k), Qbar(k));
```

```
end generate;
```

- ▶ Expanded similar to programming language “macro”
- ▶ Generates multiple copies of any given statement(s)
- ▶ Value of k inserted where specified
- ▶ Iteration number k is appended to each label F
- ▶ Result is identical to previous example
- ▶ Use for repeated constructs



# Conditional Signal Assignment

---

```
signal a,b,c,d,y: std_logic;
```

```
signal S: std_logic_vector(0 to 1);
```

```
begin
```

```
  with S select
```

```
    y <= a after 1 ns when "00",
```


```
      b after 1 ns when "01",
```

```
      c after 1 ns when "10",
```

```
      d after 1 ns when "11";
```

```
--Alternative "default": d after 1 ns when others;
```

4-to-1 Mux

 

# 32-bit-wide 4-to-1 multiplexer

---

```
signal a,b,c,d,y: bit_vector(0 to 31);
```

```
signal S: bit_vector(0 to 1);
```

```
begin
```

```
  with S select
```

```
    y <= a after 1 ns when "00",
```

```
        b after 1 ns when "01",
```


```
        c after 1 ns when "10",
```

```
        d after 1 ns when "11";
```

--a,b,c,d,y can be any type, as long as they are the same

---

4-to-1 Mux

 


# Conditional Signal Assignment – Alternate Format

---

```
y <= a after 1 ns when (S="00") else  
    b after 1 ns when (S="01") else  
    c after 1 ns when (S="10") else  
    d after 1 ns;
```

Use any boolean expression  
for each condition:
 
```
y <= a after 1 ns when (F='1') and (G='0') ...
```



# Unconstrained Vectors

---

- ▶ Allows one generic model with different sizes:

```
entity mux is
    port ( a,b: in  bit_vector; -- unconstrained
          c: out bit_vector; -- unconstrained
          s: in  bit );
end mux;
architecture x of mux is
begin
    c <= a when (s='0') else b;
end;
```



# Vector constrained when instantiated

---

```
signal s1,s2: bit;  
signal a5,b5,c5: bit_vector (0 to 4);  
signal a32,b32,c32: bit_vector (0 to 31);  
component mux  
  port (a,b: in bit_vector; -- unconstrained  
        c: out bit_vector;  
        s: in bit );  
end component;
```

```
begin
```

```
M5:  mux port map (a5,b5,c5,s1);    -- 5-bit mux  
M32: mux port map (a32,b32,c32,s2); -- 32-bit mux
```

---



# Multiplexer using an array

---

entity Mux8 is

```
port (InBus : in  STD_LOGIC_VECTOR(7 downto 0);  
      Sel :    in  INTEGER range 0 to 7;  
      OutBit : out STD_LOGIC);
```

end Mux8;

architecture Synthesis\_1 of Mux8 is

begin

```
    OutBit <= InBus(Sel);
```

end;

```
-- if sel is std_logic_vector, must convert to integer
```

```
-- OutBit <= InBus(TO_INTEGER ( UNSIGNED (Sel) ) );
```

---



# Multiplexer: Using “case” statement

(12.6.3)

---

entity Mux4 is

```
port (i: BIT_VECTOR(3 downto 0);  
      sel: BIT_VECTOR(1 downto 0); s: out BIT);
```

end Mux4;

architecture Synthesis\_I of Mux4 is

begin

```
process(sel, i) begin
```

```
  case sel is
```

```
    when "00" => s <= i(0); when "01" => s <= i(1);
```

```
    when "10" => s <= i(2); when "11" => s <= i(3);
```

```
  end case;
```

```
end process; end Synthesis_I;
```

```
-- case statement must be exhaustive to avoid priority questions
```



# Binary decoder function (12.6.4)

---

```
library IEEE; use IEEE.NUMERIC_STD.all;
use IEEE.STD_LOGIC_1164.all;
entity Concurrent_Decoder is
port ( enable : in BIT;
      Din : in STD_LOGIC_VECTOR (2 downto 0);
      Dout : out STD_LOGIC_VECTOR (7 downto 0));
end Concurrent_Decoder;
```



# Decoder using shifter

---

-- inputs enable, Din (3-bit vector), Dout (8-bit vector)

with enable select

```
Dout <= STD_LOGIC_VECTOR(UNSIGNED'(
    shift_left("00000001",TO_INTEGER (UNSIGNED(Din)))) )
    when '1',
    "00000000" when '0',
    "11111111" when others; -- default for synthesis tool
```



# Decoder – alternate model

---

```
process (Din, enable)
    variable T : STD_LOGIC_VECTOR(7 downto 0);
begin
    if (enable = '1') then
        T := "00000000";
        T(TO_INTEGER (UNSIGNED(Din))) := '1';
        Dout <= T ;
    else
        Dout <= (others => '0');
    end if;
end process;
```



# Synthesizing arithmetic circuits

(12.6.5, 12.6.9, 12.6.10)

---

- ▶ Leonardo recognizes overloaded operators and generates corresponding circuits:

“+”, “-”, “\*”, and “abs”

- ▶ Special operations:

“+|”, “-|”, unary “-”

- ▶ Relational Operators:

“=”, “/=", “<”, “>”, “<=", “>=”

- ▶ Use “ranged integers” instead of unbound to minimize generated logic.

signal i : integer range 0 to 15;

---



# Leonardo restrictions

---

- ▶ Non-integer data types (`std_logic_vector`) require operator overloading to produce arithmetic circuits (IEEE library packages)
- ▶ Multiply operator “\*” will produce a multiplier, but more efficient technology-specific modules may be better.
- ▶ Divide operator “/” only works if dividing by a power of 2, unless using a technology-specific module



# Behavioral model of an adder

---

entity adder is

```
port ( a:      in integer; -- abstract data type
      b:      in integer;
      sum:    out integer);
```

end adder ;

architecture behave of adder is

```
begin
```

```
    sum <= a + b; --synthesis should produce adder ckt
```

```
end;
```



# Adders/subtractors automatically generated for integer data

---

```
variable a,b,c: integer;
```

```
c := a + b;  -- produces 32-bit adder (signed)
```

```
variable a,b,c: integer range 0 to 255;
```

```
c := a + b;  -- produces 8-bit adder (unsigned)
```

Constant operands result in reduced logic by removing logic due to hard-wired values.

Ex: `c := a + 5;`




# Multiple adder structures

---


$z \leq a + b + c + d;$

-- 3 adders stacked 3 deep

 

$z \leq (a + b) + (c + d);$


-- 3 adders stacked 2 deep

 
 
# Resource sharing for mutually-exclusive operations

---

```
process (a,b,c,test) begin  
  if (test=TRUE) then  
    o <= a + b ; -- either this evaluates  
  else  
    o <= a + c ; -- or this evaluates  
  end if ;  
end process ;  
-- Leonardo generates two adders & one mux
```




# Equivalent model

---

```
process (a,b,c,test) begin  
    variable tmp : integer range 0 to 255 ;  
begin  
    if (test=TRUE) then -- mux will select b or c  
        tmp := b ;  
    else  
        tmp := c ;  
    end if ;  
    o <= a + tmp ; -- mux output added to a  
end process ;
```

-- one adder and one mux generated

 

# IEEE Std. 1076.3 Synthesis Libraries

Text: Chap 10.12, 12.6.5, 12.6.9

---

## ▶ Support for arithmetic models

### ▶ `numeric_std`

- ▶ defines UNSIGNED and SIGNED as arrays of `std_logic`  
type SIGNED is array(NATURAL range <>) of STD\_LOGIC;  
type UNSIGNED is array(NATURAL range <>) of STD\_LOGIC;
- ▶ defines standard arithmetic/relational operators on these types

### ▶ `numeric_bit`

- ▶ same as above except SIGNED/UNSIGNED are arrays of `bit`

### ▶ `std_logic_arith` (*from Synopsis*)

- ▶ Non-standard predecessor of `numeric_std`/`numeric_bit`
- 



# NUMERIC\_STD package contents

---

- ▶ Arithmetic functions: + - \* / rem mod
  - ▶ Combinations of operands allowed:
    - ▶ SIGNED + SIGNED return SIGNED
    - ▶ SIGNED + INTEGER return SIGNED
    - ▶ INTEGER + SIGNED return SIGNED
  - ▶ 6 relational operators for above operands
  - ▶ TO\_INTEGER(signed), TO\_SIGNED(integer,#bits)
  - ▶ RESIZE(signed,#bits) – changes # bits
  - ▶ SHIFT\_LEFT/RIGHT, ROTATE\_LEFT/RIGHT
  - ▶ PLUS: all of above with UNSIGNED/NATURAL



# Conversion of “closely-related” types


arrays of same dimension + elements of same type

---

```
library IEEE; use IEEE.STD_LOGIC_1164.all;
use IEEE.NUMERIC_STD.all;
entity Adder4 is
    port ( in1, in2 : in  STD_LOGIC_VECTOR(3 downto 0) ;
          mySum : out STD_LOGIC_VECTOR(3 downto 0) ) ;
end Adder4;
```

```
architecture Behave_B of Adder4 is
begin
    mySum <=
        STD_LOGIC_VECTOR(SIGNED(in1) + SIGNED(in2));
end Behave_B;
```

Type conversions

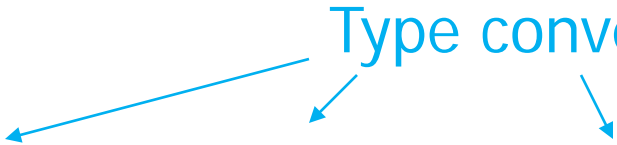

# Arithmetic with NUMERIC\_STD package

---

```
library IEEE; use IEEE.STD_LOGIC_1164.all;
use IEEE.NUMERIC_STD.all;
entity Adder4 is
    port ( in1, in2 : in  UNSIGNED(3 downto 0) ;
           mySum : out UNSIGNED(3 downto 0) ) ;
end Adder4;

architecture Behave_B of Adder4 is
begin
    mySum <= in1 + in2; -- overloaded '+' operator
end Behave_B;
```



# Example

---

```
library IEEE; use IEEE.STD_LOGIC_1164.all;
```

```
use IEEE.NUMERIC_STD.all;
```

```
ENTITY counter IS
```

```
    port( Q: out std_logic_vector(3 downto 0);
```

```
    ....
```

```
ARCHITECTURE behavior OF counter IS
```

```
    signal Qinternal: unsigned(3 downto 0);
```

```
begin
```

```
    Qinternal <= Qinternal + 1;           -- + from numeric_std
```

```
    Q <= std_logic_vector(Qinternal);    -- unsigned->std_logic
```

```
    ....
```



# Handling Overflow (Carry)

---

```
library IEEE; use IEEE.STD_LOGIC_1164.all;  
use IEEE.NUMERIC_STD.all;
```

```
entity Adder_1 is  
  port ( A, B : in  UNSIGNED(3 downto 0) ;  
        C :   out UNSIGNED(4 downto 0) ) ; -- C(4) = carry  
end Adder_1;
```

```
architecture Synthesis_1 of Adder_1 is  
begin  
  C <= ('0' & A) + ('0' & B); -- leading '0' to balance # bits  
end Behave_B;  
-- can also use: C <= resize(A,5) + resize(B,5)
```

---



# Add/Sub “Accumulator”

---

-- result\_t , xin, addout are UNSIGNED

with addsub select – combinational add/sub

```
addout <= (xin + result_t) when '1',  
          (xin - result_t) when '0',  
          (others => '-') when others;
```

process (clr, clk) begin -- register part

```
if (clr = '0') then
```

```
    result_t <= (others => '0');
```

```
elsif rising_edge(clk) then
```

```
    result_t <= addout;
```

```
end if;
```

```
end process;
```

-- “when others” creates exhaustive list of choices

---



# Simplified “accumulator” model

---

-- signal addsub eliminated – circuit will be the same


```
process (clr, clk) begin
  if (clr = '0') then
    result_t <= (others => '0');
  elsif rising_edge(clk) then
    case addsub is
      when '1'    => result_t <= (xin + result_t);
      when '0'    => result_t <= (xin - result_t);
      when others => result_t <= (others => '-');
    end case;
  end if;
end process;
```


 
# Tristate buffer example (incorrect)

---

```
library ieee;
use ieee.std_logic_1164.all;
entity tristate is
  port ( a: in bit;
         y: out std_logic;
         en: in bit);
end tristate;
architecture a1 of tristate is
begin
  y <= a after 1 ns when (en='1') else
    'Z' after 1 ns;
end;
```



--Type mismatch between y and a


---


 
# Tristate buffer example (correct)

---


```
library ieee;
use ieee.std_logic_1164.all;
entity tristate is
  port ( a: in bit;
         y: out std_logic;
         en: in bit);
end tristate;
architecture a1 of tristate is
begin
  y <= '0' after 1 ns when (en='1') and (a='0') else
    '1' after 1 ns when (en='1') and (a='1') else
    'Z' after 1 ns;
end;
```


 
# Tristate bus buffer example

---

```
library ieee;
use ieee.std_logic_1164.all;
entity tristate is
  port ( a: in bit_vector(0 to 7);
        y: out std_logicvector(0 to 7);
        en: in bit);
```



```
end tristate;
architecture a1 of tristate is
begin
  y <= to_stdlogicvector(a) after 1 ns when (en='1') else
    "ZZZZZZZZ" after 1 ns;
end;
```

