

# Computer Memory

Textbook: Chapter 1

ARM Cortex-M4 User Guide (Section 2.2 – Memory Model)

STM32F4xx Technical Reference Manual:

Chapter 2 – Memory and Bus Architecture


Chapter 3 – Flash Memory

Chapter 36 – Flexible Static Memory Controller

# Computer Memory Systems

- Memory system hierarchy
  - Disk, ROM, RAM, Cache
- Memory module (chip) organization
  - On-chip (address) decoder, cell array
- Memory system interfacing
  - Address decoding
  - Bus timing
- Direct memory access (DMA)
  - Transfer data directly between memory and I/O devices
  - Coordinated by a DMA controller

# Computer Memory Hierarchy

 

Memory Content:  $M_C \subseteq M_M \subseteq M_D$

## Memory Parameters:

- Access Time: increase with distance from CPU
- Cost/Bit: decrease with distance from CPU
- Capacity: increase with distance from CPU

# Semiconductor Memory

- RAM (Random Access Memory)
  - Constant access time, independent of location
  - A unique address for each location (generally a byte)
  - The address is decoded by one or more address decoders
- RAM (Read/Write Memory) vs. ROM (Read Only Memory)
  - RAM
    - User's application programs and data
    - Information is lost when the power is off
  - ROM
    - Embedded system program code and operating system
    - Information is retained even without power
    - Each ROM cell is simpler than a RAM cell

# Read-only memory types

- Mask-programmed ROM
  - Programmed at factory
- PROM (Programmable ROM)
  - Programmable once by users
  - Electric pulses selectively applied to “fuses”
- EPROM (Erasable PROM)
  - Repeatedly programmable/reprogrammable
  - Electric pulses for programming (seconds)
  - Ultraviolet light for erasing (minutes)
- EEPROM (Electrically Erasable PROM)
  - Electrically erasable at the single-byte level (*msec*) & programmable
- Flash EPROM
  - Electrically programmable (*µsec*) & erasable (block-by-block: *msec*~*sec*)
  - Most common program memory in embedded applications
  - Widely used in digital cameras, multimedia players, smart phones, etc.

ROM devices are “non-volatile” – they retain information, even when not powered.

# Read-write memory types

- Static RAM (SRAM)
  - Each cell is a flip-flop, storing 1-bit information
  - Information is retained as long as power is on (lost when power off)
  - Faster than DRAM
  - Requires a larger area per cell (more transistors) than DRAM
- Dynamic RAM (DRAM)
  - Each cell is a capacitor, which needs to be refreshed periodically to retain the 1-bit information
  - A refresh consists of reading followed by writing back
  - Refresh overhead

4 Mbyte DRAM: Refreshed every 4 msec


Organized as 2048 rows x 2048 columns → 2048 refreshes

1 refresh → 80 nsec

$$\frac{2048 \times 80 \times 10^{-9}}{4 \times 10^{-3}} \cong 0.041 \rightarrow 4.1\% \text{ of time spent refreshing}$$

# Memory organization (RAM)

- RAM Structure
  - Memory Cell

 


- A *byte* consists of 8 memory cells, with common control signals, *Select* and  $\overline{R/W}$ , and 8 bidirectional data lines.

Some RAMs have separate Din and Dout

- With  $n$ -bit address, the memory system can contain up to  $2^n$  bytes.  
An  $n$ -bit address is decoded by one or more address decoders to generate the control signal, *Select*.
 
# ROM/RAM device organization

Memory "organization" =  $2^n \times d$   
(from system designer's perspective)




- Size.
  - $2^n$  addressable words
  - Address width =  
 $n = r + c$
- Aspect ratio.
  - Data width  $d$ .



 
# Address Decoding

- Selecting a sub-space of memory address
  - A simple example
    - Microprocessor with 5 address bits ( $A_4 \dots A_0$ )  $\rightarrow 2^5 = 32$  bytes addressable
    - Memory chip: 4 x 8 (4 bytes)  $\rightarrow$  Decodes two address bits ( $A_1 A_0$ )
    - Can address up to 8 chips (decode address bits ( $A_4 A_3 A_2$ ) for chip enable)



# Typical generic SRAM

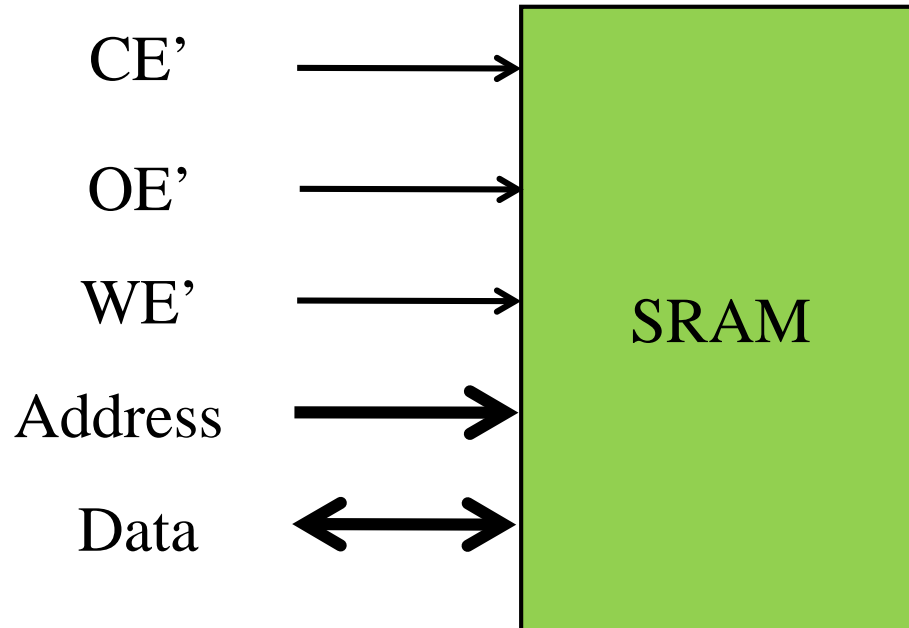

CE' = **chip enable**: initiate memory access when active


OE' = **output enable**: drive Data lines when active

WE' = **write enable**: update SRAM contents with Data

(May have one R/W' signal instead of OE' and WE')


Multi-byte data bus devices have a **byte-enable** signal for each byte.

# Generic SRAM timing

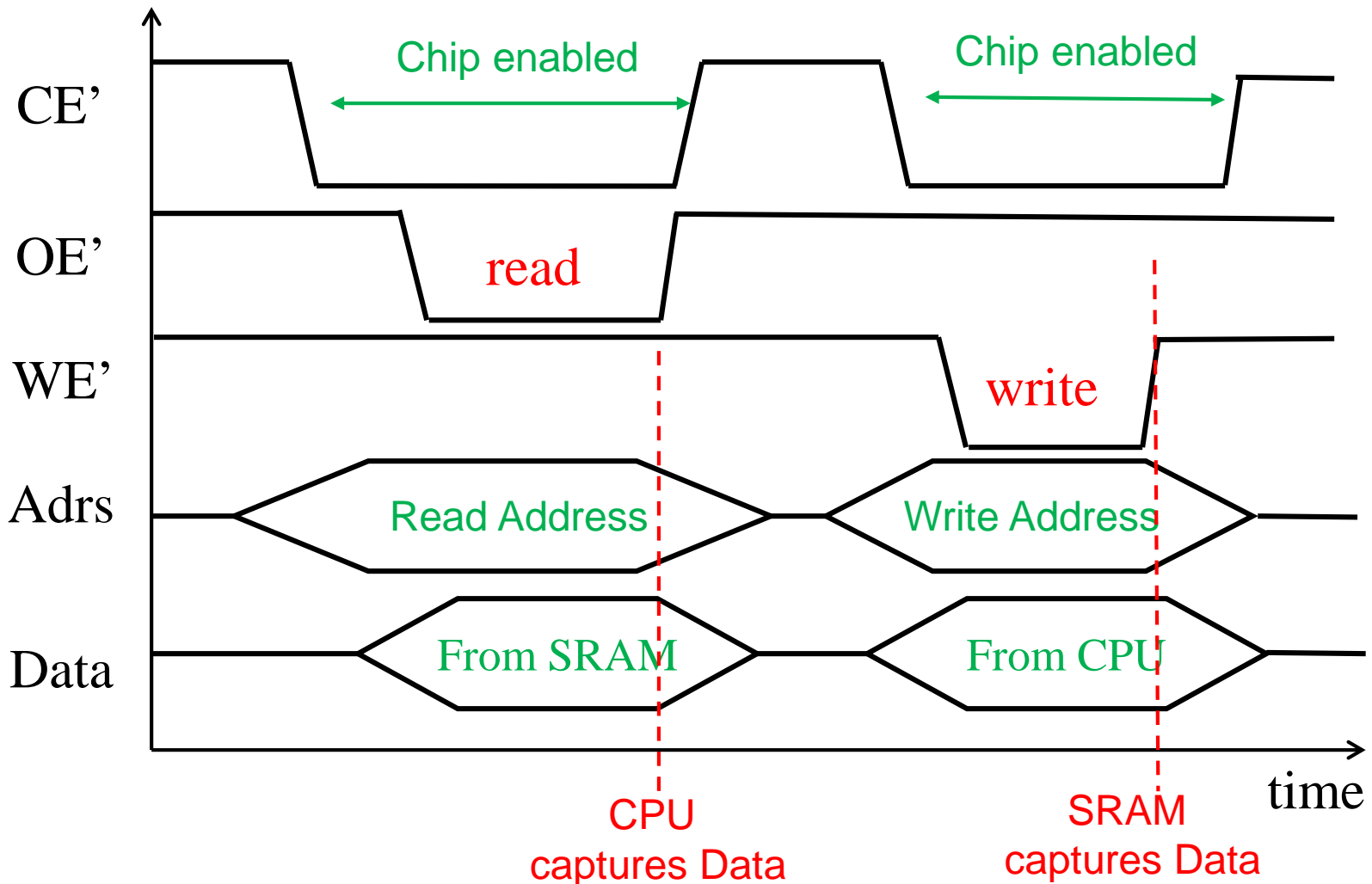

 
# Microprocessor buses

- Mechanism for communication with memories and I/O devices
- Bus components:
  - signal wires with designated functions
  - protocol for data transfers
  - electrical parameters (voltage, current, capacitance, etc.)
  - physical design (connectors, cables, etc.)
- Clock provides synchronization.
- R/W is true when reading \*\* (R/W' is false when reading).
- Address is a-bit bundle of address lines.
- Data is n-bit bundle of data lines.
- “Data ready” signals when n-bit data is ready.




\*\* Instead of R/W' some CPUs have separate RD' and WR'


# Timing diagrams

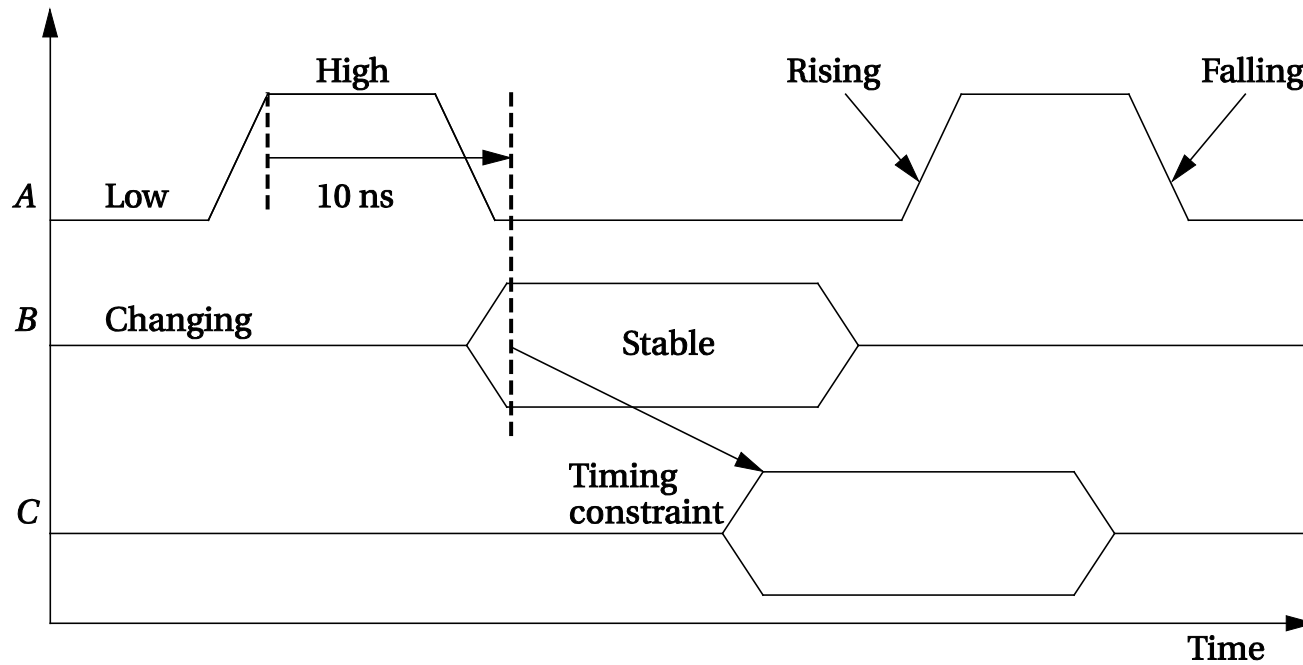

# Typical bus read and write timing


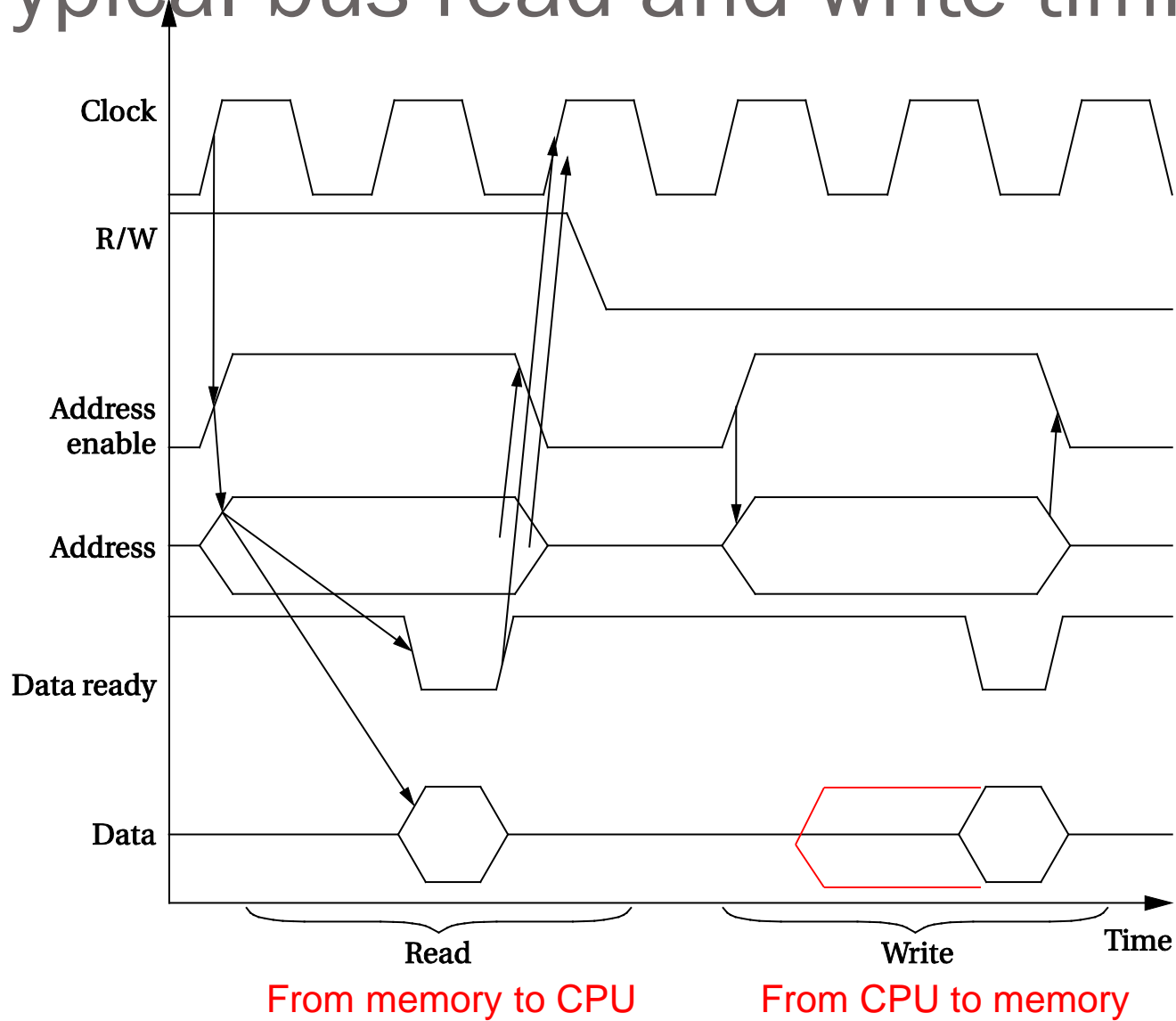


# Bus wait state

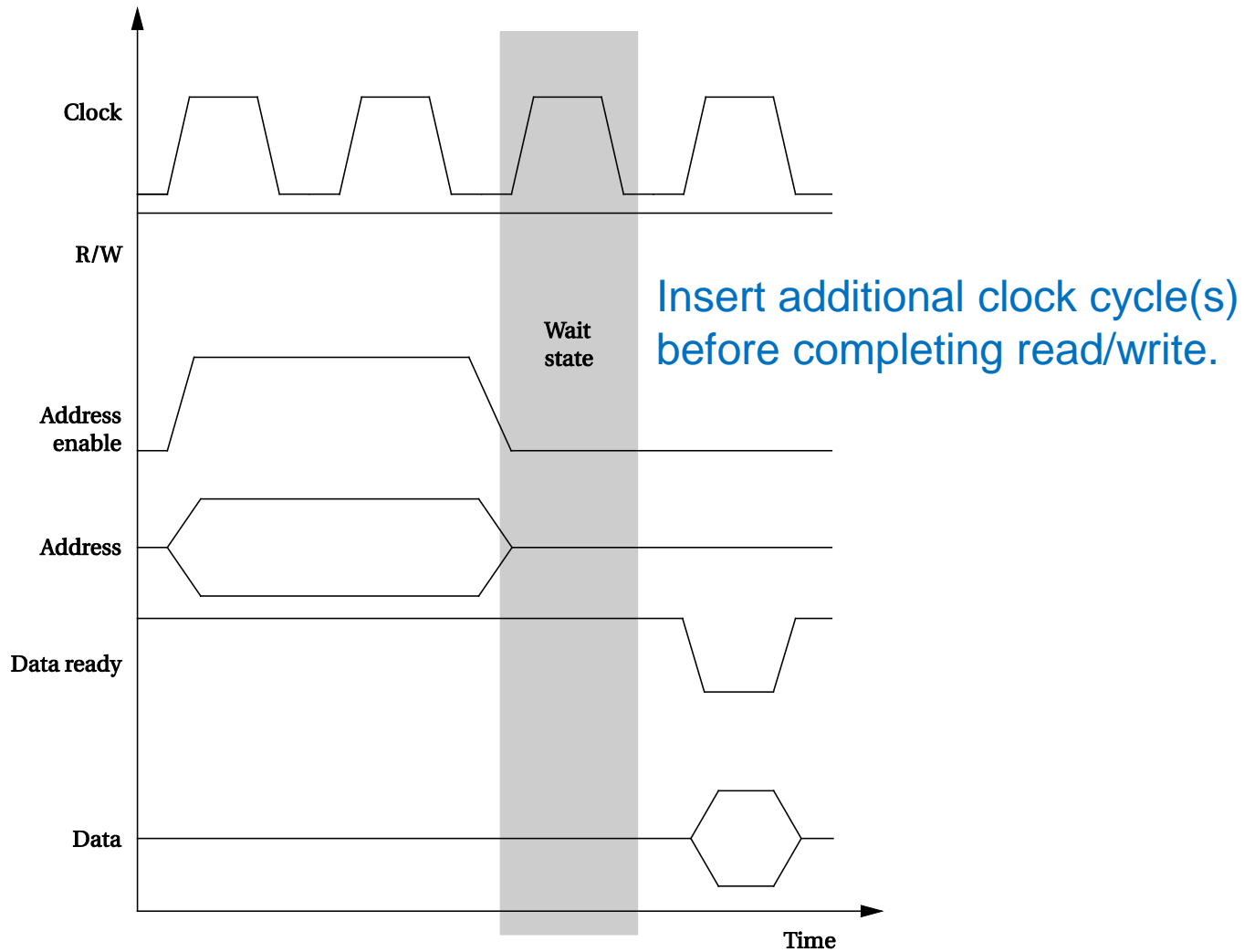


# IS61LV51216-12T: 512K x 16 SRAM

$2^{19}$

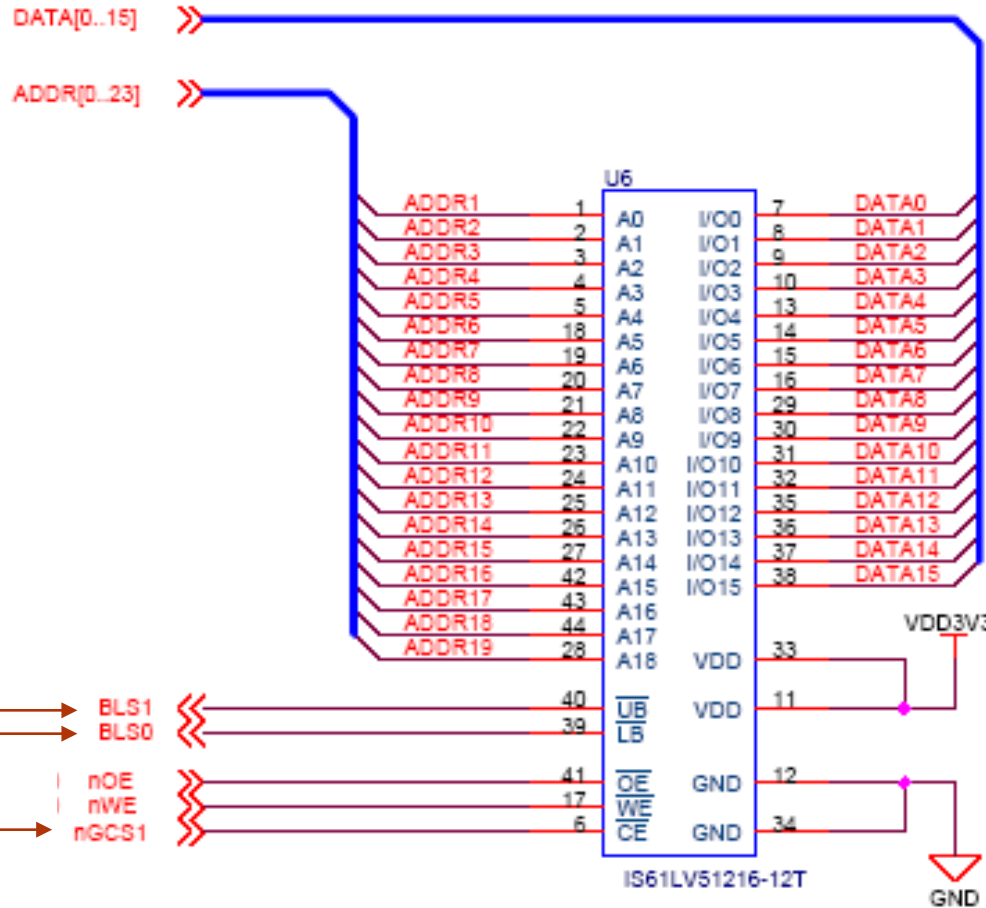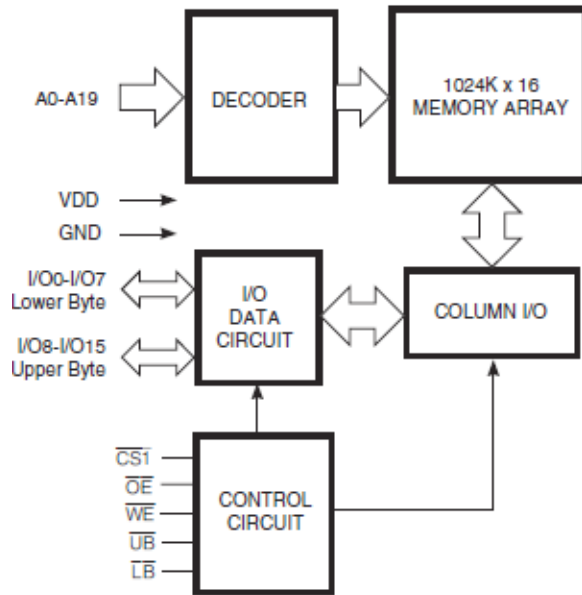


Byte Lane Select  
 - Upper byte D15-8  
 - Lower byte D7-0

Decoded  $A_{31-24}$

 



# ISSI IS61LV51216 SRAM read cycle

 

Timing Parameters:  
Max data valid times  
following activation of  
Address, CE, OE

Symbol	Parameter	-8		-10		-12		Unit
		Min.	Max.	Min.	Max.	Min.	Max.	
t <sub>RC</sub>	Read Cycle Time	8	—	10	—	12	—	ns
t <sub>AA</sub>	Address Access Time	—	8	—	10	—	12	ns
t <sub>OHA</sub>	Output Hold Time	3	—	3	—	3	—	ns
t <sub>ACE</sub>	$\overline{\text{CE}}$ Access Time	—	8	—	10	—	12	ns
t <sub>DOE</sub>	$\overline{\text{OE}}$ Access Time	—	3.5	—	4	—	5	ns

# Flash memory devices

- Available in NAND or NOR structures
  - NOR flash system interface similar to SRAM (random access)
  - NAND flash system interface typically “serial” (indirect access)
- Read operations are the default, and similar to other memory devices
- Writing/erasing is initiated by writing “*commands*” to the Flash memory controller
  - Flash is programmed at system voltages.
  - Erasure time is long, and must be erased in blocks.

	<b>SLC NAND Flash (x8)</b>	<b>MLC NAND Flash (x8)</b>	<b>MLC NOR Flash (x16)</b>
<b>Density</b>	512 Mbits <sup>1</sup> – 4 Gbits <sup>2</sup>	1Gbit to 16Gbit	16Mbit to 1Gbit
<b>Read Speed</b>	24 MB/s <sup>3</sup>	18.6 MB/s	103MB/s
<b>Write Speed</b>	8.0 MB/s	2.4 MB/s	0.47 MB/s
<b>Erase Time</b>	2.0 mSec	2.0mSec	900mSec
<b>Interface</b>	I/O – indirect access	I/O – indirect access	Random access
<b>Application</b>	Program/Data mass storage	Program/Data mass storage	eXecuteInPlace

# Ex: SST39VF1601- 1M x 16 NOR Flash

SST39VF3201=2M x 16 (4Mbyte:  $2^{22}$ ) / SST39VF6401=4M x 16 (8Mbyte:  $2^{23}$ )

D[15..0] »

A[20..1]\*\* »


2Mbyte ( $2^{21}$ ) used of  
64Mbyte ( $2^{26}$ ) addr. space

Therefore, 5 address bits  
not decoded: A[25..21]\*\*

A[0] is part of NBL[1:0]\*

NRESET »

NOE »  
NWE »  
NEx »

 

- Byte lane selects NBL[1:0] not used: all operations are “words”
- SST39VF3201 uses A[21..1], SST39VF6401 uses A[22..1]

# SST39VF1601 characteristics


- Organized as 1M x 16
  - 2K word sectors, 32K word blocks
- Performance:
  - Read access time = 70ns or 90ns
  - Word program time = 7us
  - Sector/block erase time = 18ms
  - Chip erase time = 40ms
- Check status of write/erase operation via read
  - DQ7 = complement of written value until write complete
  - DQ7=0 during erase, DQ7=1 when erase done

# SST39VF1601 command sequences

(assert WE# and CE# to write commands)

Command Sequence	1st Bus Write Cycle		2nd Bus Write Cycle		3rd Bus Write Cycle		4th Bus Write Cycle		5th Bus Write Cycle		6th Bus Write Cycle	
	Addr <sup>1</sup>	Data <sup>2</sup>	Addr <sup>1</sup>	Data <sup>2</sup>	Addr <sup>1</sup>	Data <sup>2</sup>	Addr <sup>1</sup>	Data <sup>2</sup>	Addr <sup>1</sup>	Data <sup>2</sup>	Addr <sup>1</sup>	Data <sup>2</sup>
Word-Program	5555H	AAH	2AAAH	55H	5555H	A0H	WA <sup>3</sup>	Data				
Sector-Erase	5555H	AAH	2AAAH	55H	5555H	80H	5555H	AAH	2AAAH	55H	SA <sub>X</sub> <sup>4</sup>	30H
Block-Erase	5555H	AAH	2AAAH	55H	5555H	80H	5555H	AAH	2AAAH	55H	BA <sub>X</sub> <sup>4</sup>	50H
Chip-Erase	5555H	AAH	2AAAH	55H	5555H	80H	5555H	AAH	2AAAH	55H	5555H	10H
Erase-Suspend	XXXXH	B0H										
Erase-Resume	XXXXH	30H										
Query Sec ID <sup>5</sup>	5555H	AAH	2AAAH	55H	5555H	88H						
User Security ID Word-Program	5555H	AAH	2AAAH	55H	5555H	A5H	WA <sup>6</sup>	Data				
User Security ID Program Lock-Out	5555H	AAH	2AAAH	55H	5555H	85H	XXH <sup>6</sup>	0000H				
Software ID Entry <sup>7,8</sup>	5555H	AAH	2AAAH	55H	5555H	90H						
CFI Query Entry	5555H	AAH	2AAAH	55H	5555H	98H						
Software ID Exit <sup>9,10</sup> /CFI Exit/Sec ID Exit	5555H	AAH	2AAAH	55H	5555H	F0H						
Software ID Exit <sup>9,10</sup> /CFI Exit/Sec ID Exit	XXH	F0H										


# Generic DRAM device

 


RAS' = **Row Address Strobe**: row# on Address inputs

CAS' = **Column Address Strobe**: column# on Address inputs

# Generic DRAM timing

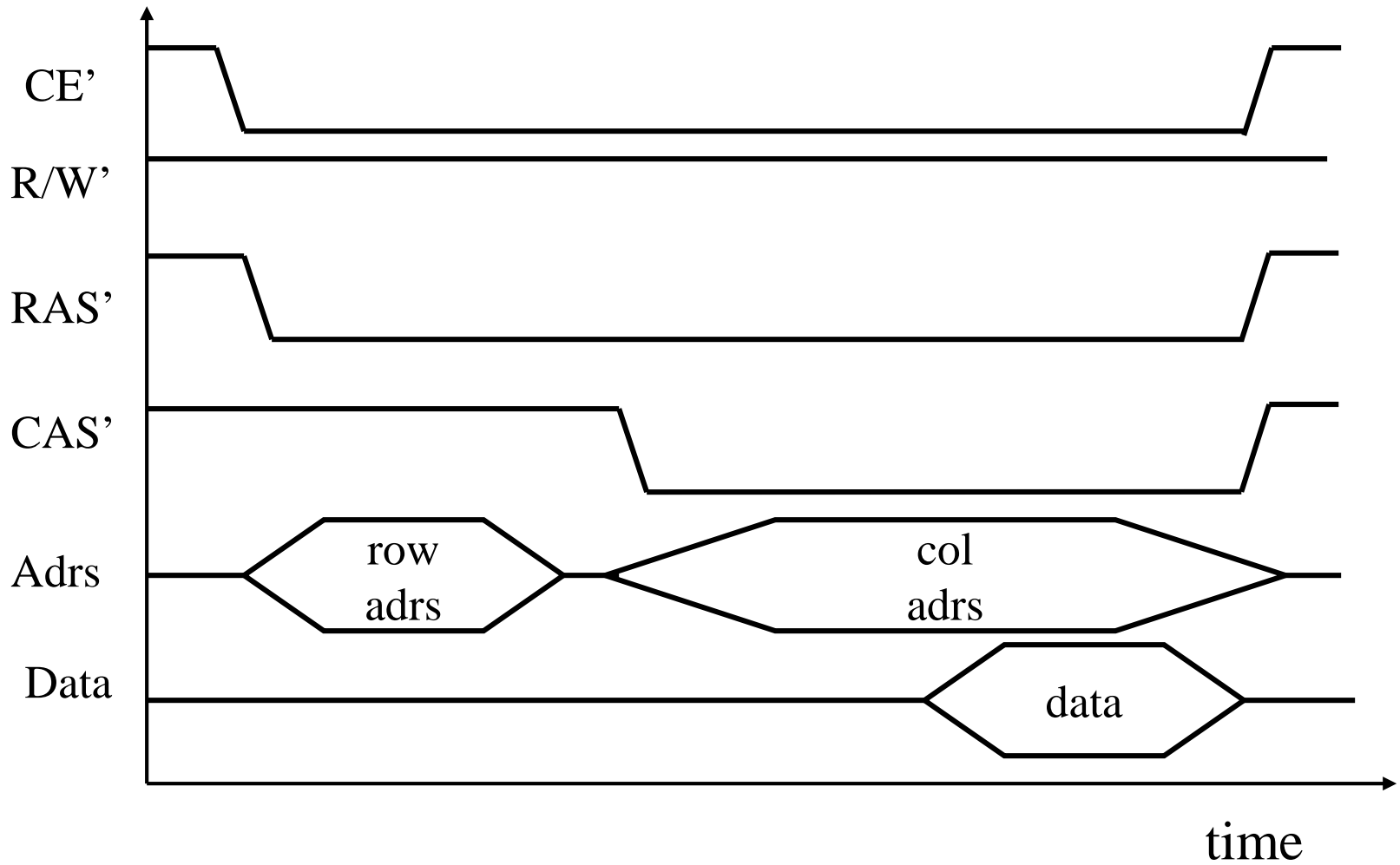


# Page mode access

 



# Bus burst read (if supported)

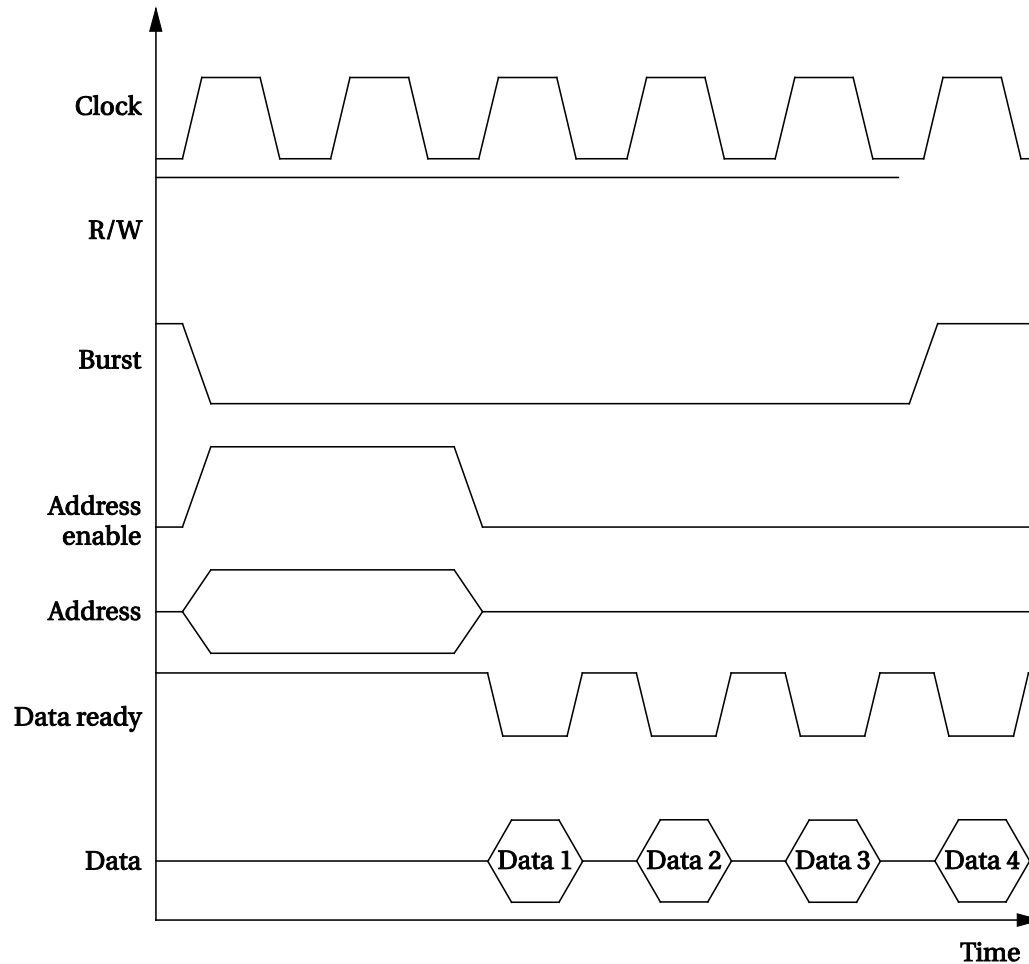


# Dynamic RAM refresh

- Value decays in approx. 1 ms.
- Refresh value by reading it.
  - Can't access memory during refresh.
- RAS-only refresh
- CAS-before-RAS refresh.
- Hidden refresh.

# Other DRAM forms

- Extended data out (EDO): improved page mode access.
- Synchronous DRAM: clocked access for pipelining.
- Double Data Rate (DDR) – transfer on both edges of clock
  - DDR-1, DDR-2, DDR-3 support increasingly higher bandwidths
- Rambus: highly pipelined DRAM.

# Cortex-M4 memory map

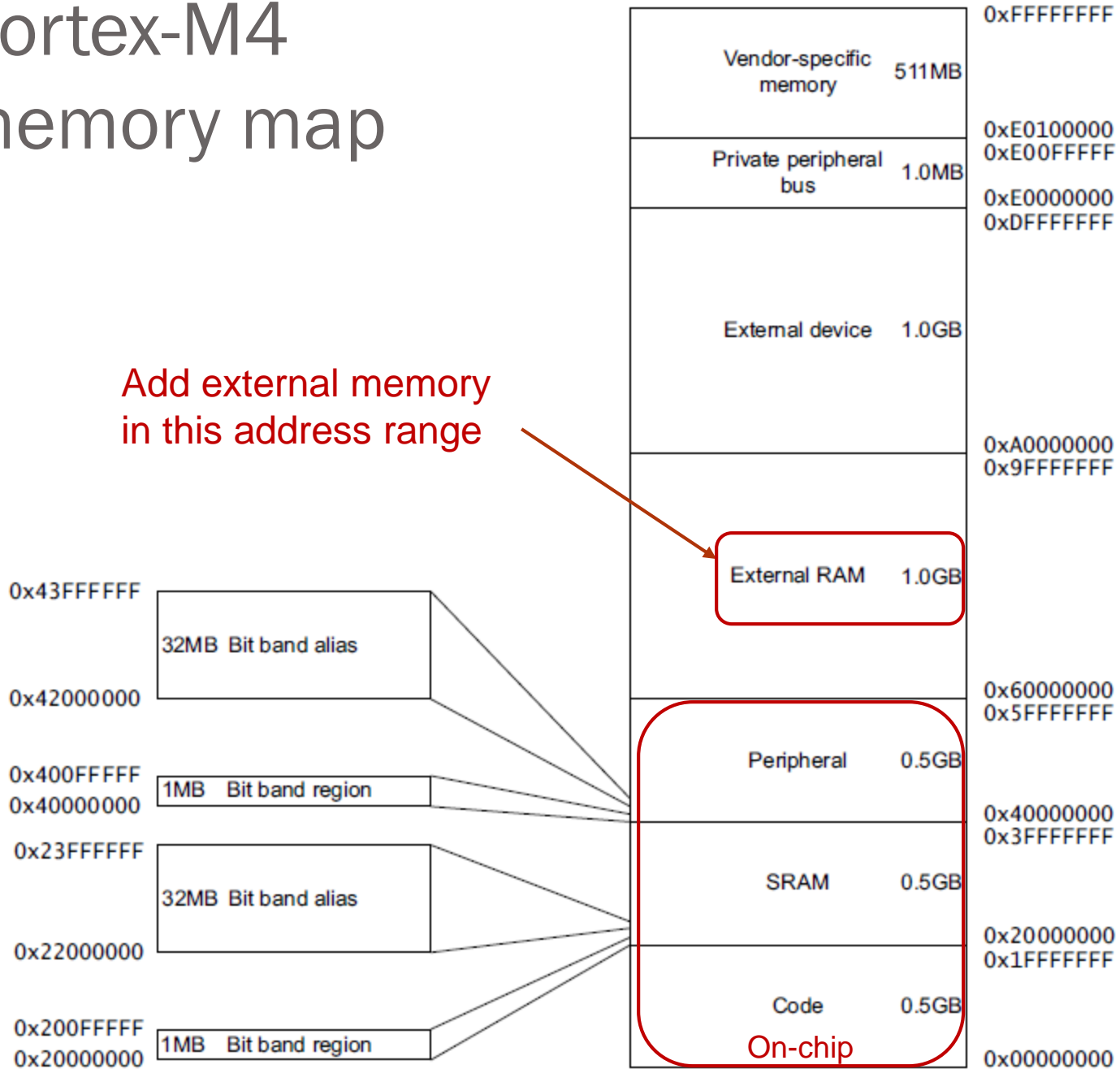


# STM32F407 Microcontroller

AHB 168MHz

APB 142MHz

APB 84MHz

 


External Bus
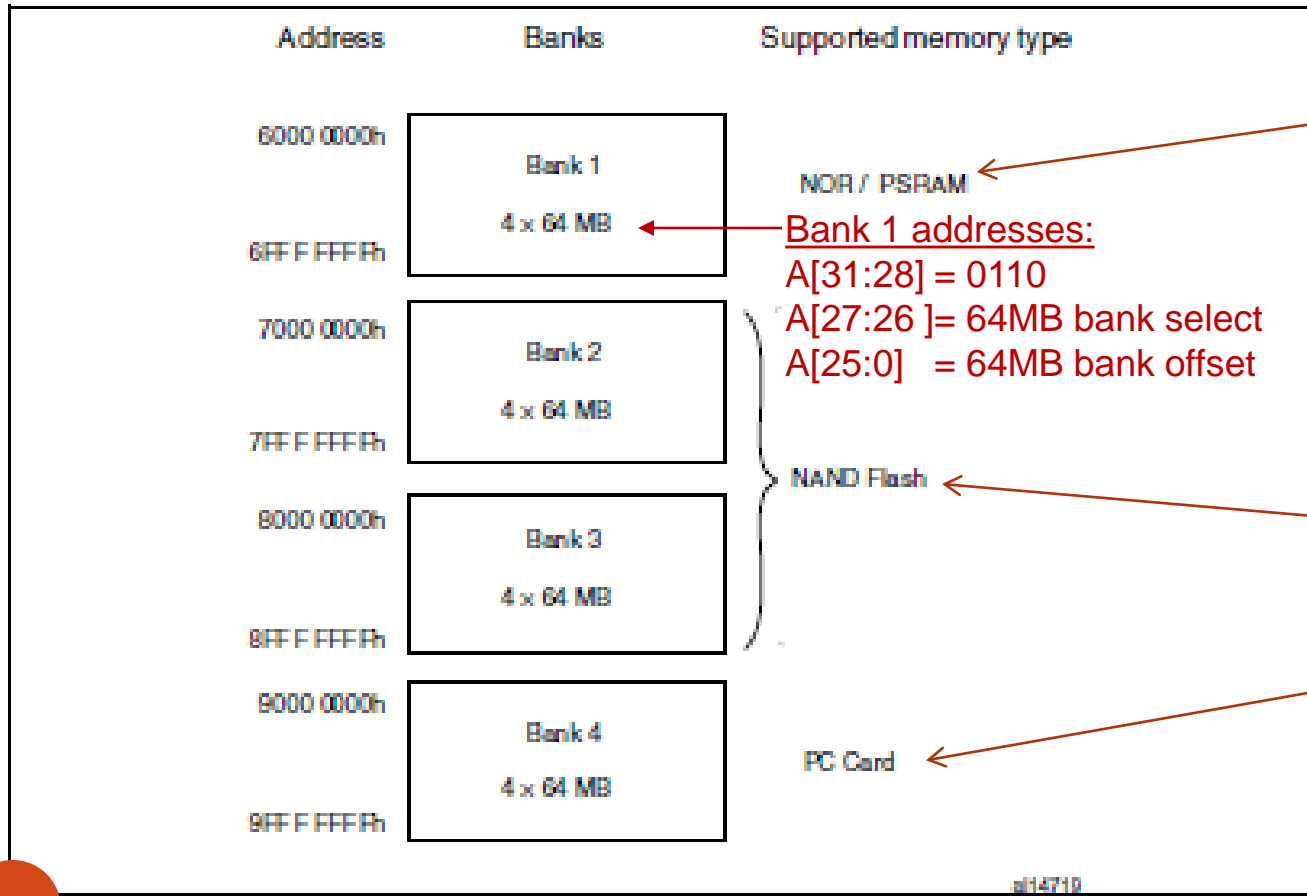
# STM32 Flexible Static Memory Controller (FSMC)

- STM32F4xx Tech. Ref. Manual, Chap. 36

- Control external memory on AHB bus in 4 - 256K banks
  - Upper address bits decoded by the FSMC



Bank 1 addresses:  
 $A[31:28] = 0110$   
 $A[27:26] = 64\text{MB bank select}$   
 $A[25:0] = 64\text{MB bank offset}$

Static memory-mapped devices:


- \* SRAM
- \* Pseudo-Static RAM
- \* NOR flash

2 banks NAND flash


16-bit PC-Card devices
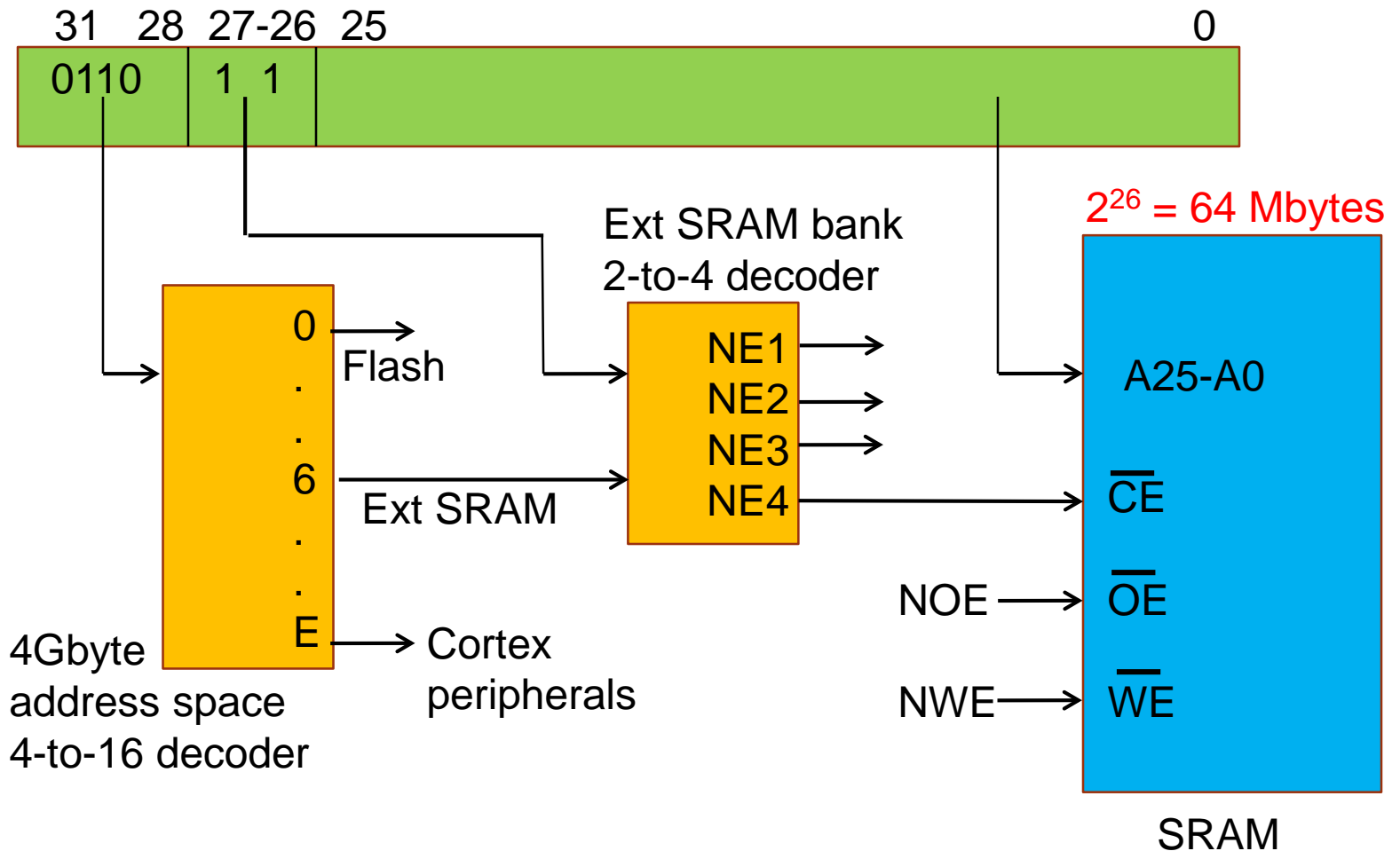
# Example SRAM address decoding

SRAM/NE4 Addresses: [ 0x6C00 0000 ... 0x6F00 0000]



# FSMC block diagram

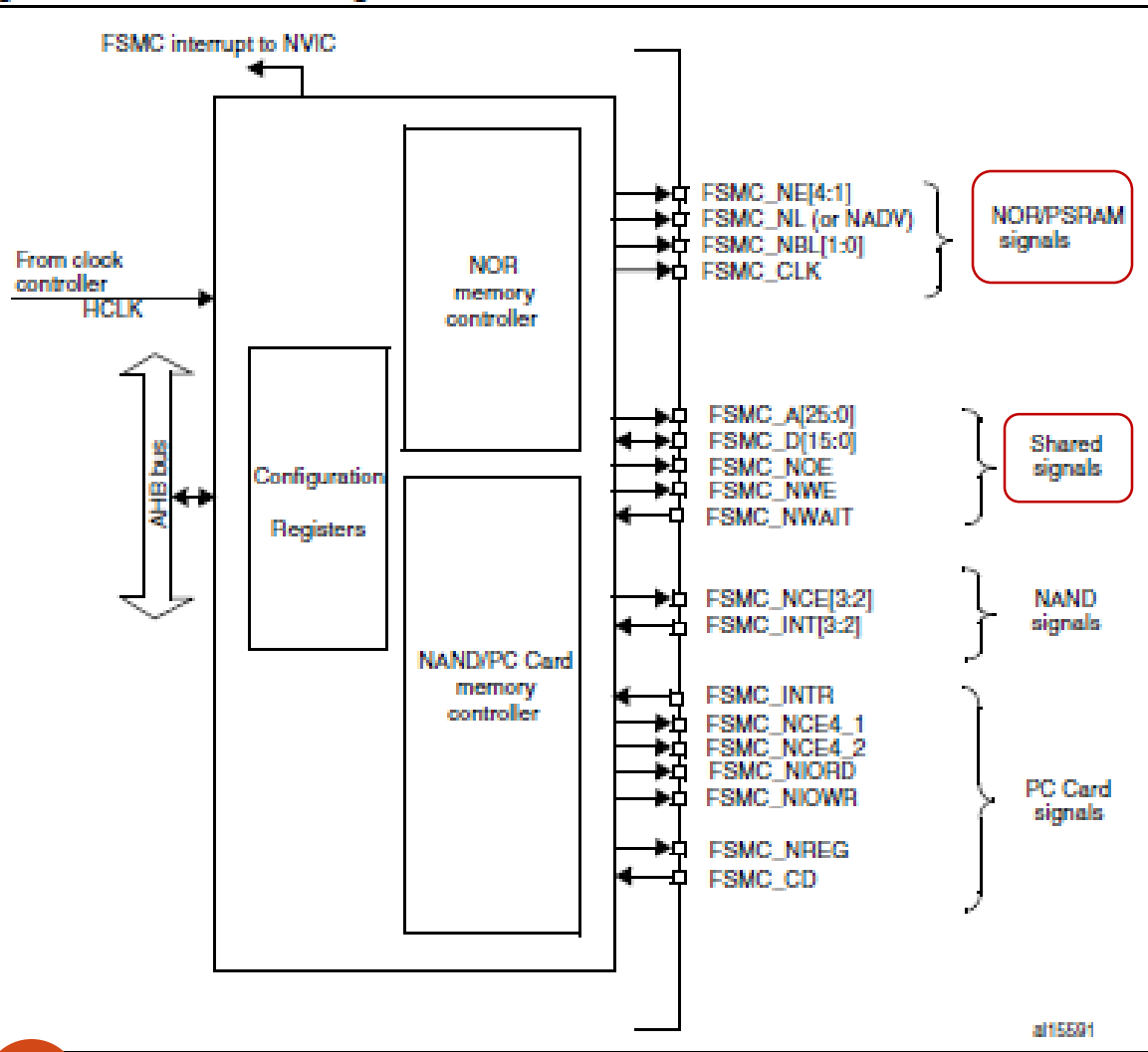

“N” = “negative” (active low)

NE[4:1] = NOR/PSRAM enable

- NE[1]: A[27:26]=00
- NE[2]: A[27:26]=01
- NE[3]: A[27:26]=10
- NE[4]: A[27:26]=11

NL = address latch/advance

NBL = byte lane

CLK for sync. Burst

A[25:0] = Address bus

D[15:0] = Data bus\*\*

NOE = output enable


NWE = write enable

NWAIT = wait request

\*\* Data bus = 8 or 16 bits



# FSMC “Mode 1” memory read

 


Other modes:

- \* Provide ADV (address latch/advance)
- \* Activate OE and WE only in DATAST
- \* Multiplex A/D bits 15-0
- \* Allow WAIT to extend DATAST

ADDSET/DATAST programmed in chip-select timing register (HCLK = AHB clock)

# Example: 512K x 16 SRAM (1 Mbyte)

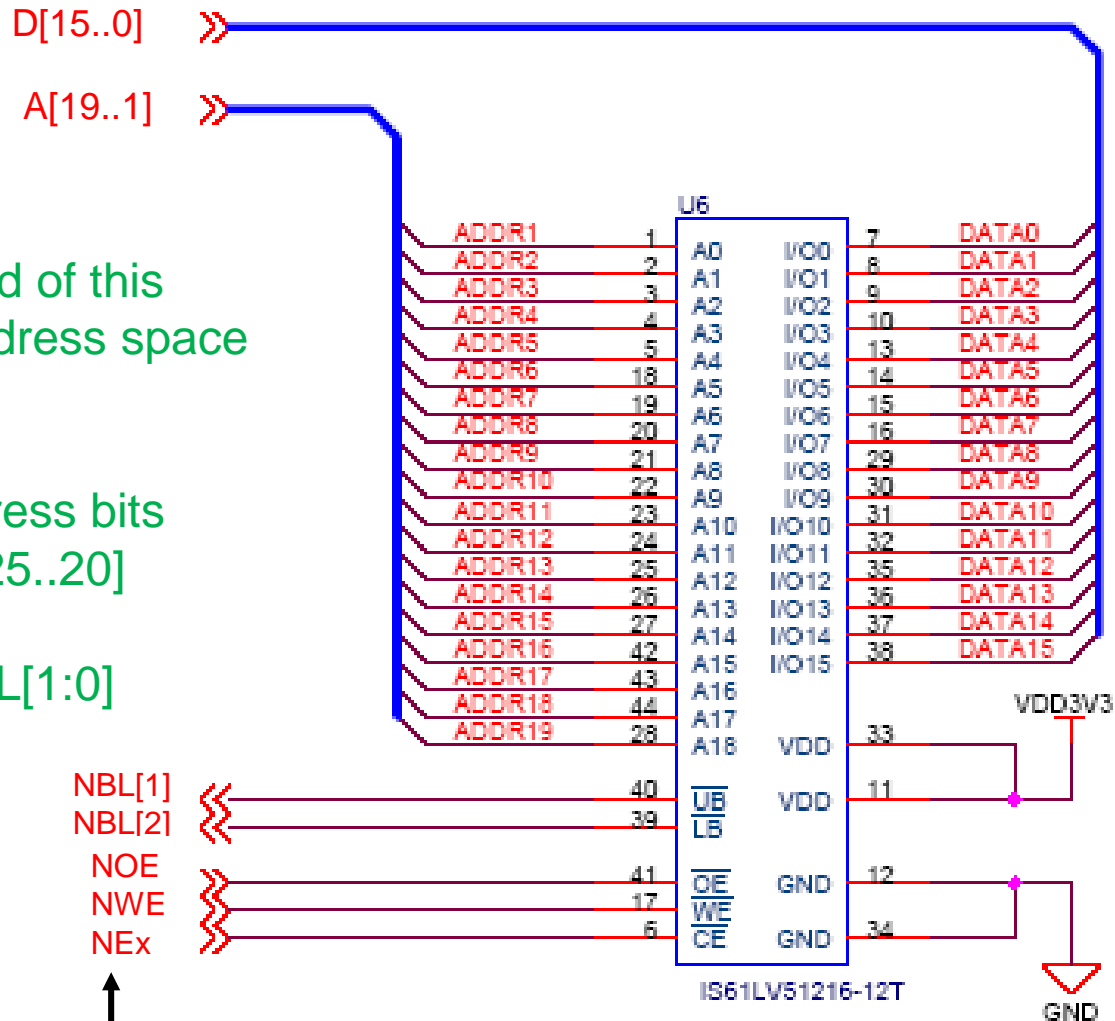

1Mbyte ( $2^{20}$ ) used of this  
64Mbyte ( $2^{26}$ ) address space  
for NEx

Therefore, 6 address bits  
not decoded: A[25..20]


A[0] is part of NBL[1:0]

Microcontroller decodes upper address bits – ADDR[31..26] – for NEx

# CPU Bus Types


- Synchronous vs. Asynchronous
  - Sync: all op's synchronized to a clock
  - Async: devices signal each other to indicate start/stop of operations
    - May combine sync/async (80x86 "Ready" signal)
- Data transfer types:
  - Processor to/from memory
  - Processor to/from I/O device
  - I/O device to/from memory (DMA)
- Data bus types
  - Parallel (data bits transferred in parallel)
  - Serial (data bits transferred serially)

# Typical bus data rates

 


Source: Peter Cheung "Computer Architecture & Systems Course Notes"

# Hierarchical Bus Architecture

 


# Example ARM System

 
 
# DMA

- ▶ Direct memory access (DMA) performs data transfers without executing instructions.
  - ▶ CPU sets up transfer by programming the DMA controller.
  - ▶ DMA engine fetches, writes.
- ▶ DMA controller is a separate unit – can become bus master.



# Bus mastership

- Bus master controls operations on the bus.
- By default, CPU is bus master and initiates transfers.
- Other devices may request bus mastership.
  - Separate set of handshaking lines.
  - CPU can't use bus when it is not master.
- Bus mastership protocol:
  - Bus request – a device requests bus mastership from CPU
  - Bus grant – CPU relinquishes and grants mastership to device
- Situations for multiple bus masters:
  - DMA data transfers
  - Multiple CPUs with shared memory
    - One CPU might be graphics/network processor



# DMA operation

- ▶ CPU configures DMA controller registers for:
  - ▶ peripheral address, memory start address, #xfers, direction (P->M or M->P)
- ▶ Peripheral issues DMA request to DMA controller.
- ▶ DMA controller takes bus mastership from CPU
- ▶ Once DMA is bus master, it transfers automatically.
  - ▶ Memory address incremented and count decremented for each transfer.
  - ▶ May run continuously until complete.
  - ▶ May use every  $n^{\text{th}}$  bus cycle.

## Bus master request

