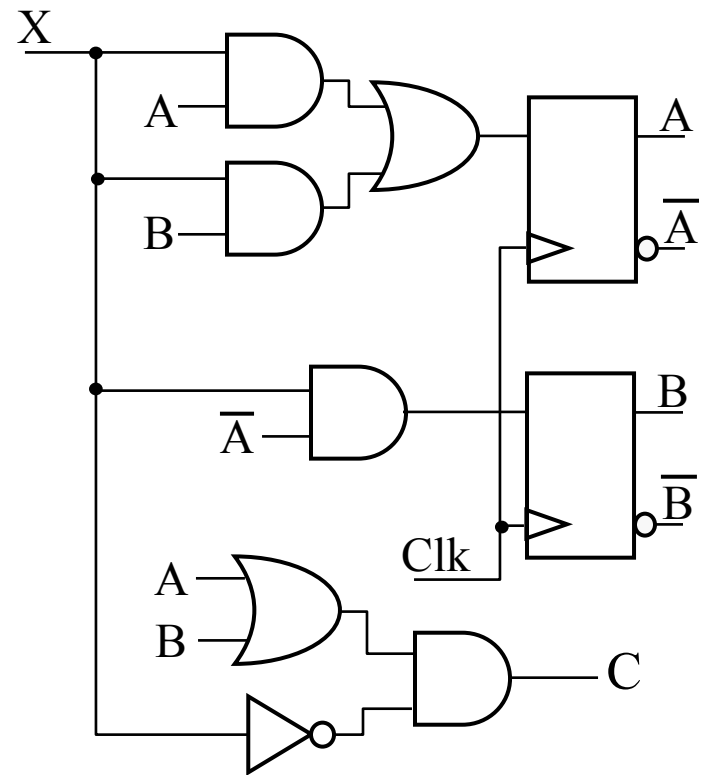


Sequential Logic Analysis

- Used to determine:
 - How a sequential logic circuit works
 - Given an initial state and an input sequence:
 - What will be the output sequence
 - What will be the final state
 - Logic simulation cannot always do this
 - Unless initial state can be set
- The opposite procedure of design
 1. Start with circuit diagram
 2. Derive output equations
 3. Derive flip-flop input equations
 4. Derive state table
 5. Derive state diagram


Analysis Example

- Given this sequential logic circuit and:
 - An initial state of $A=0$ & $B=1$
 - An input sequence $X=010011$
- What will be the final state?
- What will be the output sequence?



Analysis Example

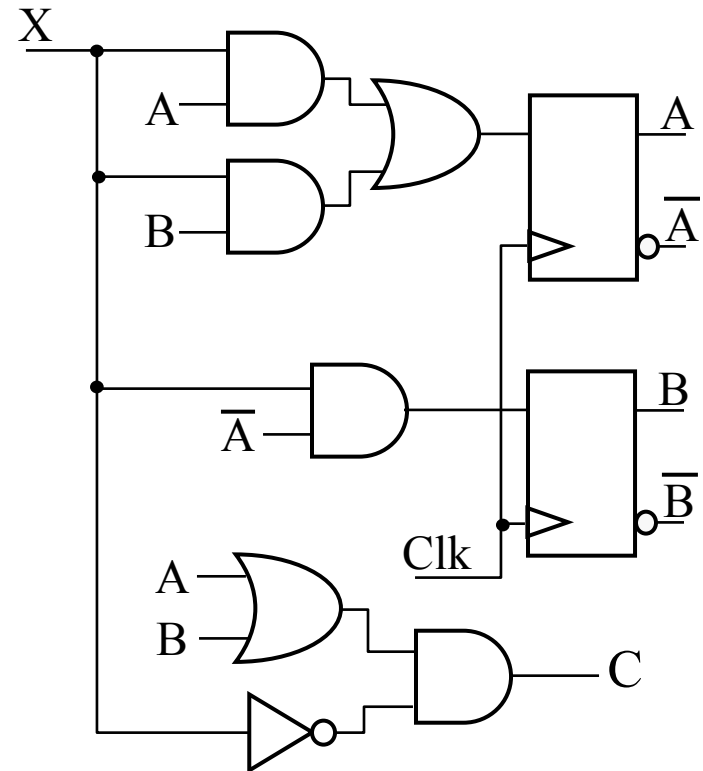- From logic diagram obtain logic equations:
 - $C = X'(A+B) = AX' + BX'$
 - $D_A = AX + BX$
 - $A^+ = D_A$ (for D flip-flop)
 - $D_B = A'X$
 - $B^+ = D_B$ (for D flip-flop)
- Next obtain state table then state diagram




Analysis Example (continued)

$$C = X'(A+B) = AX' + BX'$$

$$A^+ = AX + BX$$


$$B^+ = A'X$$

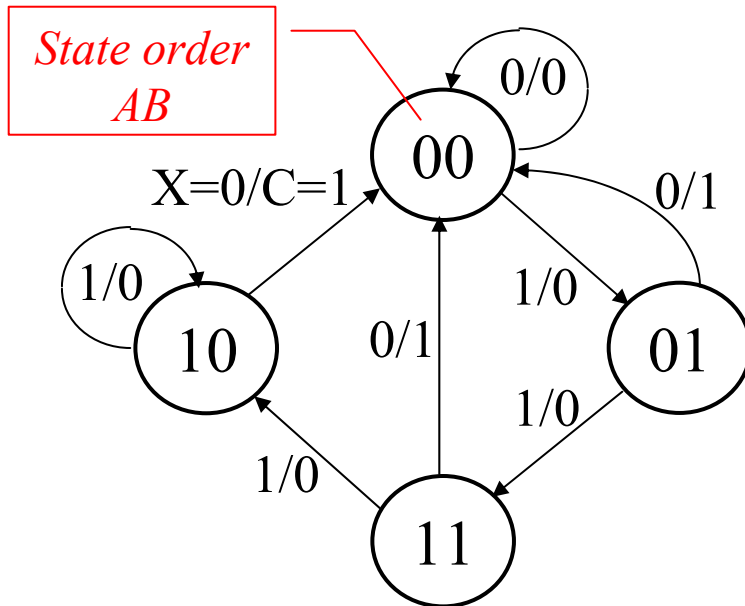

Input	Current State	Next State	Output
X	A B	A ⁺ B ⁺	C
0	0 0	0 0	0
1	0 0	0 1	0
0	0 1	0 0	1
1	0 1	1 1	0
0	1 0	0 0	1
1	1 0	1 0	0
0	1 1	0 0	1
1	1 1	1 0	0


Analysis Example (continued)

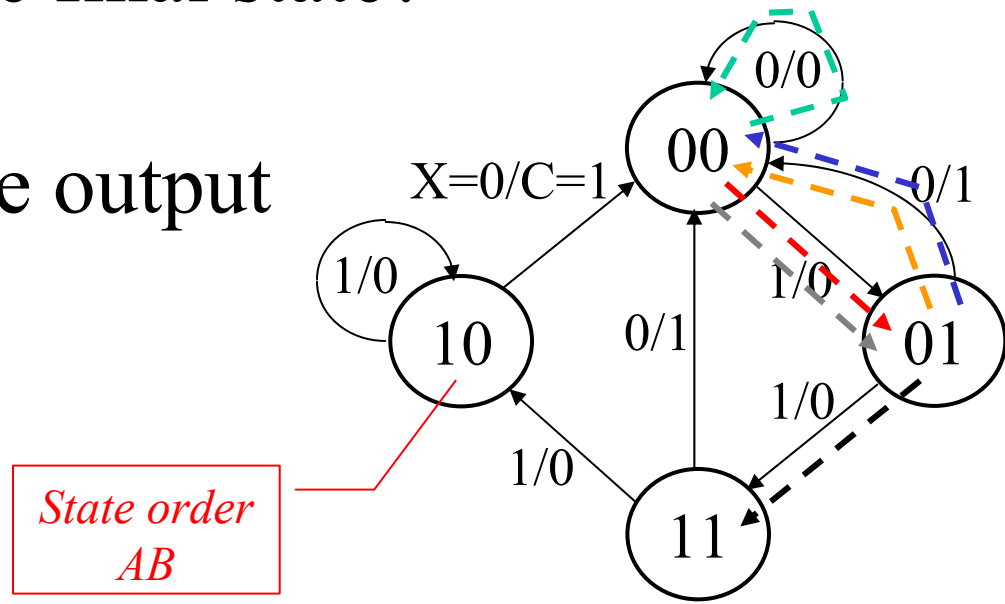- Given:
 - An initial state of $A=0$ & $B=1$
 - An input sequence $X=010011$
- What will be the final state?
 - $A=1$ & $B=1$
- What will be the output sequence?
 - $X=010011$
 - $C=101000$



Another Analysis Example

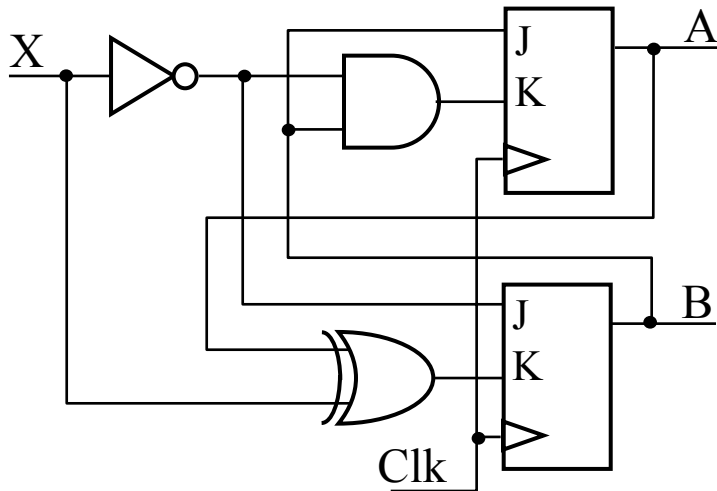- The characteristic equation for D flip-flops makes analysis a little easier than other flip-flops
- Consider this circuit with JK flip-flops
 - Here we assume that A and B are the circuit outputs



Equations for inputs to FFs:

$$J_A = B$$

$$K_A = BX'$$

$$J_B = X'$$

$$K_B = A \oplus X = AX' + A'X$$

JKFF Analysis Example

- Fill in inputs and current state as usual
- Evaluate FF inputs based on inputs and current state
- Use characteristic table to obtain next state from FF inputs

*JK FF
characteristic
table*

J	K	Q+
0	0	Q
0	1	0
1	0	1
1	1	Q'

Input X	Current State		A FF inputs		B FF inputs		Next State	
	A	B	J _A	K _A	J _B	K _B	A ⁺	B ⁺
0	0	0	0	0	1	0	0	1
1	0	0	0	0	0	1	0	0
0	0	1	1	1	1	0	1	1
1	0	1	1	0	0	1	1	0
0	1	0	0	0	1	1	1	1
1	1	0	0	0	0	0	1	0
0	1	1	1	1	1	1	0	0
1	1	1	1	0	0	0	1	1

JKFF Analysis Example (continued)

- Now obtain state diagram from state table
 - Based on inputs, current state, and next state
- Now we can analyze circuit behavior
 - Based on initial state and input sequence

Input X	Current State		Next State	
	A	B	A ⁺	B ⁺
0	0	0	0	1
1	0	0	0	0
0	0	1	1	1
1	0	1	1	0
0	1	0	1	1
1	1	0	1	0
0	1	1	0	0
1	1	1	1	1

