 


Field Programmable Gate Arrays

- Configuration Memory
- Programmable Logic Blocks (PLBs)
- Programmable Input/Output Cells
- Programmable Interconnect



Typical Complexity = 5M – 1B transistors


Basic FPGA Operation

Write Configuration Memory

- Defines system function
 - Input/Output Cells
 - Logic in PLBs
 - Connections between PLBs & I/O cells


Changing configuration memory data => changes system function

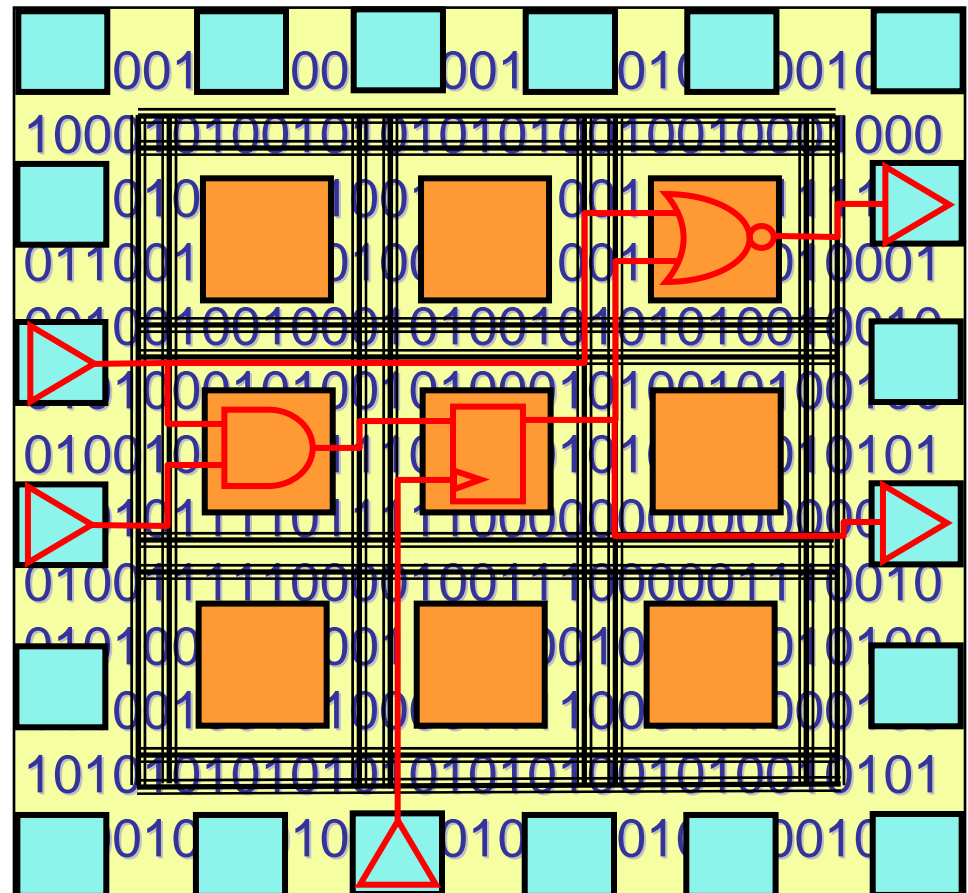- Can change at anytime
 - Even while system function is in operation
 - Run-time reconfiguration (RTR)



Basic PLB Architecture

 - Look-up Table (LUT) implements truth table
- Memory elements:
 - Flip-flop/latch
 - Some FPGAs - LUTs can also implement small RAMs
- Carry & control logic implements fast adders/subtractors



A Simple PLB

- Two 3-input LUTs
 - Can implement any 4-input combinational logic function

- 1 flip-flop

- Programmable:

- Active levels
- Clock edge
- Set/reset


- 22 configuration memory bits

- 8 per LUT

- C0-7
- S0-7


- 6 controls

- CB0-7

 

Combinational Logic Functions

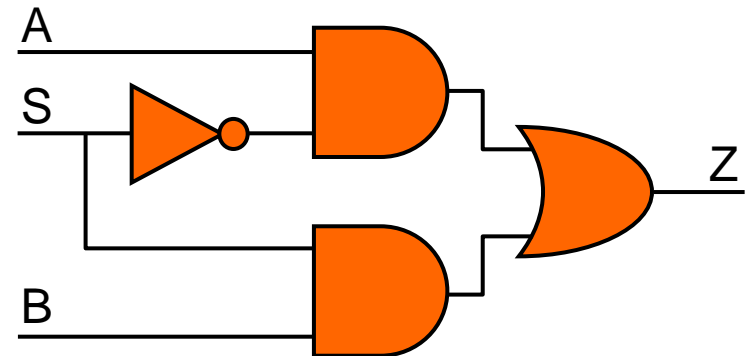
- Gates are combined to create complex circuits
- Multiplexer example
 - If $S = 0$, $Z = A$
 - If $S = 1$, $Z = B$
 - Very common digital circuit
 - Heavily used in FPGAs
 - S input controlled by configuration memory bit
 - We'll see it again



Truth table


S	A	B	Z
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

Logic symbol

 


Look-up Tables

 - Recall multiplexer example
- Configuration memory holds outputs for truth table
- Internal signals connect to control signals of multiplexers to select value of truth table for any given input value



Multiplexer

 


Truth table

S	A	B	Z
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1


Look-up Table Based RAMs

 - Normal LUT mode performs read operations
- Address decoder with write enable generates clock signals to latches for write operations
- Small RAMs but can be combined for larger RAMs




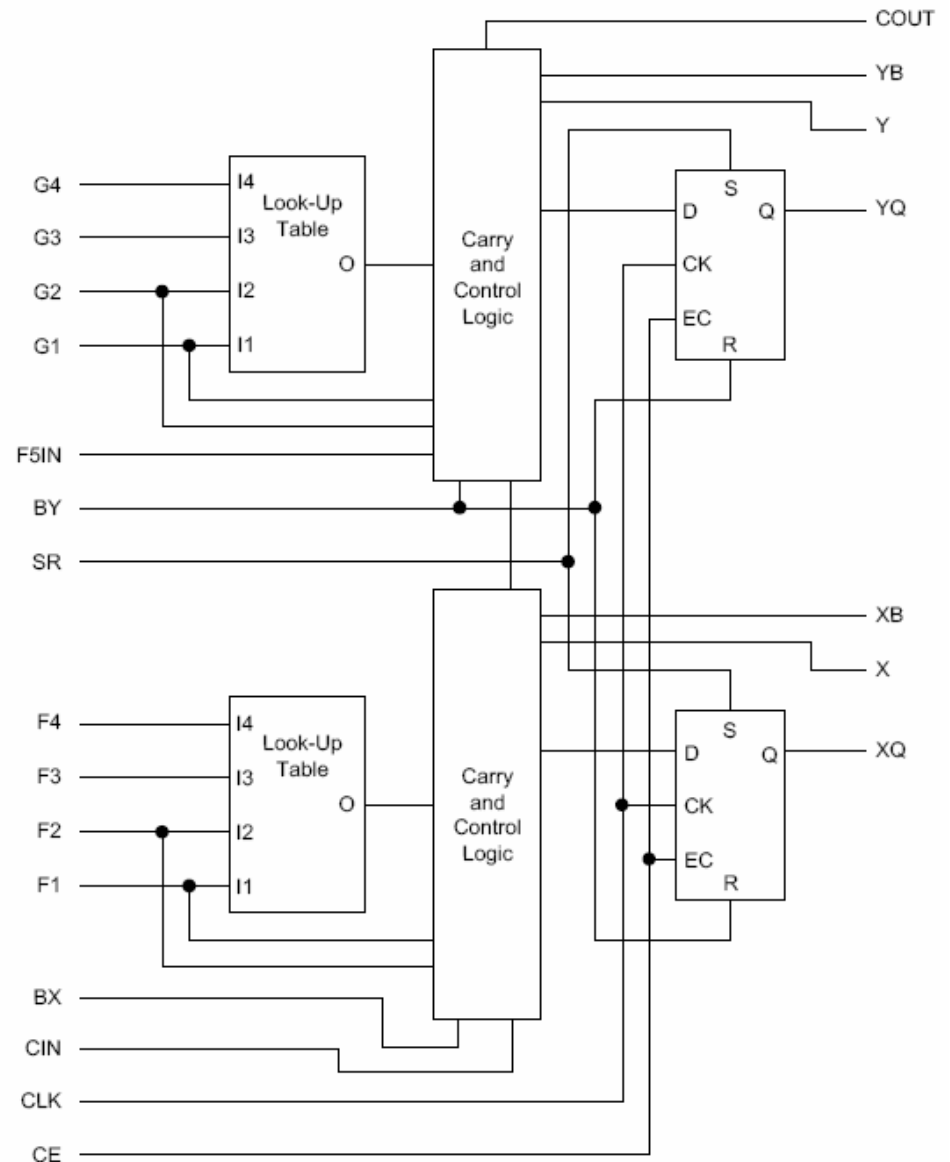Example PLB

- $\frac{1}{4}$ of a PLB (called a slice) from Xilinx Spartan 3
 - Two 4-input Look-Up Tables (LUTs)
 - Can perform any combinational logic function of up to 4 inputs
 - Can function as small RAM (16x1-bit) or shift register (up to 16-bit)
 - Two D-type flip-flops
 - Programmable as level sensitive latches
 - Programmable clock edge, clock enable, set/reset
 - Extra logic
 - Fast carry for adders
 - MUXs for Shannon expansion
 - And more




Spartan 3 PLB Slices

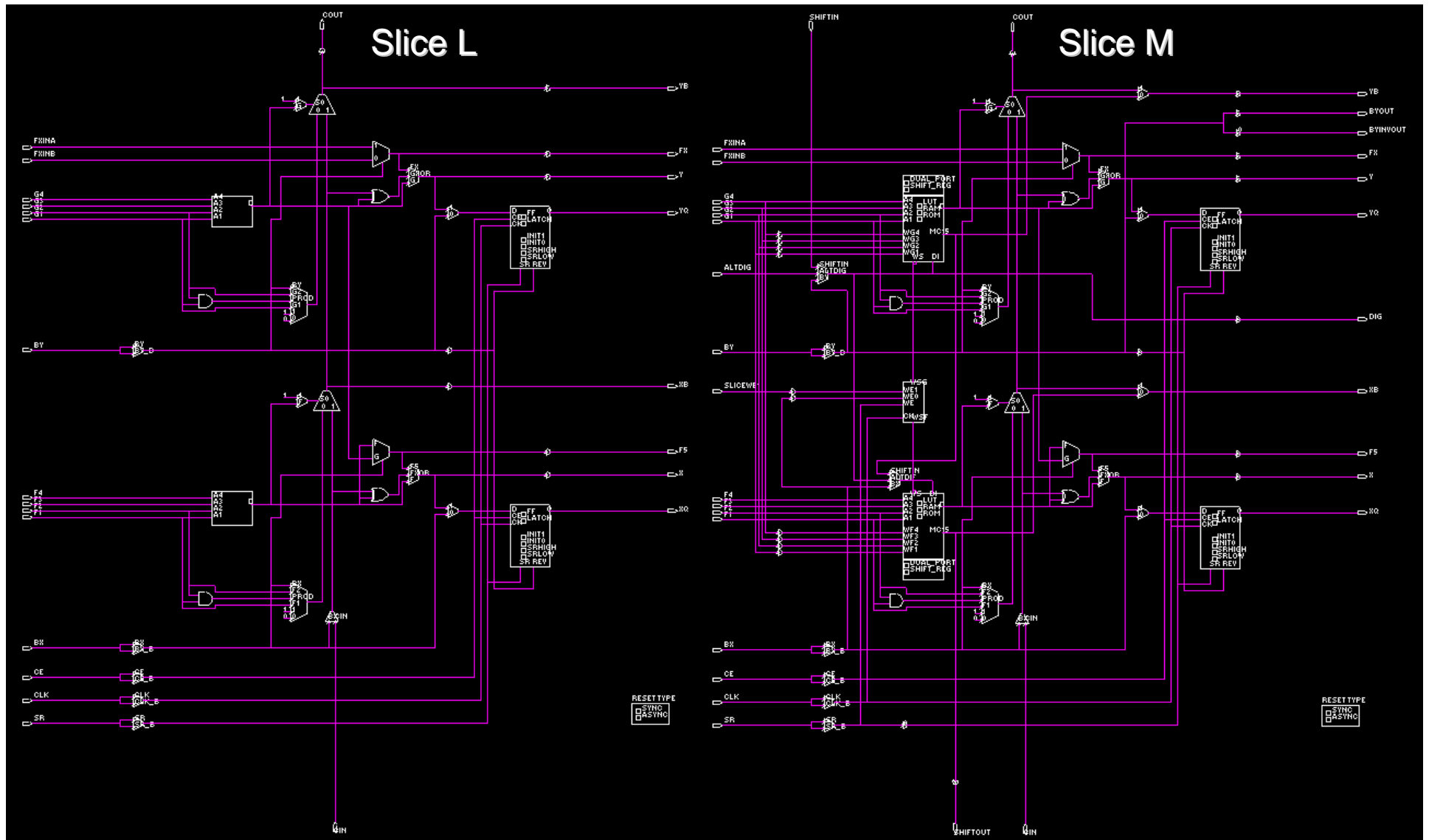


Interconnect Network

- Wire segments of varying length
 - $xN = N$ PLBs in length
 - 1, 2, 4, 6, and 8 are most common
 - $xH =$ half the array in length
 - $xL =$ length of full array
- Programmable Interconnect Points (PIPs)
 - Also known as Configurable Interconnect Points (CIPs)
 - Transmission gate connects to 2 wire segments
 - Controlled by configuration memory bit
 - 0 = wires disconnected
 - 1 = wires connected

 

PIPs

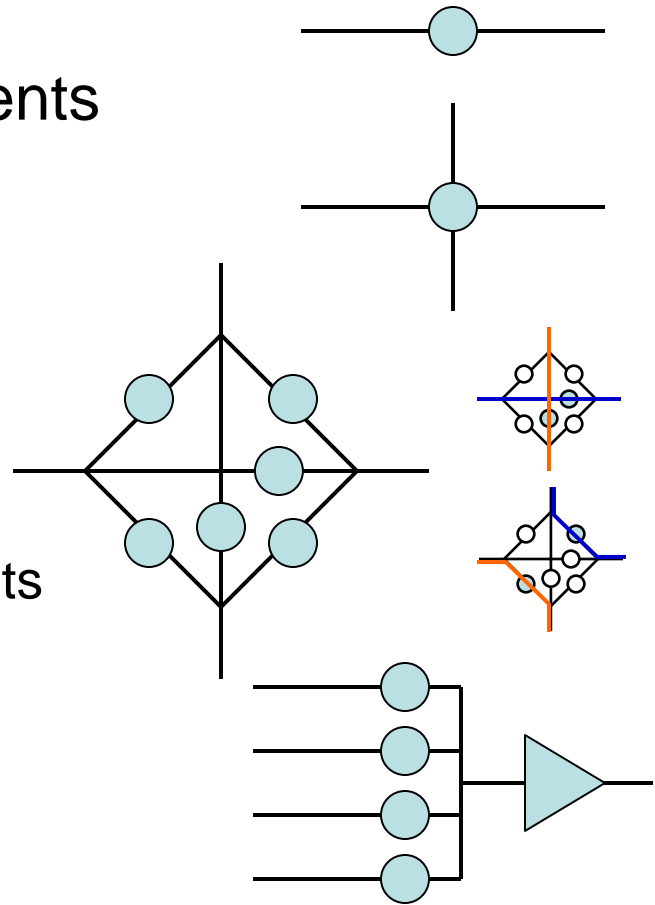- Break-point PIP
 - Connect or isolate 2 wire segments
- Cross-point PIP
 - Turn corners
- Compound cross-point PIP
 - Collection of 6 break-point PIPs
 - Can route to two isolated signal nets
- Multiplexer PIP
 - Directional and buffered
 - Select 1-of- N inputs for output
 - Decoded MUX PIP – N config bits select from 2^N inputs
 - Non-decoded MUX PIP – 1 config bit per input



Spartan 3 Routing Resources

switch matrix
over 2,400 PIPs
mostly MUX PIPs


PLB consists
of 4 slices

x6 wire
segments

x2 wire
segments

xH & xL wire
segments

over 450
total wire
segments
in PLB

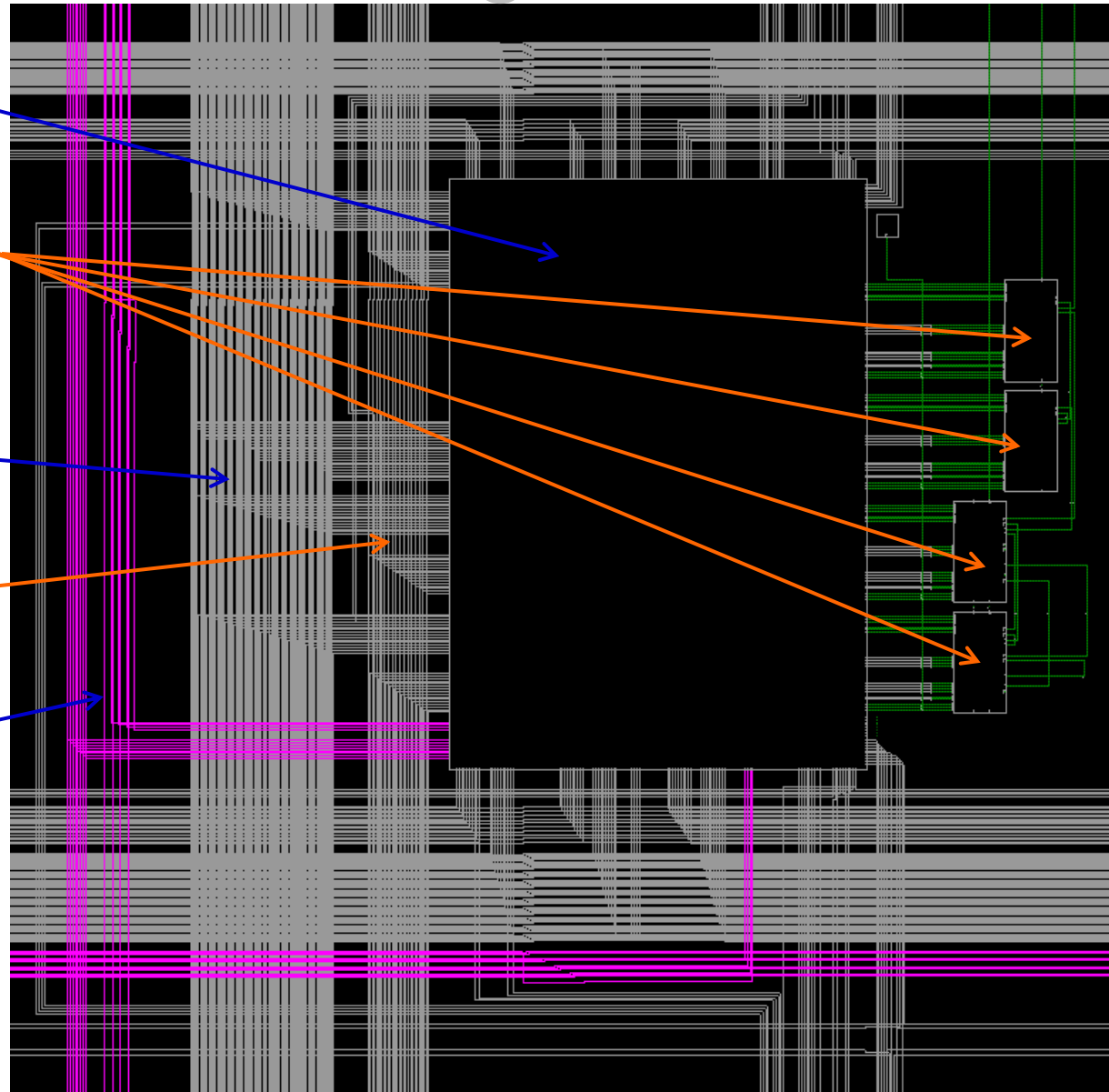

Input/Output Cells

- Bi-directional buffers
 - Programmable for input or output
 - Tri-state control for bi-directional operation
 - Flip-flops/latches for improved timing


- Set-up and hold times
- Clock-to-output delay

- Pull-up/down resistors


- Routing resources

- Connections to core of array

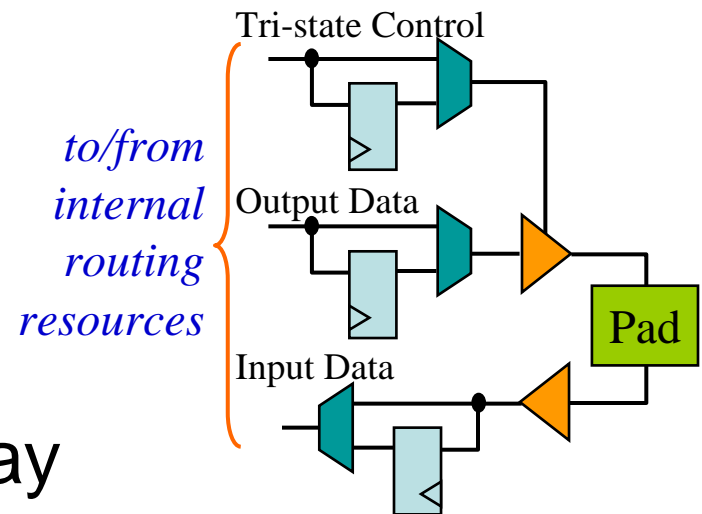- Programmable I/O voltage & current levels




Spartan 3 I/O Cell

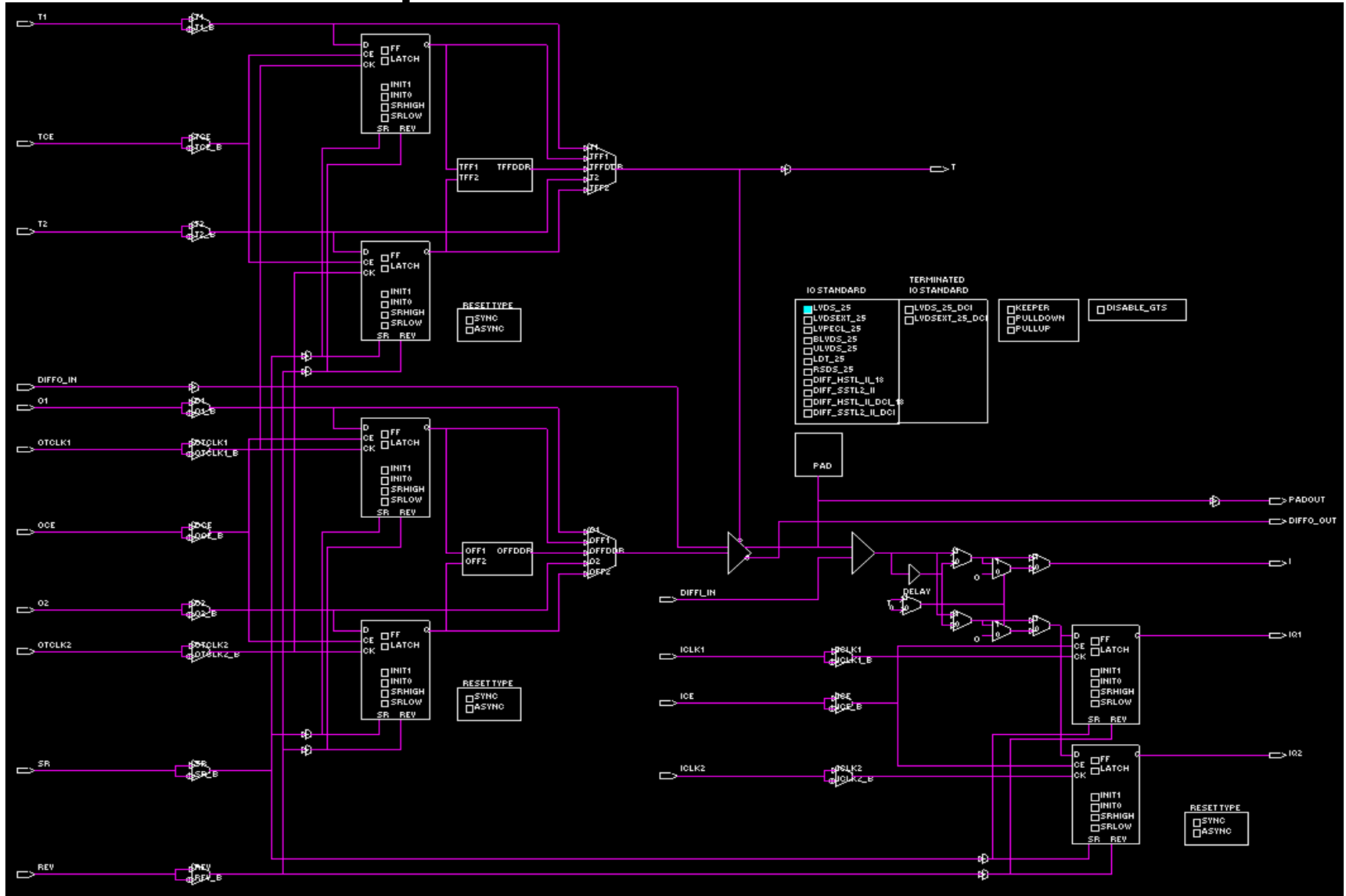

FPGAs

- Recent trend - incorporate specialized cores
 - RAMs – single-port, dual-port, FIFOs
 - 128 bits to 36K bits per RAM
 - 4 to 575 per FPGA
 - DSPs – 18x18-bit multiplier, 48-bit accumulator, etc.
 - up to 512 per FPGA
 - Microprocessors and/or microcontrollers
 - up to 2 per FPGA
 - Hard core processor
 - Support soft core processors
 - Synthesized from HDL into programmable resources

Specialized Cores

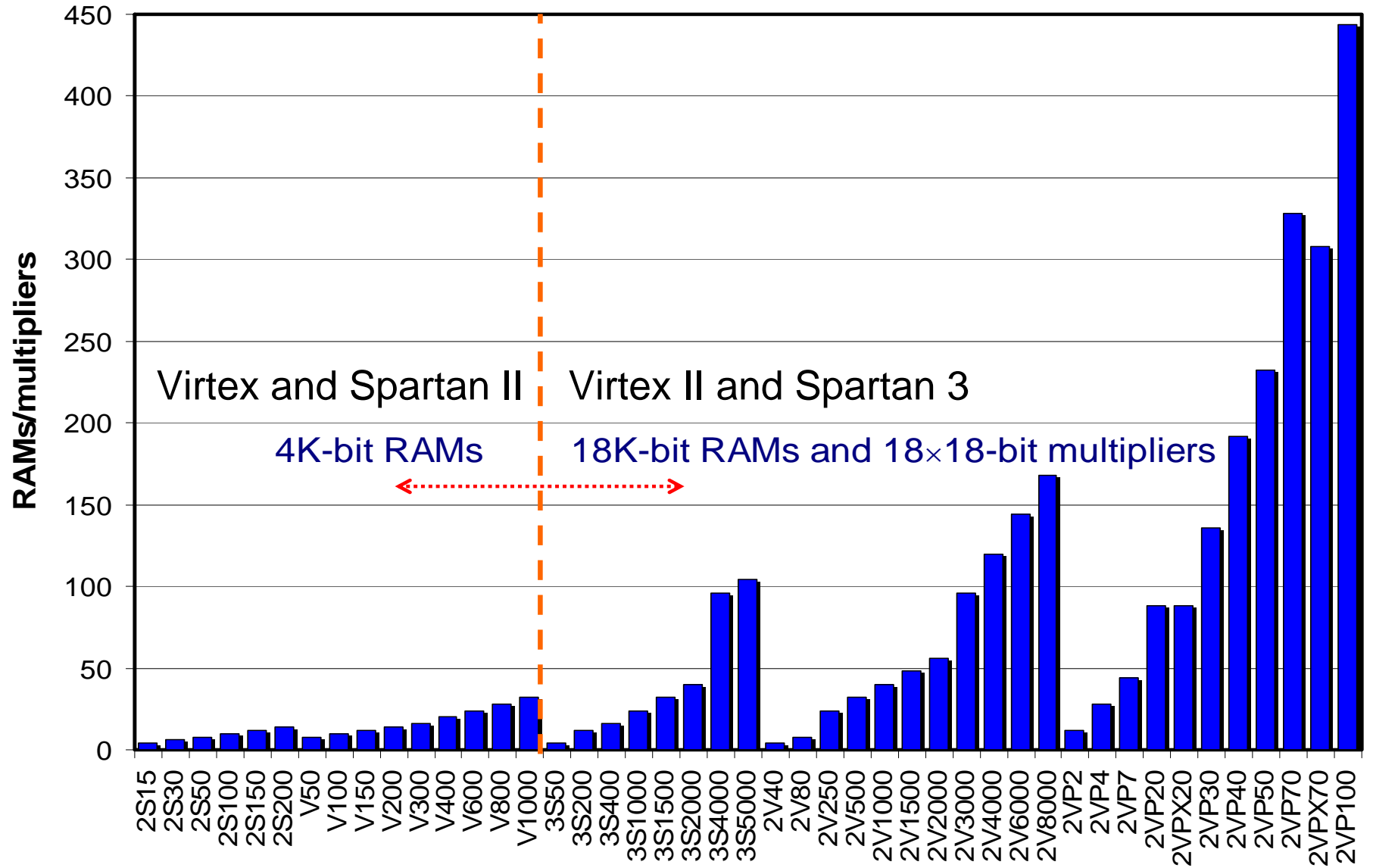


Spartan 3 Programmable RAMs

- 18 Kbit dual-port RAM
- Each port independently configurable as
 - 512 words x 36 bits
 - 32 data bits + 4 parity bits
 - 1K words x 18 bits
 - 16 data bits + 2 parity bits
 - 2K words x 9 bits
 - 8 data bits + 1 parity bit
 - 4K words x 4 bits (no parity)
 - 8K words x 2 bits (no parity)
 - 16K words x 1 bit (no parity)
- Each port has independently programmable
 - clock edge
 - active levels for write enable, RAM enable, reset

Spartan 3 (XC3S200)

 - PLBs = 24 rows x 20 columns = 480
 - 4 slices/PLB
 - 2 L slices
 - L= logic
 - 2 M slices
 - M= memory
- RAMs = 12
18Kbit dual port RAMs
- Multipliers = 12
18x18-bit signed




Ranges of Resources

FPGA Resource		Small FPGA	Large FPGA
Logic	PLBs per FPGA	256	25,920
	LUTs and flip-flops per PLB	1	8
Routing	Wire segments per PLB	45	406
	PIPs per PLB	139	3,462
Specialized Cores	Bits per memory core	128	36,864
	Memory cores per FPGA	16	576
	DSP cores	0	512
Other	Input/output cells	62	1,200
	Configuration memory bits	42,104	79,704,832

Xilinx FPGAs

- Virtex and Spartan 2
 - Array of 96 to 6,144 PLBs
 - 4 LUTs/RAMs (4-input)
 - 4 FF/latches
 - 4 to 32 4K-bit dual-port RAMs
- Virtex II, Virtex II Pro
 - Array of 352 to 11,204 PLBs
 - 8 LUTs/RAMs (4-input)
 - 8 FF/latches
 - 12 to 444 18K-bit dual-port RAMs
 - 12 to 444 18×18-bit multipliers
 - 0 to 2 PowerPC processor cores
- Virtex 4
 - Array of 1,536 to 22,272 PLBs
 - 4 LUTs/RAMs (4-input)
 - 4 LUTs (4-input)
 - 8 FF/latches
 - 48 to 552 18K-bit dual-port RAMs
 - Also operate as FIFOs
 - 32 to 512 DSP cores include:
 - 0 to 2 PowerPC processor cores

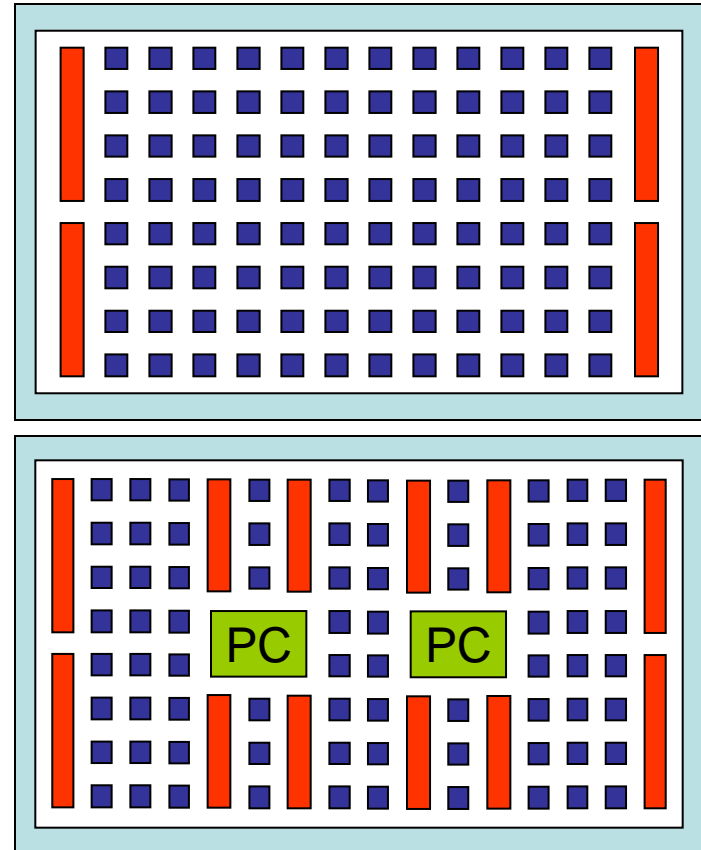

- Spartan 3
 - 480 – Array of 192 to 8,320 PLBs
 - 4 LUTs/RAMs (4-input)
 - 4 LUTs (4-input)
 - 8 FF/latches
 - 12 – 4 to 104 18K-bit dual-port RAMs
 - 12 – 4 to 104 18×18-bit multipliers

3S200