

# Combinational Logic Design Process

- Create truth table from specification
- Generate K-maps & obtain logic equations
- Draw logic diagram (sharing common gates)
- Simulate circuit for design verification
  - Debug & fix problems when output is incorrect
    - Check truth table against K-map population
    - Check K-map groups against logic equation product terms
    - Check logic equations against schematic
- Circuit optimization for area and/or performance
  - Analyze verified circuit for optimization metric
    - $G$ ,  $G_{IO}$ ,  $G_{del}$ ,  $P_{del}$
  - Use Boolean postulates & theorems
- Re-simulate & verify optimized design

# K-mapping & Minimization Steps

Step 1: generate K-map

- Put a 1 in all specified minterms
- Put a 0 in all other boxes (optional)

Step 2: group all adjacent 1s without including any 0s

- All groups (aka *prime implicants*) must be rectangular and contain a “power-of-2” number of 1s
  - 1, 2, 4, 8, 16, 32, ...
- An essential group (aka *essential prime implicant*) contains at least 1 minterm not included in any other groups
  - A given minterm may be included in multiple groups

Step 3: define product terms using variables common to all minterms in group

Step 4: sum all essential groups plus a minimal set of remaining groups to obtain a minimum SOP

# K-map Minimization Goals


- Larger groups:
  - Smaller product terms
    - Fewer variables in common
  - Smaller AND gates
    - In terms of number of inputs
- Fewer groups:
  - Fewer product terms
    - Fewer AND gates
    - Smaller OR gate
      - In terms of number of inputs
- Alternate method:
  - Group 0s
    - Could produce fewer and/or smaller product terms
  - Invert output
    - Use NOR instead of OR gate

# K-map example (text)

**FIGURE 1-3:**  
**Four-Variable**  
**Karnaugh Maps**

	<i>AB</i>				
<i>CD</i>		00	01	11	10
00		0	4	12	8
01		1	5	13	9
11		3	7	15	11
10		2	6	14	10

(a) Location of minterms

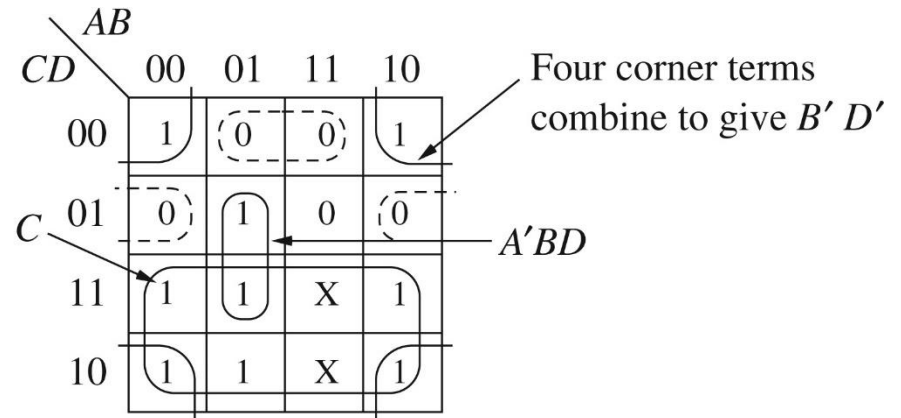

$$F = \sum m(0, 2, 3, 5, 6, 7, 8, 10, 11) + \sum d(14, 15)$$

$$= C + B'D' + A'BD$$

(b) Looping terms

# Circuit Analysis


- We can implement different circuits for same logic function that are *functionally equivalent* (produce the correct output response for all input values)
  - Which implementation is the best?
    - Depends on design goals and criteria
- Area analysis
  - Number of gates,  $G$  (most commonly used)
  - Number of gate inputs and outputs,  $G_{IO}$  (more accurate)
    - Bigger gates take up more area
- Performance analysis (*worst case path from inputs to outputs*)
  - Number of gates in worst case path from input to output,  $G_{del}$
  - More accurate delay measurement per gate
    - Propagation delay = intrinsic (*internal*) delay + extrinsic (*external*) delay
    - Relative prop delay,  $P_{del} = \# \text{ inputs to gate (intrinsic)} + \# \text{ loads (extrinsic)}$

# Circuit Analysis Example

- From previous example:

$$Z = (A + B')C + A'BC'$$

 - # gates:  $G = 7$
- # gate I/O:  $G_{IO} = 19$
- Gate delay:  $G_{del} = 4$ 
  - worst case path:  $B \rightarrow Z$
- Prop delay:  $P_{del} = 12$ 
  - worst case path:  $B \rightarrow Z$



# Design Verification Guidelines

- Use all audits and analysis aids possible to help find potential design bugs
  - Investigate and correct all errors/warnings
- Simulate thoroughly but use stimuli that “eat their way into the design” testing one function at a time
  - more important for complex circuits
- When circuit doesn’t work, see what works and what doesn’t to narrow down the search space for the problem
  - Which outputs work
  - Which outputs fail and under what conditions
  - Monitor lots of internal nodes
  - Additional simulations (with different vectors) can be helpful
- “Debugging is just like solving a puzzle”
  - “If something doesn’t look right, stop and check it out”
    - Don’t overlook potential bugs
  - “When you’ve found the problem, everything starts makes sense”
- Always re-run audits and simulation after correcting any problem (or after making any changes)
  - Another bug could be lurking, or
  - The fix may have messed up something else





# Sequential Logic Design Steps

- Derive circuit state diagram from design specs
- Create state table
- Choose flip-flops (D, T, SR, JK)
- Create circuit excitation table
  - use flip-flop excitation tables
- Construct K-maps for:
  - flip-flop inputs
  - primary outputs
- Obtain minimized SOP equations
- Draw logic diagram
- Simulate to verify design & debug as needed
- Perform circuit analysis & logic optimization



# Flip-Flop Excitation Tables & State Diagrams


<b>Q Q+</b>	<b>D</b>	<b>T</b>	<b>SR</b>	<b>JK</b>
0 0	0	0	0X	0X
0 1	1	1	10	1X
1 0	0	1	01	X1
1 1	1	0	X0	X0

    

# Sequential Design Example

Design a 3-bit gray code counter with active low synchronous reset (R)

*State Diagram*

 

Inputs R	Current state (X Y Z)	Next state (X Y Z)
0	XXX	000
1	000	001
1	001	011
1	010	110
1	011	010
1	100	000
1	101	100
1	110	111
1	111	101

*State Table*

# 3-bit Gray Code Counter

- Choose flip-flops:
  - Let X be a JK
  - Let Y be a D
  - Let Z be a SR
- Create circuit excitation table

Inputs R	Current state (X Y Z)	Next state (X Y Z)	QX		QY	QZ	
			J <sub>x</sub>	K <sub>x</sub>	D <sub>y</sub>	S <sub>z</sub>	R <sub>z</sub>
0	X X X	0 0 0	0	1	0	0	1
1	0 0 0	0 0 1	0	X	0	1	0
1	0 0 1	0 1 1	0	X	1	X	0
1	0 1 0	1 1 0	1	X	1	0	X
1	0 1 1	0 1 0	0	X	1	0	1
1	1 0 0	0 0 0	X	1	0	0	X
1	1 0 1	1 0 0	X	0	0	0	1
1	1 1 0	1 1 1	X	0	1	1	0
1	1 1 1	1 0 1	X	0	0	X	0

# 3-bit Gray Code Counter (cont)

- Generate K-Maps & obtain minimized SOPs

		YZ			
		00	01	11	10
RX	00				
	01				
	11	X	X	X	X
	10				1

$$J_x = RYZ'$$

		YZ			
		00	01	11	10
RX	00				
	01				
	11				1
	10		1	1	1

$$D_y = RYZ' + RX'Z$$

		YZ			
		00	01	11	10
RX	00				
	01				
	11			X	1
	10	1	X		

$$S_z = RXY + RX'Y'$$

		YZ			
		00	01	11	10
RX	00	1	1	1	1
	01	1	1	1	1
	11	1	0	0	0
	10	X	X	X	X

$$K_x = R' + Y'Z'$$

Further reductions:

$$R_z = R' + X \oplus Y$$


$$\begin{aligned} S_z &= R(X \oplus Y)' \\ &= (R' + X \oplus Y)' \\ &= R_z' \end{aligned}$$

		YZ			
		00	01	11	10
RX	00	1	1	1	1
	01	1	1	1	1
	11	X	1		
	10			1	X

$$R_z = R' + XY' + X'Y$$

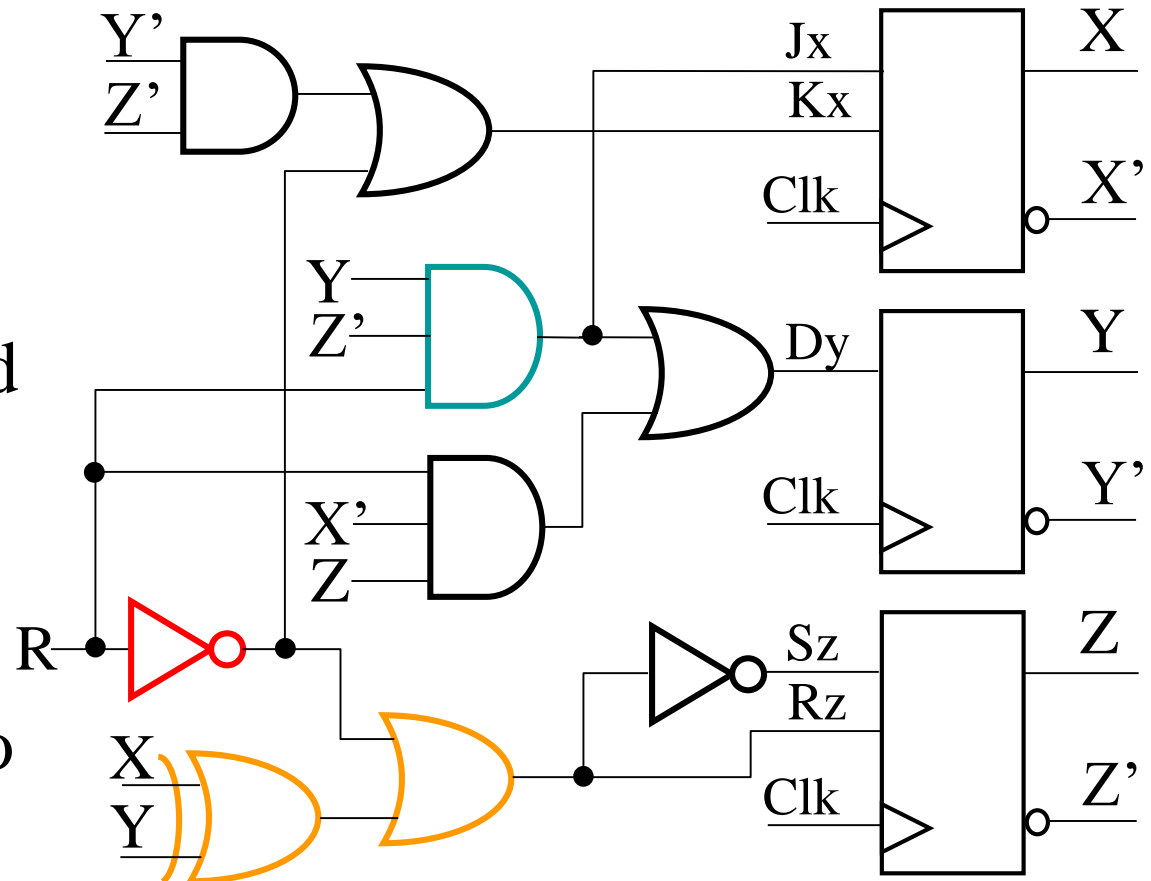
# 3-bit Gray Code Counter (cont)

- Logic diagram
- Then design verification via logic simulation
  - Debug as needed to obtain working circuit
  - Update logic diagram, logic equations, etc. to reflect fixes


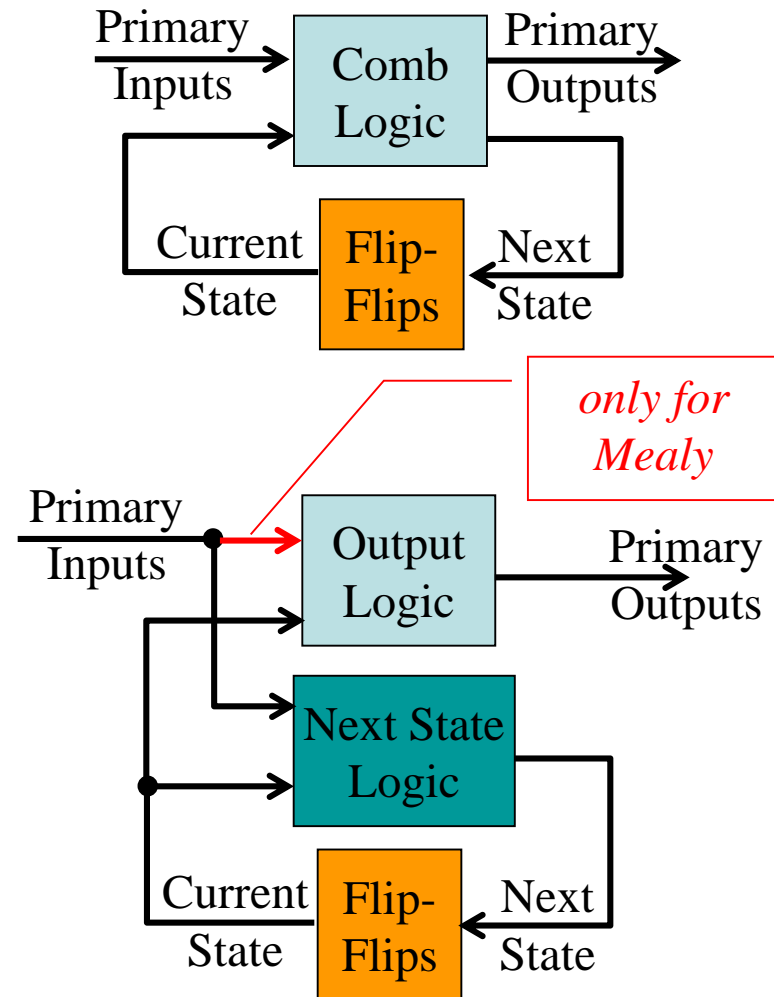
# Sequential Logic Models


- Huffman model consists of two types:
  - Mealy model (aka Mealy machine)
    - Outputs are function inputs and current state
      - Outputs can change when inputs change or when current state changes
  - Moore model (aka Moore machine)
    - Outputs are function of current state only
      - Outputs can change only when current state changes


 
# Mealy & Moore State Diagrams


- **Mealy** model

- Outputs associated with state transition
- Output values shown with inputs





- **Moore** model

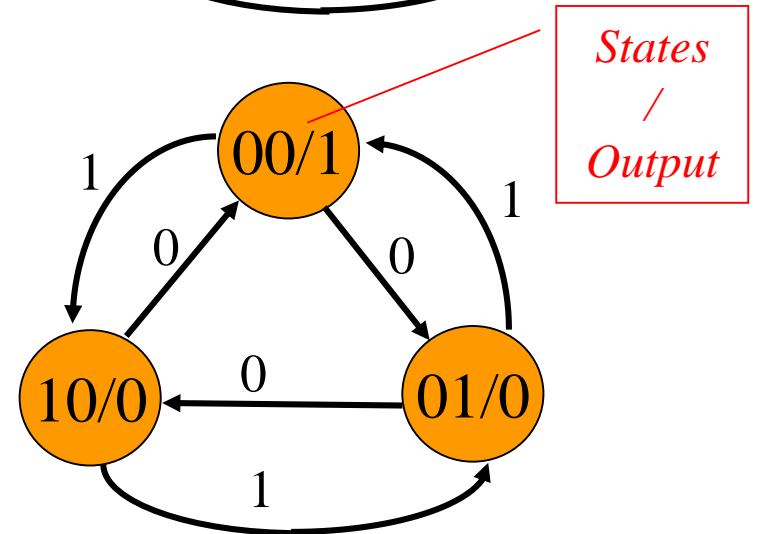- Outputs associated with states only
- Output values shown with states



# Mealy & Moore State Tables

  

In	X	Y	X <sup>+</sup>	Y <sup>+</sup>	D <sub>X</sub>	D <sub>Y</sub>	O <sub>Mealy</sub>	O <sub>Moore</sub>
0	0	0	0	1	0	1	1	1
0	0	1	1	0	1	0	0	0
0	1	0	0	0	0	0	1	0
1	0	0	1	0	1	0	1	1
1	0	1	0	0	0	0	1	0
1	1	0	0	1	0	1	0	0
0	1	1	X	X	X	X	X	X

*Note: next state (next state logic) is same for both Mealy & Moore – only output is different*



# Mealy & Moore Design Examples

In this example the Dx and Dy circuits are the same for both Mealy and Moore  
But the outputs circuits are different with the Moore being a function of X and Y only

In \ X Y	00	01	11	10
0	0	1	X	0
1	1	0	X	0

$$D_X = In'Y + InX'Y'$$

In \ X Y	00	01	11	10
0	1	0	X	1
1	1	1	X	0

$$O_{Mealy} = In'Y' + InX'$$

In \ X Y	00	01	11	10
0	1	0	X	0
1	0	0	X	1

$$D_Y = InX + In'X'Y'$$

In \ X Y	00	01	11	10
0	1	0	X	0
1	1	0	X	0

$$O_{Moore} = X'Y'$$



# Mealy & Moore Design Examples

$$O_{\text{Mealy}} = \text{In}'Y' + \text{In}X'$$

$$D_X = \text{In}'Y + \text{In}X'Y'$$

$$D_Y = \text{In}X + \text{In}'X'Y'$$

$$O_{\text{Moore}} = X'Y'$$

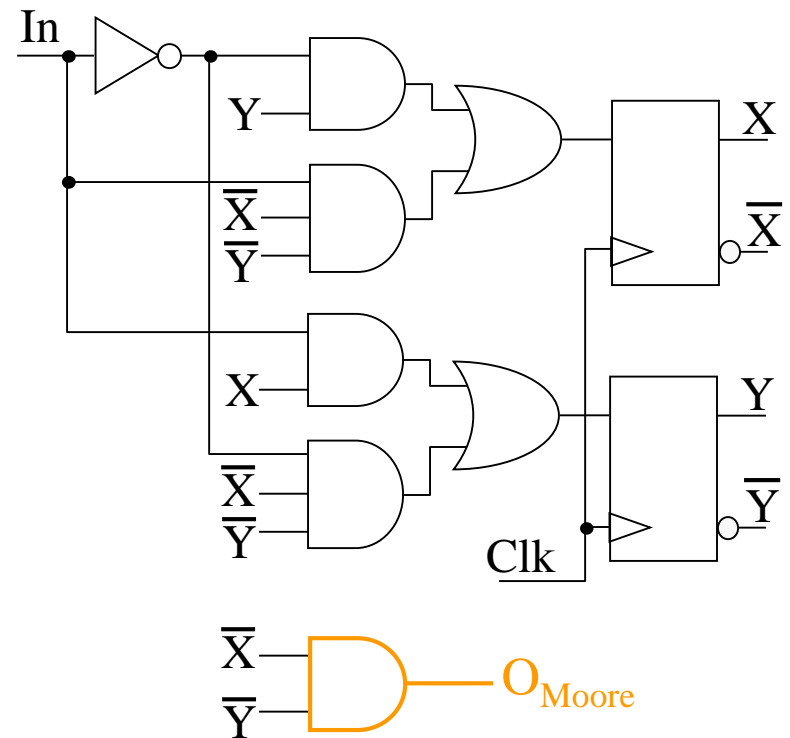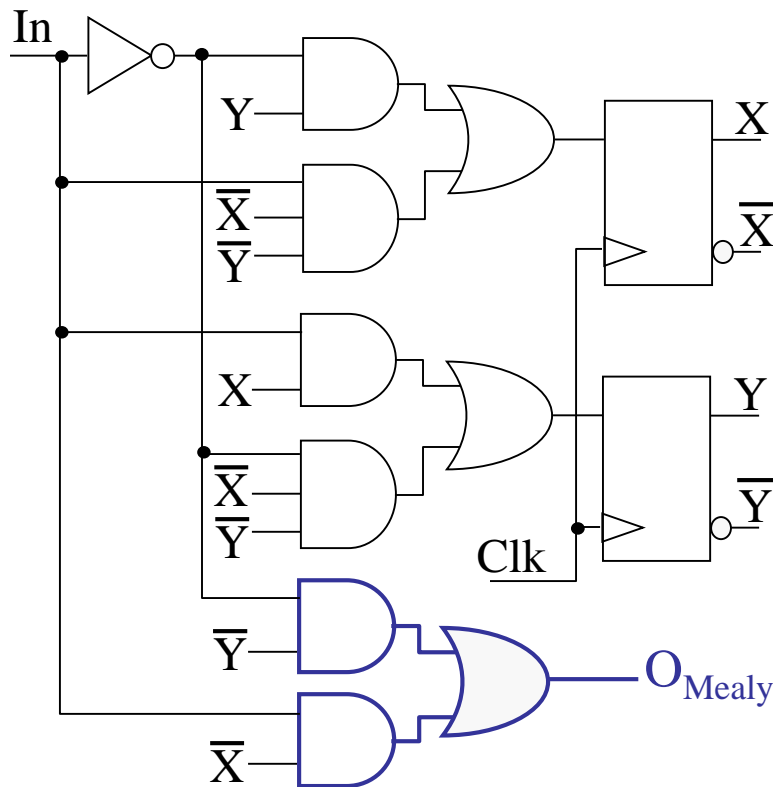


Note:  $O_{\text{Mealy}}$  *is* a function of In but  $O_{\text{Moore}}$  *is not* a function of In
 
# Flip-Flop Initialization

- Preset (aka set)  $\Rightarrow Q^+ = 1$
- Clear (aka reset)  $\Rightarrow Q^+ = 0$
- Some flip-flops have:
  - Both preset and clear (set and reset)
  - A preset or a clear
  - Neither (JK & SR flops have set/reset functions)
- Preset and/or clear can be
  - Active high or active low
  - Synchronous  $\Rightarrow$  with respect to active edge of clock
  - Asynchronous  $\Rightarrow$  independent of clock edges
- Initialization important for:
  - logic simulation to remove undefined logic values
    - 2, 3, U, etc.
  - system operation to put system in a known state


*Typical logic symbol  
with active high preset  
and active low clear  
Cannot determine sync  
or async from symbol*



# Synchronous vs. Asynchronous


- Synchronous => states of memory elements change only with respect to active edge of clock
- Asynchronous => states of memory elements can change without an active edge of clock
  - Asynchronous designs often have timing problems

 *Example: assume active high sync preset and active low async clear*


 
# System-Level Timing

- System set-up time:  $P_{deli} + P_{bufi} + t_{su} - P_{clk(min)}$ 
  - $P_{deli} + P_{bufi} + t_{su}$
- System hold time:  $t_h + P_{clk} - P_{deli(min)} - P_{bufi(min)}$ 
  - $t_h + P_{clk}$
- System clock-to-output:  $t_{co} + P_{delo} + P_{bufo} + P_{clk}$
- *Minimum times are difficult to guarantee*
  - *Typically assume 0*



# System-Level Timing

- System set-up time:  $P_{bufi} + t_{su(latch)} - P_{clk(input)min}$
- System hold time:  $t_{h(latch)} + P_{clk(input)} - P_{bufi(min)}$
- System clock-to-output:  $t_{co} + P_{bufo} + P_{clk(output)}$
- Improvement techniques:
  - Re-clock signals onto/off subcircuit, chip, PCB, or system
  - Fanout clock into input, main, and output clocks
  - 0-hold-time latches on input signals

