

**Tuesday 2/19/19**

## **Nonlinear Oscillators**

Our definition: an oscillator with a periodic non-sinusoidal output, such as a square wave.

- 1) Sinusoidal oscillator circuit with really high amplifier gain, much higher than necessary to satisfy the BSC


Let's revisit the Wein bridge oscillator (shown on next page)

$R_3$  of 15 k $\Omega$  achieved oscillation. Let's make  $R_3$  by 25 k $\Omega$  and evaluate the difference. As  $R_3$  gets large, the tops of the output signal flatten out, more closely approximating a square wave. This forces more of the time varying signal to reside in the nonlinear range of the op amp, effectively clipping it.

However, the bottom part of the output square wave is close to -4V, not 0V, as would be expected of a digital signal. A clipping diode can be added off the op amp output signal and applied to a 100 k $\Omega$  load resistor. This removes most of the negative going part of the periodic signal.

Two CMOS inverters were added after the 100 k $\Omega$  load resistor, and fed to another 100 k $\Omega$  load resistor to square up the signal <see below>.
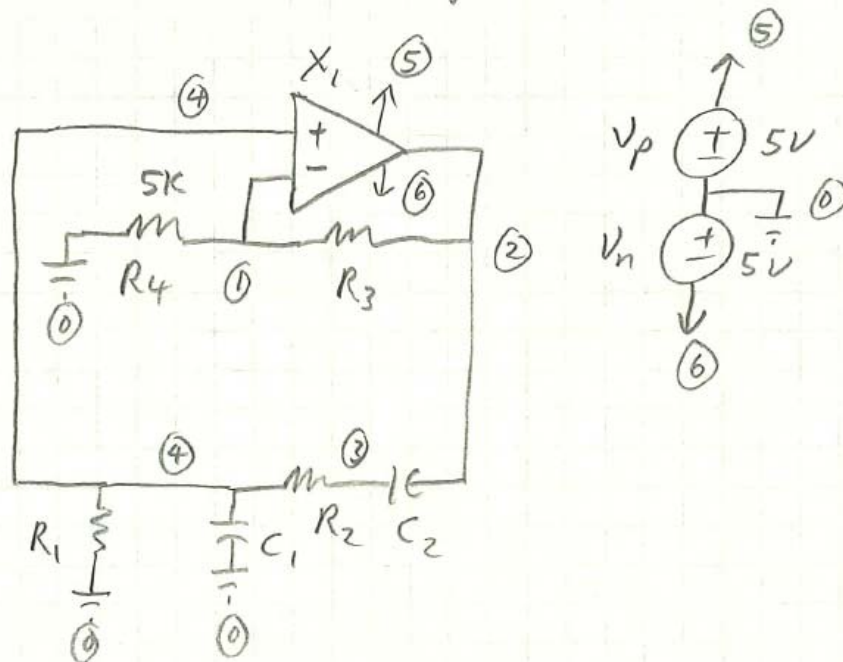
## PSpice Simulated Wein Bridge Oscillator



$$f = \frac{1}{2\pi RC} = \frac{1}{2\pi(159.155)(1 \times 10^{-6})} = 1000 \text{ kHz}$$

$$C_1 = C_2 = 1 \mu\text{F}$$

$$R_1 = R_2 = 159.155 \Omega$$

$$1 + \frac{R_3}{R_4} = 3 \rightarrow R_4 = 5 \text{ K}\Omega, R_3 = 10 \text{ K}\Omega$$

$X_1$ : AD8610 op amp  $\rightarrow$  25MHz GBW product


Result  $\rightarrow$  no oscillation

$\therefore R_3$  increased to 15 K $\Omega$  to achieve oscillation


Output: Distorted sinusoid:  $f = 857.93 \text{ Hz}$

Possible causes for lower freq:

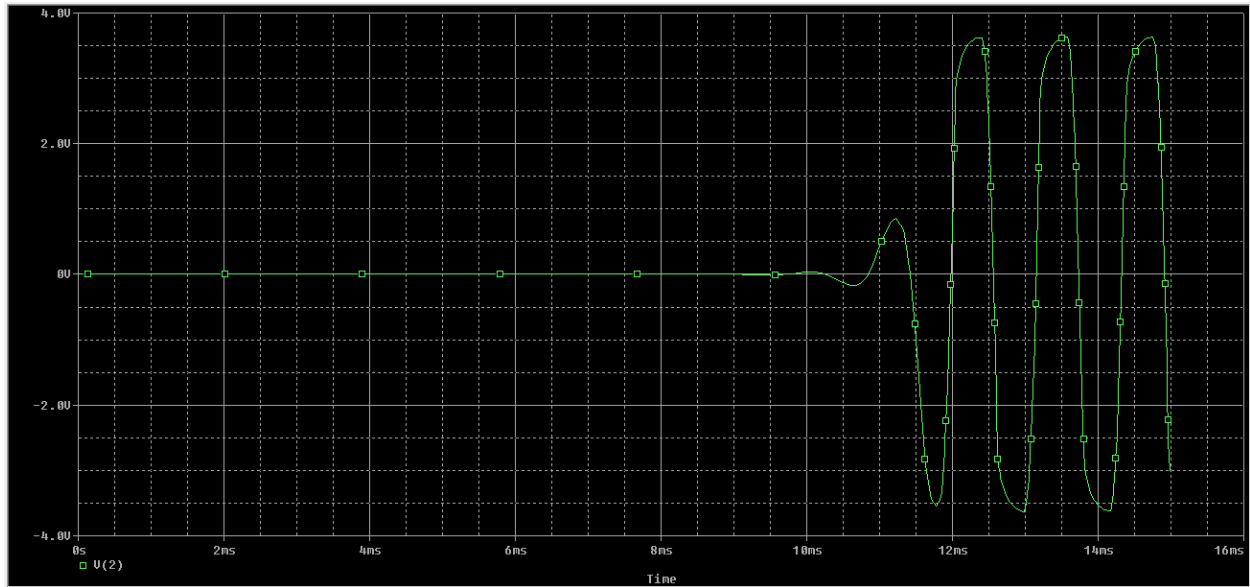
- ① phase shift in op amp
- ② nonlinear distortion near power supply rails




V(2) with  $R_3 = 15\text{ k}\Omega$

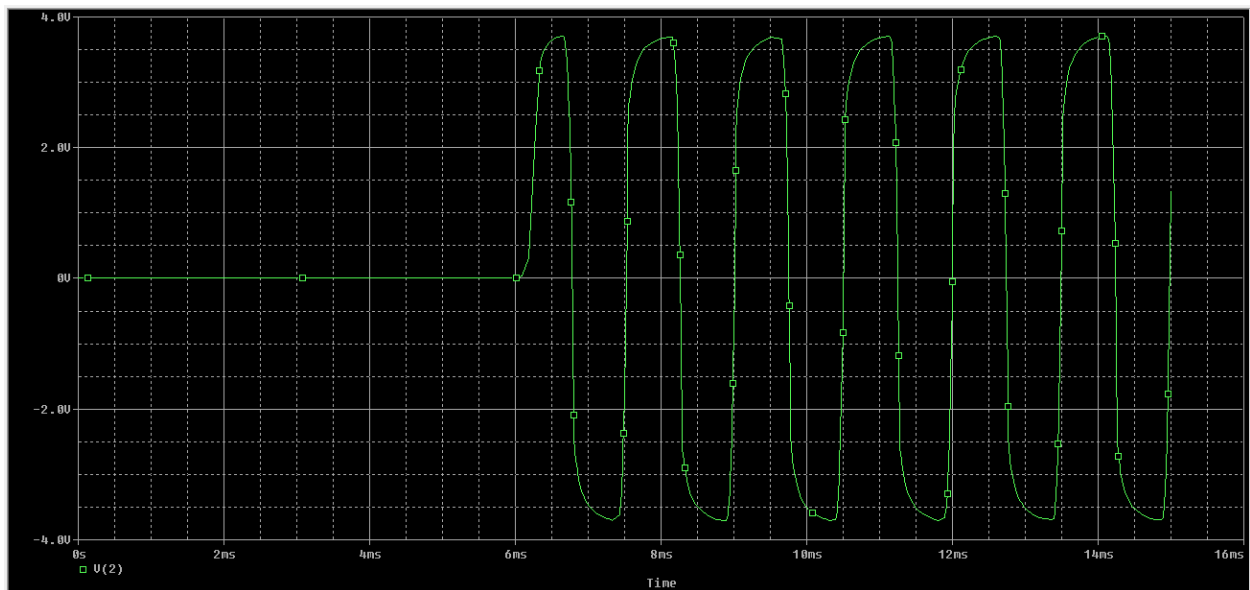

V(2) with  $R_3 = 25\text{ k}\Omega$

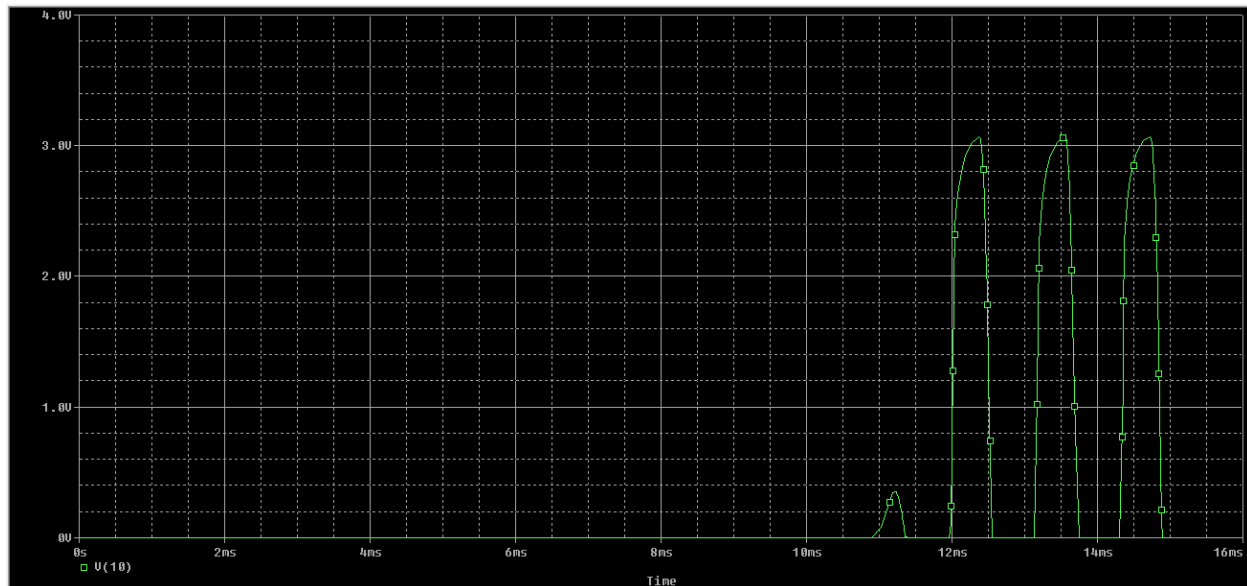

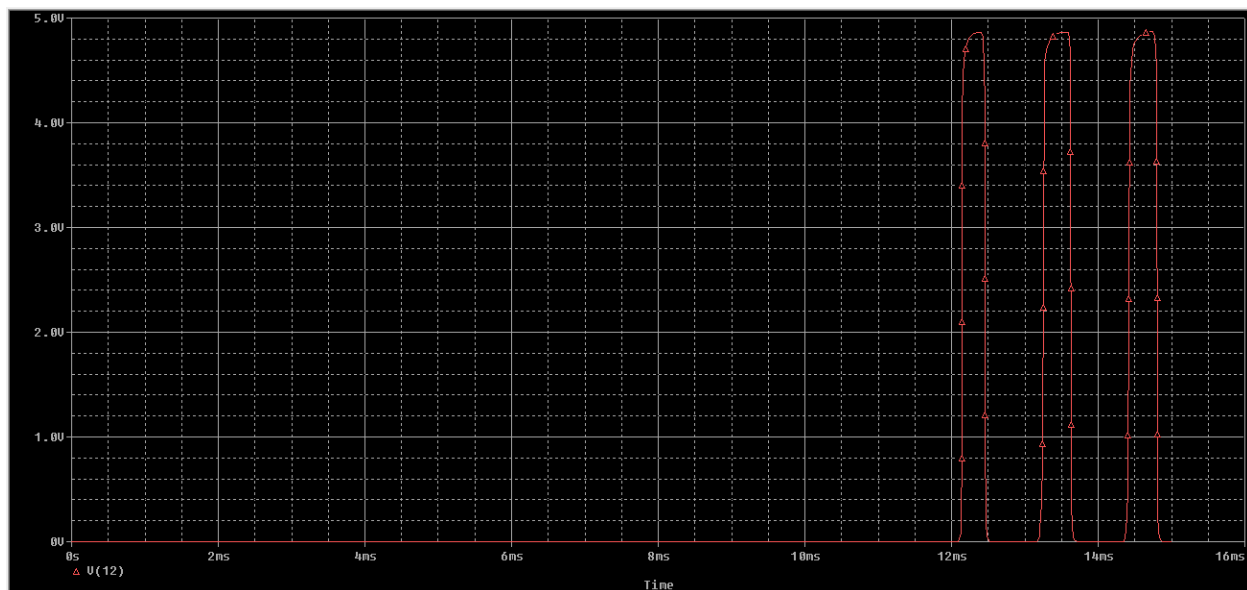
Voltage waveform after the diode. Observe that the peak voltage has dropped due to the voltage drop across the diode.



Voltage waveform after two CMOS inverters following the clipping diode circuit.

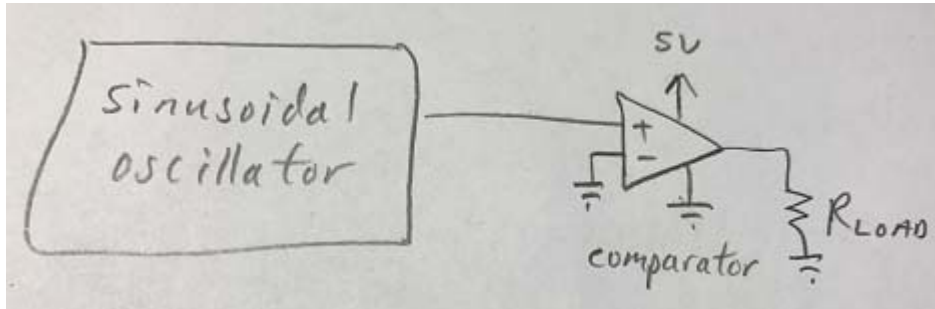2) A rail-to-rail comparator added to the sinusoidal oscillator's output

This circuit can convert the sinusoidal output voltage to a square wave.



### More on Nonlinear Oscillators

#### a. Terminology

The term Multivibrator is often used in texts describing nonlinear oscillators. A multivibrator is an electronic circuit that switches between 2 states and consists of two amplifying devices cross coupled with resistors and capacitors:


1. **Astable Multivibrator:** a multivibrator circuit where neither state is stable. It continually switches back and forth between the two states.
2. **Monostable Multivibrator:** a multivibrator circuit with one stable state and one unstable state. A trigger pulse causes the circuit to temporarily switch to the unstable state, where the circuit eventually switches back to the stable state and then stays there until another trigger pulse is applied. A One Shot is a multivibrator.
3. **Bistable Multivibrator:** a multivibrator with two stable states. A trigger pulse is required to change either state. A flipflop is a bistable multivibrator.

A Relaxation Oscillator is an astable multivibrator that uses an active circuit element to charge an inductor or a capacitor through a resistor until a threshold current or voltage is reached, where the circuit then changes states and discharges or recharges the inductor or capacitor. The time constant of the inductor or capacitor circuit determines the oscillation frequency.

A Ring Oscillator consists of an odd number of inverters (NOT gates) connected in a continuous chain. The odd number results in the impossibility of a stable condition, so the circuit oscillates, and the oscillation frequency is due to the propagation delay through each inverter. Adding more inverters to the chain reduces the oscillation frequency.

b. Time constant trigger for a state change

Consider the RC circuit below:

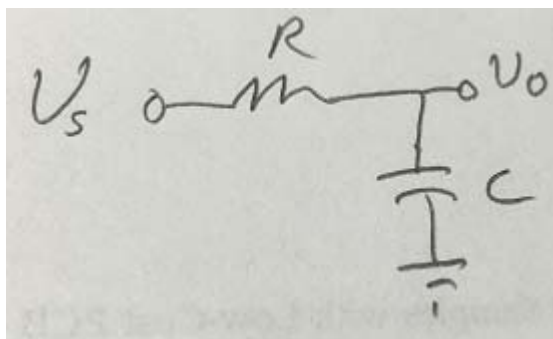

Initially, C has no stored charge ( $V_o = 0V$ ). At  $t=0$ , a positive DC voltage,  $V_s$ , is applied to the resistor.  $V_o$  will increase until it reaches a trip voltage level,  $t_{tr}$  sec later.

$$V_o(s) = V_s(s) \frac{\frac{1}{sC}}{R + \frac{1}{sC}}$$

$$V_o(s) = V_s(s) \frac{\frac{1}{RC}}{s + \frac{1}{RC}}$$

$$V_s(s) = \frac{v_s}{s}$$

$$V_o(s) = \frac{v_s}{s} \frac{\frac{1}{RC}}{s + \frac{1}{RC}} = \frac{A}{s} + \frac{B}{s + \frac{1}{RC}}$$

Using partial fraction expansion:

$$A = \frac{v_s \frac{1}{RC}}{0 + \frac{1}{RC}} = v_s$$

$$B = \frac{v_s \frac{1}{RC}}{-\frac{1}{RC}} = -v_s$$

Therefore:

$$V_o(s) = \frac{v_s}{s} - \frac{v_s}{s + \frac{1}{RC}}$$

$$v_o(t) = v_s(1 - e^{-\frac{t}{RC}})$$

Rearranging terms:

$$\frac{v_o}{v_s} = 1 - e^{-\frac{t}{RC}}$$

$$e^{-\frac{t}{RC}} = 1 - \frac{v_o}{v_s}$$


$$-\frac{t}{RC} = \ln\left(1 - \frac{v_o}{v_s}\right)$$

$$t = -RC \left[ \ln\left(1 - \frac{v_o}{v_s}\right) \right]$$

$\tau$  is the time,  $t$ , it takes  $v_o(t)$  to reach a trip voltage to cause the multivibrator circuit to change states. For an astable multivibrator with 2 time constant trip circuits,  $\tau_1$  and  $\tau_2$ :

$$T \approx \tau_1 + \tau_2 .$$

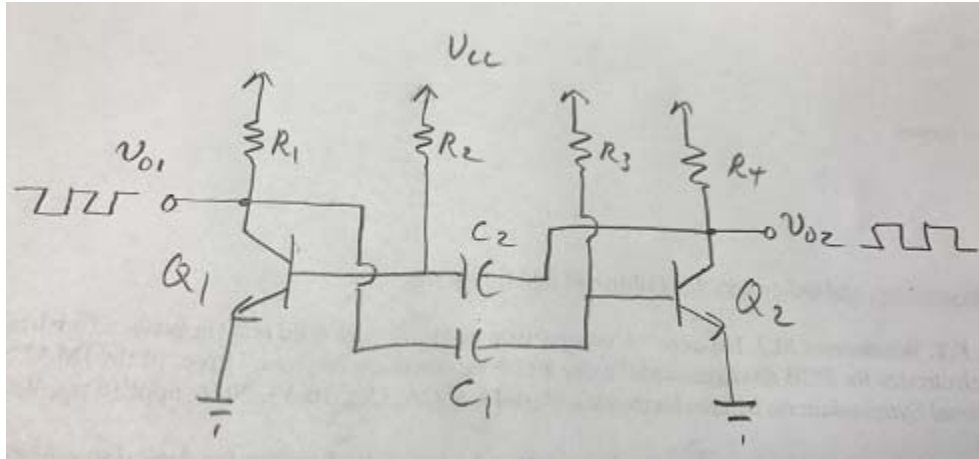c. 2 transistor classical astable multivibrator circuit



$Q_1$  and  $Q_2$  are identical NPN transistors.

$$C_1 = C_2$$

$R_1 = R_4$ , and are relatively small

$$R_2 = R_3$$

For  $V_{BE} < 0.7V$ ,  $Q_1$  and  $Q_2$  are in cutoff ( $I_c = 0A$ )

Assume that  $Q_1$  is on ( $V_{BE} = 0.7V$ ) and  $Q_2$  is in cutoff.

The left plate of  $C_1$  is approximately at 0V (gnd) while the right plate is tied to  $V_{cc}$  through  $R_3$ , charging it up.

The left plate of  $C_2$  is held at approx. 0.7 V ( $V_{BE}$  of  $Q_1$ ) while the right plate is held at approximately  $V_{cc}$  through  $R_4$  with  $Q_2$ 's  $I_c = 0V$




Once the right plate of  $C_1$  reaches 0.7V,  $Q_2$  turns on (the right plate of  $C_2$  drops to approx. 0V (gnd). Since the voltage across a capacitor cannot change instantaneously, the left plate voltage of  $C_2$  drops from 0.7V to -4.3V, turning off  $Q_1$ .

$C_2$  then starts charging through  $R_2$  until the  $Q_1$ 's  $v_{BE}$  reaches 0.7V ...

Therefore,  $\tau_1$  is set by  $C_1R_3$  and  $\tau_2$  is set by  $C_2R_2$ .

$$f \approx \frac{1}{\tau_1 + \tau_2}$$

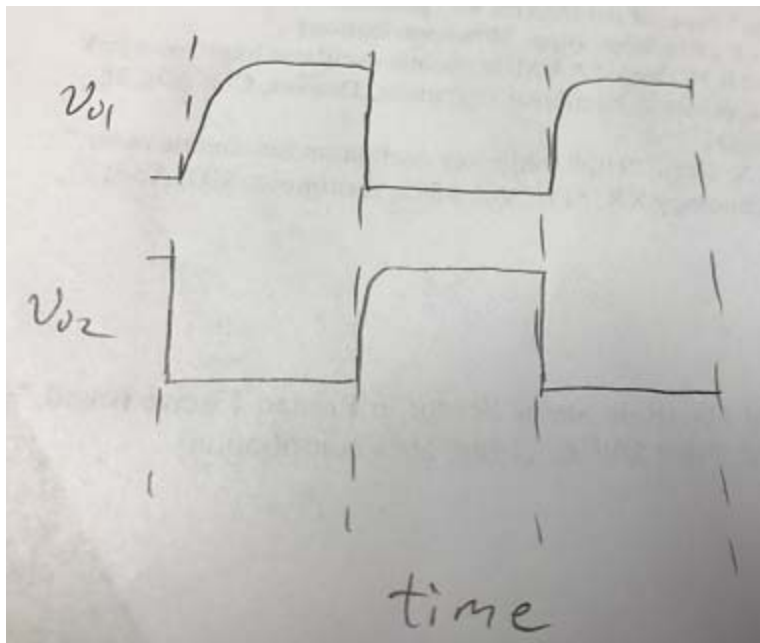

Approximate waveforms for  $v_{o1}(t)$  and  $v_{o2}(t)$ .

The output voltages,  $v_{o1}(t)$  and  $v_{o2}(t)$ , are inverted. The logic level 1 is  $V_{cc}$ . The exponential rise when either output voltage goes high is due to the capacitors charging through  $R_1$  and  $R_4$ , respectively.

### Application

Let  $V_{cc}$  be 12V and “gnd” be -12V. Connect  $v_{o1}(t)$  to  $v_{o2}(t)$  through the secondary of a 10:1 transformer. The voltage across the primary of the transformer switches between 120V and -120V and is approximately a square wave. The circuit is now a simple DC to AC inverter for power applications, useful for non-sinusoidal power applications.