

# Lecture 4 – Finite State Machines


# Modeling Finite State Machines (FSMs)

---

- “Manual” FSM design & synthesis process:
  1. Design state diagram (behavior)
  2. Derive state table
  3. Reduce state table
  4. Choose a state assignment
  5. Derive output equations
  6. Derive flip-flop excitation equations
- Steps 2-6 can be automated, given a state diagram
  1. Model states as enumerated type
  2. Model output function (Mealy or Moore model)
  3. Model state transitions (functions of current state and inputs)
  4. Consider how initial state will be forced

# FSM structure


---

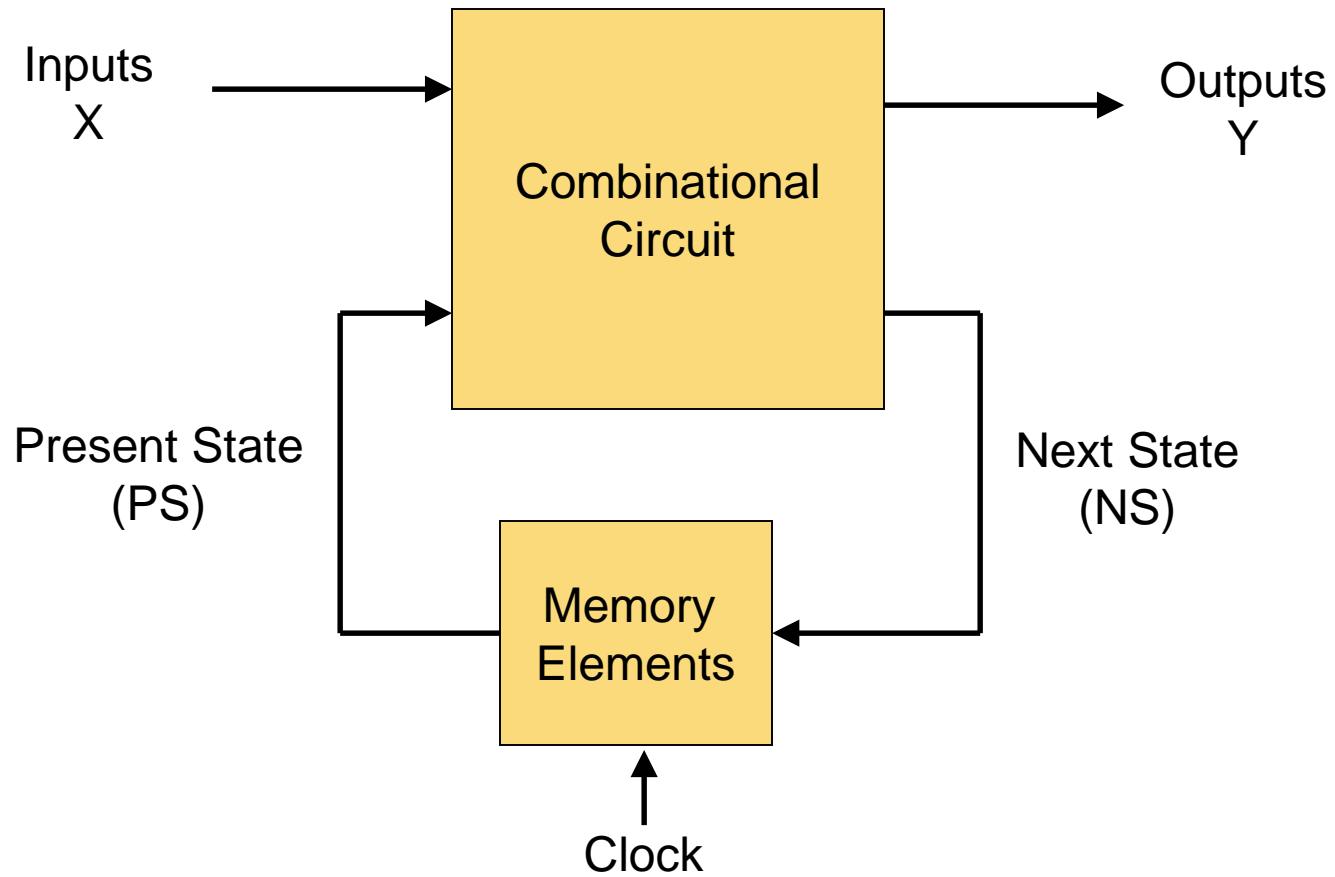


# Mealy Machine and Moore Machine

---


**Mealy Machine**

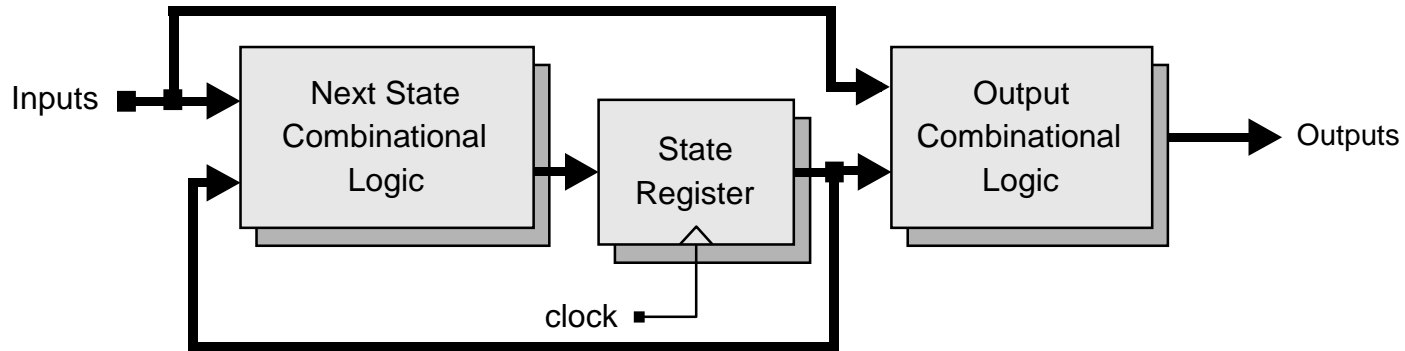

**Moore Machine**

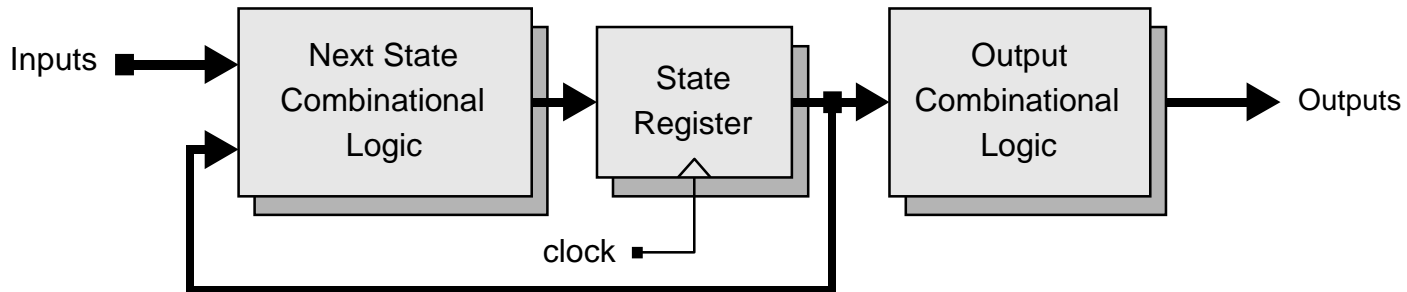

# FSM example – Mealy model

 

entity seqckt is

```

port ( x: in  std_logic;  -- FSM input
      z: out std_logic;  -- FSM output
      clk: in std_logic ); -- clock
end seqckt;
```

# FSM example - behavioral model

---

architecture behave of seqckt is

type states is (A,B,C); -- symbolic state names  
(enumerate)

signal state: states; --state variable

begin

-- Output function (combinational logic)

z <= '1' when ((state = B) and (x = '1')) --all conditions  
          or ((state = C) and (x = '1')) --for which z=1.  
          else '0'; --otherwise z=0

-- State transitions on next slide

# FSM example – state transitions

---

```
process (clk) – trigger state change on clock transition
begin
  if rising_edge(clk) then -- change state on rising clock edge
    case state is -- change state according to x
      when A => if (x = '0') then
                  state <= A;
                else -- if (x = '1')
                  state <= B;
                end if;
      when B => if (x='0') then
                  state <= A;
                else -- if (x = '1')
                  state <= C;
                end if;
      when C => if (x='0') then
                  state <= C;
                else -- if (x = '1')
                  state <= A;
                end if;
    end case;
  end if;
end process;
```

# FSM example – alternative model

---

architecture behave of seqckt is

type states is (A,B,C); -- symbolic state names  
(enumerate)

signal pres\_state, next\_state: states;

begin

-- Model the memory elements of the FSM

process (clk)

begin


if (clk'event and clk='1') then

pres\_state <= next\_state;

end if;

end process;

(continue on next slide)

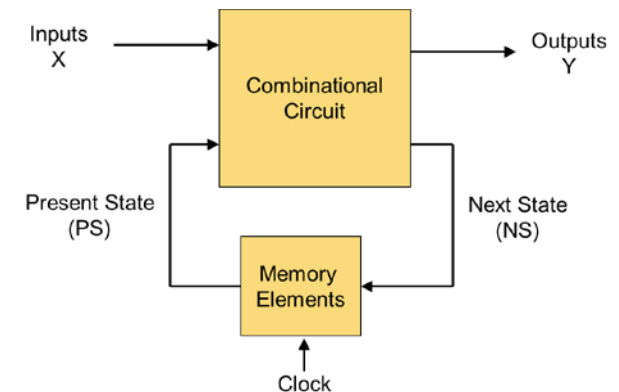



# FSM example (alternate model, continued)

- Model next-state and output functions of the FSM
- as combinational logic

```
process (x, pres_state) -- function inputs
begin
    case pres_state is -- describe each state
        when A => if (x = '0') then
            z <= '0';
            next_state <= A;
        else -- if (x = '1')
            z <= '0';
            next_state <= B;
        end if;
```

(continue on next slide for pres\_state = B and C)

# FSM example (alternate model, continued)

---

```
when B => if (x='0') then
    z <= '0';
    next_state <= A;
else
    z <= '1';
    next_state <= C;
end if;
when C => if (x='0') then
    z <= '0';
    next_state <= C;
else
    z <= '1';
    next_state <= A;
end if;

end case;
end process;
```

# Alternative form for output and next state functions (combinational logic)


## -- Next state function (combinational logic)

```
next_state <= A when ((curr_state = A) and (x = '0'))
                or ((curr_state = B) and (x = '0'))
                or ((curr_state = C) and (x = '1')) else
    B when ((curr_state = 1) and (x = '1')) else
    C;
```

## -- Output function (combinational logic)

```
z <= '1' when ((curr_state = B) and (x = '1'))    --all conditions
                or ((curr_state = C) and (x = '1')) --for which z=1.
                else '0';                          --otherwise z=0
```

# Moore model FSM

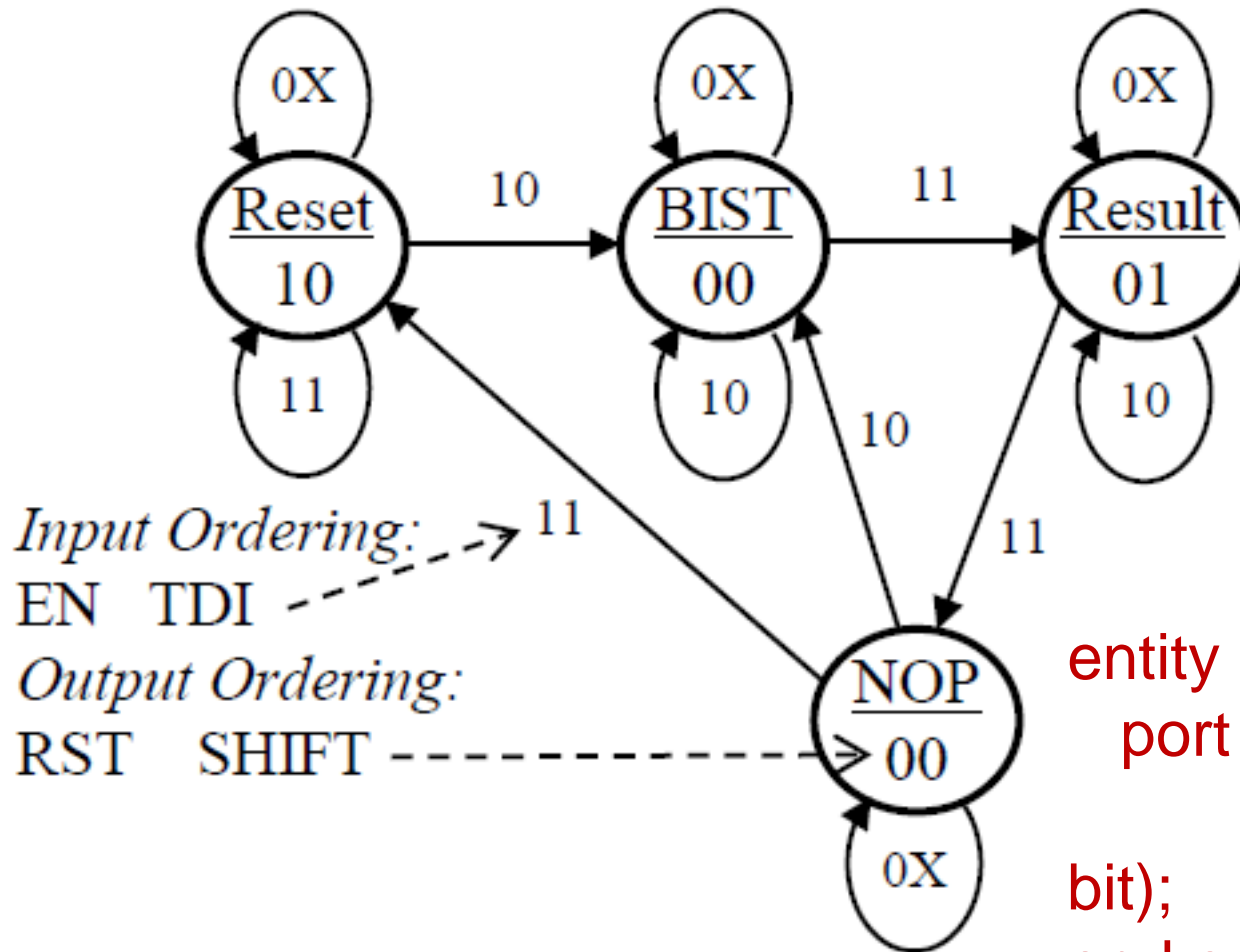


entity FSM is  
port (CLK, EN, TDI: in bit;  
RST, SHIFT: out  
bit);  
end entity FSM;

Write a VHDL code using three process blocks!
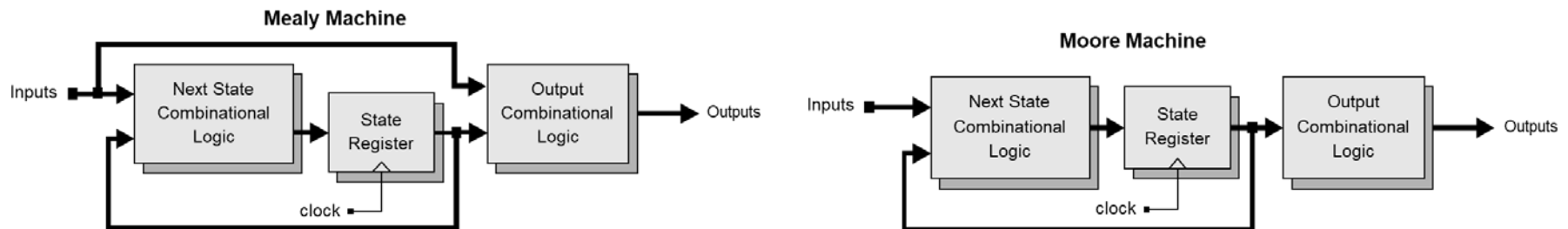
# How Verilog Explicit FSM Works

- The nonblocking and blocking assignments are scheduled in the same time step of the simulation in a particular order
  1. The nonblocking assignments in the edge-sensitive behavior are sampled first at the beginning of the time step (i.e. before any assignments are made)
  2. The blocking assignments in level-sensitive behavior are then executed (with the previous register value because there is no assignment done in Step 1)
  3. After Step 2, the nonblocking assignments are completed by assigning LHS variables with the values that were sampled at Step 1



# Verilog Explicit FSM Design and Synthesis Tips

---

- Use 2 cyclic behaviors for an explicit state machine
  - One level-sensitive behavior for combinational logic to describe the next state and output logic
  - One edge-sensitive behavior for state flip-flops to synchronize state transition
- In the level-sensitive behavior for N/S and O/P
  - Use blocked assignments/procedural assignments “=”
  - Completely specify all outputs
    - Can be achieved by initializing all outputs in the beginning
- In the edge-sensitive behavior for state transition
  - Use nonblocking assignments “<=”
    - For state transition
    - For register transfer of a data path
- Always decode all possible states in the level sensitive behavior
  - To avoid unnecessary latches

# Decode All Possible States!


---

- Matching simulation results between behavioral model and a synthesized circuit does NOT guarantee that an implementation is correct !
  - Unless exercising all possible input sequences
    - Which is almost impossible to do
  - Because, if the testbench exercises the circuit only allowable input sequences, then it is not sufficient to verify the circuit's behaviors that are not covered by the exercise of the testbench



# Verilog: Mealy Machine


---

 
 
# Verilog: Mealy Machine– Cont.

```
module mealy_2processes(input clk,  
input reset, input x, output reg  
parity);  
reg state, nextstate;  
parameter S0=0, S1=1;
```



```
always @(posedge clk or posedge  
reset)  
if (reset)  
state <= S0;  
else  
state <= nextstate;
```



```
always @(state or x)  
begin  
parity = 1'b0;  
case(state)  
S0: if(x)  
begin  
parity = 1; nextstate = S1;  
end  
else  
nextstate = S0;  
S1: if(x)  
nextstate = S0;  
else  
begin  
parity = 1; nextstate = S1;  
end  
default:  
nextstate = S0;  
endcase  
end  
endmodule
```

\*Xilinx Documentation

# Verilog: Mealy Machine– Cont.

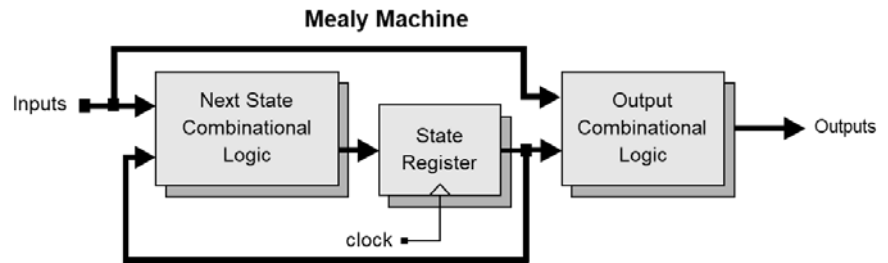 

```
module mealy_3processes(input clk, input
reset, input x, output reg parity);
reg state, nextstate;
```

```
parameter S0=0, S1=1;
```



```
always @(posedge clk or posedge reset)
if (reset)
    state <= S0;
else state <= nextstate;
```

```
always @(state or x) //Output Logic
begin
    parity = 1'b0;
    case(state)
    S0: if(x)
        parity = 1;
    S1: if(!x)
        parity = 1;
    endcase
end
```

```
always @(state or x) // Nextstate Logic
begin
    nextstate = S0;
    case(state)
    S0: if(x) nextstate = S1;
    S1: if(!x) nextstate = S1;
    endcase
end
endmodule
```

\*Xilinx Documentation

# Verilog: Moore Machine

  

```
module mealy_3processes(input clk, input
reset, input x, output reg parity);
reg state, nextstate;
```

```
parameter S0=0, S1=1;
```

```
always @(posedge clk or posedge reset)
if (reset)
    state <= S0;
else state <= nextstate;
```

\*Xilinx Documentation

```
always @(state) // Output Logic
begin
    case(state)
        S0: parity = 0;
        S1: parity = 1;
    endcase
end
```

```
always @(state or x) // Nextstate Logic
begin
    nextstate = S0;
    case(state)
        S0: if(x) nextstate = S1;
        S1: if(!x) nextstate = S1;
    endcase
end
endmodule
```

# FSM Example: BCD-to-Excess-3 Code Converter (Mealy)



---

- BCD-to-Excess-3 Code Converter for manual design
  - A serially-transmitted BCD (8421 code) word is to be converted into an Excess-3 code
    - $B_{in}$  transmitted in sequence, LSB first
  - An Excess-3 code word is obtained by adding 3 to the decimal value and taking the binary equivalent.
    - Excess-3 code is self-complementing

Decimal Digit	8-4-2-1 Code (BCD)	Excess-3 Code
0	0000	0011
1	0001	0100
2	0010	0101
3	0011	0110
4	0100	0111
5	0101	1000
6	0110	1001
7	0111	1010
8	1000	1011
9	1001	1100

9's complement can be obtained by inverting

# BCD-to-Excess-3 Code Converter (cont.)

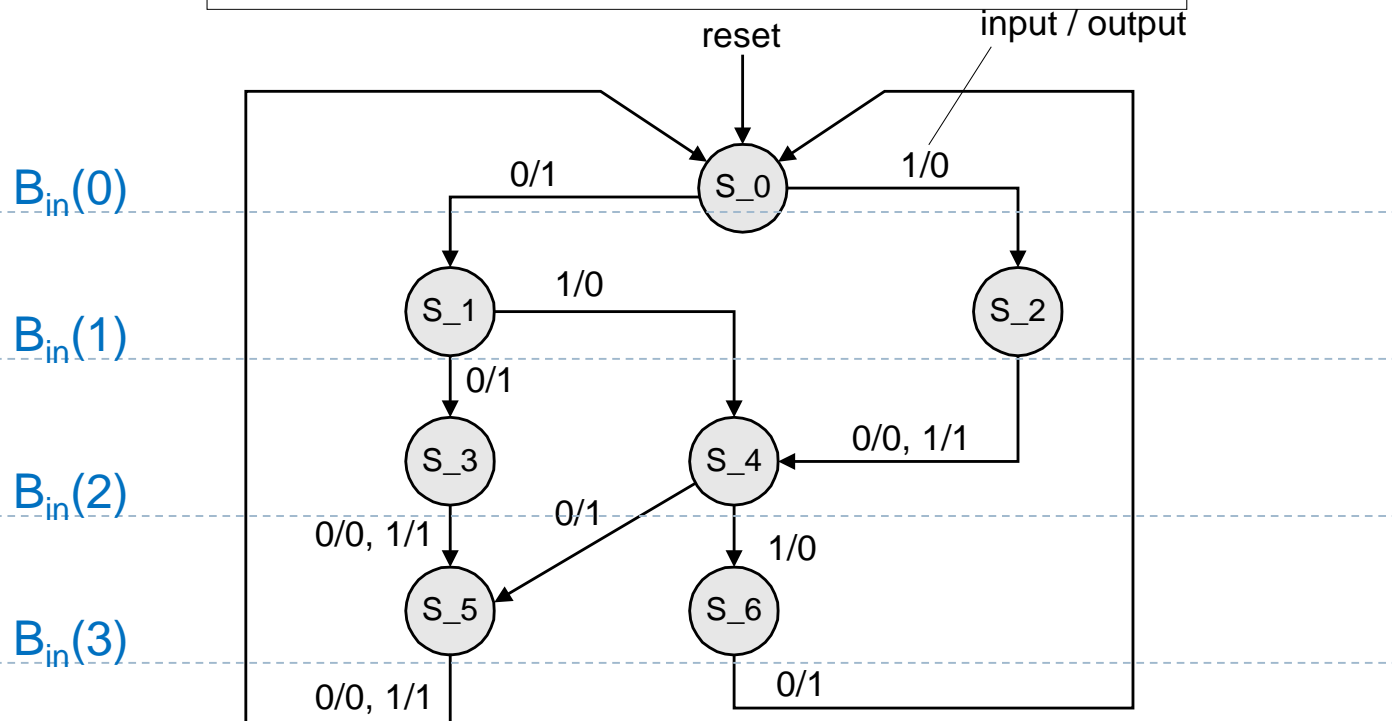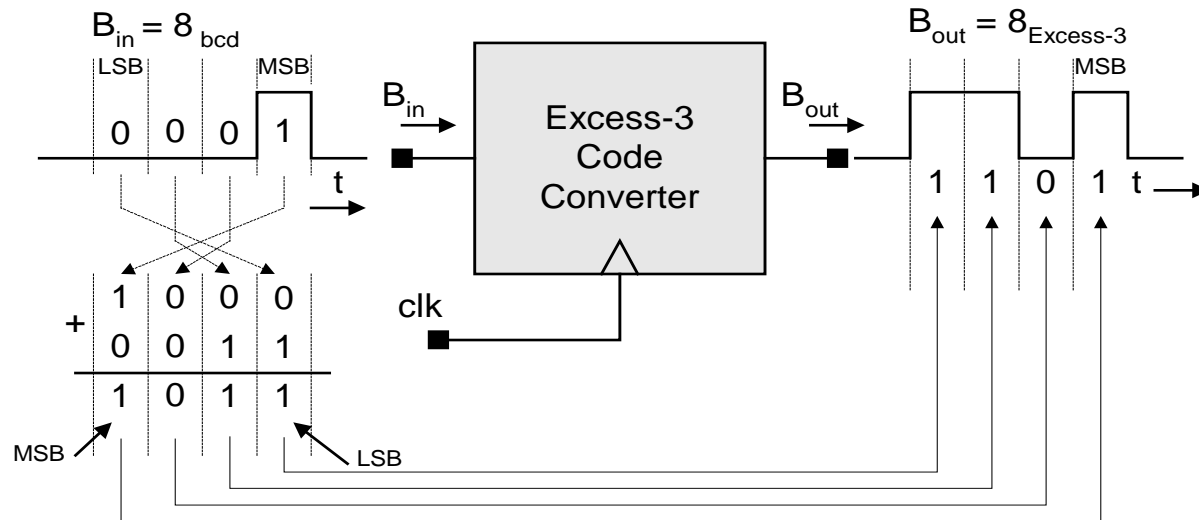

# BCD-to-Excess-3 Code Converter (cont.)

---

```
module BCD_to_Excess_3b (B_out, B_in, clk, reset_b);
  output      B_out;
  input       B_in, clk, reset_b;
  parameter   S_0 = 3'b000,      // State assignment, which may be omitted
              S_1 = 3'b001,      // If omitted, allow synthesis tool to assign
              S_2 = 3'b101,
              S_3 = 3'b111,
              S_4 = 3'b011,
              S_5 = 3'b110,
              S_6 = 3'b010,
              dont_care_state = 3'bx,
              dont_care_out = 1'bx;

  reg[2: 0]   state, next_state;
  reg         B_out;
```

# BCD-to-Excess-3 Code Converter (cont.)

---

```
always @ (posedge clk or negedge reset_b) // edge-sensitive behavior with NBAs
  if (reset_b == 0) state <= S_0; else state <= next_state;
```



```
always @ (state or B_in) begin // level-sensitive behavior with blocking assignments
  B_out = 0; // initialize all outputs here
  case (state) // explicit states
    S_0: if (B_in == 0) begin next_state = S_1; B_out = 1; end
        else if (B_in == 1) begin next_state = S_2; end // Mealy machine
    S_1: if (B_in == 0) begin next_state = S_3; B_out = 1; end
        else if (B_in == 1) begin next_state = S_4; end
    S_2: begin next_state = S_4; B_out = B_in; end
    S_3: begin next_state = S_5; B_out = B_in; end
    S_4: if (B_in == 0) begin next_state = S_5; B_out = 1; end
        else if (B_in == 1) begin next_state = S_6; end
    S_5: begin next_state = S_0; B_out = B_in; end
    S_6: begin next_state = S_0; B_out = 1; end
    /* default: begin next_state = dont_care_state;
        B_out = dont_care_out; end */
  endcase
end
endmodule
```


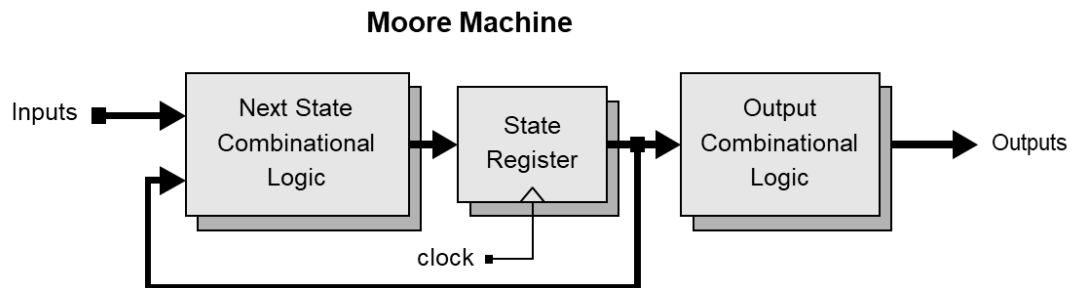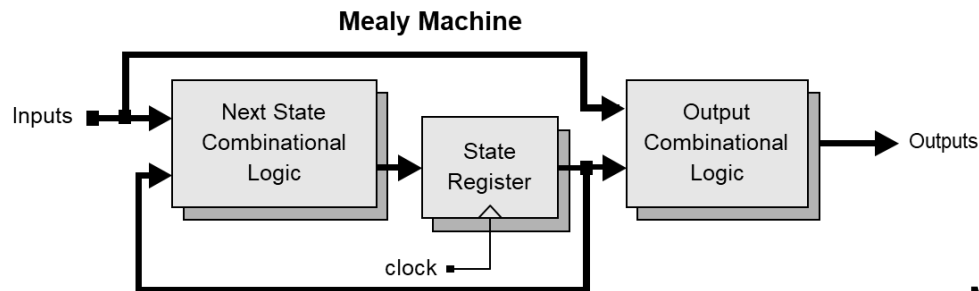
# State Encoding

---

- The task of assigning a code to the states of an FSM
  - Also described as “state assignment”
- Number of flip-flops that are required to represent a state
  - Influence the complexity of the combinational logic for the next state and outputs



# General Guidelines for State Encoding

---

- If two states have the same next state for a given input
  - Give them logically adjacent state assignments
- Assign logically adjacent state codes to the next state of a given state
- Assign logically adjacent state codes to the states that have the same outputs for a given input
- Designers can choose state assignments or allow synthesis tool to determine state encoding

# State Assignment Codes

#	Binary	One-Hot	Gray	Johnson
0	0000	000000000000000001	0000	00000000
1	0001	000000000000000010	0001	00000001
2	0010	000000000000000100	0011	00000011
3	0011	000000000000001000	0010	00000111
4	0100	00000000000010000	0110	00001111
5	0101	0000000000100000	0111	00011111
6	0110	000000001000000	0101	00111111
7	0111	0000000010000000	0100	01111111
8	1000	0000000100000000	1100	11111111
9	1001	0000001000000000	1101	11111110
10	1010	0000010000000000	1111	11111100
11	1011	0000100000000000	1110	11111000
12	1100	0001000000000000	1010	11110000
13	1101	0010000000000000	1011	11100000
14	1110	0100000000000000	1001	11000000
15	1111	1000000000000000	1000	10000000

# State Assignment Codes (cont.)

---

- Binary coded decimal (BCD) format
  - Uses the minimal number of flip-flops
  - Does not necessarily lead to an optimal realization of the combinational logic used to decode the next state and output of the machine.
    - Example: If a machine has more than 16 states, a binary code will result in a relatively large amount of next-state logic
      - The machine's speed will also be slower than alternative encoding.
- Gray code
  - Uses the same number of bits as a binary code
  - Has the feature that two adjacent codes differ by only one bit
    - Can reduce the electrical noise in a circuit.
    - Gray encoding is recommended for machines having more than 32 states because it requires fewer flip-flops than one-hot encoding, and is more reliable than binary encoding because fewer bits change simultaneously
- Johnson code
  - Has the same property as Gray code
    - Two adjacent codes differ by only one bit
  - Uses more bits.
- A code that changes by only one bit between adjacent codes will reduce the simultaneous switching of adjacent physical signal lines in a circuit, thereby minimizing the possibility of electrical crosstalk.
  - These codes also minimize transitions through intermediate states.

# One-Hot Encoding (or One-Cold)

---

- One flip-flop for each state
  - Usually more than minimum numbers of flip-flops
  - Reduces the decoding logic for next state and output
    - Hence offset the extra flip-flops
  - One-hot encoding usually does not correspond to the optimal state assignment
    - Combination usage of FF and decoding logic
- Complexity does not increase as states are added to the machine
  - Tradeoff: speed is not compromised by the time required to decode the state
- Cost: area of the additional flip flops and signal routing

# One-Hot Encoding (or One-Cold) (cont.)

---

- A one-hot encoding with an “*if*” statement that tests individual bits might provide simpler decoding logic than decoding with a “*case*” statement
  - Because “case” implicitly references all bits
  - While “if” only references to individual bits
- In FPGA, saving flip-flops may not be beneficial
  - Because FF already built inside FPGA
    - Even don’t use them, you do not save FF
  - If decoding logic requires more logic than are more than on a configurable logic block (CLB)
    - Then one-hot is preferred
    - Because no interconnection required between CLBs
  - Hence, **use one-hots in FPGAs to reduce the use of CLBs**
- Note: in large machines, one-hot encoding will have several unused states, in addition to requiring more registers than alternative encoding
- Caution: if a state assignment does not exhaust the possibilities of a code, then additional logic will be required to detect and recover from transitions into unused states.

# Zero Detector


- Asserting its output when a 0 is detected in a stream of 1s.

Present State		Input	Next State		Output
A	B	x	A	B	y
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	1	0
1	0	0	0	0	1
1	0	1	1	0	0
1	1	0	0	0	1
1	1	1	1	0	0

Present State		Next State				Output	
		x = 0		x = 1		x = 0	x = 1
A	B	A	B	A	B	y	y
0	0	0	0	0	1	0	0
0	1	0	0	1	1	1	0
1	0	0	0	1	0	1	0
1	1	0	0	1	0	1	0

# Zero Detector: Mealy Machine

---

 



# Zero Detector: Mealy Machine

---

```
//Verilog 2001, 2005 syntax
module Mealy_Zero_Detector (
  output reg y_out,
  input x_in, clock, reset
);
reg [1: 0] state, next_state;
parameter S0 = 2'b00, S1 = 2'b01,
S2 = 2'b10, S3 = 2'b11;

  always @ (state, x_in) // Mealy output
  case (state)
    S0: y_out = 0;
    S1, S2, S3: y_out = ~x_in;
  endcase


endmodule

always @ ( posedge clock, negedge reset)
  if (reset == 0) state <= S0;
  else state <= next_state;

always @ (state, x_in) // Next state
  case (state)
    S0: if (x_in) next_state = S1; else next_state = S0;
    S1: if (x_in) next_state = S3; else next_state = S0;
    S2: if (~x_in) next_state = S0; else next_state = S2;
    S3: if (x_in) next_state = S2; else next_state = S0;
  endcase
```

# Binary Counter: Moore Machine

---

 

# Binary Counter: Moore Machine

---

- Write a Verilog code for Binary Counter (Moore Machine).