



LOW POWER DESIGN OF ELECTRICAL CIRCUITS PROJECT

Very low voltage operation
of a 16-bit counter

Ziyan Xu
12/04/07

Introduction

- Course of project — Reduction of voltage supply
- Aim — Finding an optimum voltage
- Theory

Dynamic Power


$$P = CV_{DD}^2f$$

Delay

$$\text{Delay} = KV_{DD} / (V_{DD} - V_t)^{\alpha}$$


Circuit Design

- 16 bit counter

 


Circuit Design

- Rising Edge Triggered D Flip-Flop

 

Circuit Design

- Waveform

 

Simulation

- Device 0.5 μ m process
 $V_{th}=0.6V$
- Simulator
 Cadence Spectre
- Clock Frequency
 Clock Period=16ns
- Analysis Time
 $T = 4\mu s$

Simulation

- Results


$$\text{Power} = V_{dd} * \int I \, dt / T$$

$$\text{Delay} = 16 * \text{Delay}_{\text{clk-Q}_o}$$

Vdd(V)	Power(W)	Delay(s)	Power*Delay(W.S)
1.5	176.8E-6	5.24E-9	9.26E-13
1.3	112.5E-6	5.68E-9	6.39E-13
1.1	73.0E-6	7.49E-9	5.47E-13
0.9	45.1E-6	1.23E-8	5.55E-13
0.7	24.7E-6	3.20E-8	7.90E-13
0.6	11.2E-6	7.95E-8	8.9E-13
0.5	Fail to work		


Simulation

- Power

 


Simulation

- Delay

 

Simulation

- Power-Delay Product

 

Conclusion

- Substantial decrease in power by decreasing voltage.
- At lower voltages the increase in delay is greater than at higher voltages.
- The optimum supply voltage is between $0.9V \sim 1.1V$.

Extension

- Low –voltage limitation of MOSFETs

$$V_{gs} = V_t + \sqrt{\frac{I_d}{K} \frac{L}{W}}$$

V_t : Threshold Voltage

L and W : Effective dimensions of the gate length and width

I_d : Drain current


K : Transconductance factor for the MOSFET

1100

-

Multithreshold Technique

 On non-critical path, high threshold transistor can be assigned, while on the critical path, we use low threshold transistor.



Reference

- Dr. V. Agrawal's ELEC 6970 slides, Lecture 5
- Wayn Wolf, Modern VLSI Design, Third Edition, Prentice-Hall, p.250-p.260
- B. Hoppe, Chr. Kroh, H.Meuth and M.Stohr ,A 440MHZ 16 Bit Counter in Cmos Standard Cells, ASIC Conference 1998. Proceedings. Eleventh Annual IEEE International p.241-p.244
- H.Zhang, J.She n, X.Gu, Design of Low-power D Flip-flop Based on Multithreshold Technique, Journal of Zhejiang University(Science Edition), 2005, 32(2), p.165-p.168
- E.Sinencio, A.Andreou, Low-Voltage/Low-Power Integrated Circuits and Systems, Wiley-Interscience, 1998, p.68-p.70



Thanks!